

# Diode Application



---

WED DK2 9-10am

THURS DK6 2-4pm

# Simple Diode circuit

## Series diode configuration

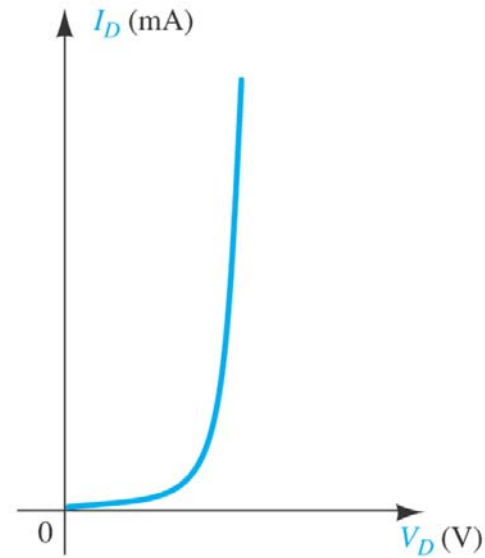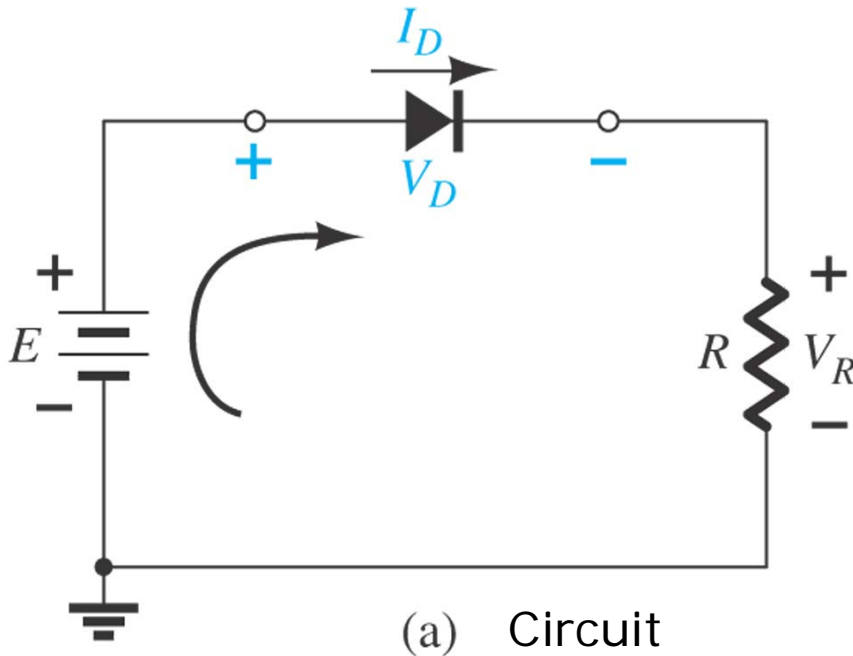


From Kirchoff's Voltage Law

$$E = V_D + I_D R$$

From previous lecture

$$I_D = I_S \left( e^{V_D / nV_T} - 1 \right)$$

# Load line analysis

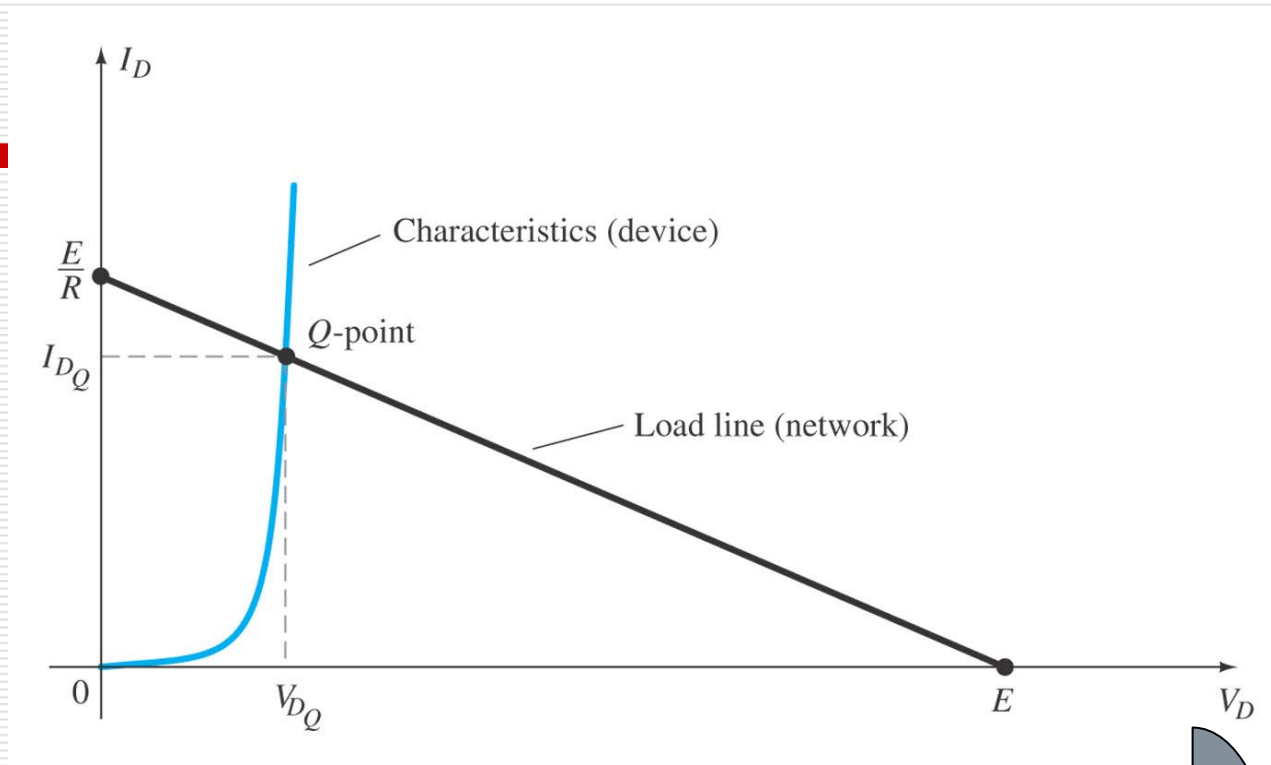


When  $V_D = 0$  V then


$$I_D = \frac{E}{R} \Big|_{V_D=0V}$$

When  $I_D = 0$  A then

$$V_D = E \Big|_{I_D=0A}$$

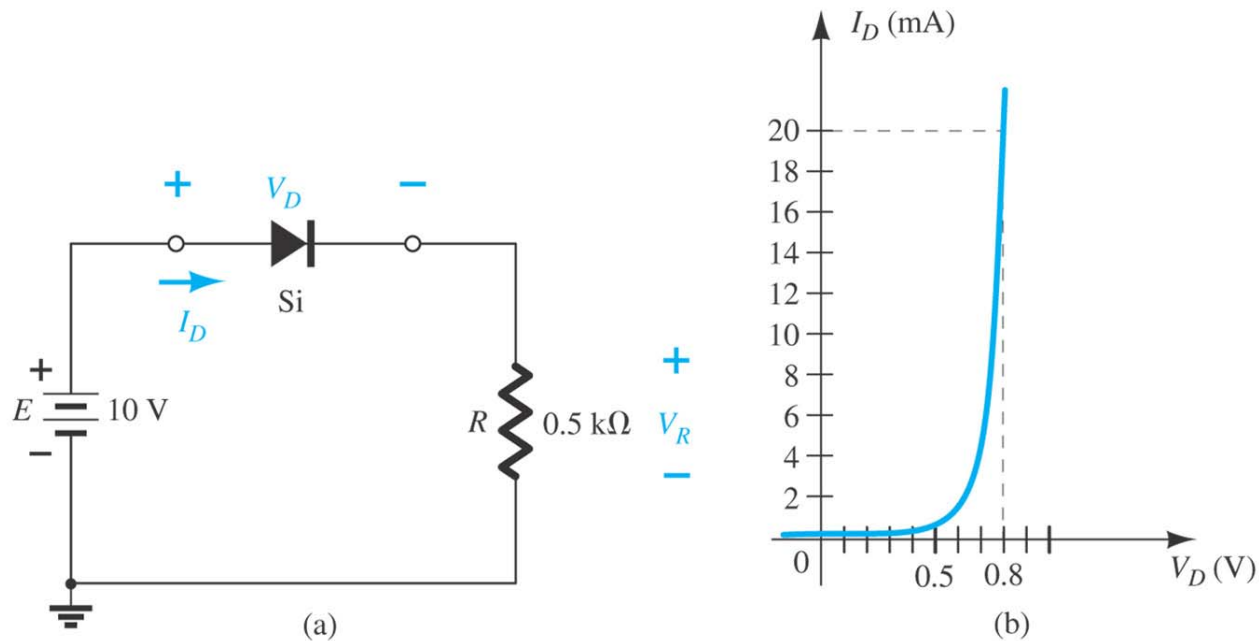**Example** For the series diode below employing the diode characteristic beside it, determine  $V_{DQ}$ ,  $I_{DQ}$  and  $V_R$ ,



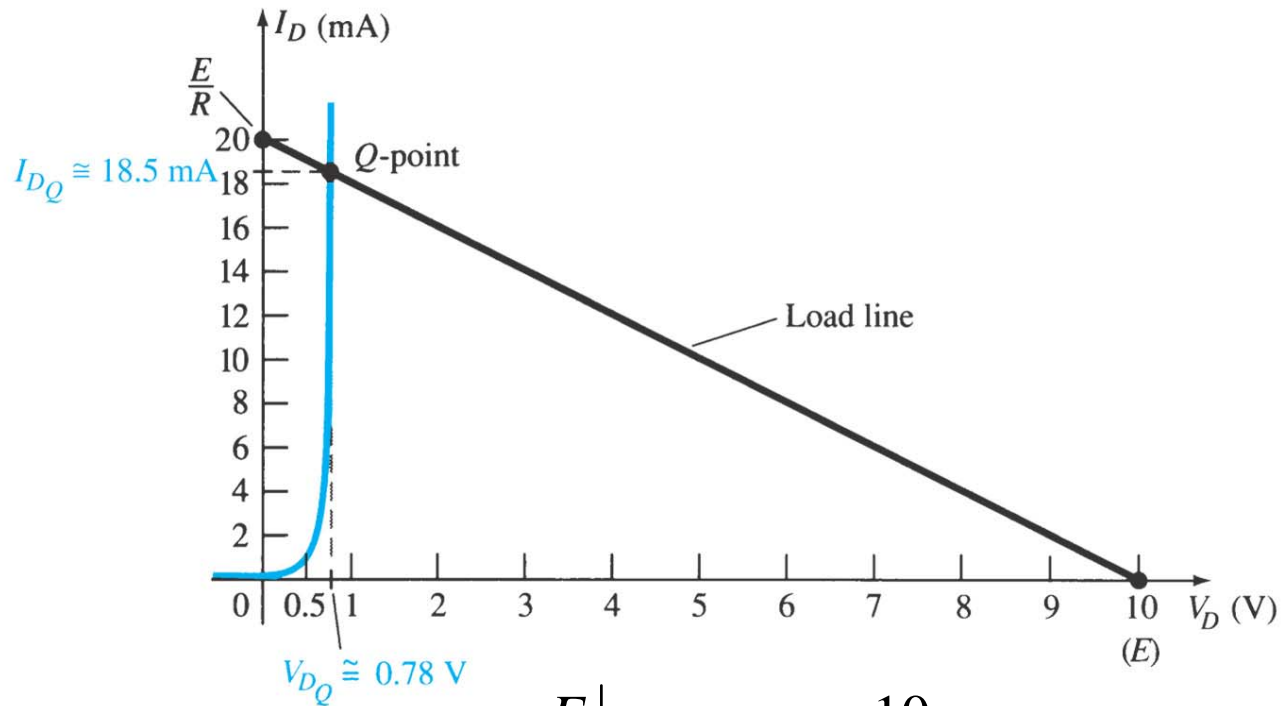

For load line


$$I_D = \frac{E}{R} \Big|_{V_D=0V} = \frac{10}{0.5k\Omega} = 20 \text{ mA}$$

$$V_D = E \Big|_{I_D=0A} = 10V$$


By drawing the load line on the diode characteristic we obtained the

$$V_{DQ} = 0.78V \qquad I_{DQ} = 18.5 \text{ mA}$$
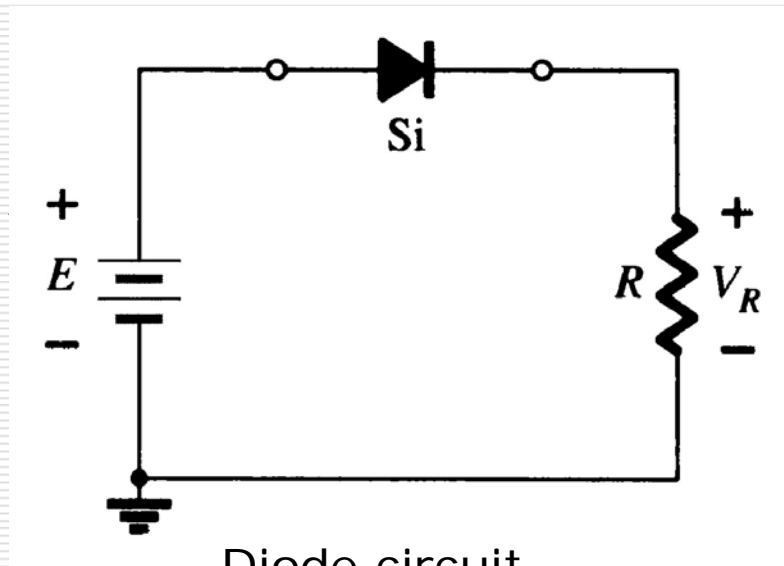
$$V_R = I_R R = I_{DQ} R = 18.5 \text{ mA} \times 1 \text{ k}\Omega = 18.5 \text{ V}$$




Diode circuit

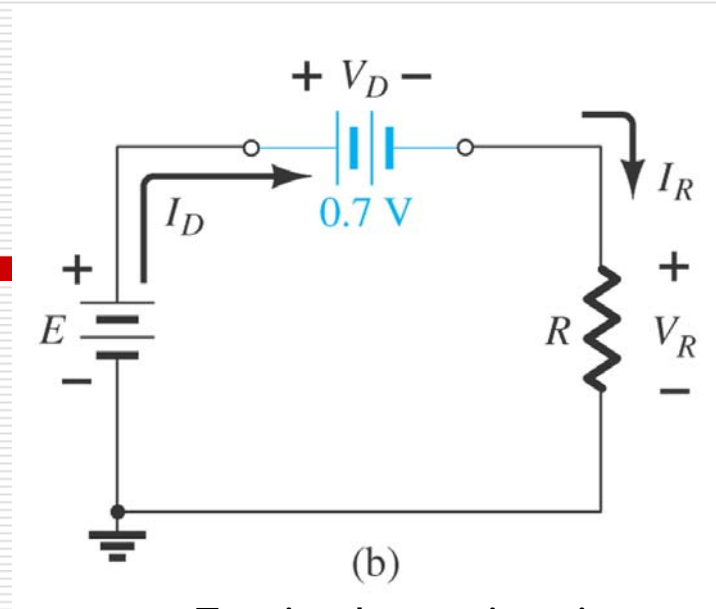


Equivalent circuit

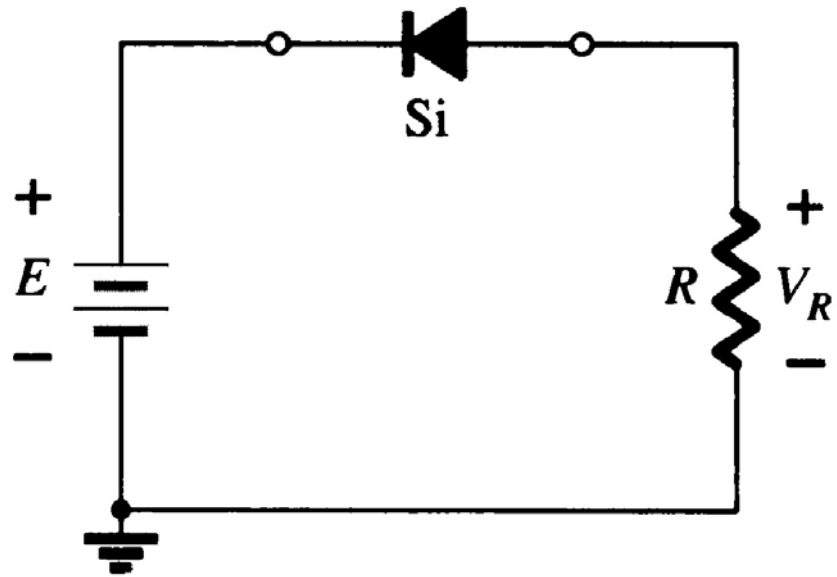A diode is "ON" state if the current established by the applied sources is such that its direction matches that of the arrow in the diode symbol and  $V_D \geq 0.7\text{V}$  for Si,  $V_D \geq 0.3\text{V}$  for Ge,  $V_D \geq 1.2\text{V}$  for GaAs




Diode circuit

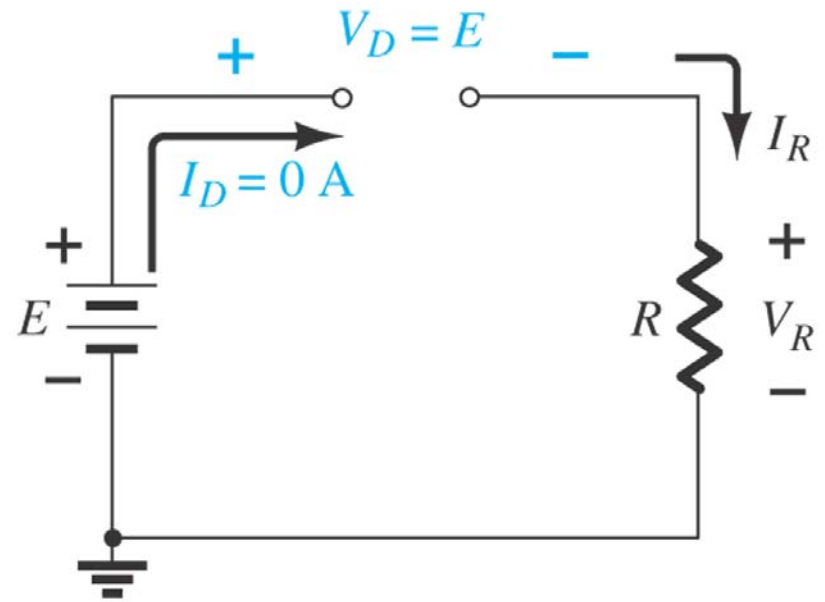

Equivalent circuit

A diode is "OFF" state if the current established by the applied sources is reversed the direction of the arrow in the diode symbol. Then  $I_D = 0$

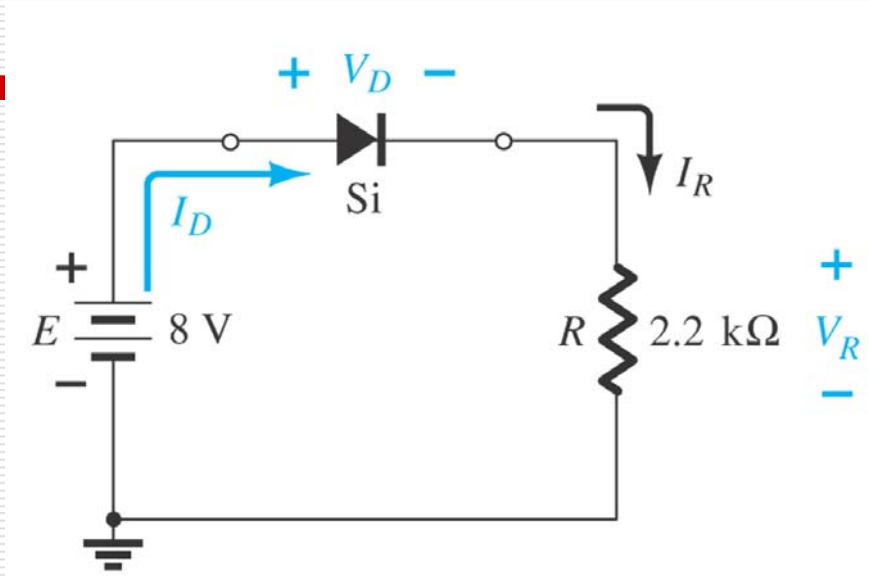For the diode below determine  $V_D$ ,  $V_R$  and  $I_D$



$$V_D = 0.7V$$


Using equivalent circuit and KVL

$$V_R = E - V_D = 8V - 0.7V = 7.3V$$

$$I_D = I_R = \frac{V_R}{R} = \frac{7.3V}{2.2k\Omega} = 3.32mA$$



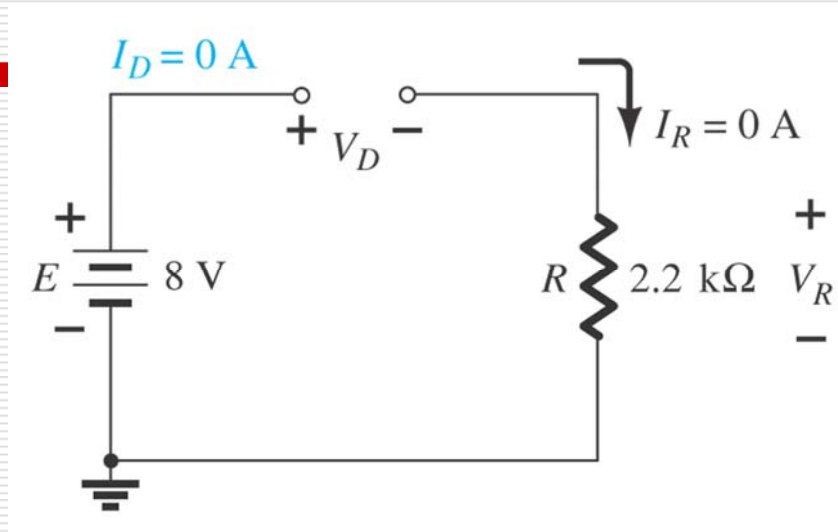Repeat Example with the diode reverse. Thus the equivalent circuit is




$$I_D = 0\text{ A}$$

$$V_R = I_R R = I_D R = 0\text{ V}$$


Using equivalent circuit and KVL

$$V_D = E - V_R = 8\text{ V} - 0\text{ V} = 8\text{ V}$$

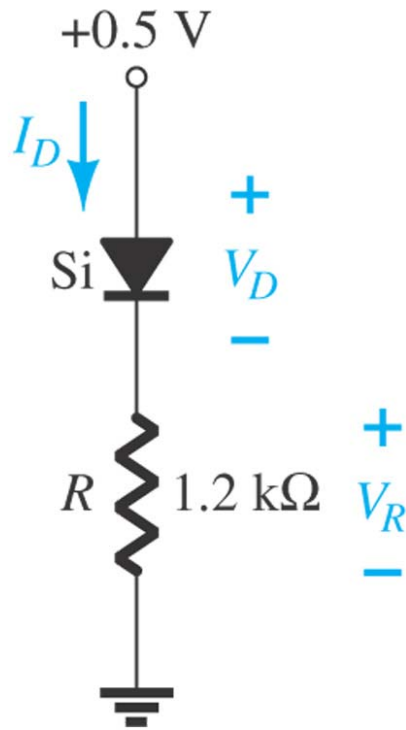
If the diode is biased with the voltage source less than  $V_D$ , the diode also acting like open circuit



Diode Circuit

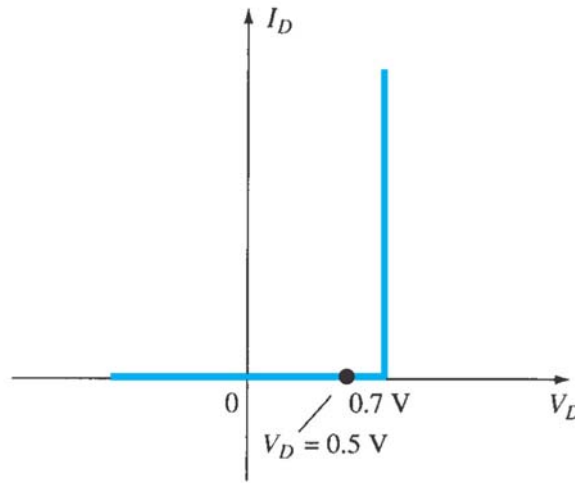


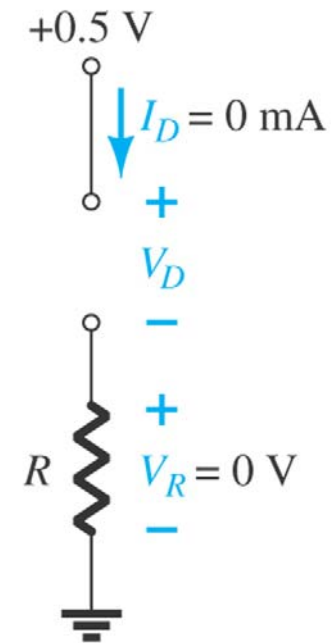Diode Characteristic  
With biasing less than 0.7V



Equivalent cct

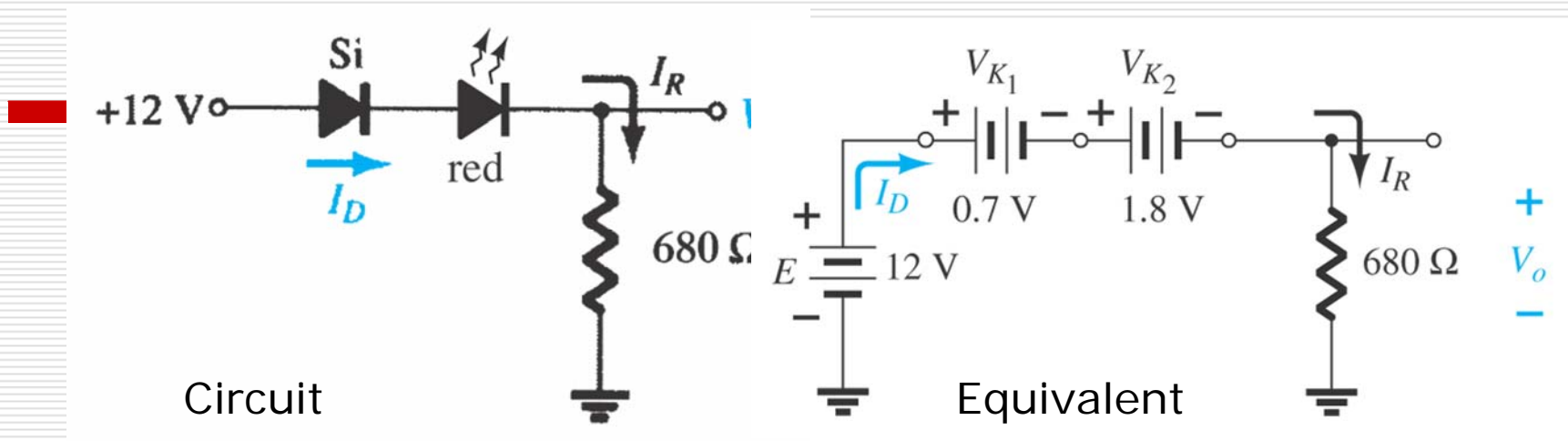Determine  $V_o$  and  $I_D$  for the series circuit below






Using equivalent circuit and KVL

$$V_o = E - V_{K1} - V_{K2} = 12\text{V} - 0.7\text{V} - 1.8\text{V} = 9.5\text{V}$$

$$I_D = I_R = \frac{V_R}{R} = \frac{9.5\text{V}}{680\ \Omega} = 13.97\text{mA}$$

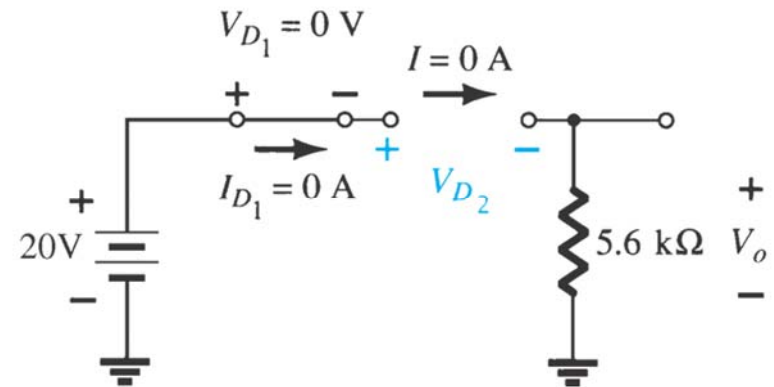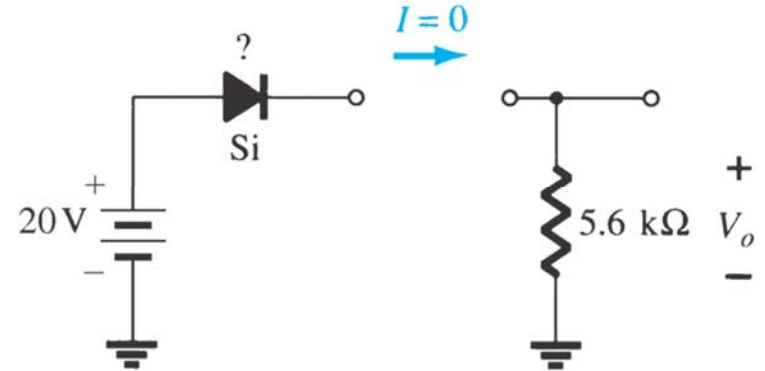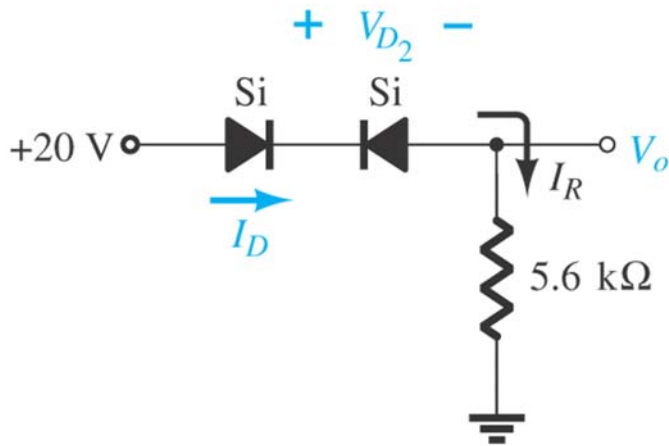Determine  $I_D$ ,  $V_D$  and  $V_o$  for the circuit below



Since open circuit


$$I_D = 0 \text{ mA} \quad V_{D1} = 0 \text{ V}$$

$$V_o = I_R R = I_D R = 0 \times R = 0 \text{ V}$$

And using KVL we have

$$V_{D2} = E - V_{D1} - V_o = 20 \text{ V} - 0 \text{ V} - 0 \text{ V} = 20 \text{ V}$$

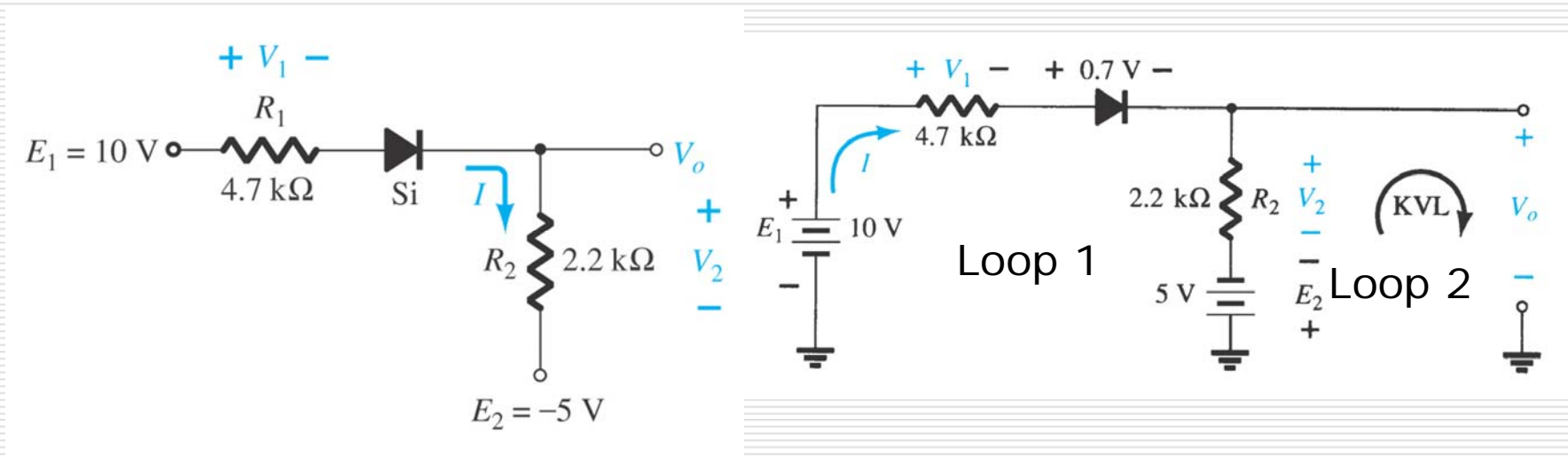Determine  $I$ ,  $V_1$ ,  $V_2$  and  $V_o$  for the series circuit below



Applying KVL in loop 1

$$I = \frac{E_1 + E_2 - V_D}{R_1 + R_2} = \frac{10V + 5V - 0.7V}{4.7k\Omega + 2.2k\Omega} = 2.07mA$$


$$V_1 = IR_1 = 2.07mA \times 4.7k\Omega = 9.73V$$

$$V_2 = IR_2 = 2.07mA \times 2.2k\Omega = 4.55V$$

And using KVL in loop 2

$$V_o = V_2 - E_2 = 4.55V - 5V = -0.45V$$

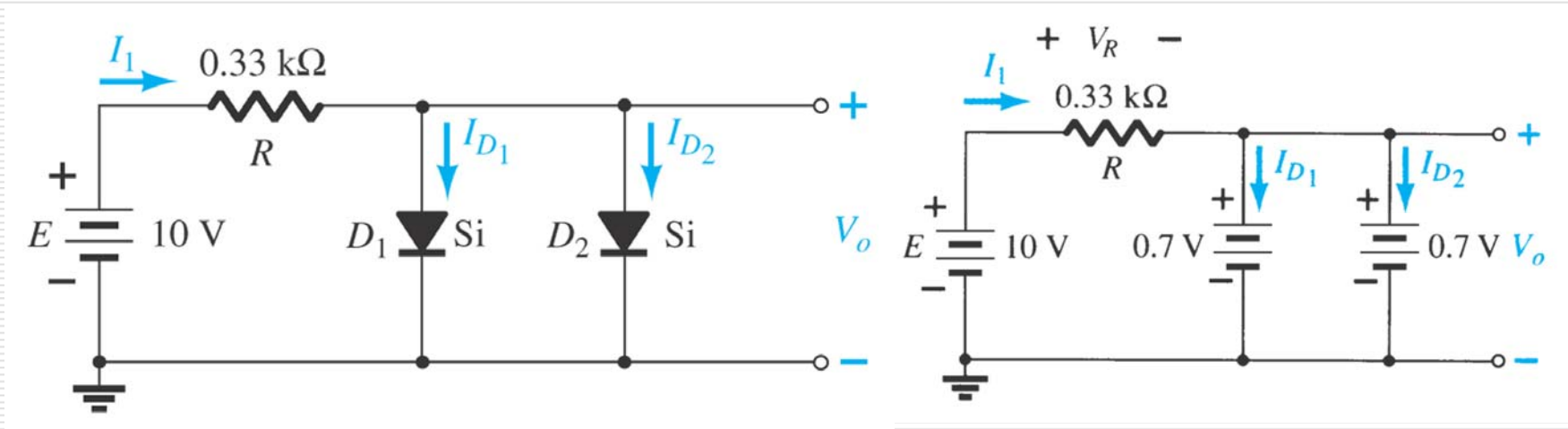Determine  $V_o$ ,  $I_1$ ,  $I_{D1}$  and  $I_{D2}$  for the parallel diode below




Since the source voltage is greater than the diode then the current flow and the voltage across diode is 0.7V, thus  $V_o = 0.7V$

The current is 
$$I_1 = \frac{V_R}{R} = \frac{E - V_D}{R} = \frac{10V - 0.7V}{330\Omega} = 28.18mA$$

Since diodes are similar thus the current will be same, then

$$I_{D1} = I_{D2} = \frac{I_1}{2} = \frac{28.18mA}{2} = 14.09mA$$

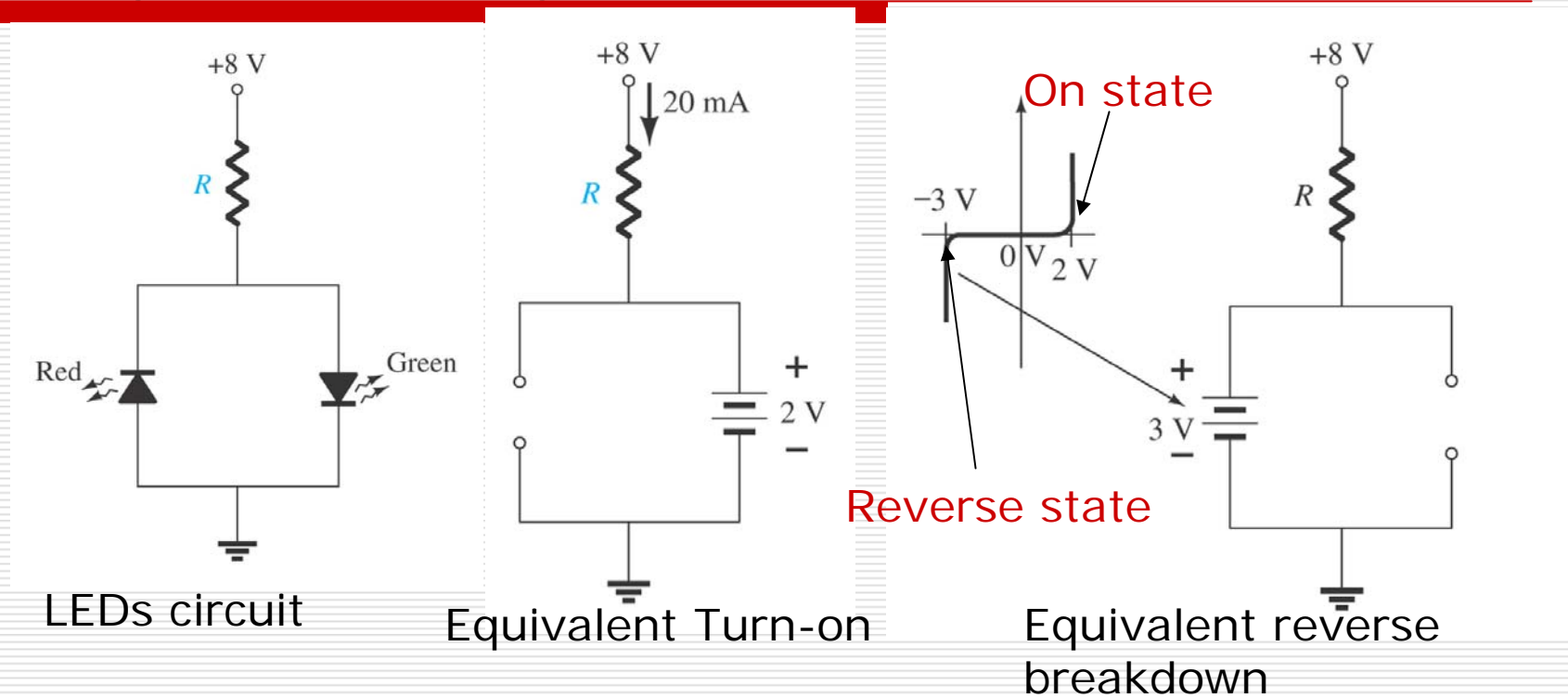Two LEDs are used for polarity detection. Positive green and negative red. Find  $R$  to ensure 20mA through "on" diode. Both diodes have a reverse breakdown voltage of 3V and an average turn-on voltage of 2V



Note: Since the turn-on voltage is 2V so it does not exceed the reverse breakdown (3V) of the red LED. Otherwise it will damage the red diode.

## Solution

---

Applying Ohm's law. The current is

$$I = 20mA = \frac{E - V_{LED}}{R} = \frac{8V - 2V}{R}$$

Therefore

$$R = \frac{6V}{20mA} = 300\Omega$$




What happen if we replace with LED having turn-on voltage is 5V?

Applying Ohm's law. The current now is


$$I = 20mA = \frac{E - V_{LED}}{R} = \frac{8V - 5V}{R}$$

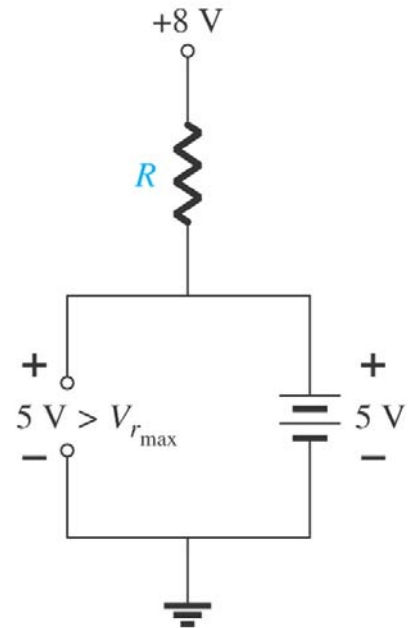Therefore 
$$R = \frac{3V}{20mA} = 150\Omega$$





But this time the reverse biased for red LED will be 5V and exceed the breakdown voltage. The red LED will damage.

## Protective Measure for such case

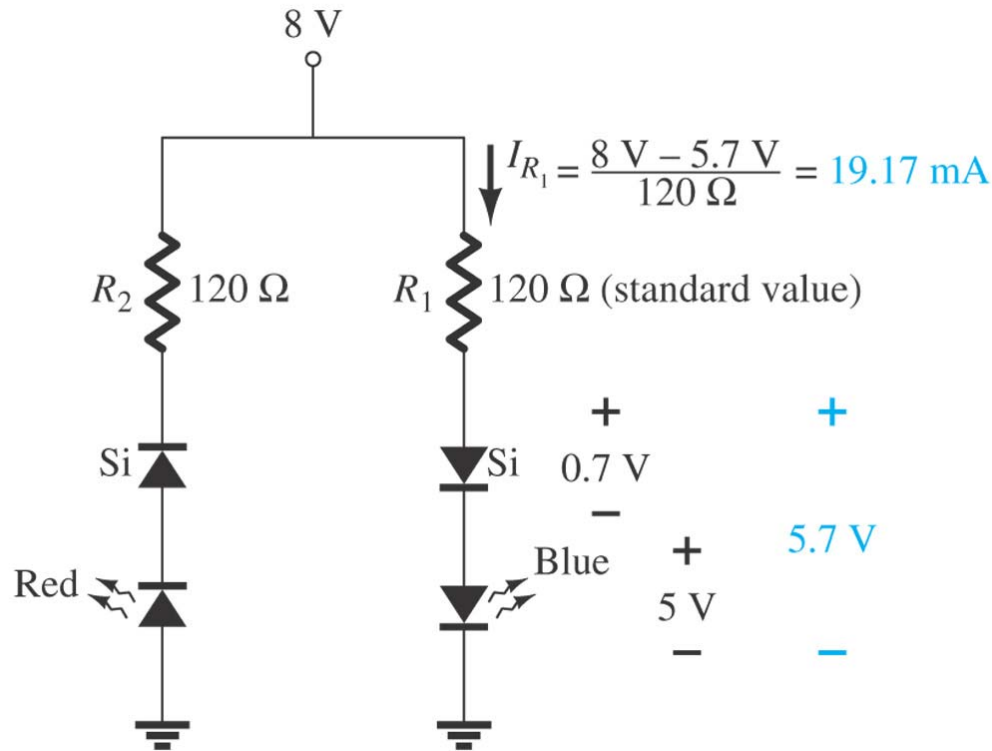

The Si diode has a breakdown voltage of 20V which will stay "off" state when the apply voltage is less than 20V. So will protect the red LED.

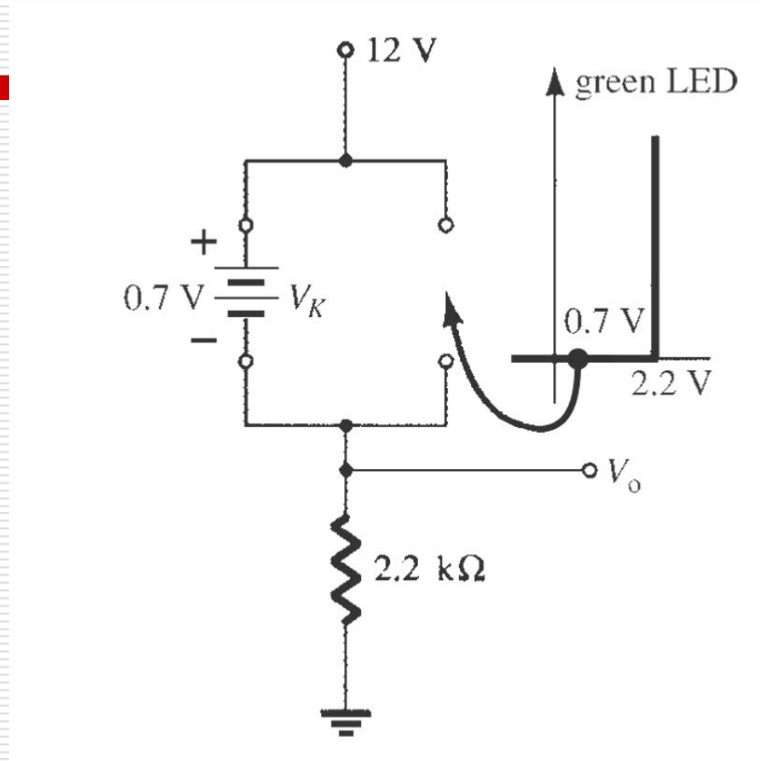
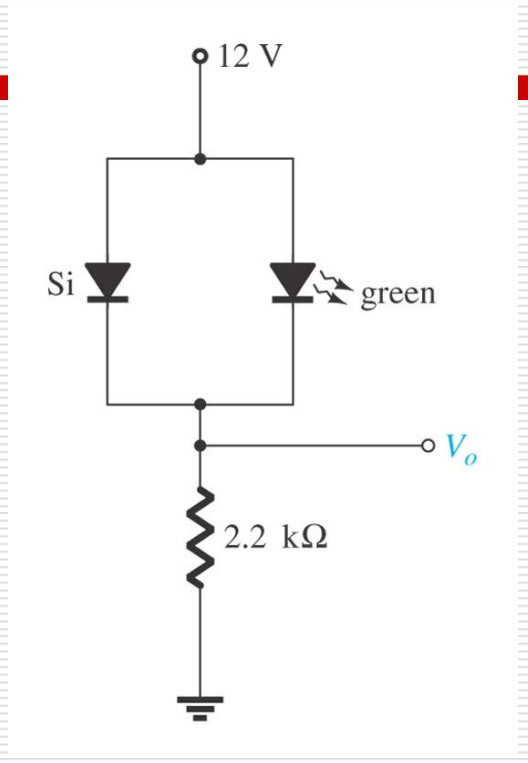
## Determine the voltage $V_o$ for the network below



The voltage across diode is the lowest one since it will “on” first and the other still stay “off” state. Thus

$$V_o = 12V - 0.7V = 11.3V$$

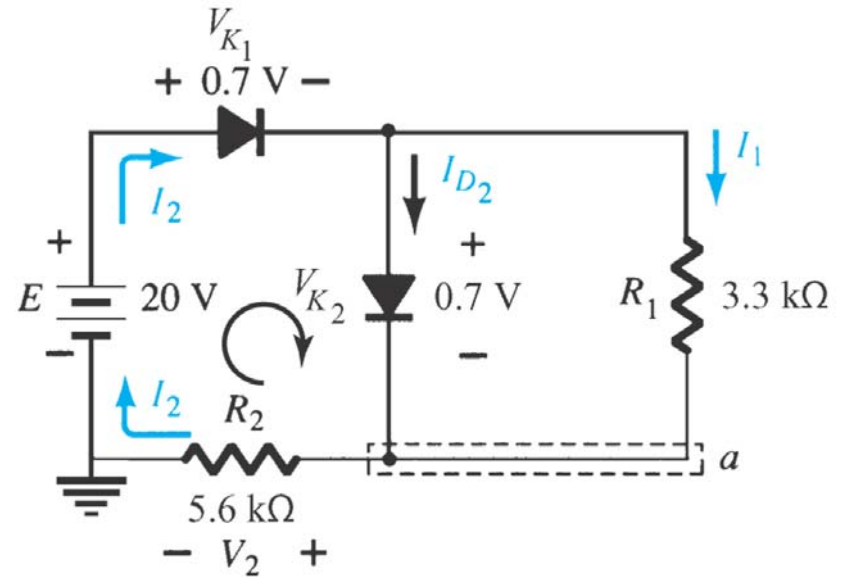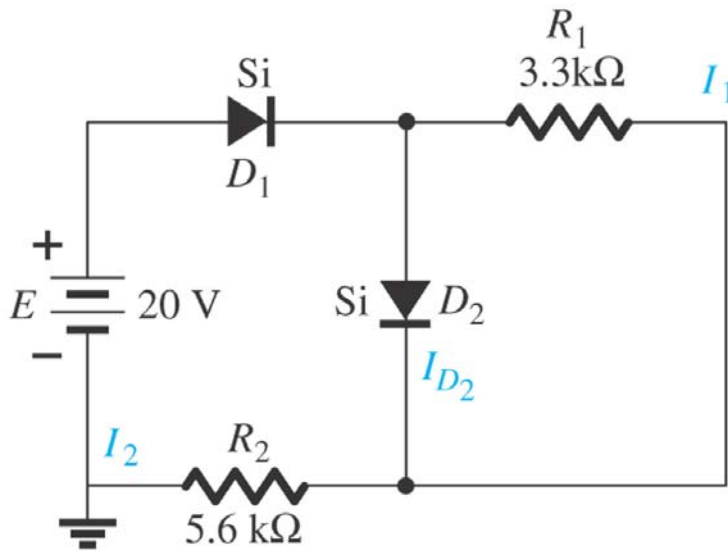Determine the currents  $I_1$ ,  $I_2$  and  $I_D$  for the network below



Since  $R_1$  is //  $D_2$  then  
voltage is same

$$I_1 = \frac{V_{K_2}}{R_1} = \frac{0.7V}{3.3k\Omega} = 0.212mA$$

Applying KVL in loop 1

$$V_2 = E - V_{K_1} - V_{K_2} = 20V - 0.7V - 0.7V = 18.6V$$

Therefore


$$I_2 = \frac{V_2}{R_2} = \frac{18.6V}{5.6k\Omega} = 3.32mA$$

and

$$I_{D_2} = I_2 - I_1 = 3.32mA - 0.212mA \cong 3.11mA$$
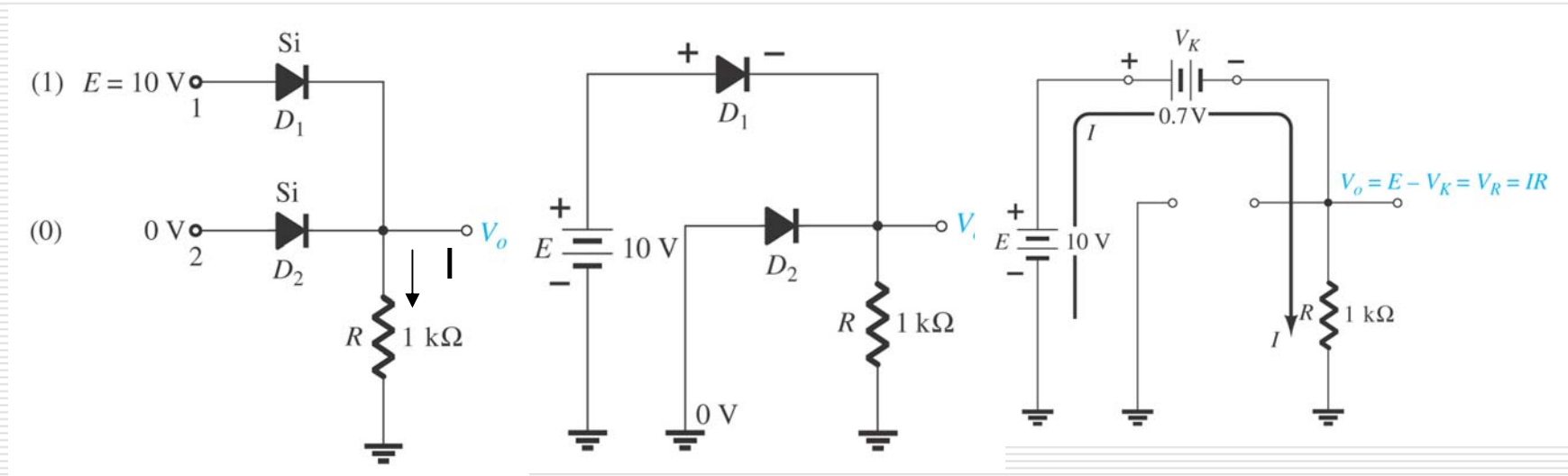
# OR Gate

Determine  $V_o$  and  $I$  for network below



From fig. on the right apply KVL



$$V_o = E - V_D = 10\text{V} - 0.7\text{V} = 9.3\text{V}$$

and

$$I = \frac{E - V_{D1}}{R} = \frac{10\text{V} - 0.7\text{V}}{1\text{k}\Omega} = 9.3\text{mA}$$
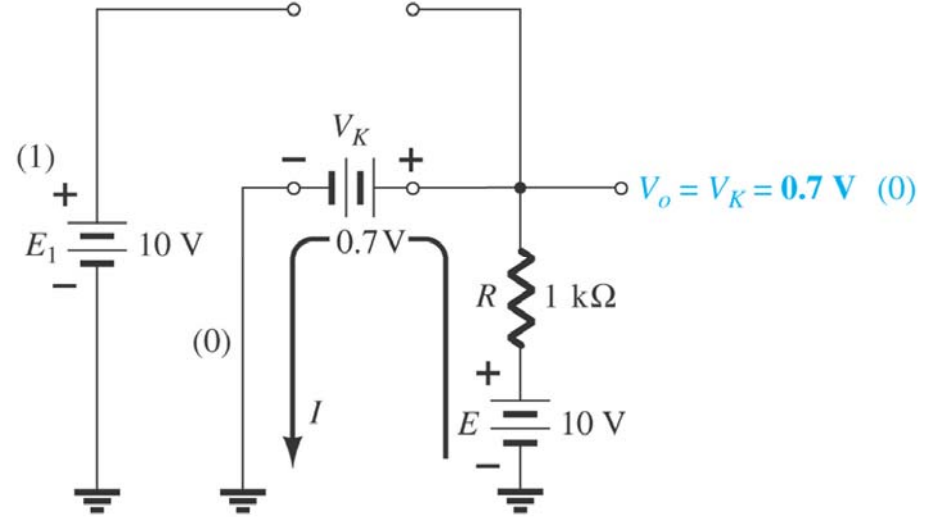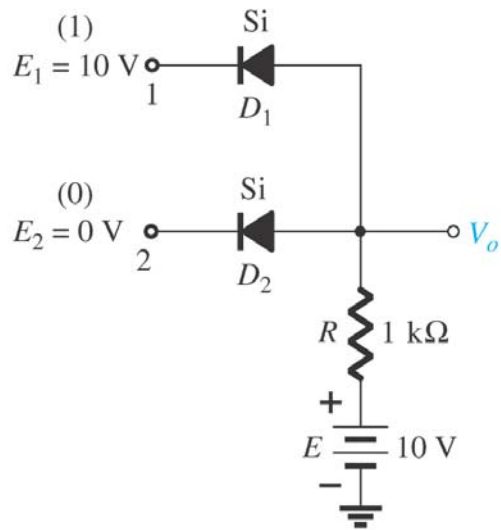
# OR gate

Determine the output level for the positive logic AND gate below





Due to forward bias of  $D_2$  the output voltage is  $V_o = 0.7V$


From fig. on the right apply KVL

$$I = \frac{E - V_K}{R} = \frac{10V - 0.7V}{1k\Omega} = 9.3mA$$

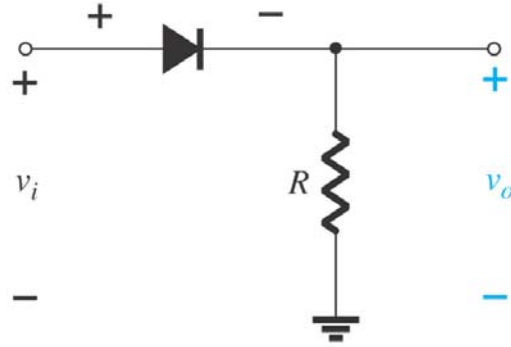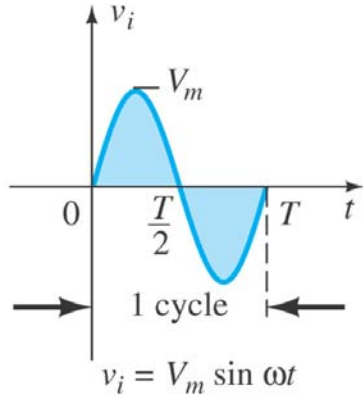
# Half-Wave Rectification- Sinusoidal Input




Sinusoidal input

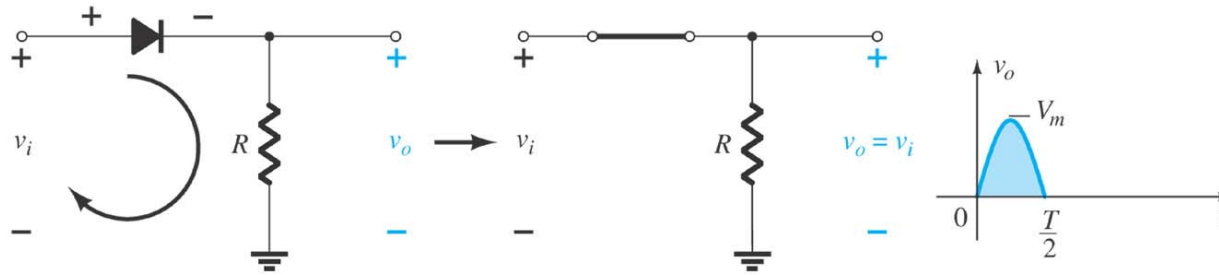

Forward bias

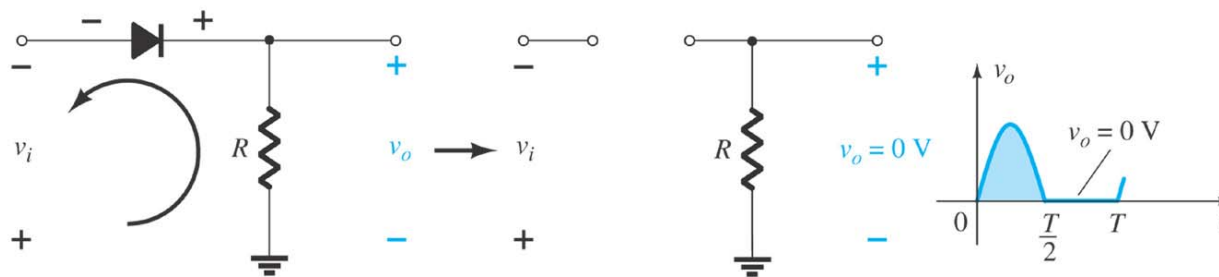




Reverse bias

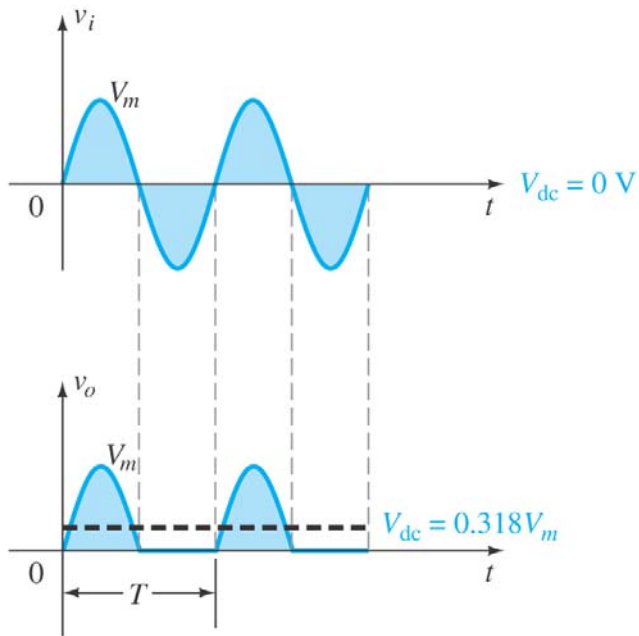

For ideal rectifier the dc voltage (rms) =  $0.318V_m$  but the diode is conducted after the voltage supplied is more than  $0.7\text{V}$  as shown below so the dc voltage will be reduced. Thus  $V_{dc}$  is

$$V_{dc} \cong 0.318(V_m) \quad \text{ideal}$$

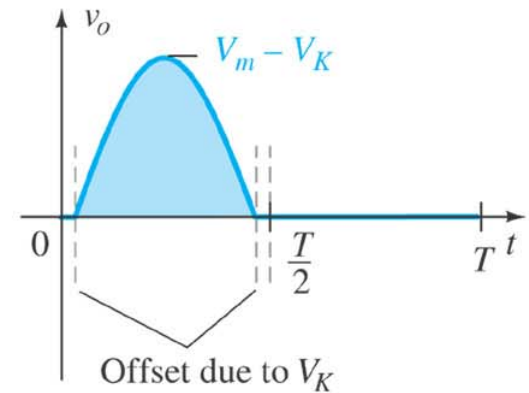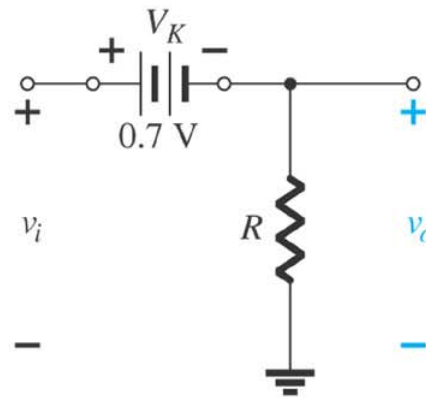
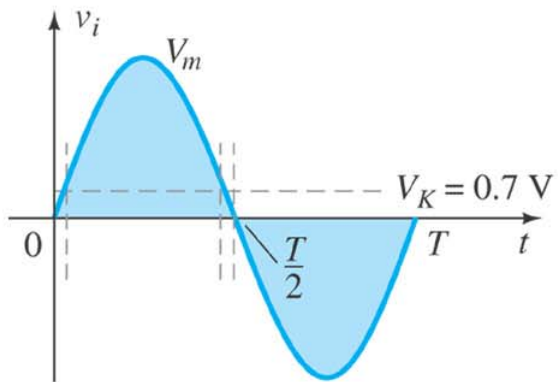
$$V_{dc} \cong 0.318(V_m - V_K) \quad \text{practical}$$






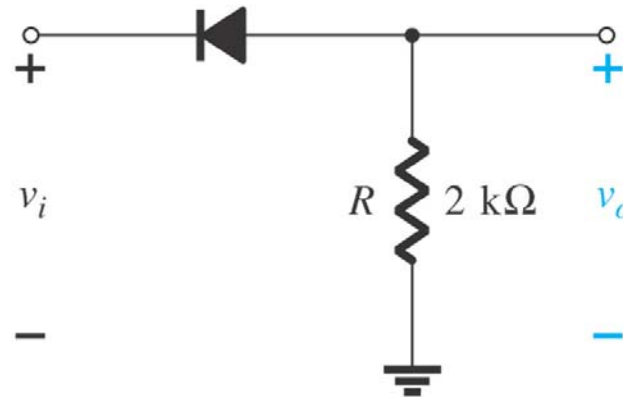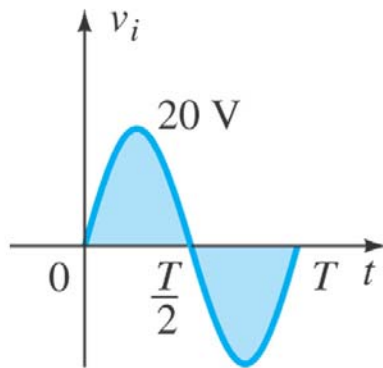Example; Circuit as below

- Sketch the output  $v_o$  and determine dc level of the output voltage for ideal diode
- What is the practical diode
- The  $V_m$  is increase to 200V




# Solution

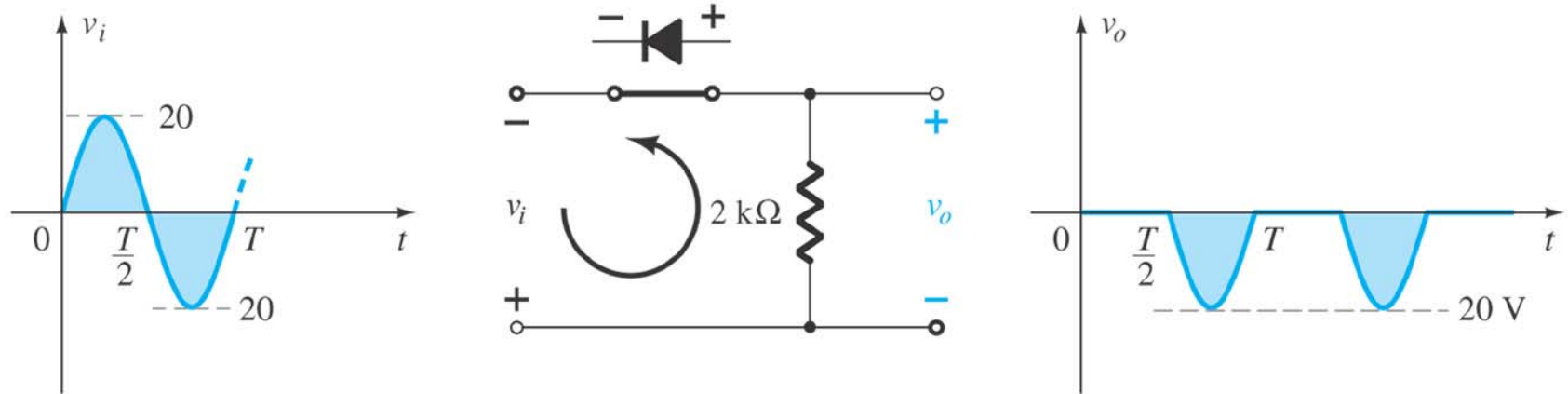

Ideal diode circuit

$$V_{dc} \cong 0.318(V_m) = -0.318(20V) = -6.36V$$

(b)

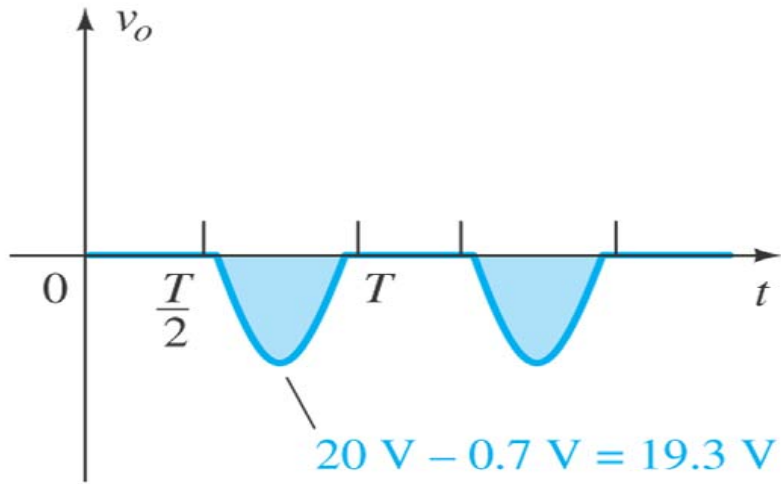

$$V_{dc} \cong 0.318(V_m - V_K) = -0.318(20\text{V} - 0.7\text{V}) = -6.14\text{V}$$


Drop about 0.22V or 3.5 %

$$(b) \quad V_{dc} \cong 0.318(V_m) = -0.318(200\text{V}) = -63.6\text{V} \quad (\text{ideal})$$

$$V_{dc} \cong 0.318(V_m - V_K) = -0.318(200\text{V} - 0.7) = -63.38\text{V} \quad (\text{practical})$$

Drop about 0.22V or 0.35%


# Diode Rating

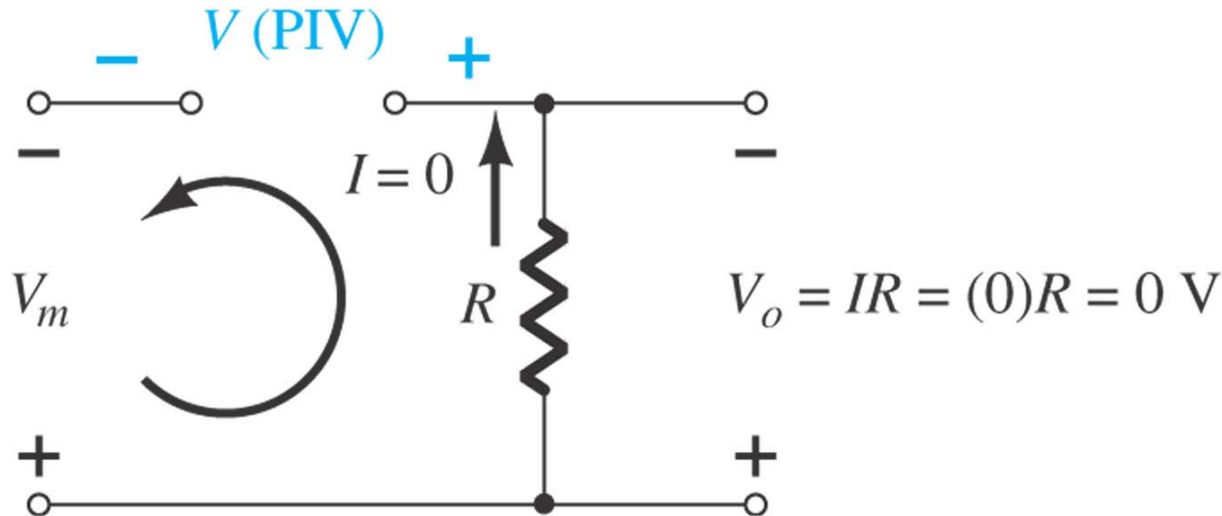

The diode rating is stated as peak inverse voltage (PIV) or peak reverse Voltage (PRV). PIV of diode must be greater than the applied voltage otherwise the diode will damage or enter the Zener avalanche region





$$\text{PIV}(\text{rating}) \geq V_m \text{ half -wave rectifier}$$

# Full-wave rectifier



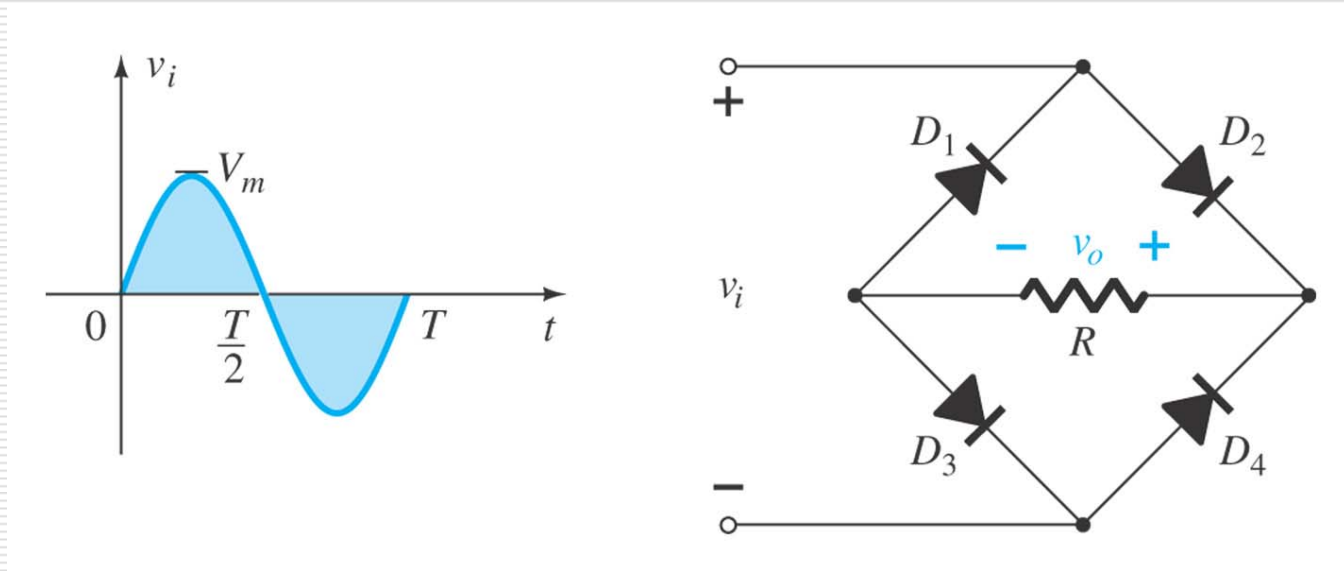




Using four diode in certain arrangement such that the circuit are able to rectifier another half of the sinusoidal wave.

# First half

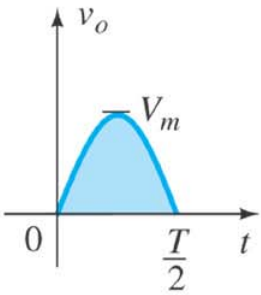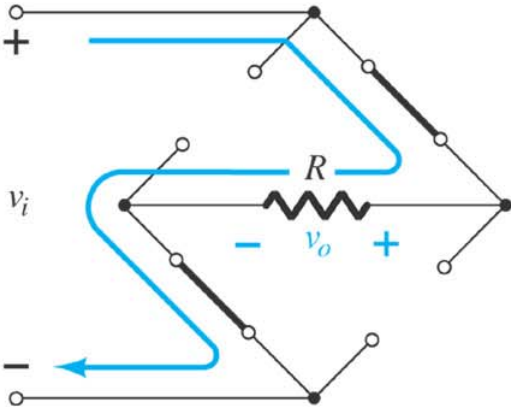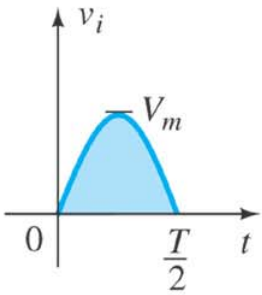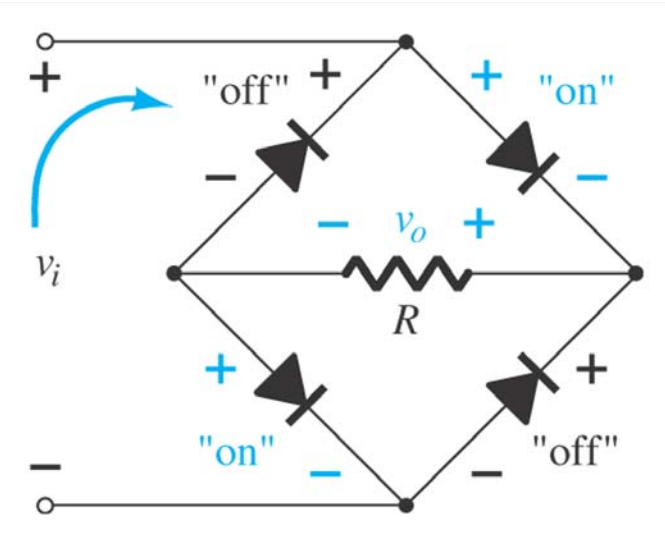



## Second half

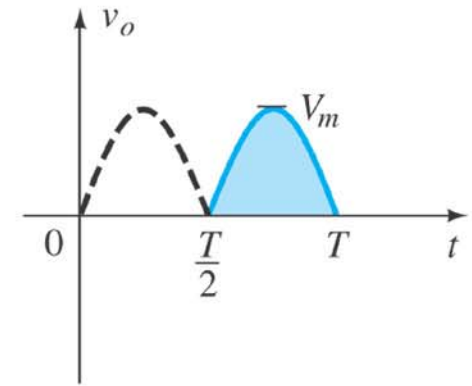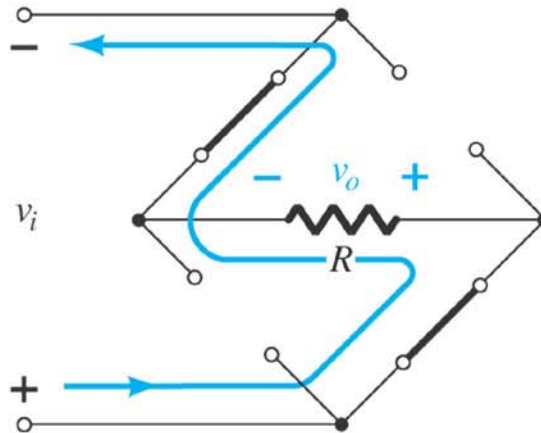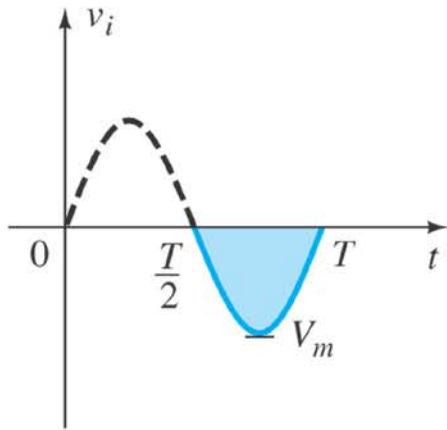

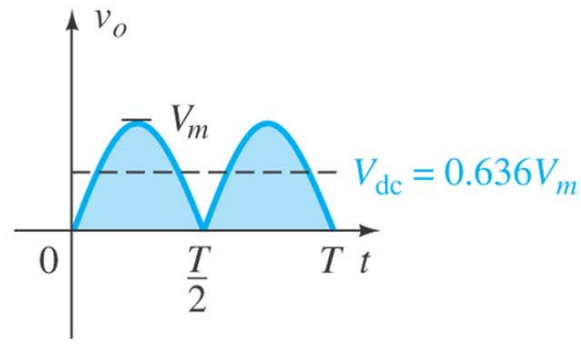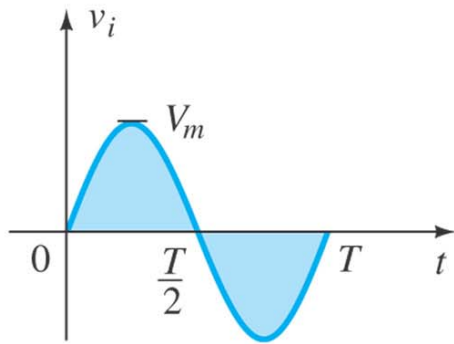

ideal

$$V_{dc} = 2(0.318V_m) = 0.636V_m$$

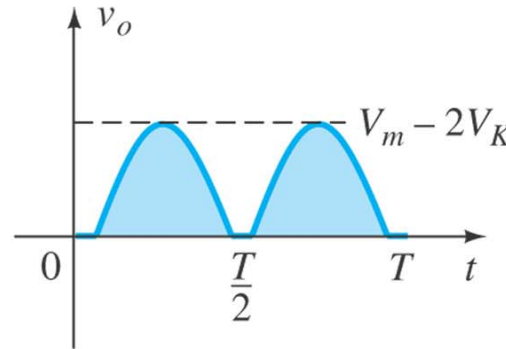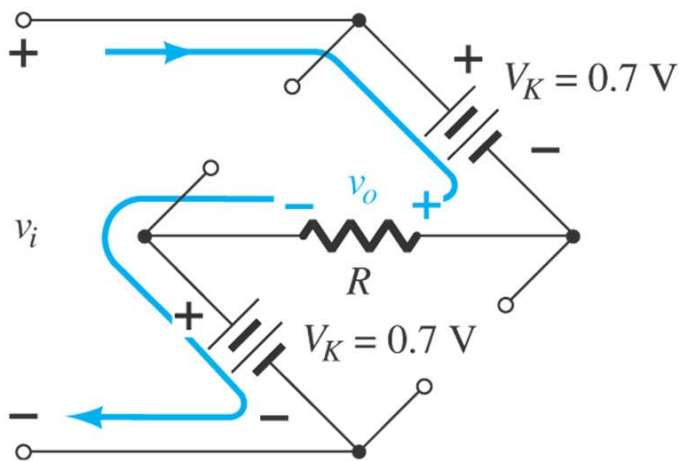


Practical diode

$$V_{dc} \cong 0.636(V_m - V_K)$$




# Diode Rating

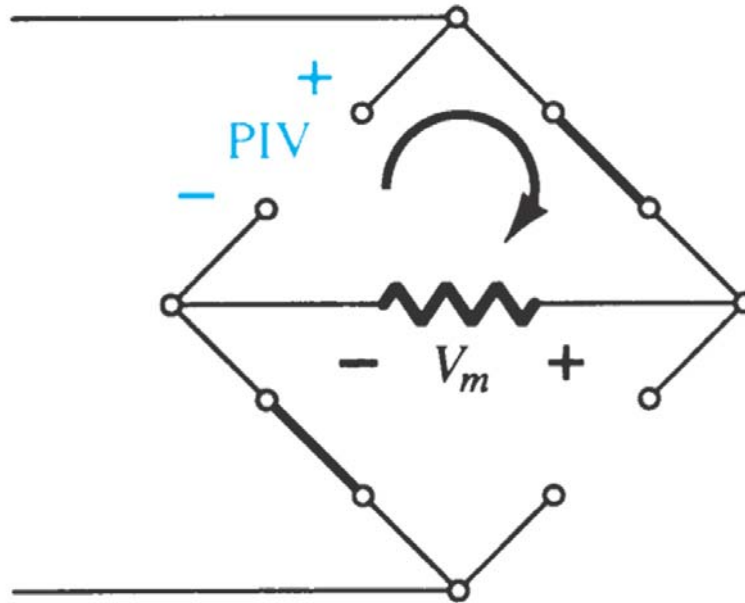


$$PIV \geq V_m$$

# Center-Tapped Transformer

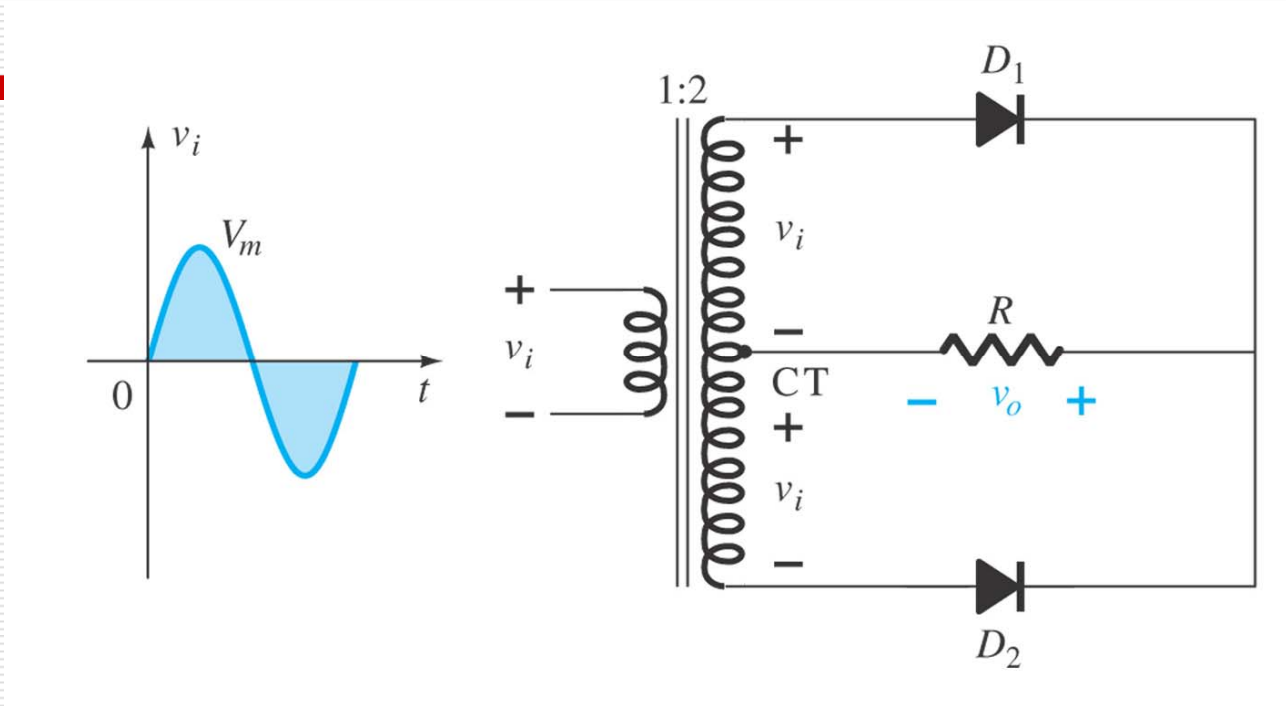


This is another way to get a full-wave rectification. However the  $PIV \geq 2 V_m$

# How this works.

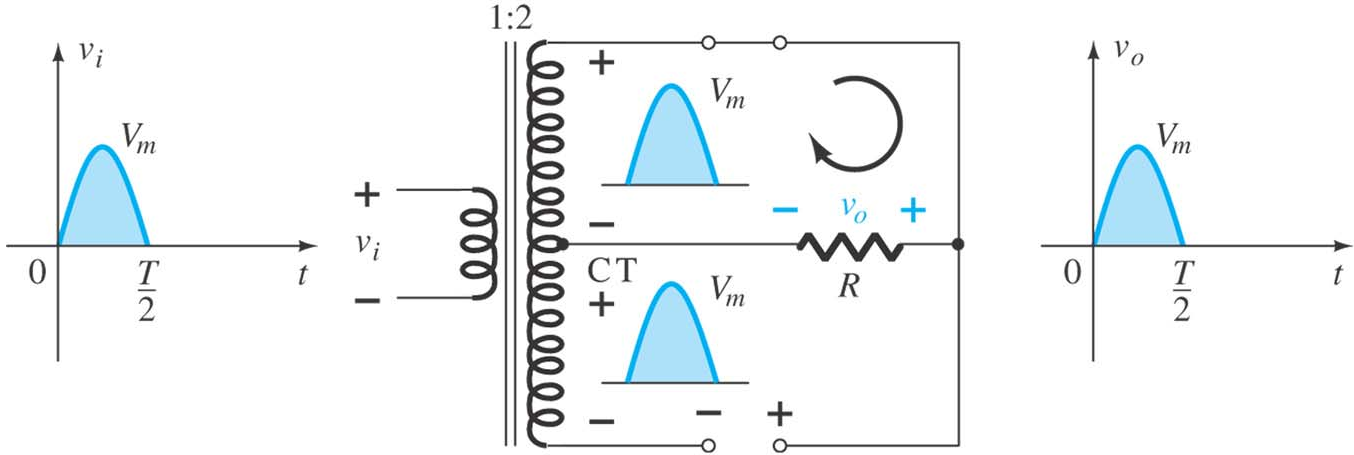


1<sup>st</sup> half

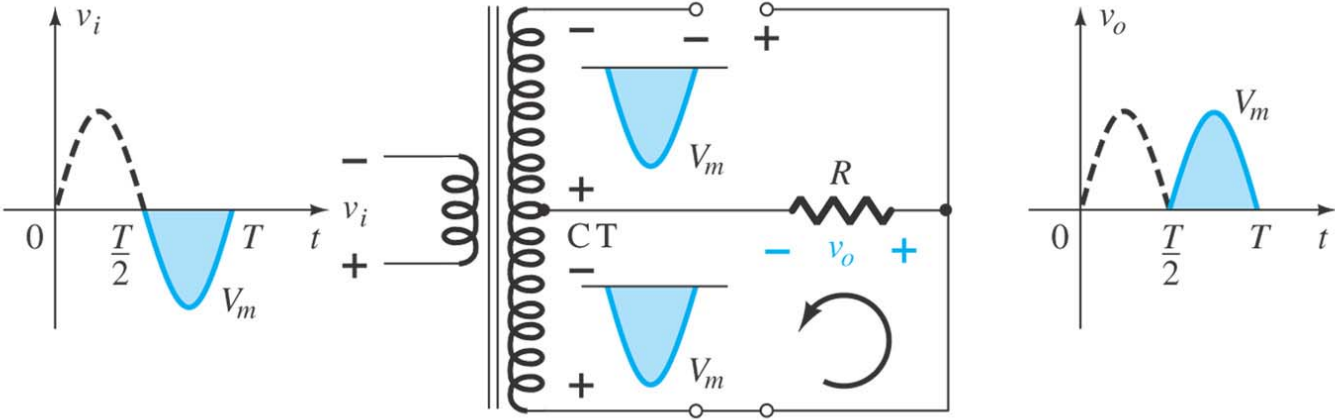

2<sup>nd</sup> half



PIV.

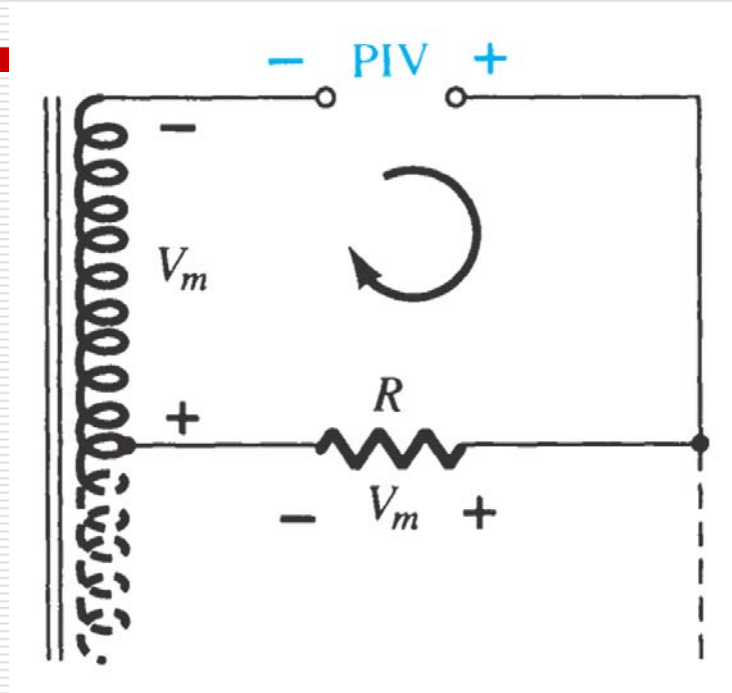



Apply KVL  $PIV = V_{secondary} + V_R = V_m + V_m = 2V_m$

Therefore  $PIV \geq 2V_m$

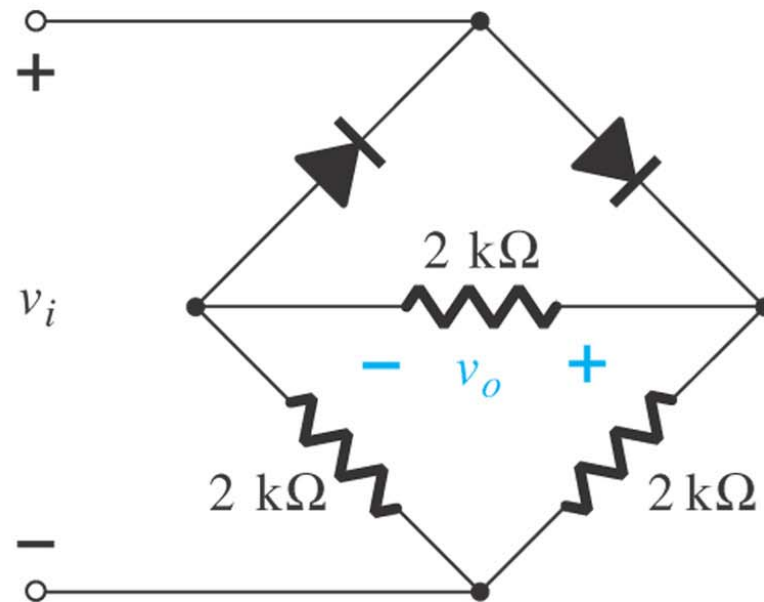
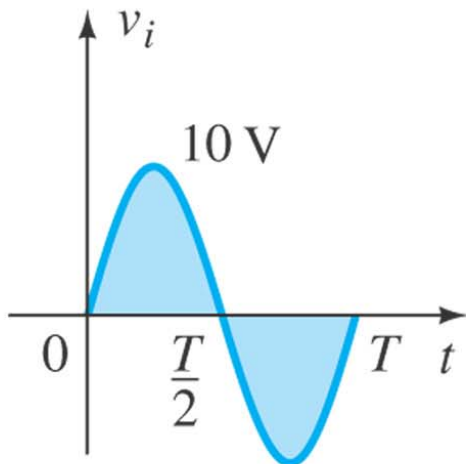
Determine the output for the network below and calculate the output dc level and the required PIV of each diode.



# Solution

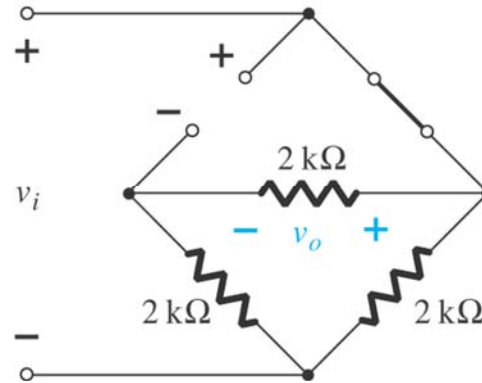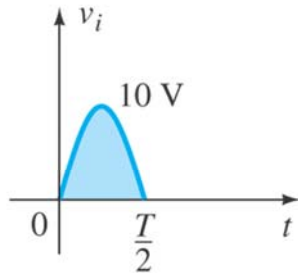

Equivalent circuit

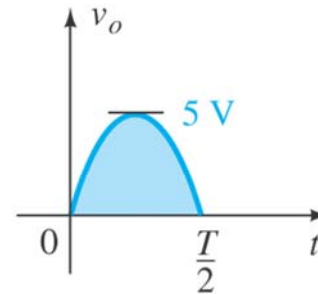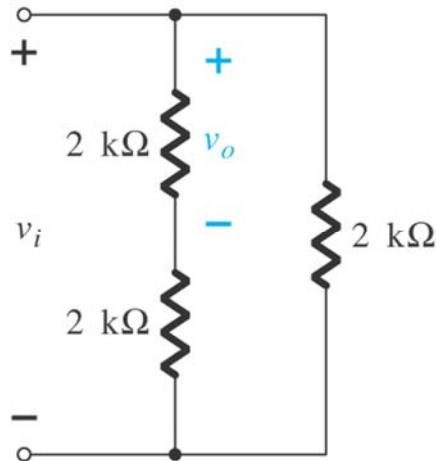

Redrawn network

From the 2<sup>nd</sup> Fig 
$$V_o = \frac{1}{2} V_i = \frac{1}{2} (10V) = 5V$$


Therefore 
$$V_{dc} = 0.636(V_o) = 0.6363(5V) = 3.18V$$

---

$$PIV \geq V_m = 5V$$
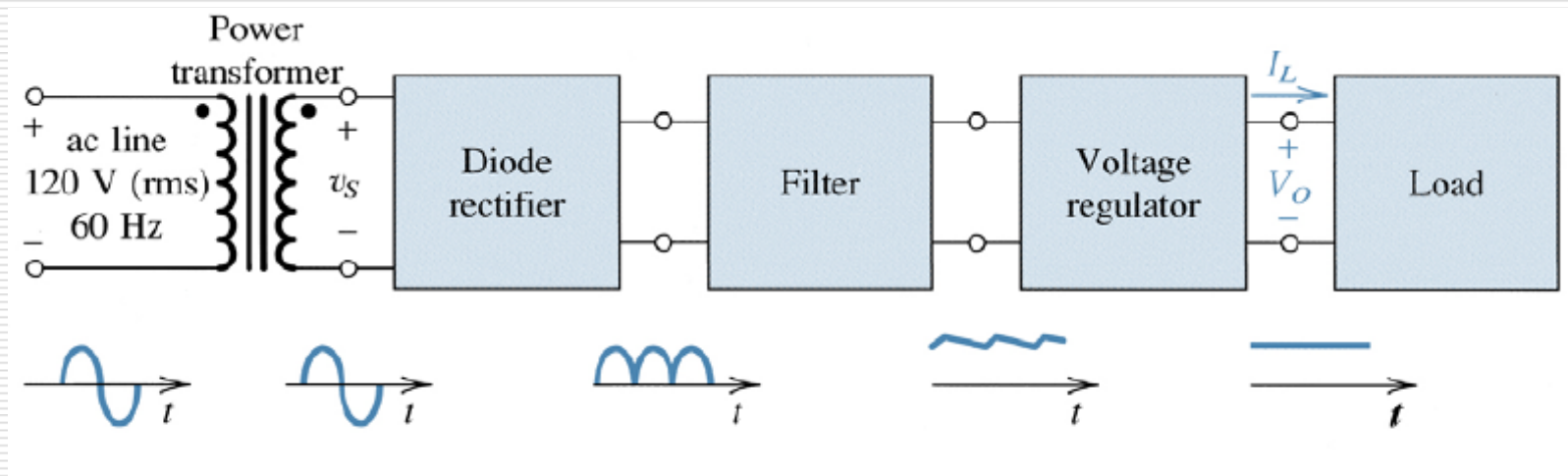
# Rectifier Circuits

- One of the most important applications of diodes is in the design of rectifier circuits. Used to convert an AC signal into a DC voltage used by most electronics.




# Simple Half-Wave Rectifier

- Only lets through positive voltages and rejects negative voltages

- This example assumes an ideal diode



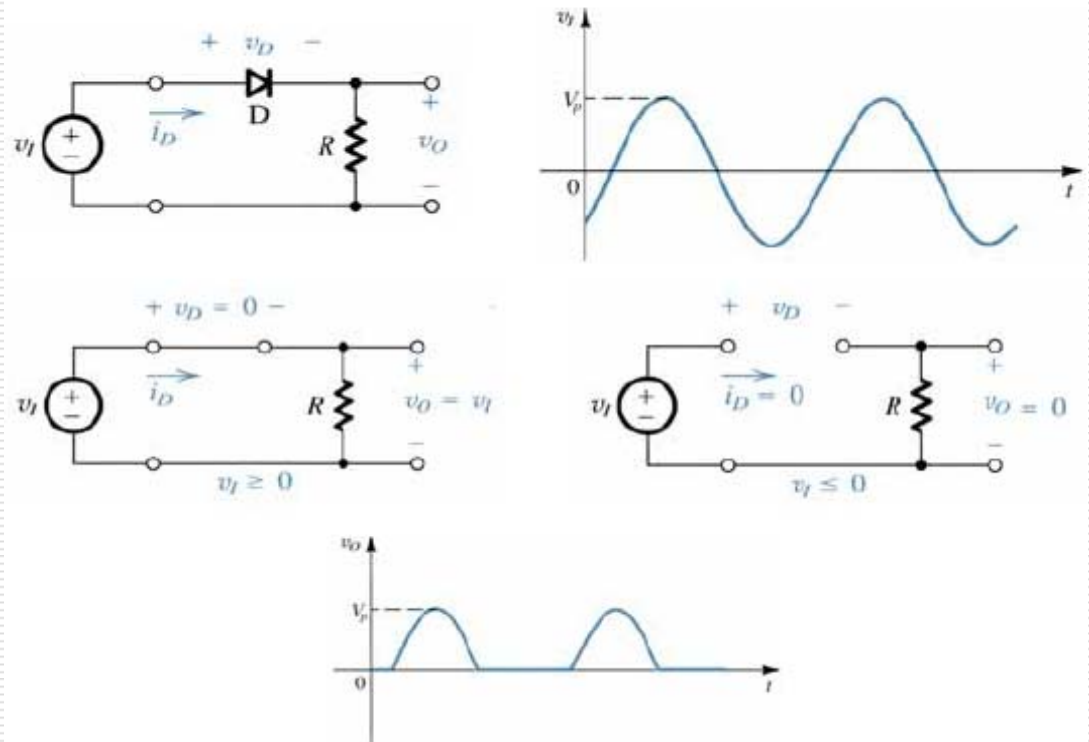
- What would the waveform look like if not an ideal diode?





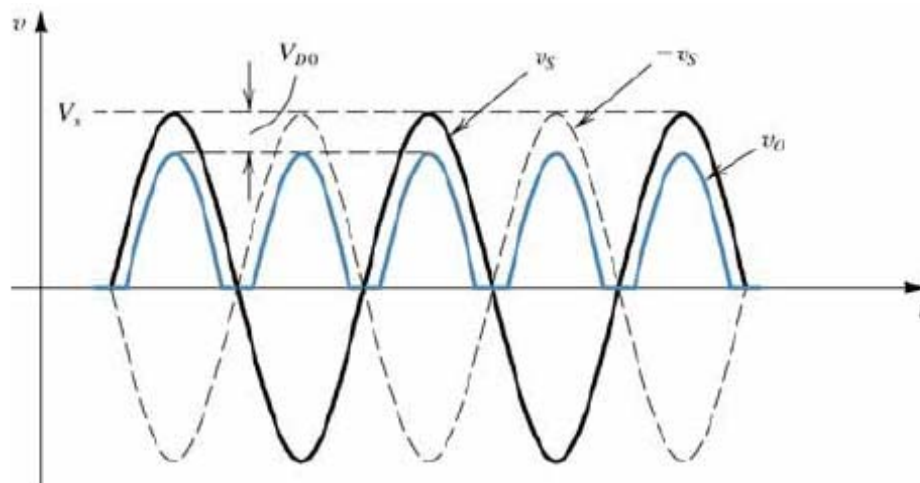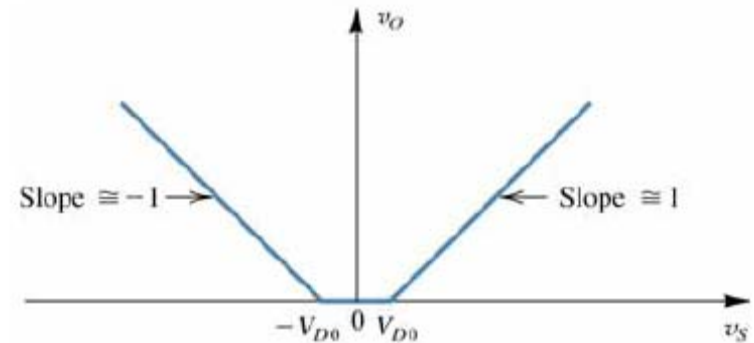
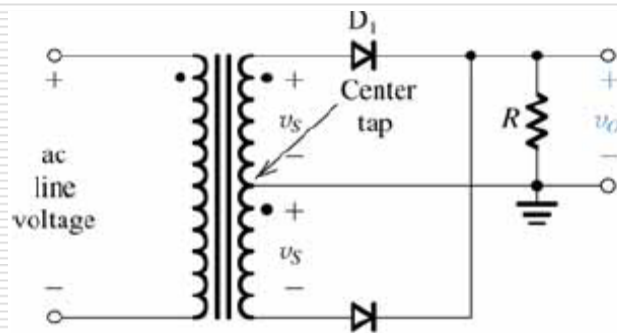
# Full-Wave Rectifier

- To utilize both halves of the input sinusoid use a center-tapped transformer...




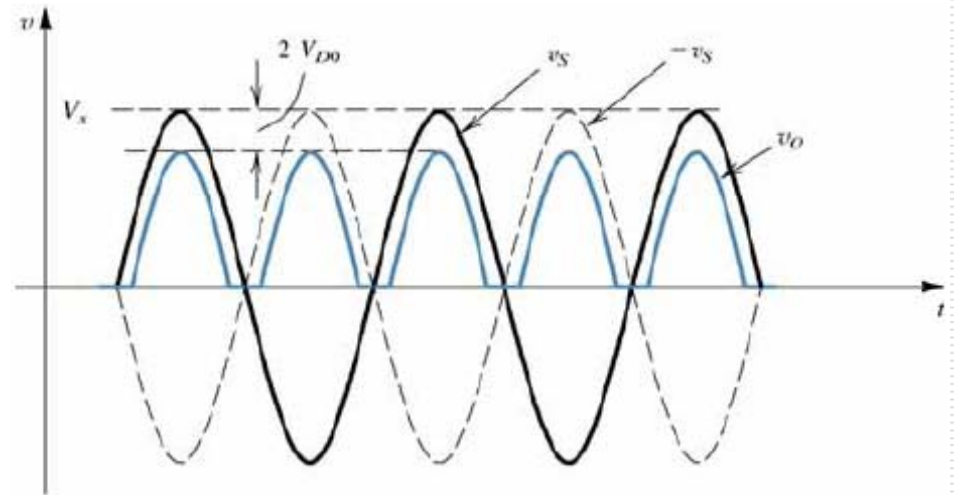
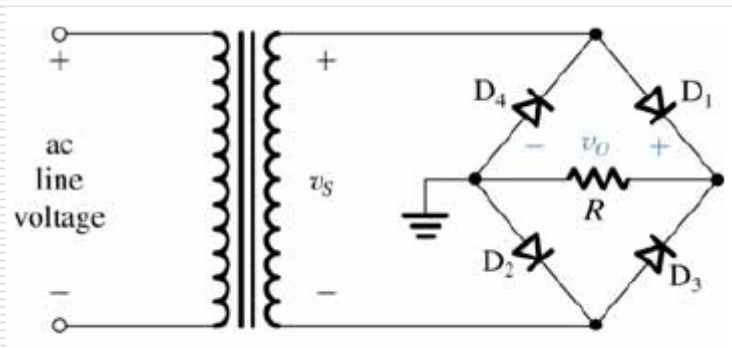
# Bridge Rectifier

- Looks like a Wheatstone bridge. Does not require a center-tapped transformer.




- Requires 2 additional diodes and voltage drop is double.

# Peak Rectifier (filtering)

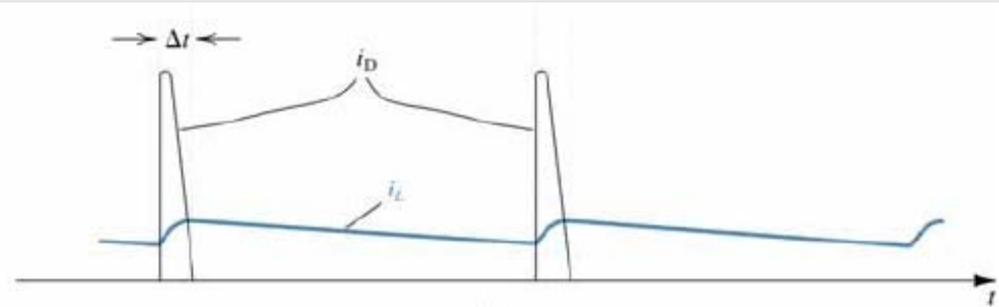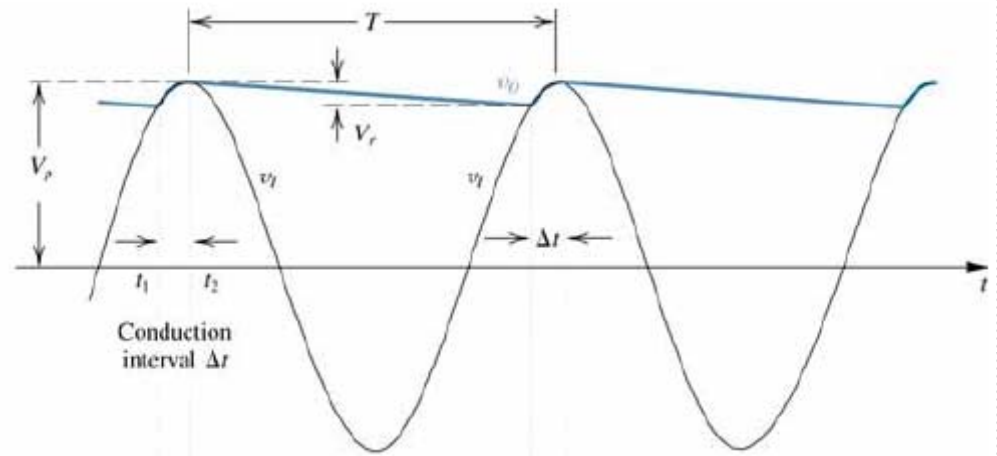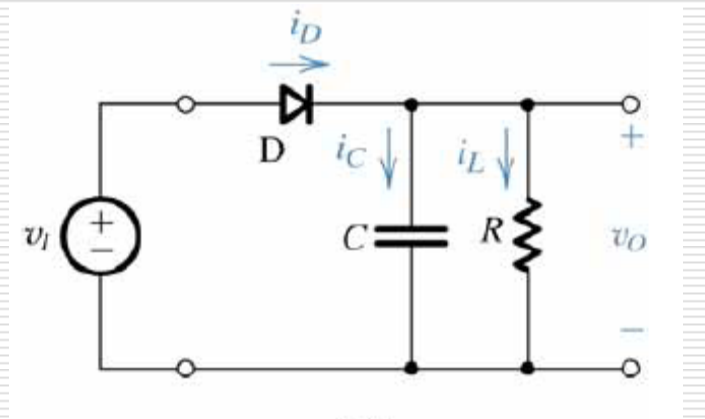

# BATTERY CHARGER

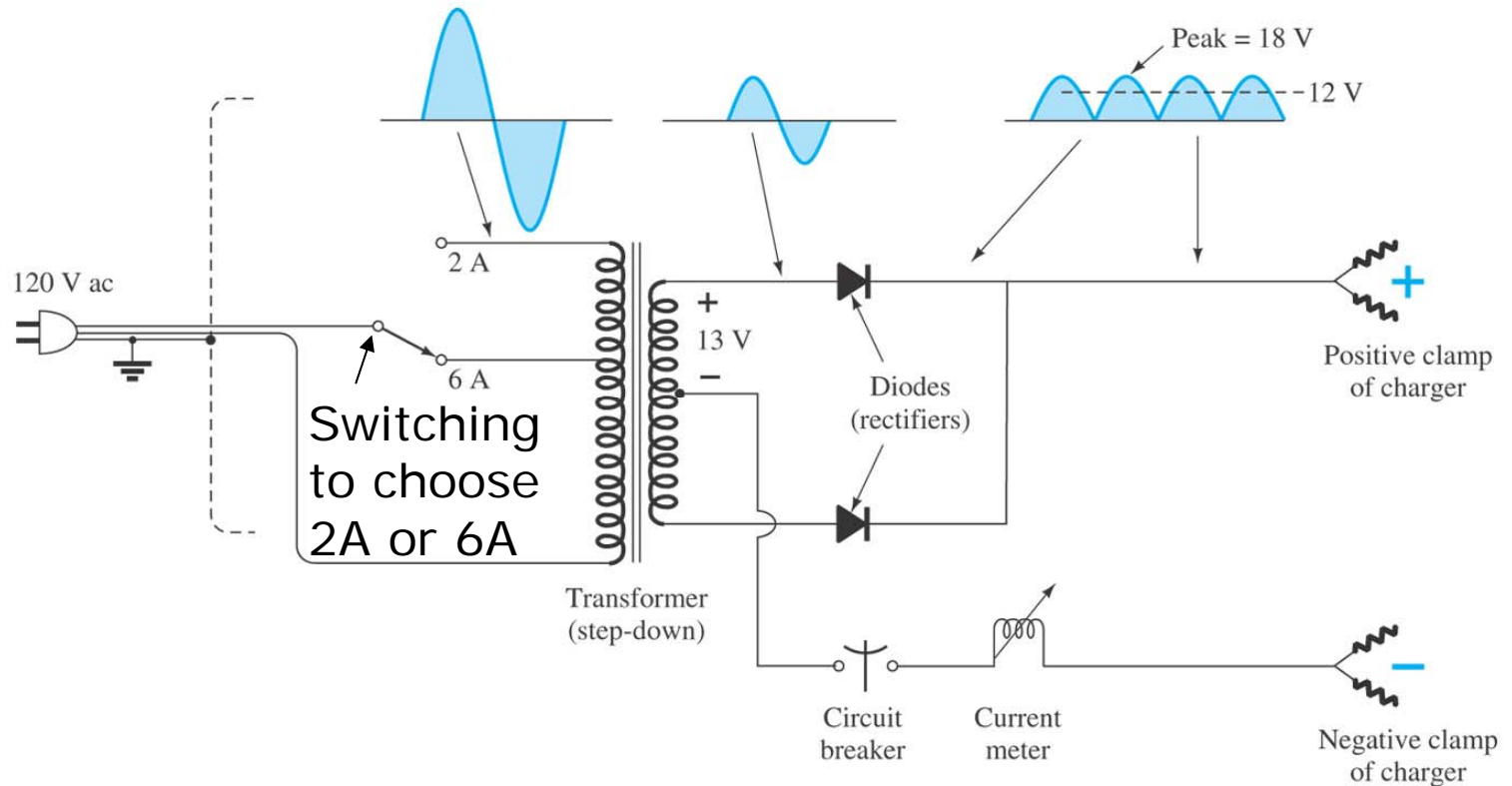


Diode rectifier to change the sinusoidal wave from transformer to develop the dc current. Some charger may have filtering and regulator to improve dc level. Transformer is to step down the main voltage to required one.

# CLIPPERS.

Clippers are networks that employ diodes to “clip” away a portion of an input signal without distorting the remaining part of the applied waveform. The simplest form of diode clipper is one resistor and a diode similar like half-wave rectifier. There are two categories: **series** and **parallel**

## Series clipper (diode in series)


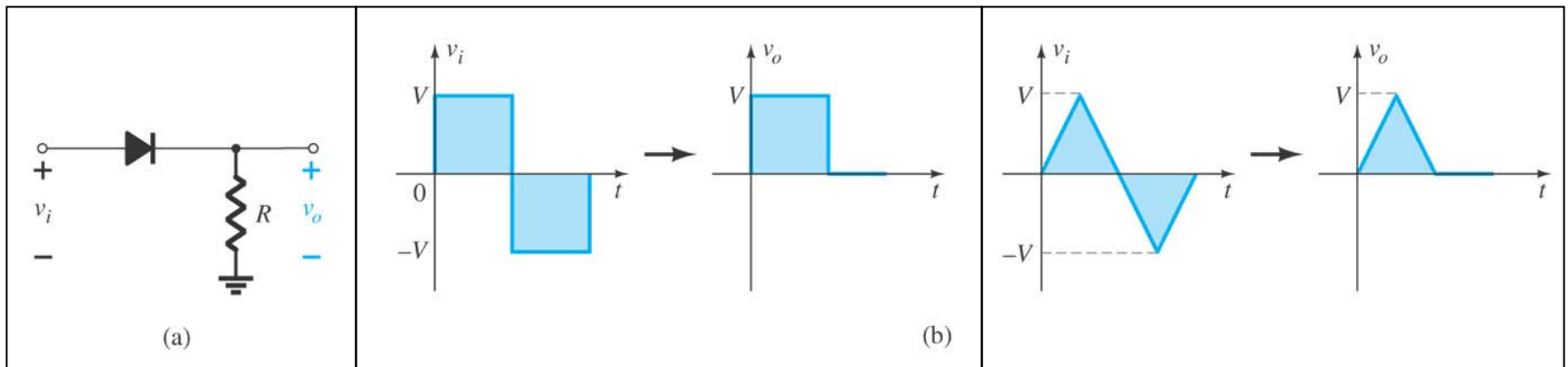


Circuit


Squared waveform

Triangular waveform

# CLIPPER WITH DC SUPPLY.

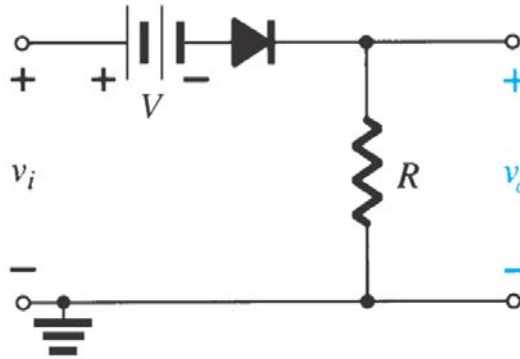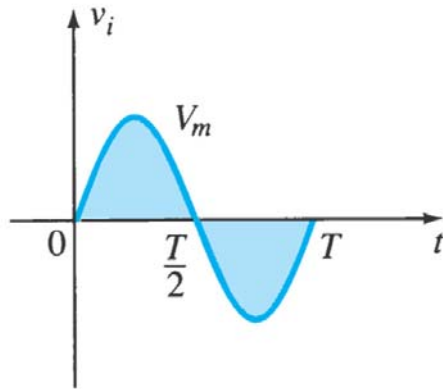

Circuit

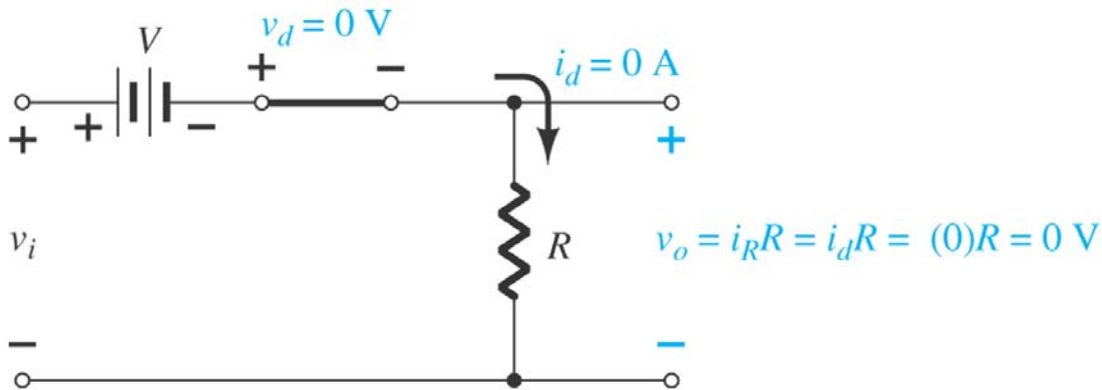

Analysis

First where the output is?

In this case it is at R

---

Secondly see any dc supply that oppose the input signal. The system will be “off” state until the input voltage is greater than the diode and the opposed voltage

$$V_m = V_{dc} + V_{diode}$$

Output  $V_o = V_m - V_{dc} - V_{diode}$



For ideal case  $V_o = V_m - V_{dc}$

At transition state

$$V_o = I_R R = (0)R = 0V$$


---

## Analysis for ideal diode

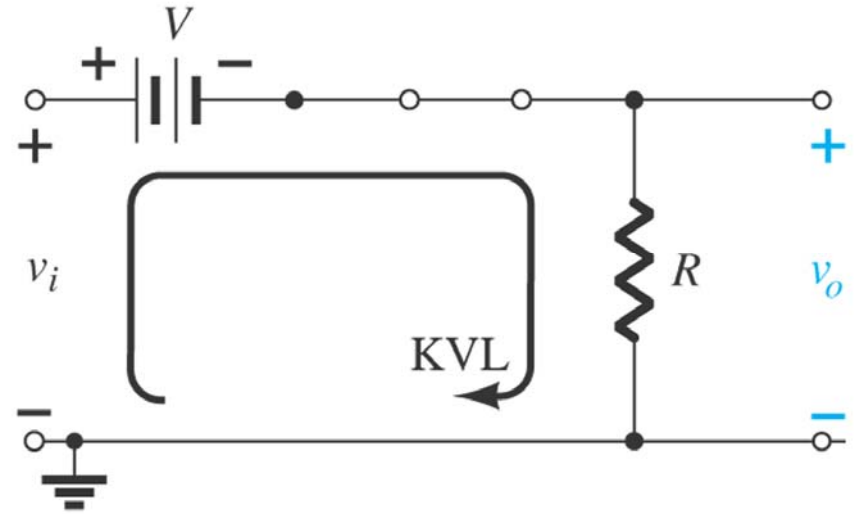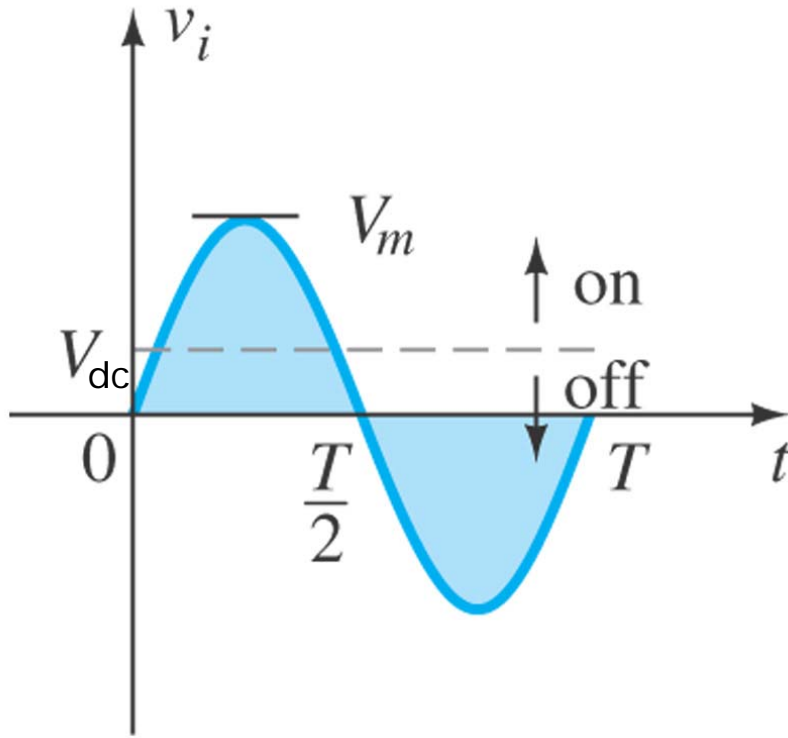




After conduction

$$V_o = V_m - V_{dc}$$

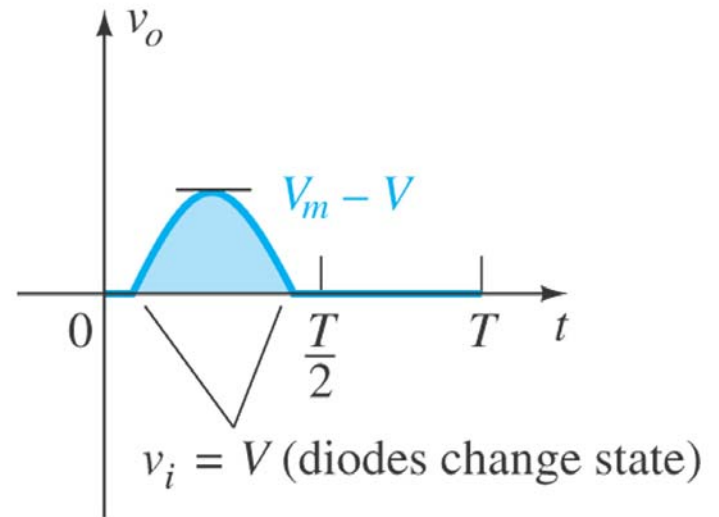



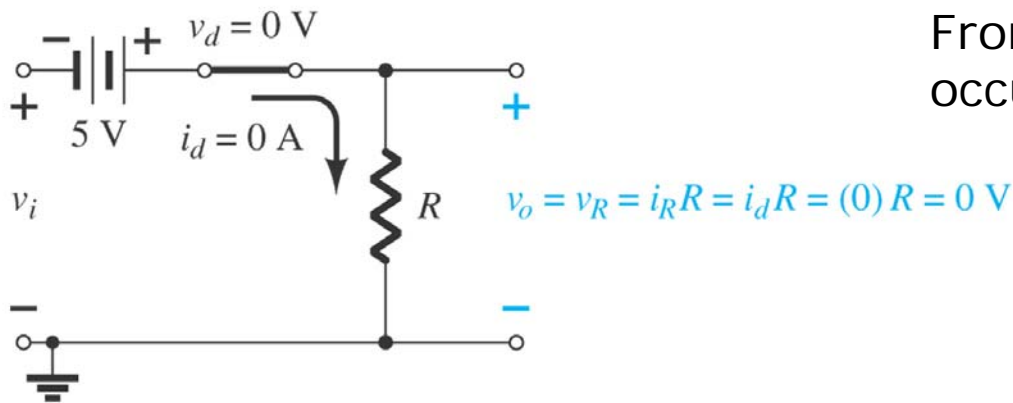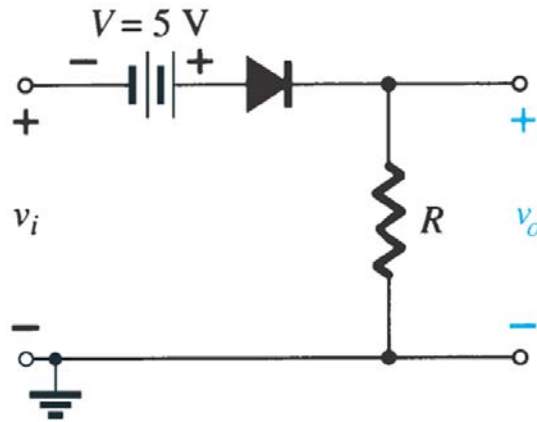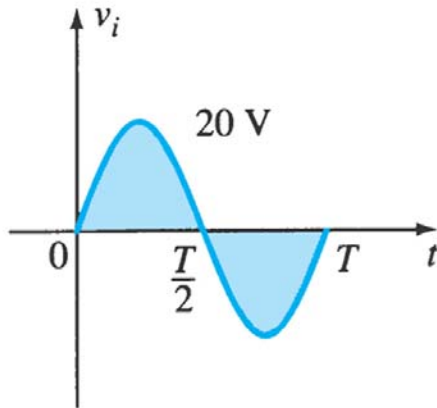
# Determine the output waveform for the sinusoidal input



From Fig. transition state will occur at

$$V_i + 5V = 0V$$

$$V_i = -5V$$

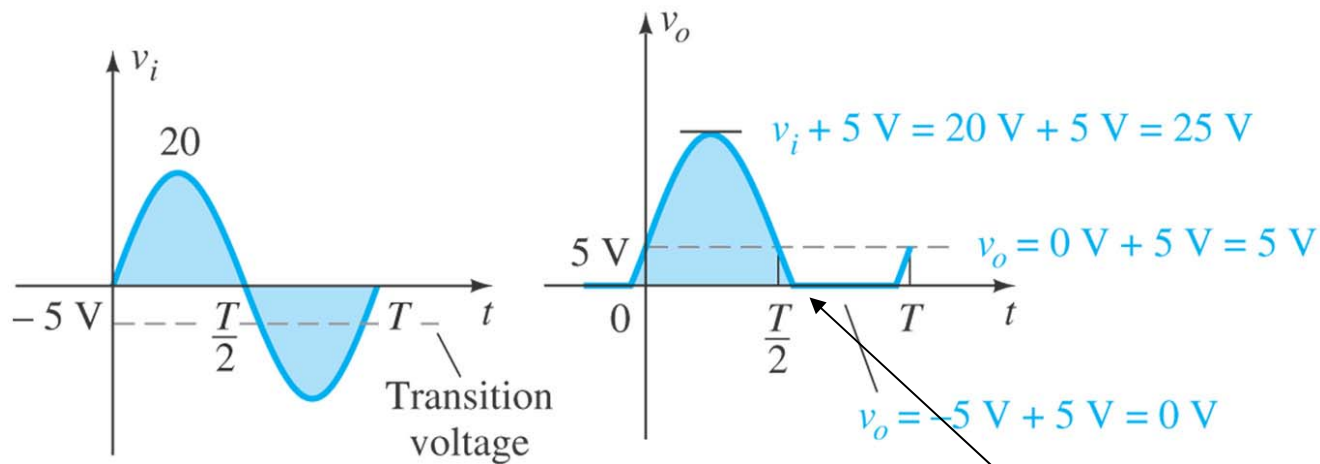

Transition at  $-5\text{V}$



After transition using KVL, the peak is

$$V_o = V_m + 5\text{V}$$

$$V_o = 20\text{V} + 5\text{V} = 25\text{V}$$


The waveform is seen to be off-set by  $5\text{V}$

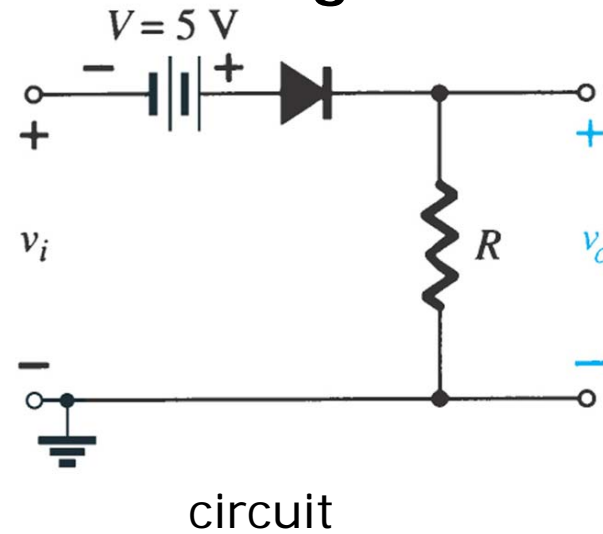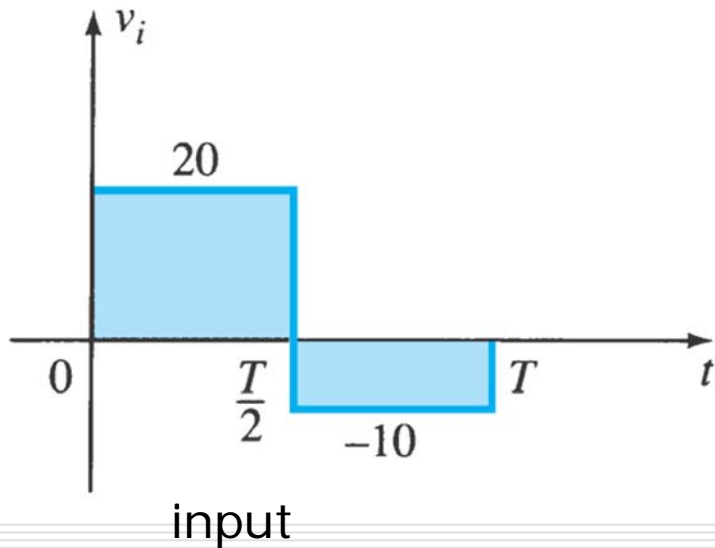Determine the output waveform for the square wave input as shown in the Fig.






For  $0 \rightarrow T/2$        $V_o = 20V + 5V = 25V$

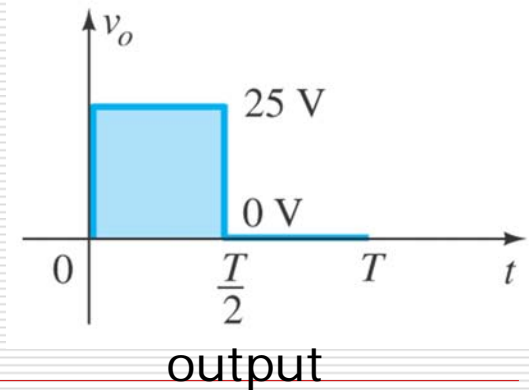For  $T/2 \rightarrow T$        $V_o = 0V$







# Parallel Clipper

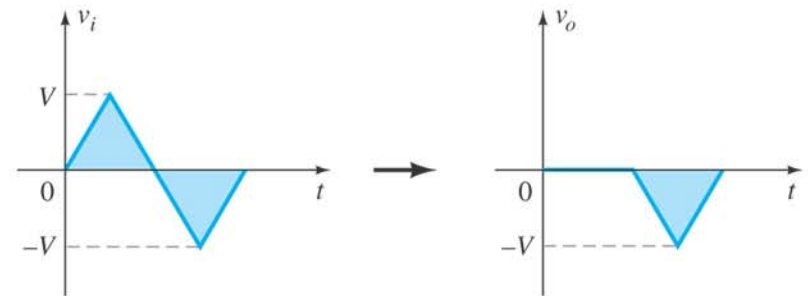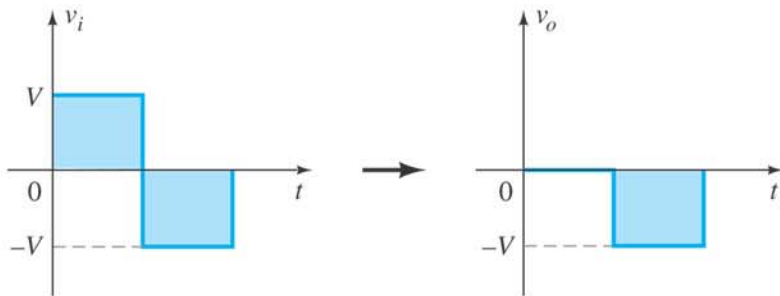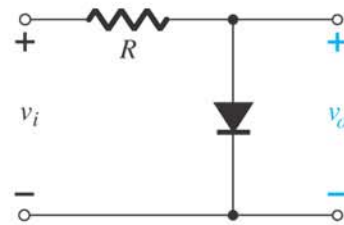

\*Here, the diode is shunted in the circuit

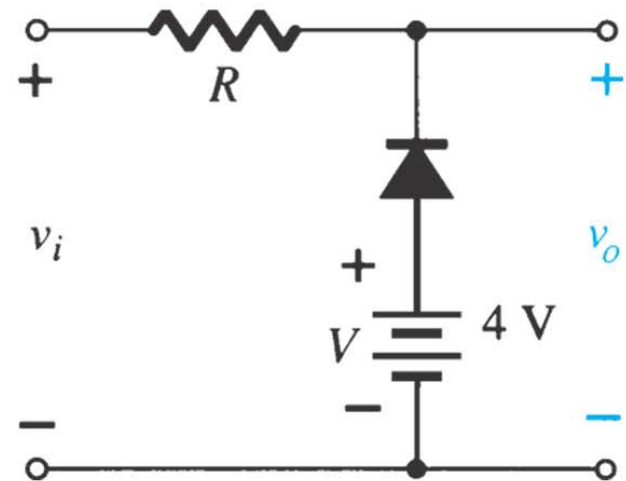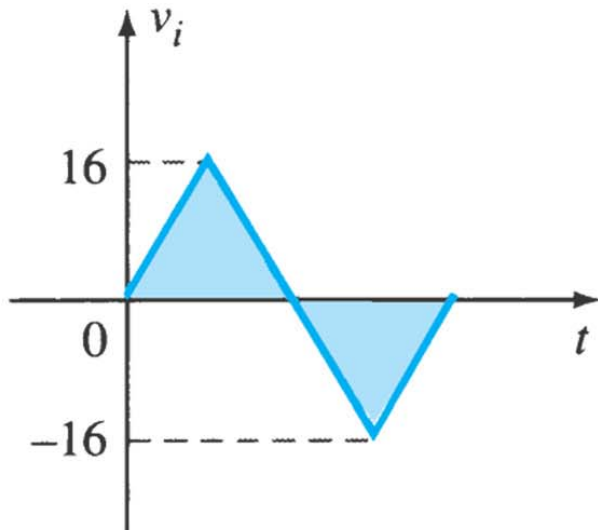Determine  $V_o$  for the following network



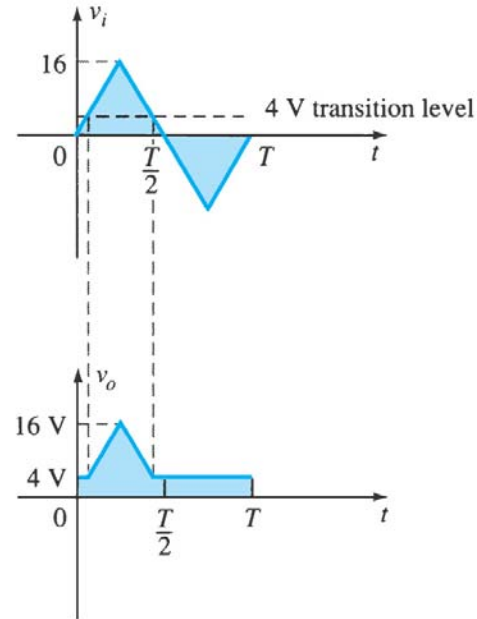
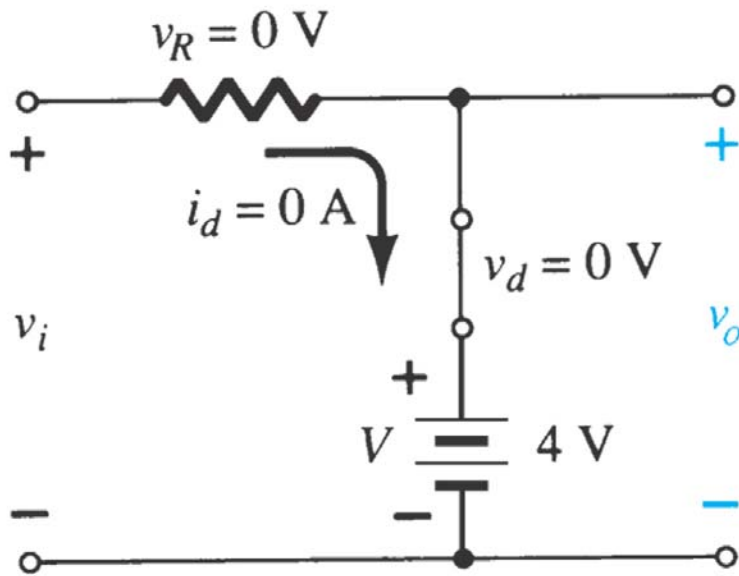


The transition level will be at  $V_i = 0$  since  $i_d = 0$

When  $V_i$  more than  $V = 4 \text{ V}$ ,  $V_o$  will follow  $V_i$

When  $V_i$  less than  $V = 4 \text{ V}$ ,  $V_o$  will stay at  $V = 4 \text{ V}$

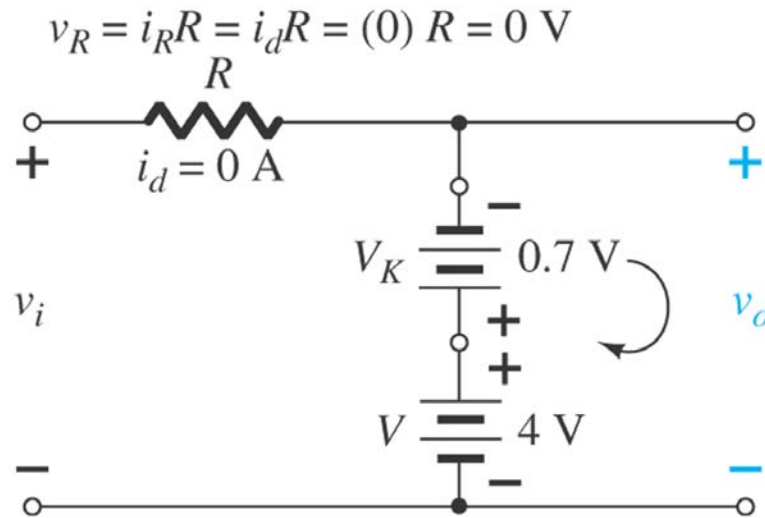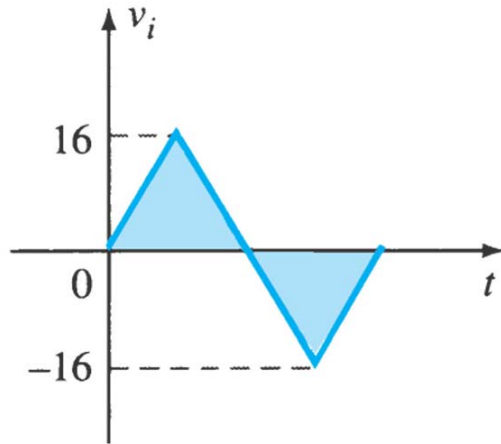
If the diode has  $V_K=0.7V$ , find  $V_o$ .



Applying KVL at transition will be

$$V_i + V_K - V = 0V$$

$$V_i = V - V_K = 4V - 0.7V = 3.3V$$

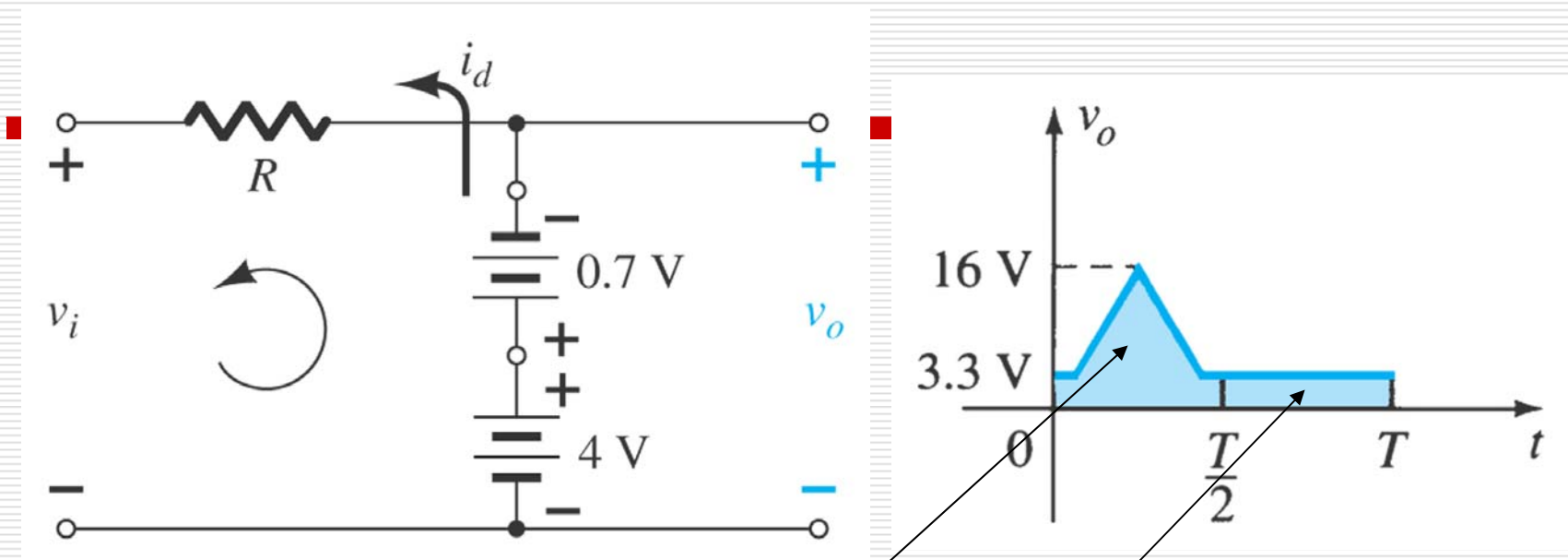

When  $V_i > 3.3\text{V}$  then  $V_o = V_i$


When  $V_i < 3.3\text{V}$  then

$$V_o = 4\text{V} - 0.7\text{V} = 3.3\text{V}$$




### Simple Series Clippers (Ideal Diodes)



POSITIVE

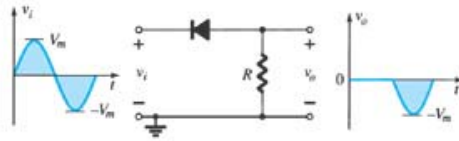



NEGATIVE

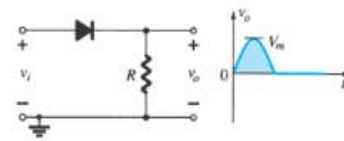
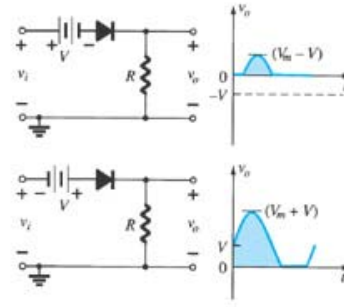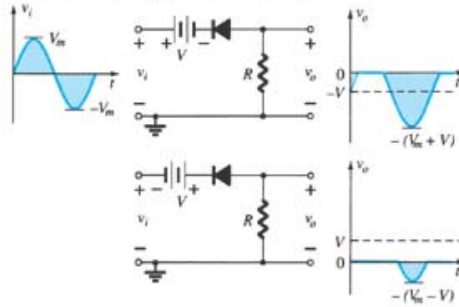
### Biased Series Clippers (Ideal Diodes)


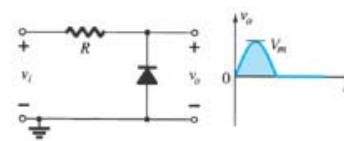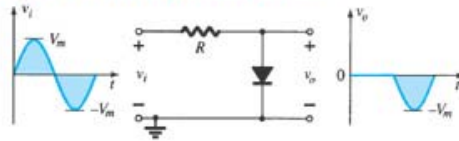
### Simple Parallel Clippers (Ideal Diodes)



### Biased Parallel Clippers (Ideal Diodes)

