
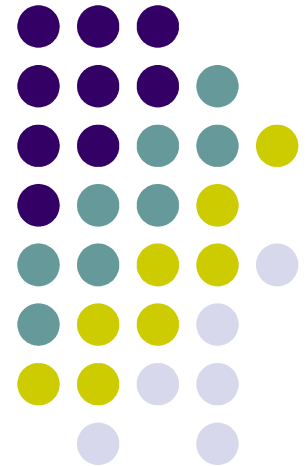


Filter Circuit


- ✓ First Order
- ✓ Second Order

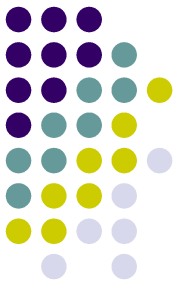


Ideal frequency filter




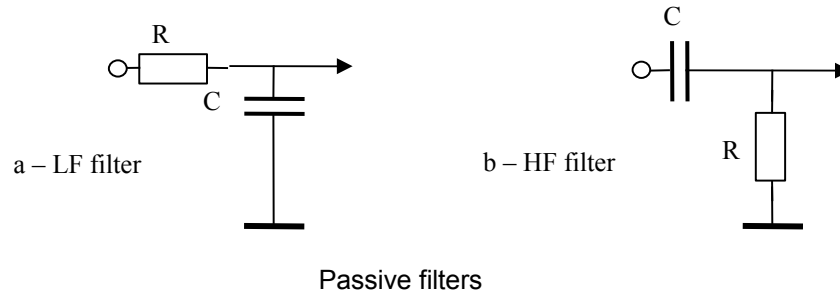- is a device having a constant and nonzero transfer characteristic within a specific frequency range (called a filter passband), and a zero one in the rest range (called a suppressed band).



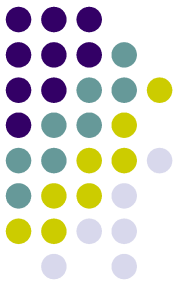

1st Order active filter..

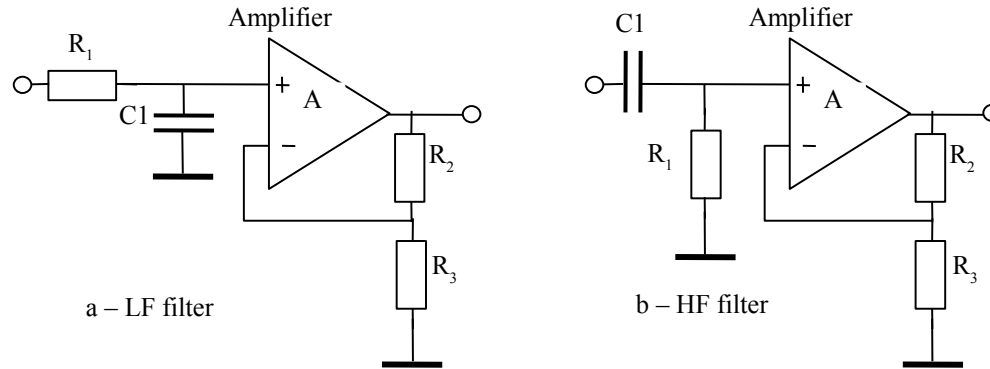

a – LF filter


b – HF filter

Elementary first-order active filters with an impedance converter


$$A(p) = \frac{A_0}{1 + a_1 p}$$

$$A(p) = \frac{(1 + R_2/R_3)}{1 + p R_1 \cdot C_1}$$

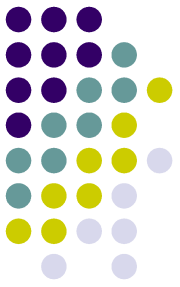To obtain a HF filter, it is necessary to replace p with $1/p$ in the expression. In the circuit it will be enough to interchange R_1 and C_1



1st Order active filter..


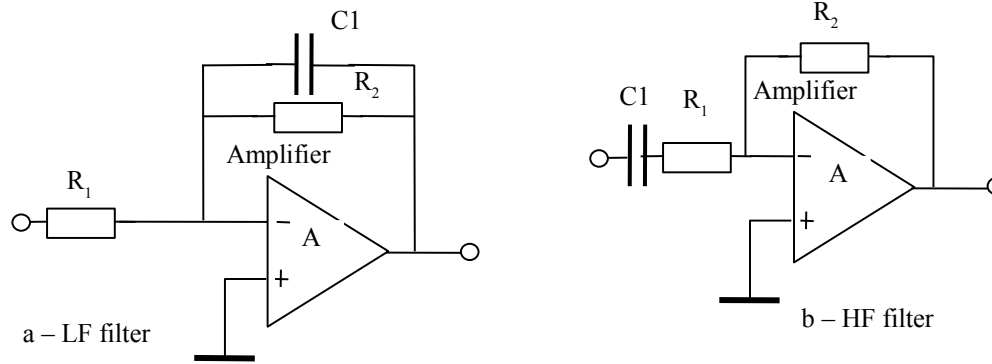


First-order active filters with a frequency-dependent feedback

$$A(p) = \frac{A_0}{1 + a_1 p}$$

$$A(p) = -\frac{R_2/R_1}{1 + pR_2 \cdot C_1}$$



Negative Impedance Converter

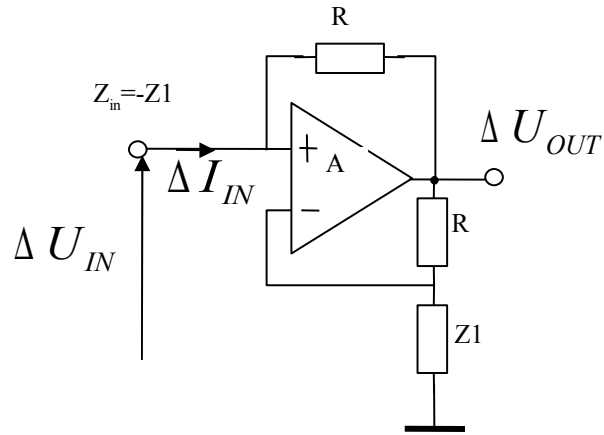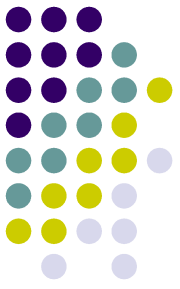

Negative impedance converter Circuit

If Z_1 is capacitor. $Z=j/\omega C$



Gyrator

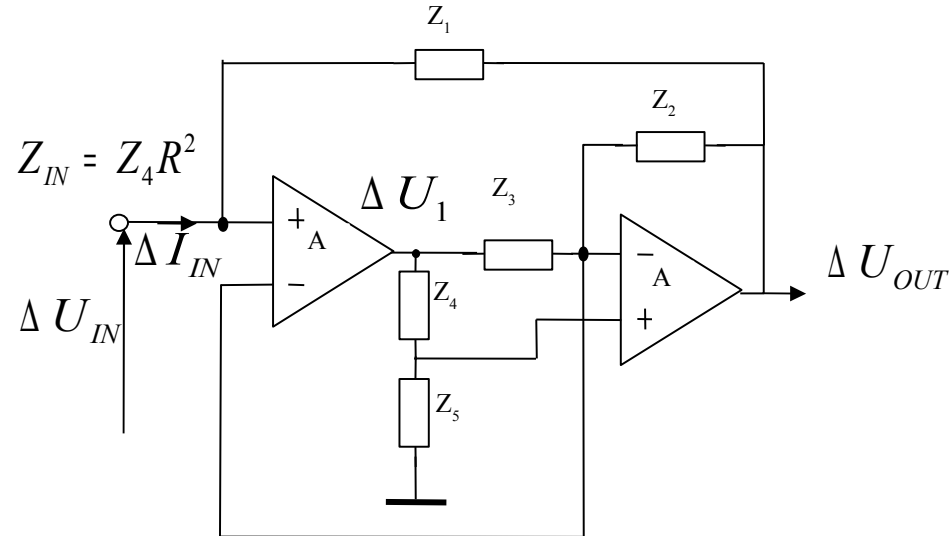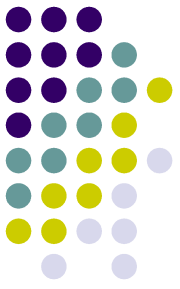



$$\Delta U_1 = \frac{\Delta U_{IN}(Z_4 + Z_5)}{Z_5}$$

$$\frac{\Delta U_1 - \Delta U_{IN}}{Z_3} = \frac{\Delta U_{IN} - \Delta U_{OUT}}{Z_2}$$

Gyrator

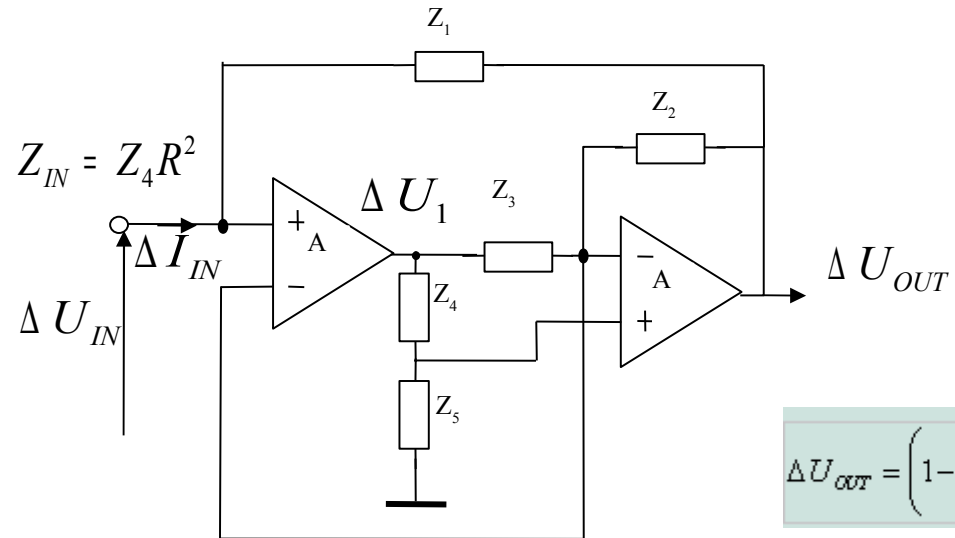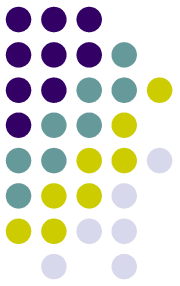



Gyrator

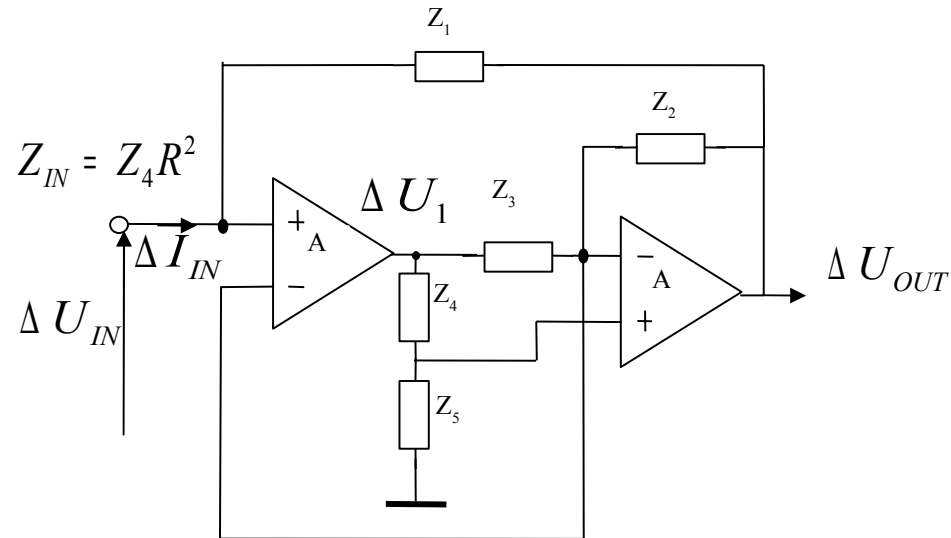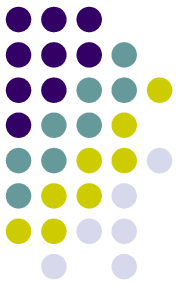

$$\Delta I_{IN} = \frac{\Delta U_{IN} - \Delta U_{IN} \left(1 - \frac{Z_4 Z_2}{Z_3 Z_5}\right)}{Z_1} = \frac{Z_4 Z_2}{Z_1 Z_3 Z_5} \Delta U_{IN}$$

$$Z_{IN} = \frac{\Delta U_{IN}}{\Delta I_{IN}} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$

2nd order Filter

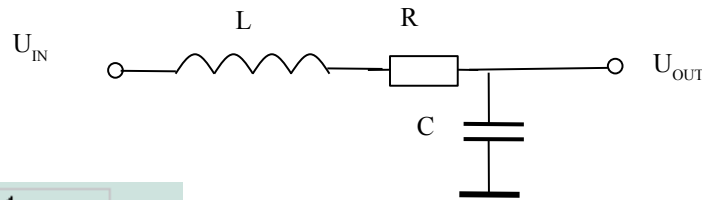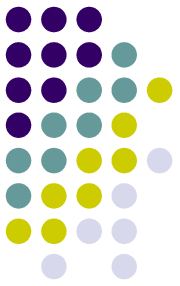

$$A(p) = \frac{A_0}{1 + a_1 p + a_2 p^2}$$

$$A(p) = \frac{1}{1 + \omega_c R C p + \omega_c^2 L C p^2}$$

$$R = \frac{a_1}{2\pi f_c C}$$

$$L = \frac{a_2}{4\pi^2 f_c^2 C}$$

IF $f_c=10\text{Hz}$, $C=10\mu\text{F}$, then $R=2.25\text{K}\Omega$, $L=25.3\text{H}$

2nd order Filter

