

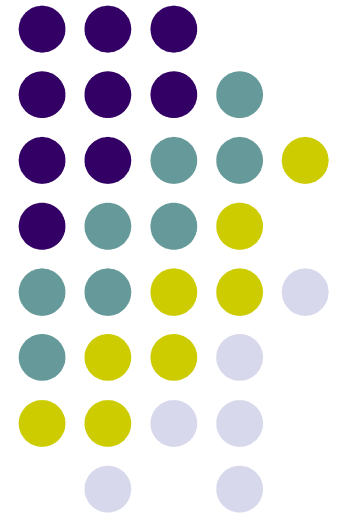


# Oscillator

- ✓ Basic
- ✓ Type of Oscillator

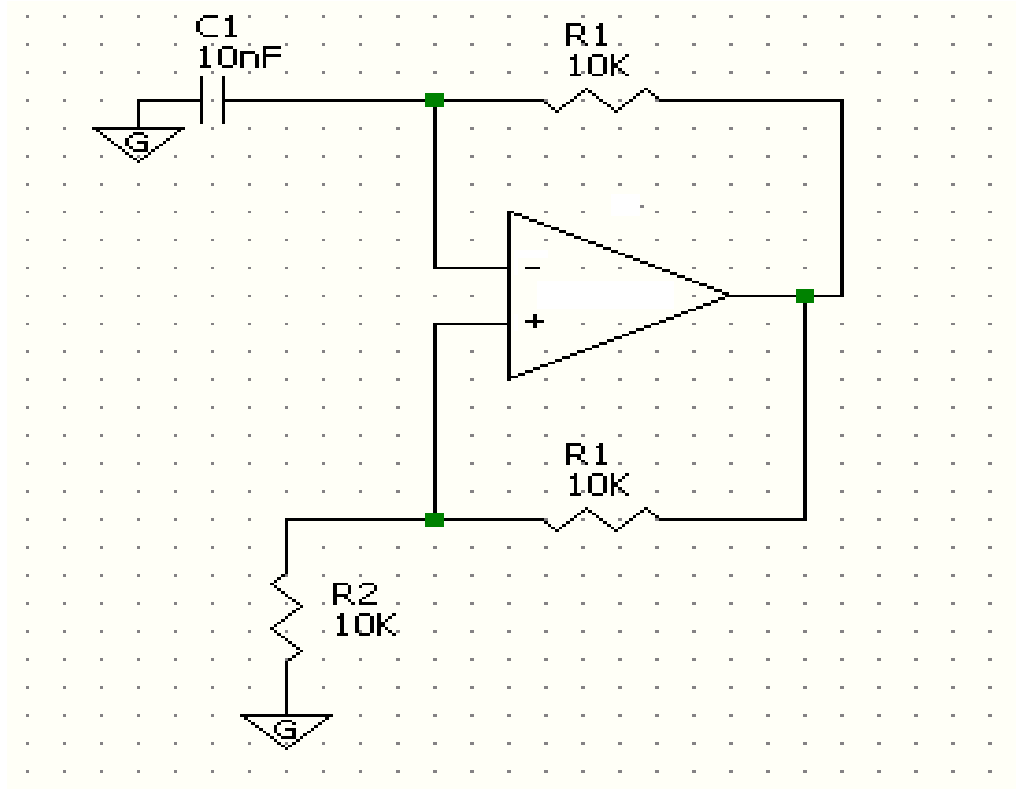

# RC Oscillator

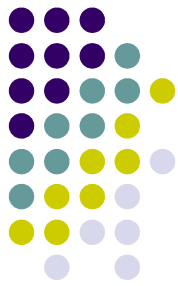


$$T=2.2RC$$

# Wein Bridge Oscillator





$$f = 1/2\pi RC$$

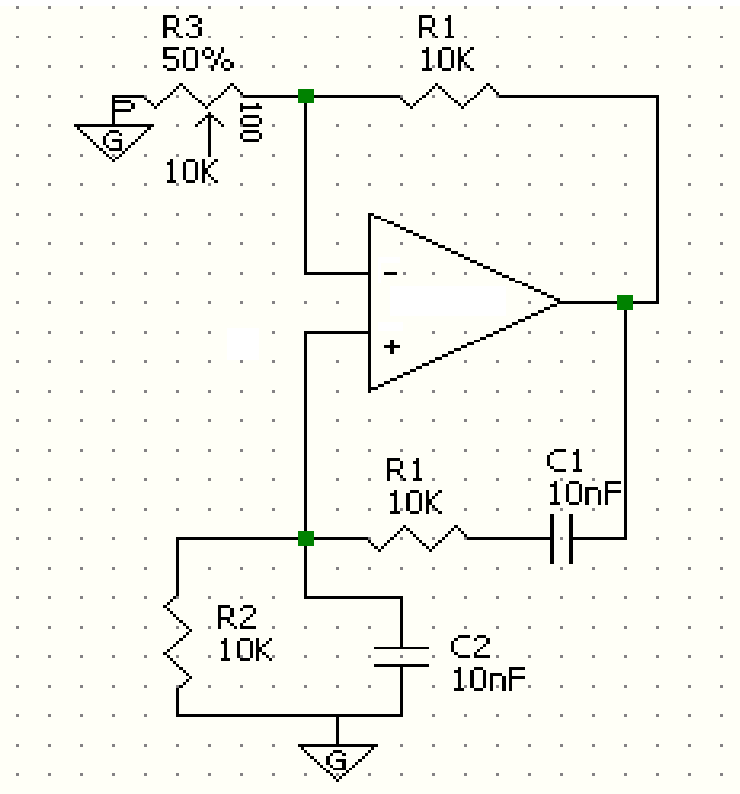

- Positive Feedback

# CMOS Inverter Oscillator

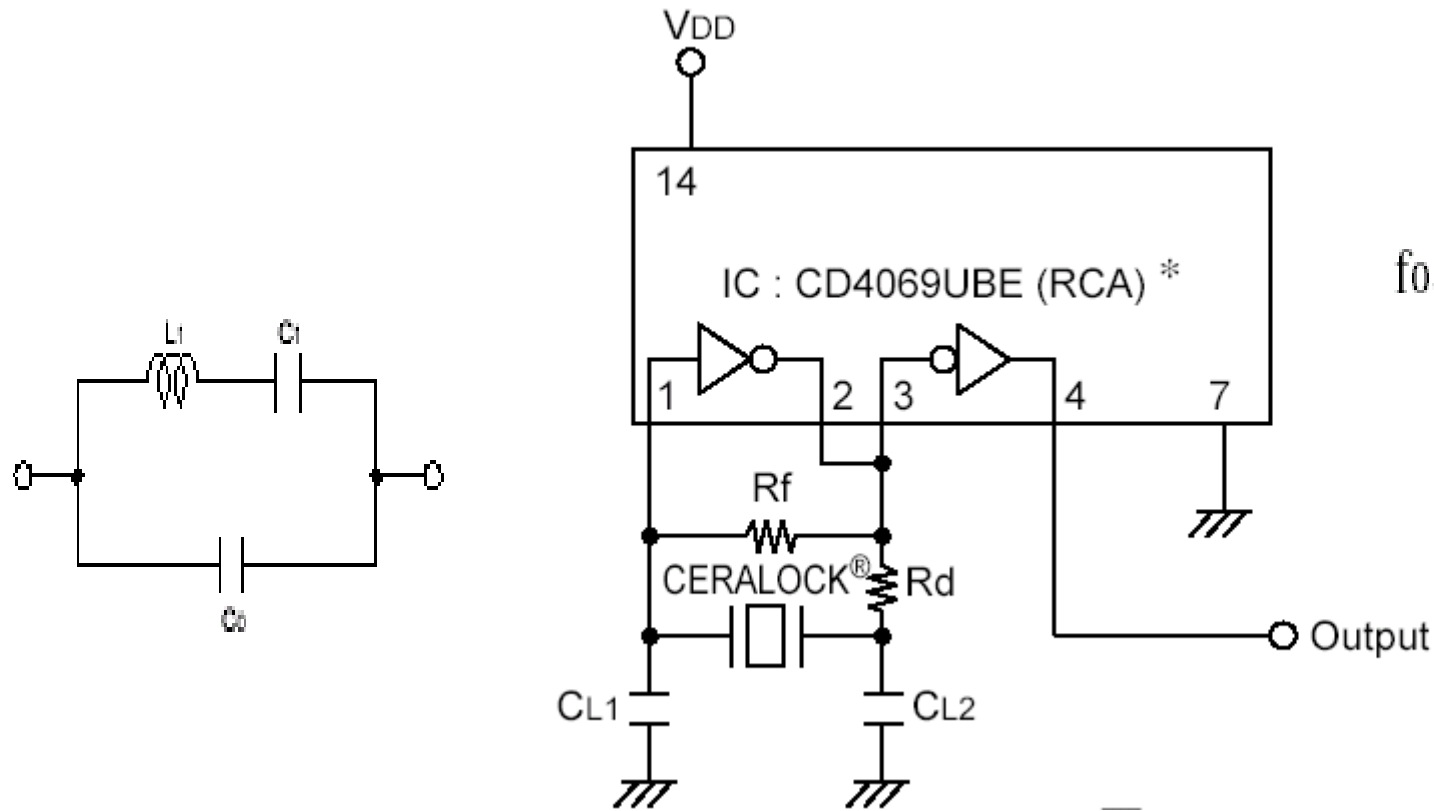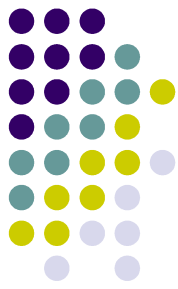


$$f_{osc.} = F_r \sqrt{1 + \frac{C_1}{C_0 + C_L}}$$

$$C_L = \frac{C_{L1} \cdot C_{L2}}{C_{L1} + C_{L2}}$$

- The feedback resistance  $R_f$  provides negative feedback around the inverter in order to put it in the linear region, so the oscillation will start, when power is applied.



# Ring Oscillator

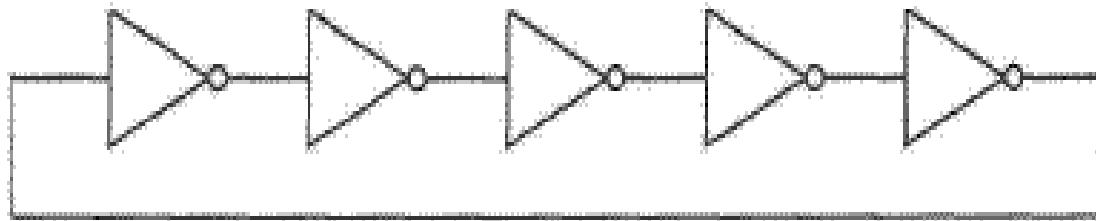

$$f = \frac{1}{T} = \frac{1}{2 \cdot n \cdot \tau_{INV}}$$



- Every half-period the signal moves at a circle motion with inversion. For example, let us consider the first inverter output changing by 1. This change will be transferred through all five inverters in a time  $T/2$ , when the first inverter output will change to 0; then in a time  $T/2$  the first inverter output will change back to 1 and so on.

# Negative Resistance Oscillator

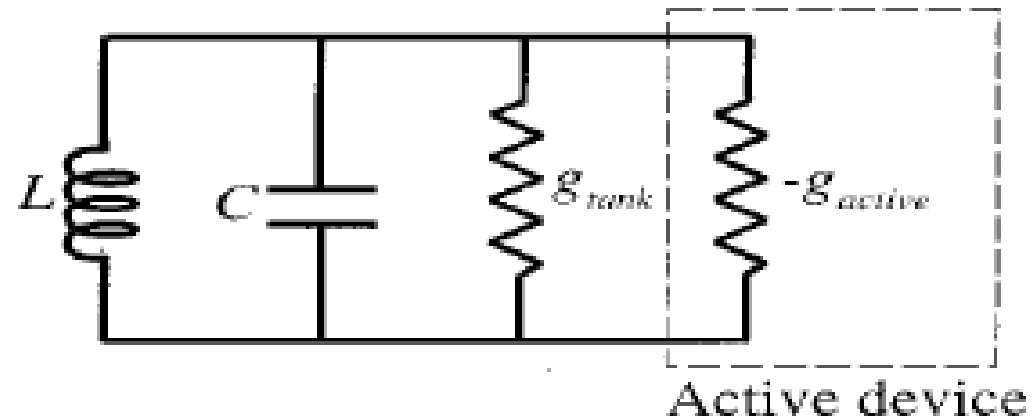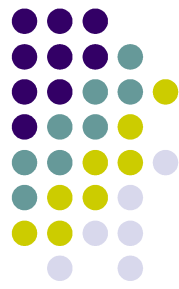

$$\omega = 1/\sqrt{LC}$$

# Negative Resistance Oscillator

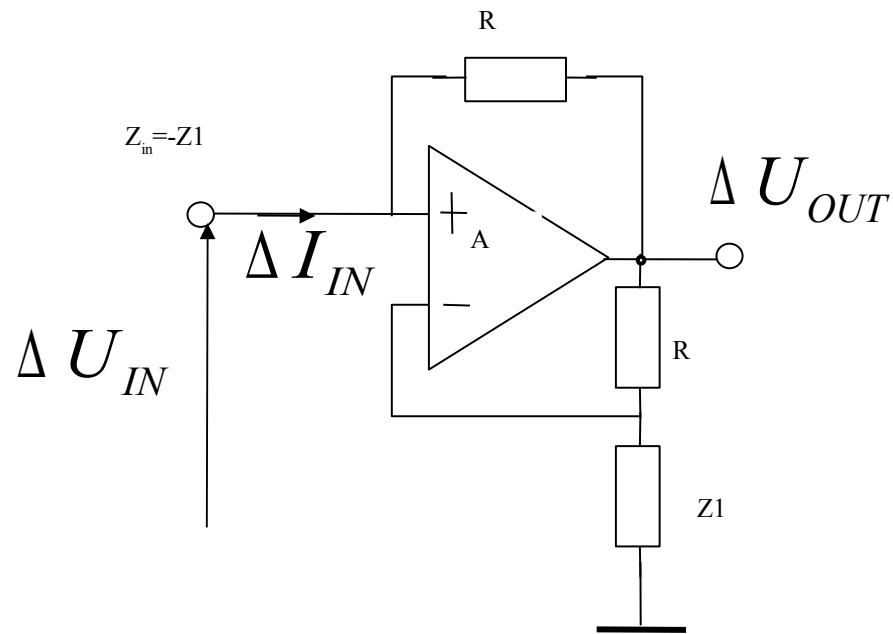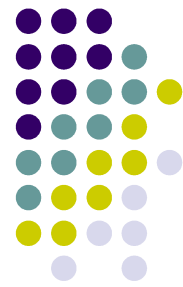

Negative impedance converter Circuit