

4. (a). Determine Logic Function F.

Tentukan rangkap logic F. (4 pts)

(b). Design a circuit to implement the same logic function, but using NOR gates. Draw a transistor-level schematic and use NMOS Enhancement-Depletion technology.

Dengan menggunakan get TAK ATAU, reka litar yang mempunyai rangkap logic yang sama. Lukis skema aras transistor dan guna teknologi peningkatan-kesusutan NMOS. (8 pts)

(c). Design a circuit to implement the same logic function, but using AND-OR-INVERT gate. Draw a transistor level schematic and use CMOS technology.


Dengan menggunakan get DAN-ATAU-SONSANG, reka litar yang mempunyai rangkap logic yang sama. Lukis skema aras transistor dan guna teknologi CMOS. (8 pts)

5.(a). Calculate  $W_L/L_L$  such that  $V_{OL}$  does not exceed 0.3 V.

$$V_{T,load} = -3V, V_{T,driver} = 1V$$

Kira  $W_L/L_L$  bagi  $V_{OL}$  tidak lebih daripada 0.3 V. (7 pts)

$$V_{T,load} = -3V, V_{T,driver} = 1V$$

 

(b). Draw stick diagram for the above circuit.

Lukis gambarajah lidi untuk litar di atas. (6 pts)

(c). Design and draw an 8-bit serial to parallel converter using flip-flop.

Reka dan lukis penukar siri kepada selari 8-bit menggunakan flip-flop. (7pts).


Solutions.

4. (a).

$$F = A\bar{B} + \bar{A}B = A \oplus B$$

(b).

 
$$F = A\bar{B} + \bar{A}B = (A + B)(\bar{A} + \bar{B}) = \overline{\overline{(A + B)} + \overline{(\bar{A} + \bar{B})}}$$



(c).

$$\overline{F} = AB + \overline{A}\overline{B}$$
 
$$F = \overline{\overline{F}} = \overline{AB + \overline{A}\overline{B}}$$



5 (a).

(b)  $V_{OL}$  maximum occurs when  $A=1, D=0$  and either (but not both)  $B=1$  or  $C=1$ . Under these conditions, the circuit may be simplified as a depletion load inverter with the equivalent driver W/L given below.

$$\left. \frac{L}{W} \right|_{equiv} = \frac{4}{8} + \frac{4}{4} = \frac{3}{2}$$

$$\therefore \left. \frac{W}{L} \right|_{equiv} = \frac{2}{3}$$

When  $V_{OL} = 0.3$  V,  $V_{IN} = 5$  V, the load is saturated and driver is linear region.

$$\frac{k'}{2} \left( \frac{W}{L} \right)_{load} (V_{GS,load} - V_{T,load})^2 = k' \frac{2}{3} \left[ (V_{IN} - V_{T,driver})V_{out} - \frac{1}{2} V_{out}^2 \right]$$

$$\frac{k'}{2} \left( \frac{W}{L} \right)_{load} (0+3)^2 = k' \frac{2}{3} \left[ (5-1) \times 0.3 - \frac{1}{2} \times 0.3^2 \right]$$

$$(W/L)_{load} = 0.171$$

Therefore  $(W/L)_{load} \leq 0.171$  for  $V_{OL} \leq 0.3$  V.

- (b) poly A,B,C and D must vertically drawn. Each source/drain must be pointed clearly.
- (c) Drawing should include at least 8 flip-flops. Triggering method and clocking method.