

4. (a). Explain at least two applications of CMOS transmission gate.

Terangkan sekurang-kurangnya dua kegunaan get hantaran CMOS. (4 pts)

(b). IF V_{IN} and V_A is V_{DD} explain the state of operation for NMOS and PMOS when $|V_{TP}| < V_{OUT} < |V_{DD} - V_{TN}|$

Sekiranya V_{IN} dan V_A adalah V_{DD} , terangkan operasi NMOS dan PMOS apabila

$|V_{TP}| < V_{OUT} < |V_{DD} - V_{TN}|$


(8 pts)

(c). Draw the layout of the CMOS transmission gate efficiently.

Lukis bentangan bagi get hantaran CMOS yang efektif . (8 pts)

5

 - a). Determine logic function F. Tentukan logic F.
Kirakan W_L/L_L sekiranya V_{OL} tidak melebihi 0.3 V.
Calculate W_L/L_L such that V_{OL} does not exceed 0.3 V.
 $V_{T,load} = -3V$, $V_{T,driver} = 1 V$ (7pts).




- (b). Draw stick diagram for the above circuit.
Lukis gambarajah lidi untuk litar di atas. (6 pts)
- (c). Design and draw an 8-bit parallel to serial converter using flip-flop.
Reka dan lukis penukar selari kepada siri 8-bit menggunakan flip-flop. (7pts).

Solutions.

4(a). Combinational Logic gate and Switch.

(b). PMOS in linear region. NMOS in saturation region. Answer must be coupled with explanation using at least drain current equation.

(c).

 

5 (a).

$$(a) F = \overline{A(B+C)+D}$$

(b) V_{OL} maximum occurs when A=1, D=0 and either (but not both) B=1 or C=1. Under these conditions, the circuit may be simplified as a depletion load inverter with the equivalent driver W/L given below.

$$\frac{L}{W} \Big|_{equiv} = \frac{4}{8} + \frac{4}{4} = \frac{3}{2}$$

$$\therefore \frac{W}{L} \Big|_{equiv} = \frac{2}{3}$$

When $V_{OL} = 0.3$ V, $V_{IN} = 5$ V, the load is saturated and driver is linear region.

$$\frac{k'}{2} \left(\frac{W}{L} \right)_{load} \left(V_{GS,load} - V_{T,load} \right)^2 = k' \frac{2}{3} \left[(V_{IN} - V_{T,driver}) V_{out} - \frac{1}{2} V_{out}^2 \right]$$

$$\frac{k'}{2} \left(\frac{W}{L} \right)_{load} (0+3)^2 = k' \frac{2}{3} \left[(5-1) \times 0.3 - \frac{1}{2} \times 0.3^2 \right]$$

$$(W/L)_{load} = 0.171$$

Therefore $(W/L)_{load} \leq 0.171$ for $V_{OL} \leq 0.3$ V.

- (b) poly A,B,C and D must vertically drawn. Each source/drain must be pointed clearly.
- (c) Drawing should include at least 8 flip-flops. Triggering method and clocking method.