
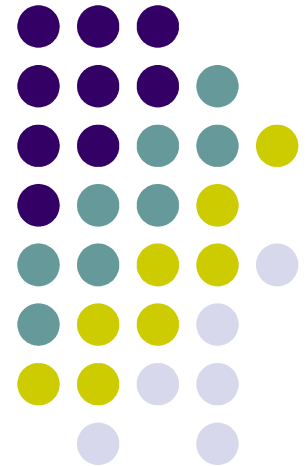



Voltage Reference Circuit

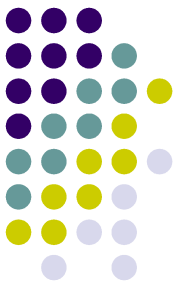- ✓ Reference Circuit
- ✓ Regulator Circuit






Shunt Voltage Reference


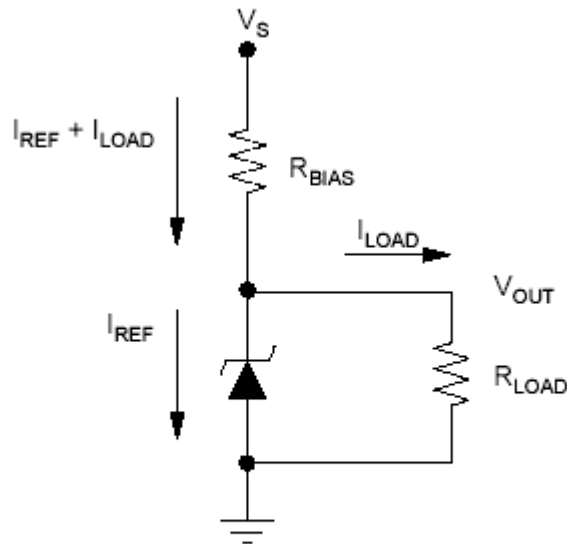

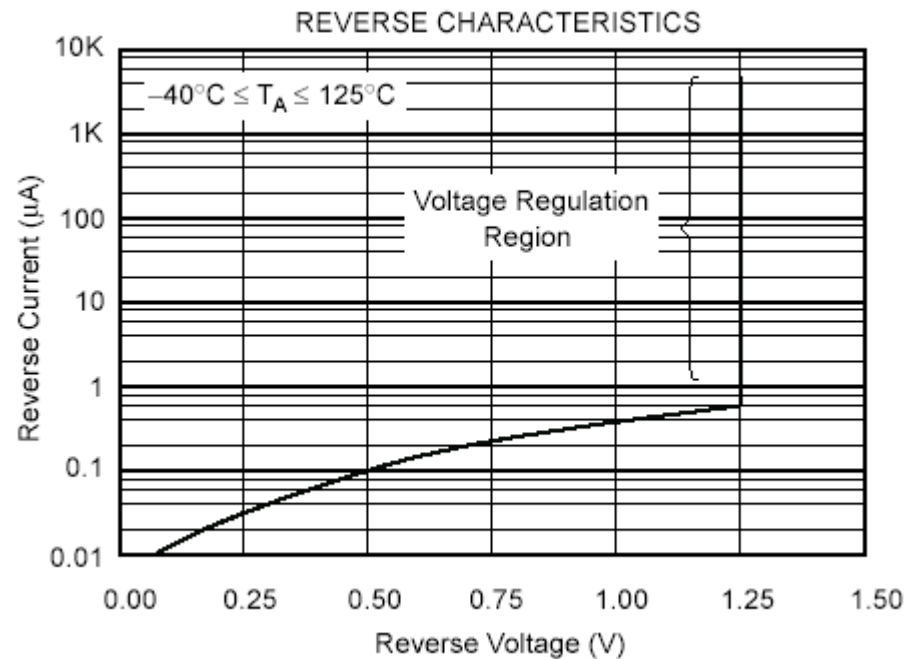
$$R_{BIAS} = \frac{V_S - V_D}{I_{LOAD} + I_{REF}}$$



Adjustable

3

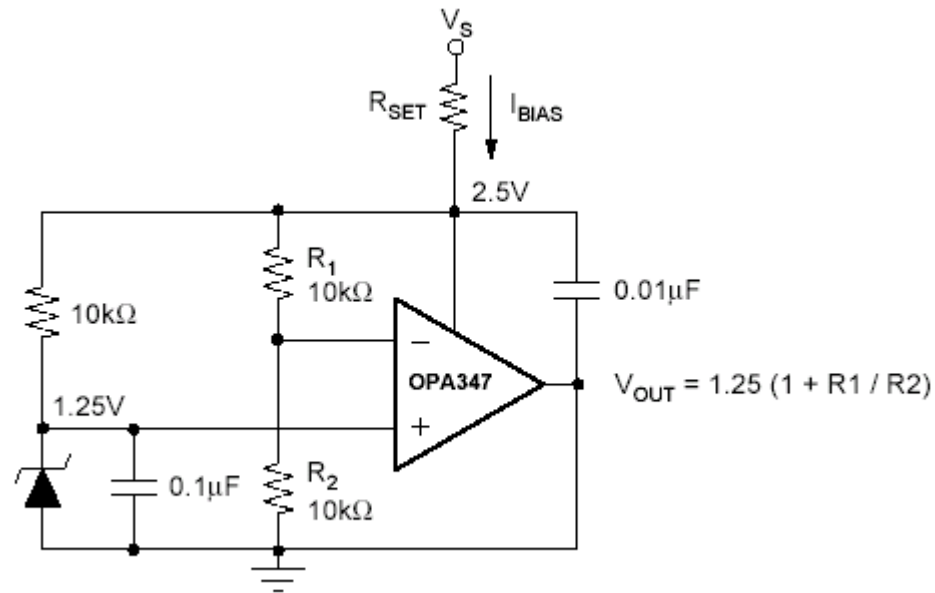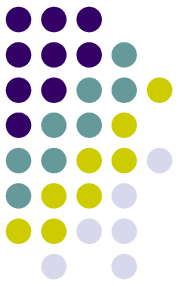


Regulator

- maintain a constant **voltage** level.
- PERCENT OF REGULATION

$$(\%V_{\text{reg}}) = \frac{V_{\text{NL}} - V_{\text{FL}}}{V_{\text{FL}}} \times 100\%$$
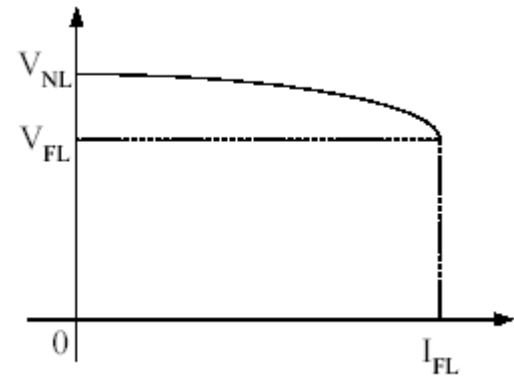
$$\%V_{\text{reg}} = \frac{\left(\frac{\Delta V_{\text{O}}}{V_{\text{O}}} \right)}{\Delta V_{\text{in}}} \times 100\%$$



4



Regulating Element



- Power Transistor
 - High Current
 - Low R_{ds}

5





Power Supply

6

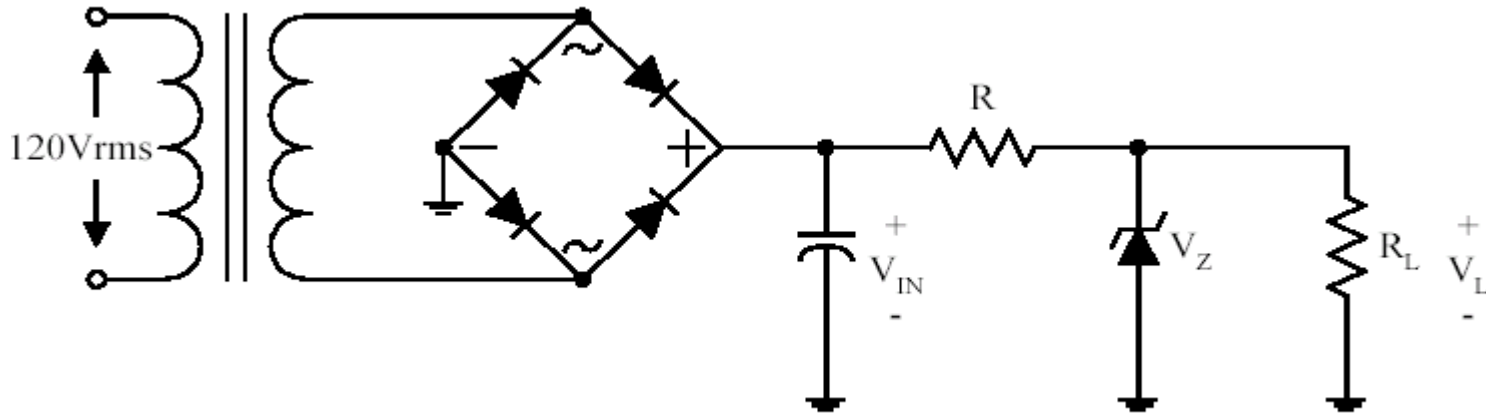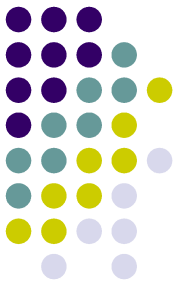

- $V_{in} > V_Z$
- Load Current sensitive

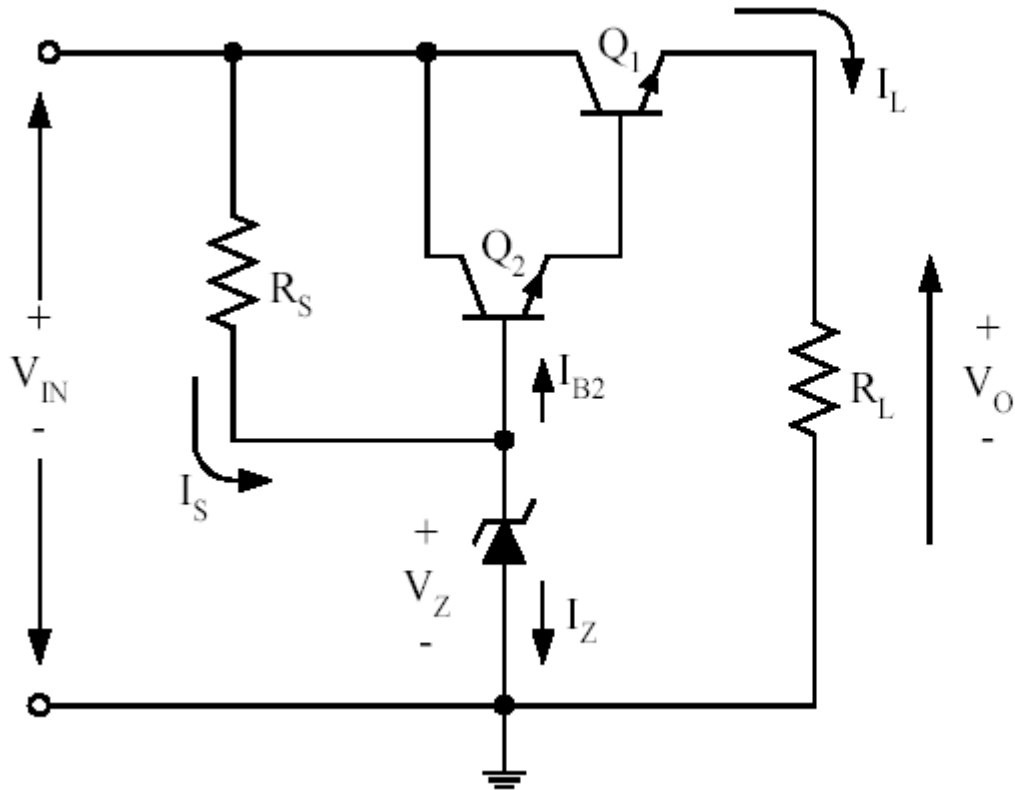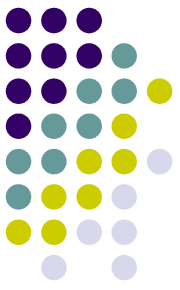Add Emitter Follower to reduce the sensitivity of load current



$$I_{B2} = \frac{I_{E1}}{\beta_{DP}} = \frac{I_L}{\beta_{DP}}$$



$$\beta_{DP} = \beta_1 + \beta_2 + \beta_1\beta_2$$

$$I_Z = I_S - I_{B2}$$

$$= I_S - \frac{I_L}{\beta_{DP}}$$

$$V_O = V_Z - 2V_{BE}$$

With Feedback

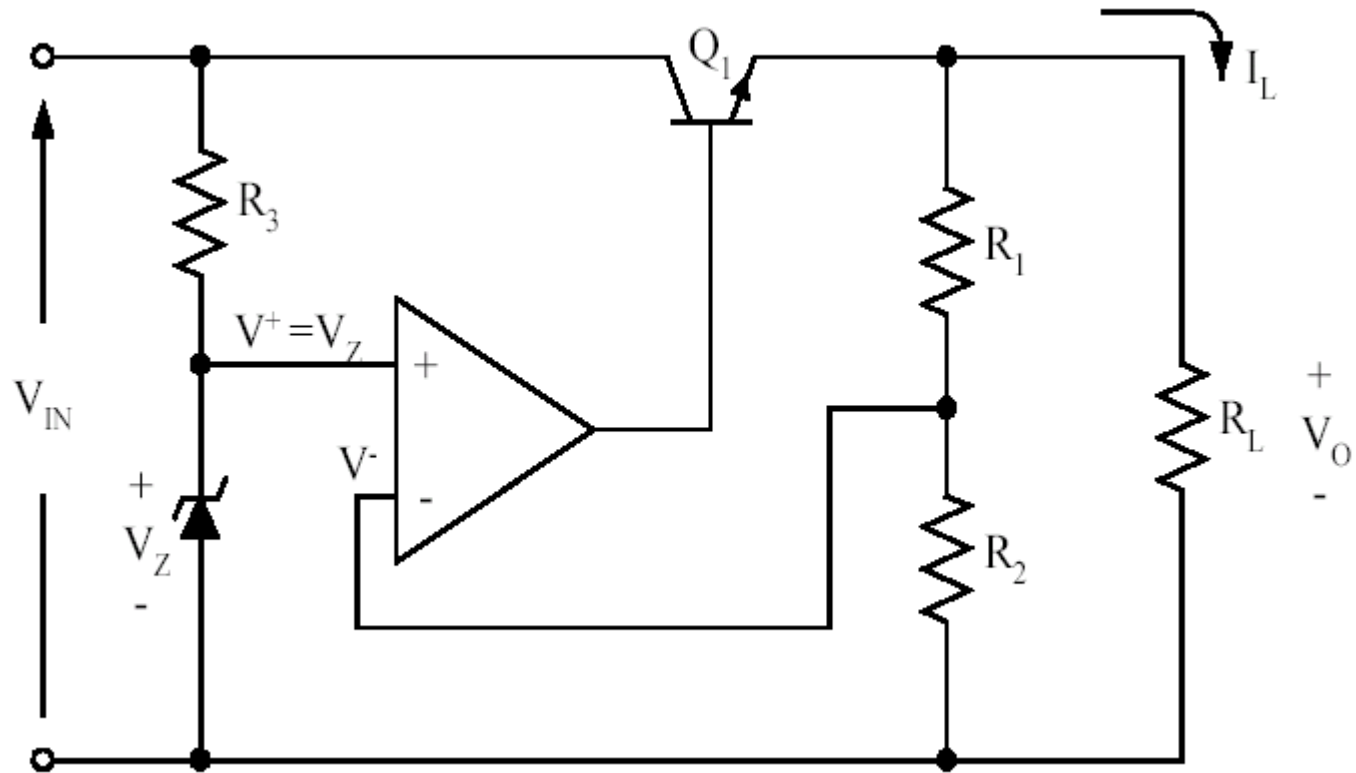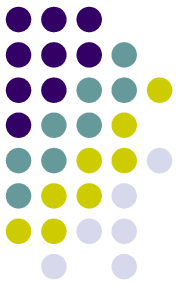

Shunt

