
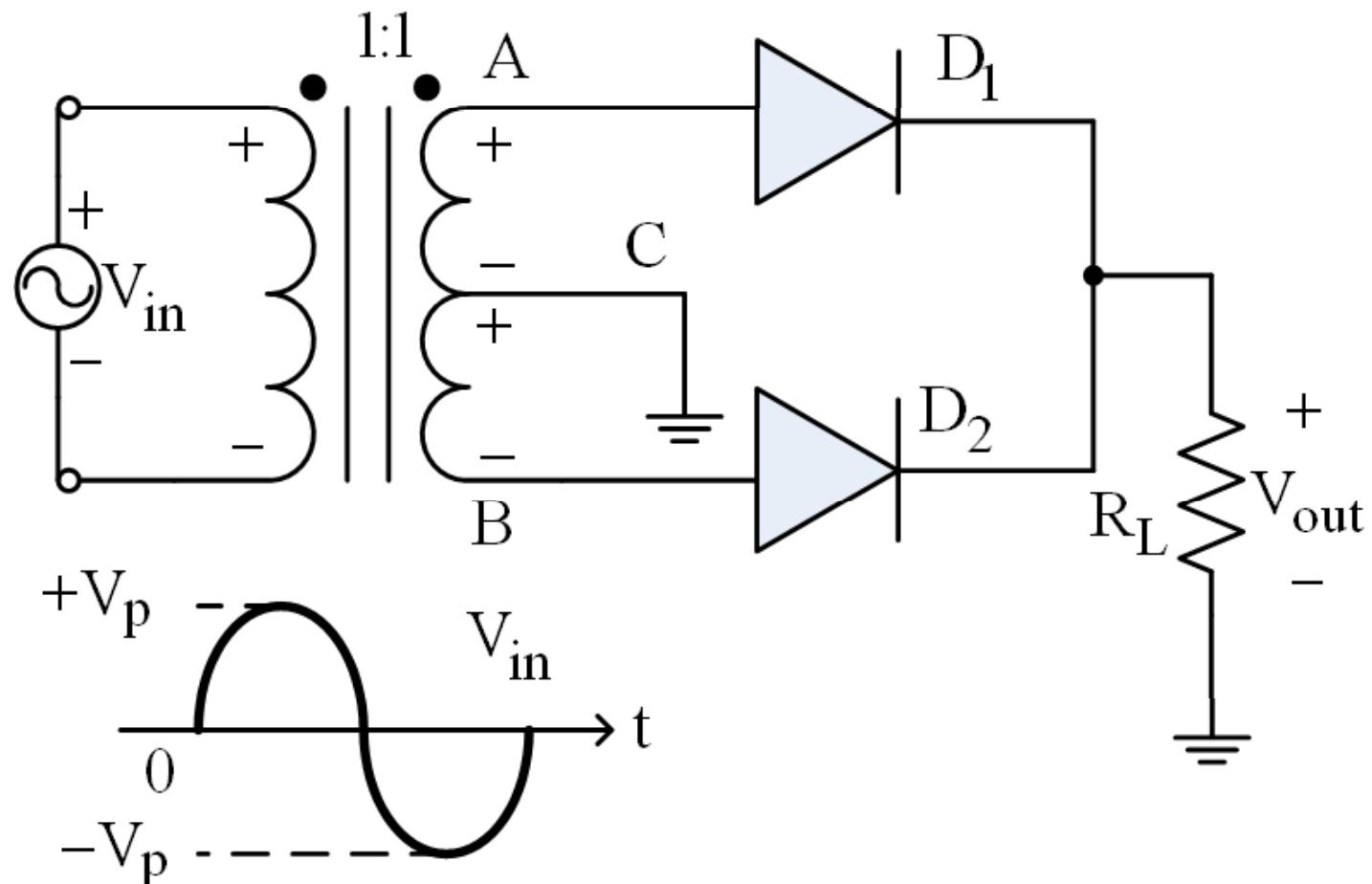



CLASS 10



Centre-tap full wave rectifier



Centre-tap full-wave rectifier

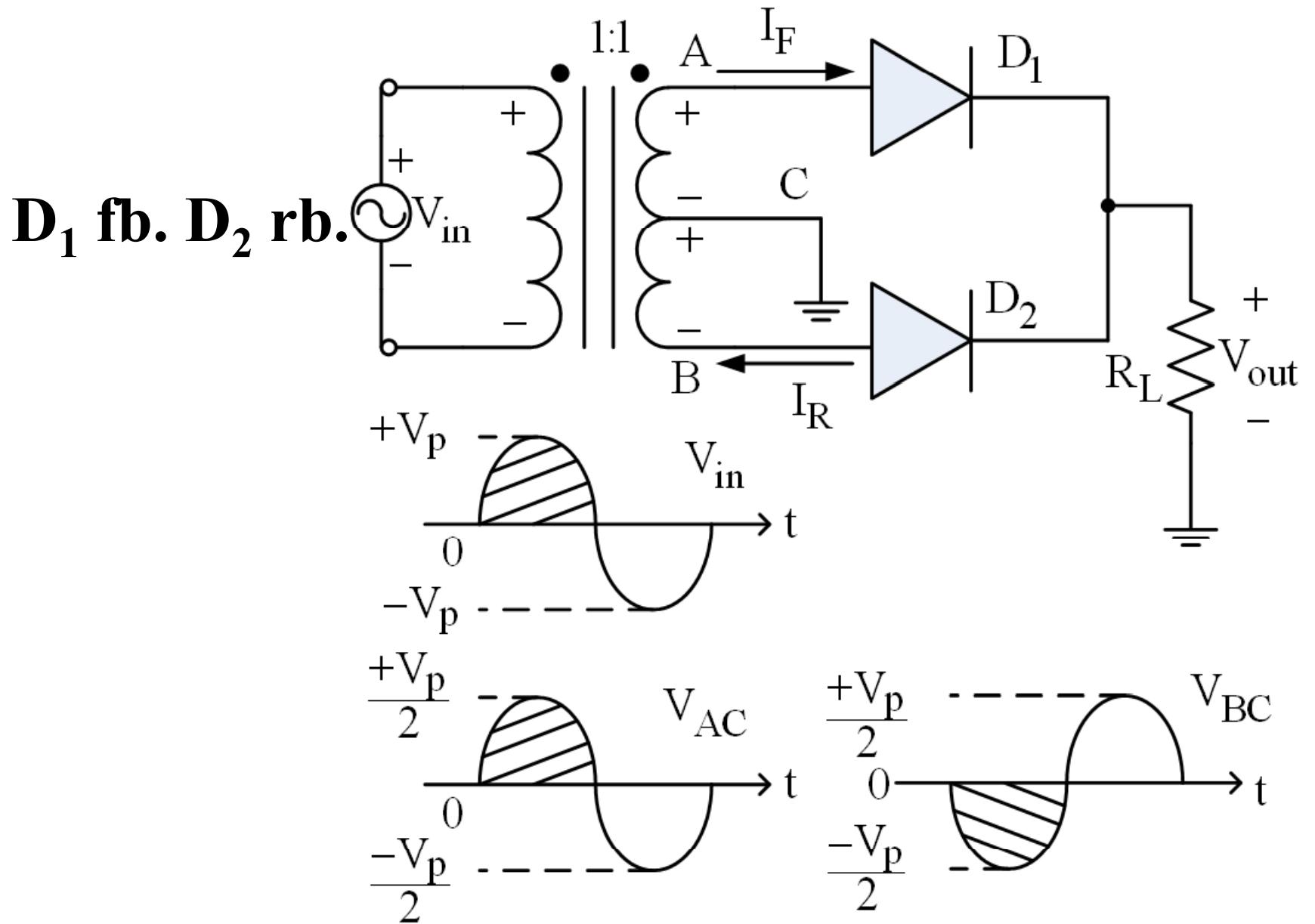




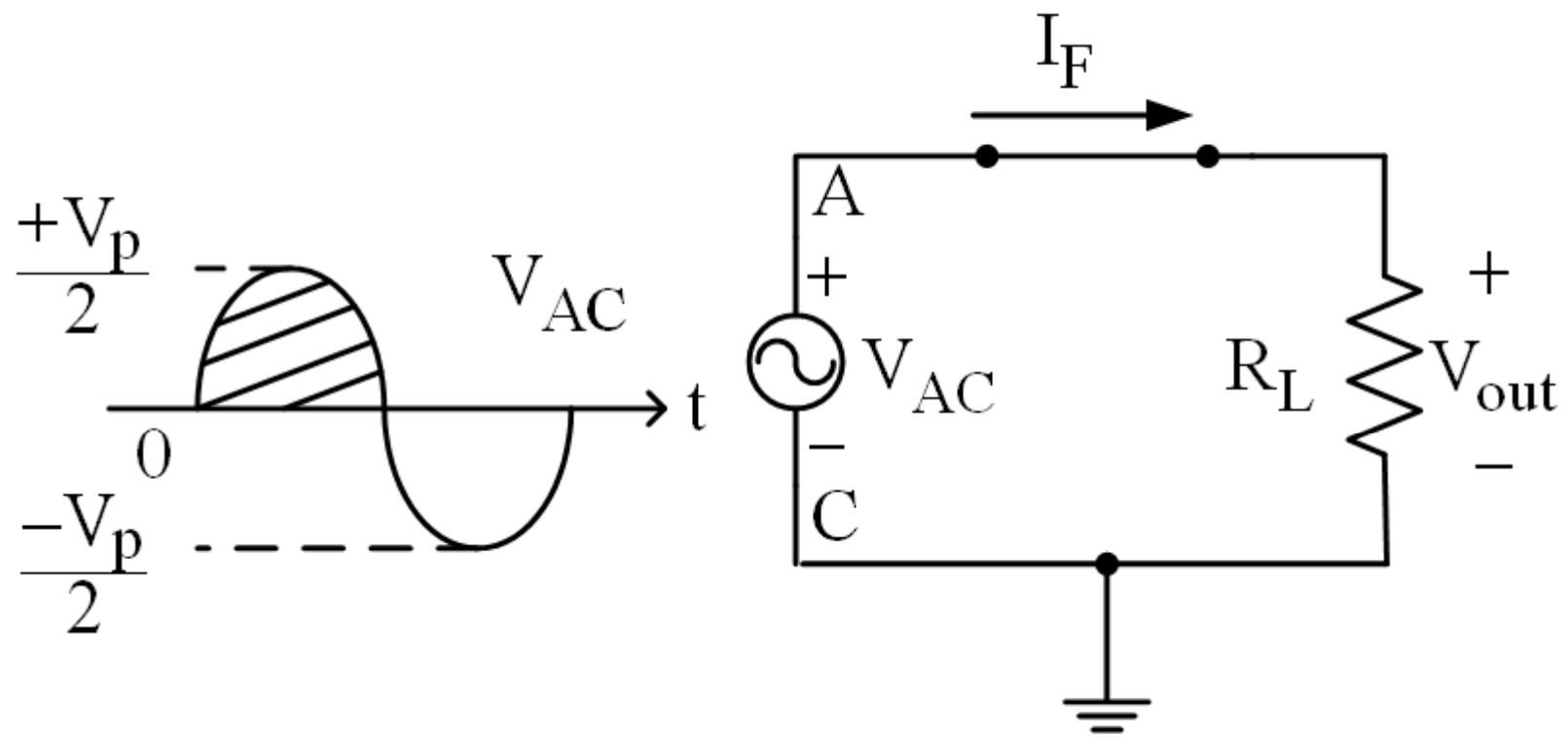


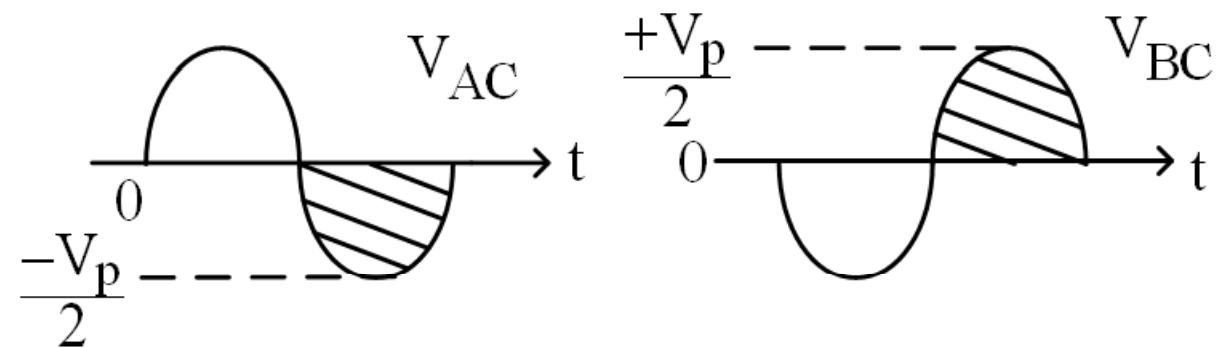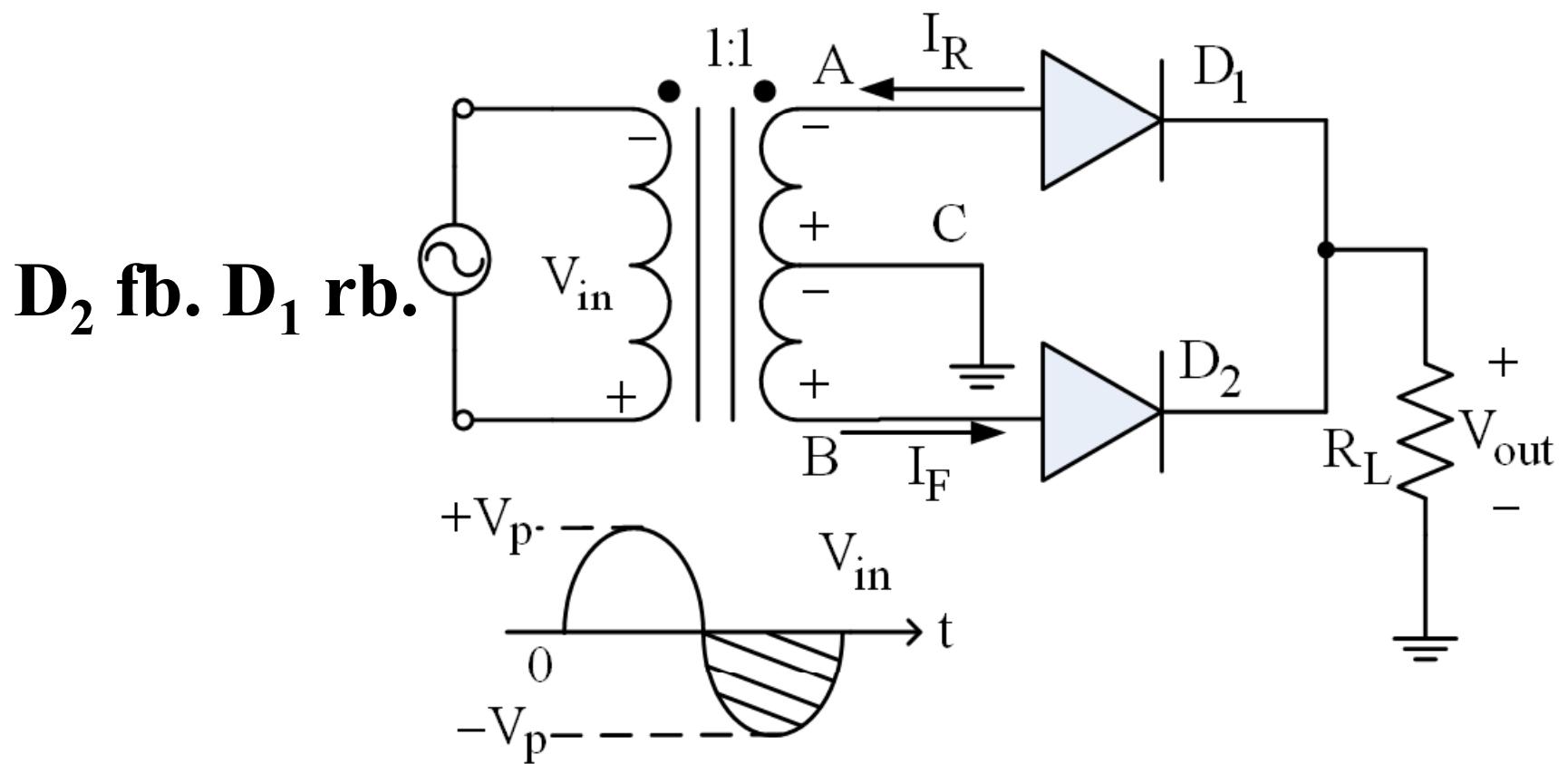


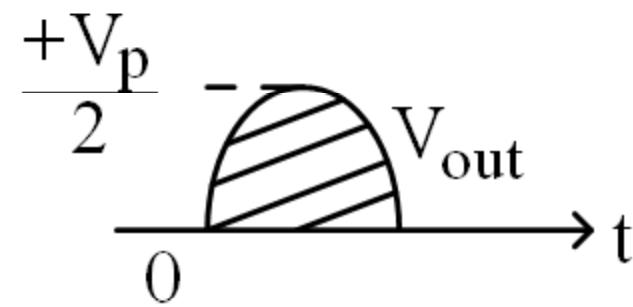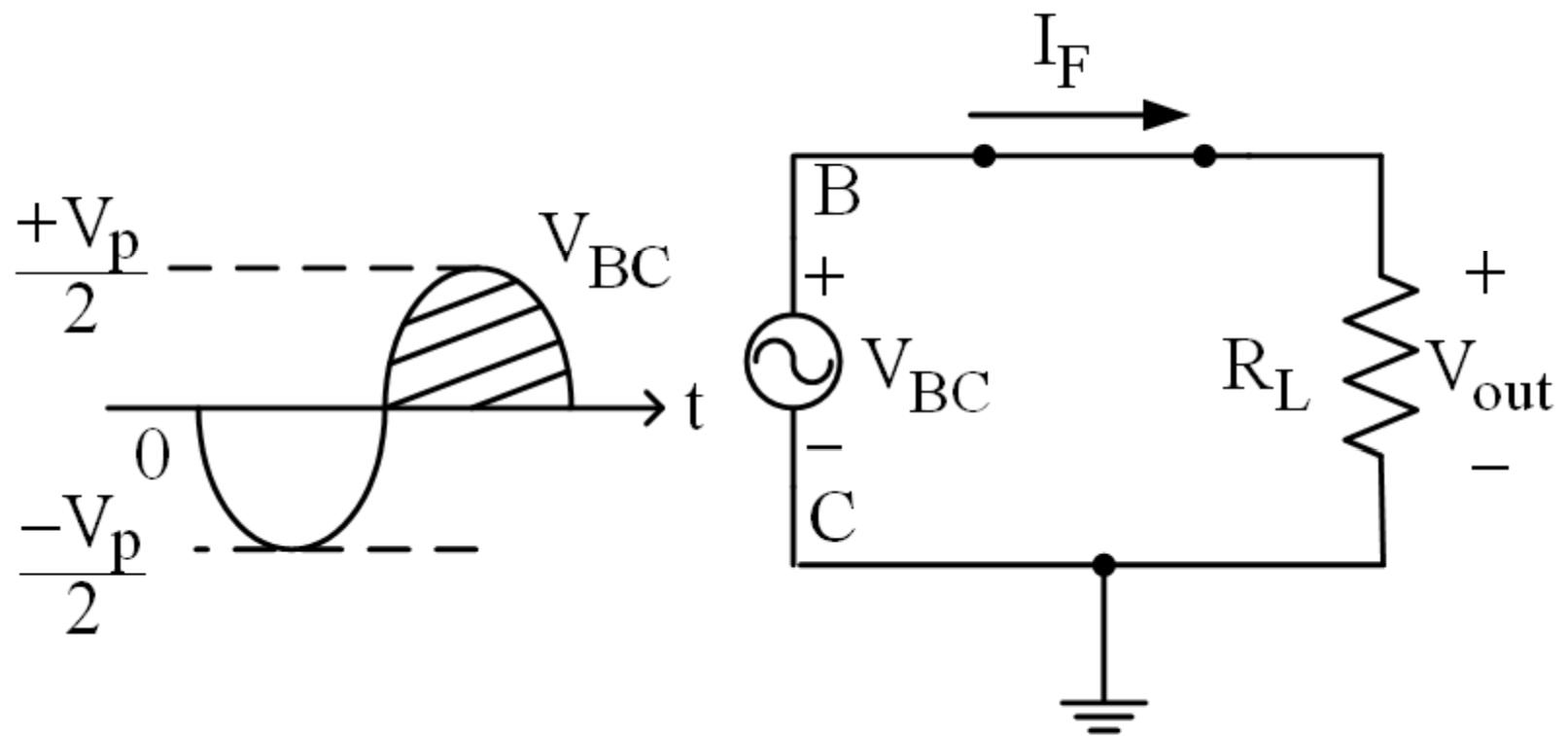

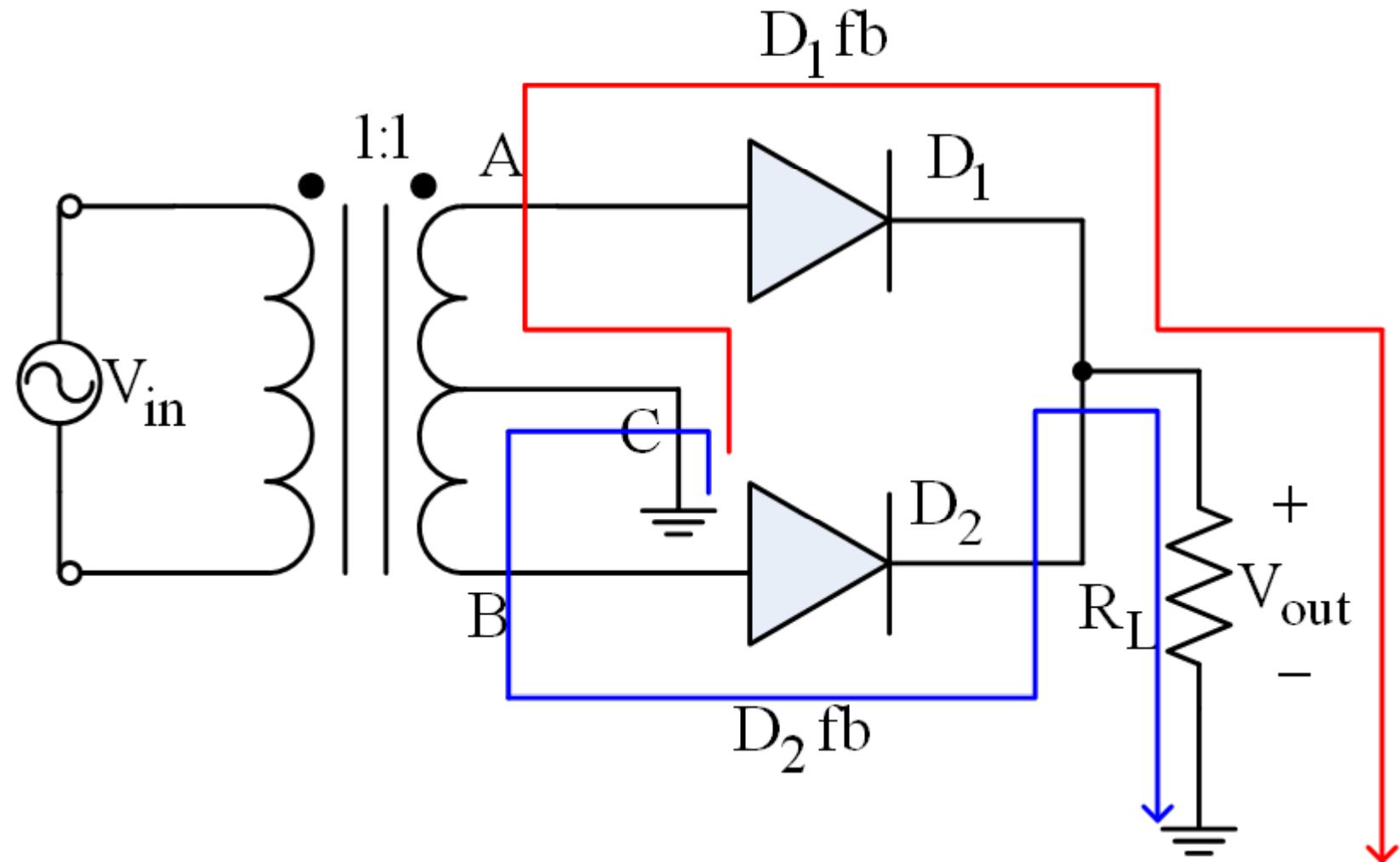

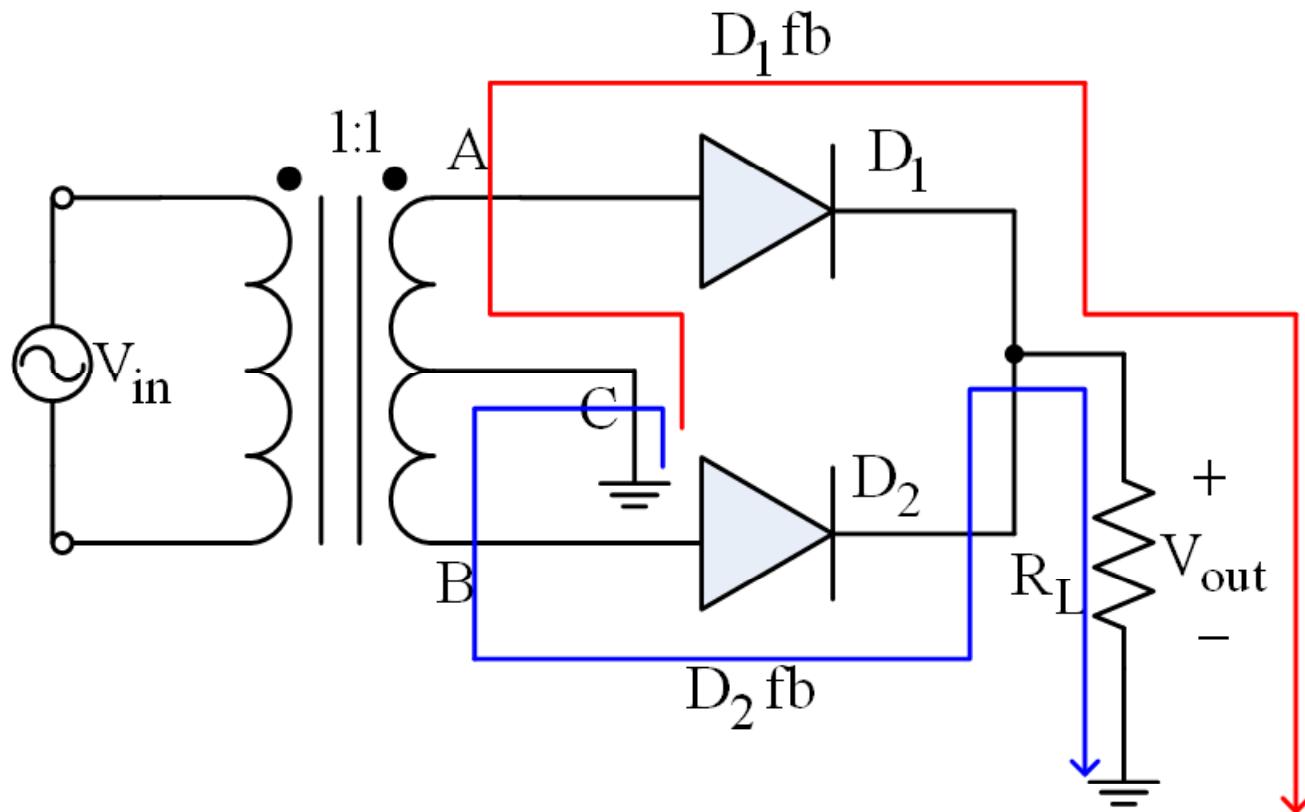Current flowing through R_L will always be in the same direction, independent of whether D_1 or D_2 that was fb.




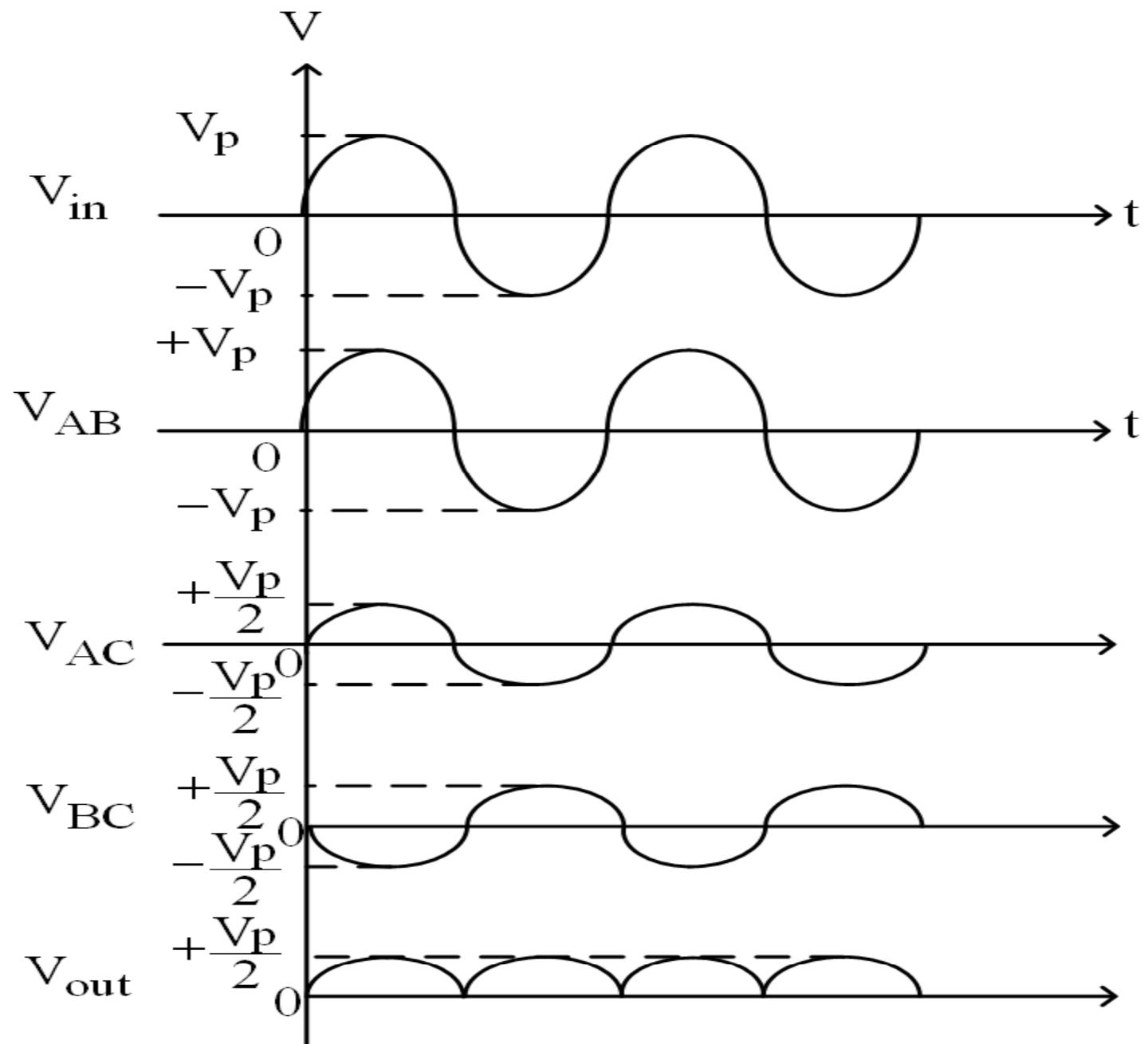

Centre-tap full wave rectifier with potential barrier effect considered

**During the +ve half cycle, D_1 will be fb if $V_{AC} > V_o$.
 D_1 is a s/c. $V_{AC} = V_o + V_{out}$. $V_{out} = V_{AC} - V_o$.**

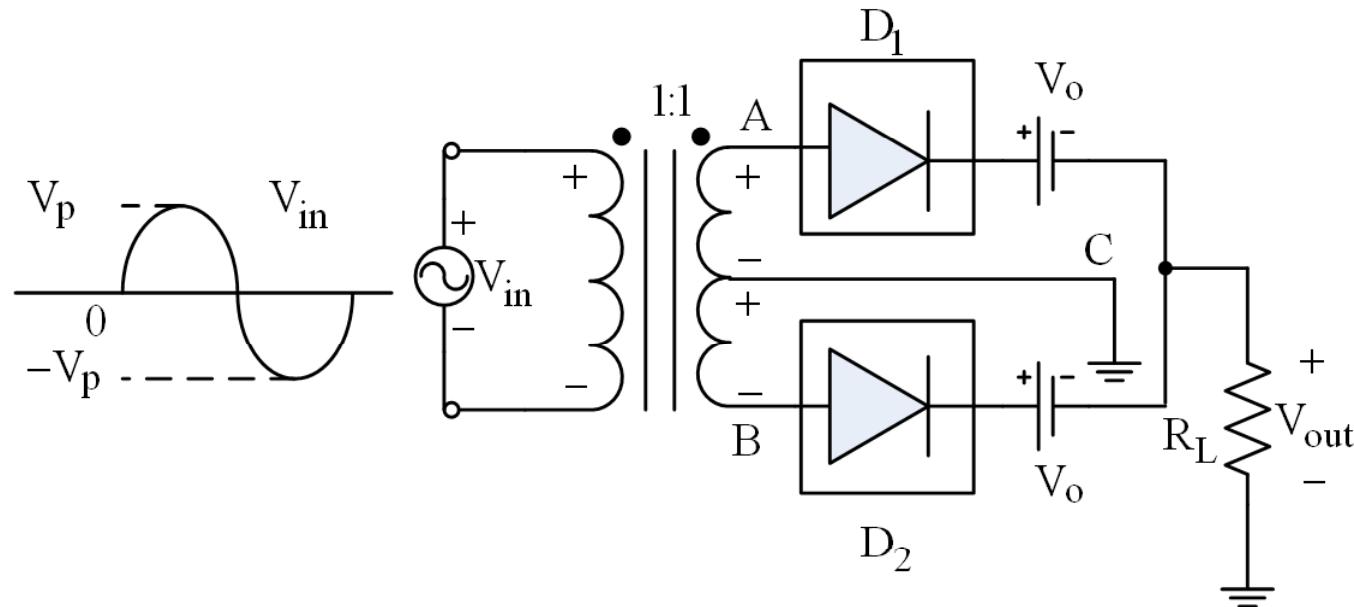**During the -ve half cycle, D_2 will be fb if $V_{BC} > V_o$.
 D_2 is a s/c. $V_{BC} = V_o + V_{out}$. $V_{out} = V_{BC} - V_o$.**




During the +ve half cycle, D_1 will be fb.

$V_{out} = V_{AC} - V_o$. Max.
 V_{AC} is $V_p/2$. Hence,
 $V_{out(max)} = V_p/2 - V_o$.

During the -ve half cycle, D_2 will be fb.

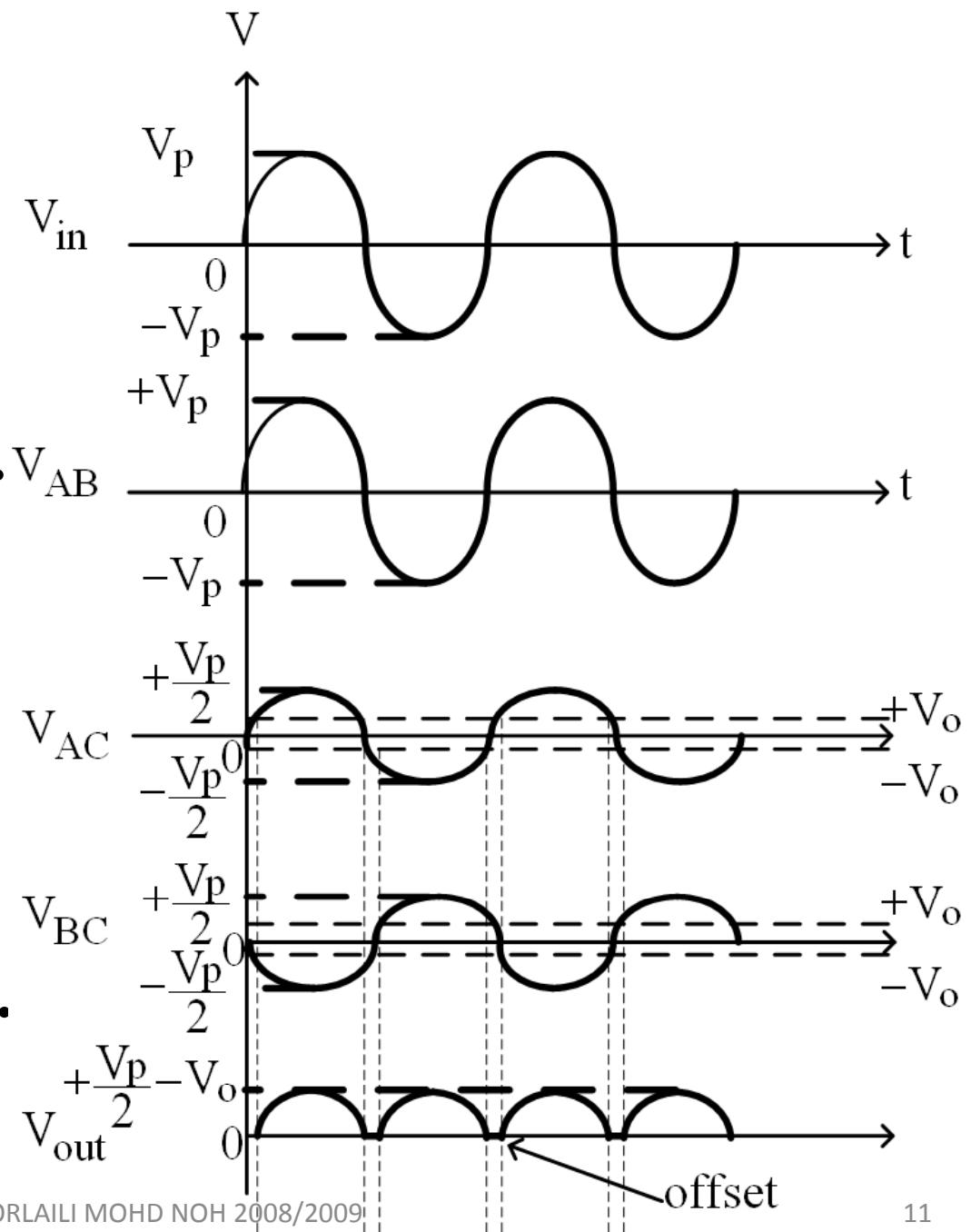
$V_{out} = V_{BC} - V_o$. Max.
 V_{BC} is $V_p/2$. Hence,
 $V_{out(max)} = V_p/2 - V_o$.



Average voltage of a full-wave rectifier

$$V_{\text{avg}} = \frac{\text{Area}}{T} = \frac{\text{Area}}{2\pi}$$
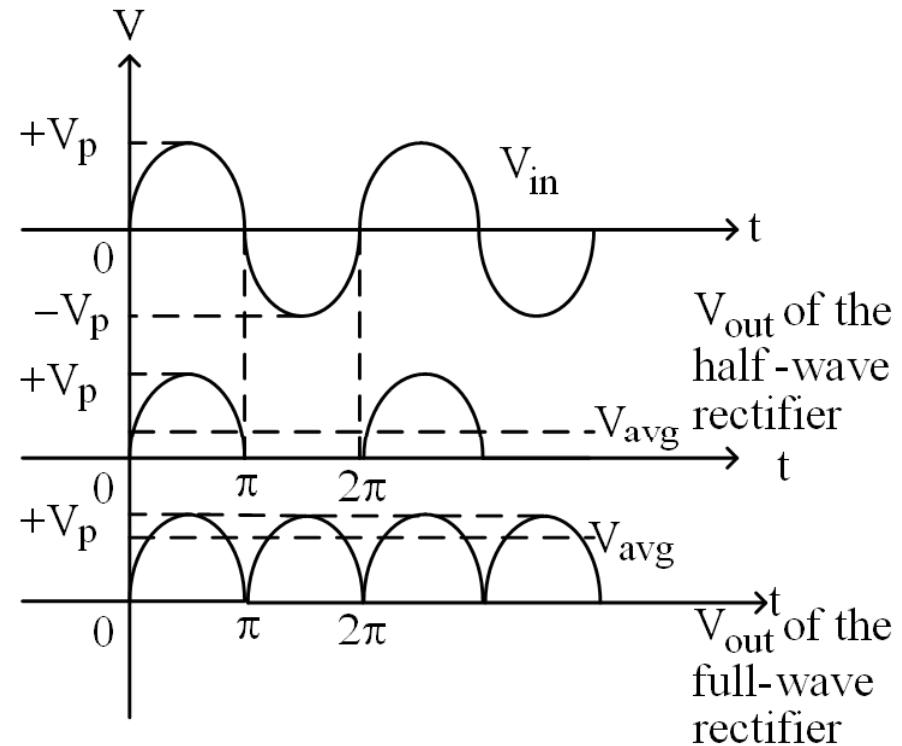
$$\begin{aligned} V_{\text{avg}} &= \frac{1}{2\pi} \times 2 \int_0^{\pi} V_p \sin \theta \, d\theta \\ &= \frac{V_p}{\pi} [-\cos \theta]_0^{\pi} \\ &= \frac{2V_p}{\pi} \end{aligned}$$



If the input to the half-wave rectifier is the same as the input to the full-wave rectifier, i.e. V_{in} , the out signal of the half-wave rectifier has an average value of, $V_{\text{avg}} = V_p/\pi$.

Thus, $V_{\text{avg_Half-wave}} = \frac{1}{2} V_{\text{avg_Full-wave}}$

Duration=1/frequency

$$T = 1/f$$

$$T_{\text{Half-wave}} = T_{\text{input}}$$


$$f_{\text{Half-wave}} = f_{\text{input}}$$

$$T_{\text{Full-wave}} = \frac{1}{2} T_{\text{Half-wave}}$$

$$f_{\text{Full-wave}} = 2f_{\text{Half-wave}}$$

Hence,
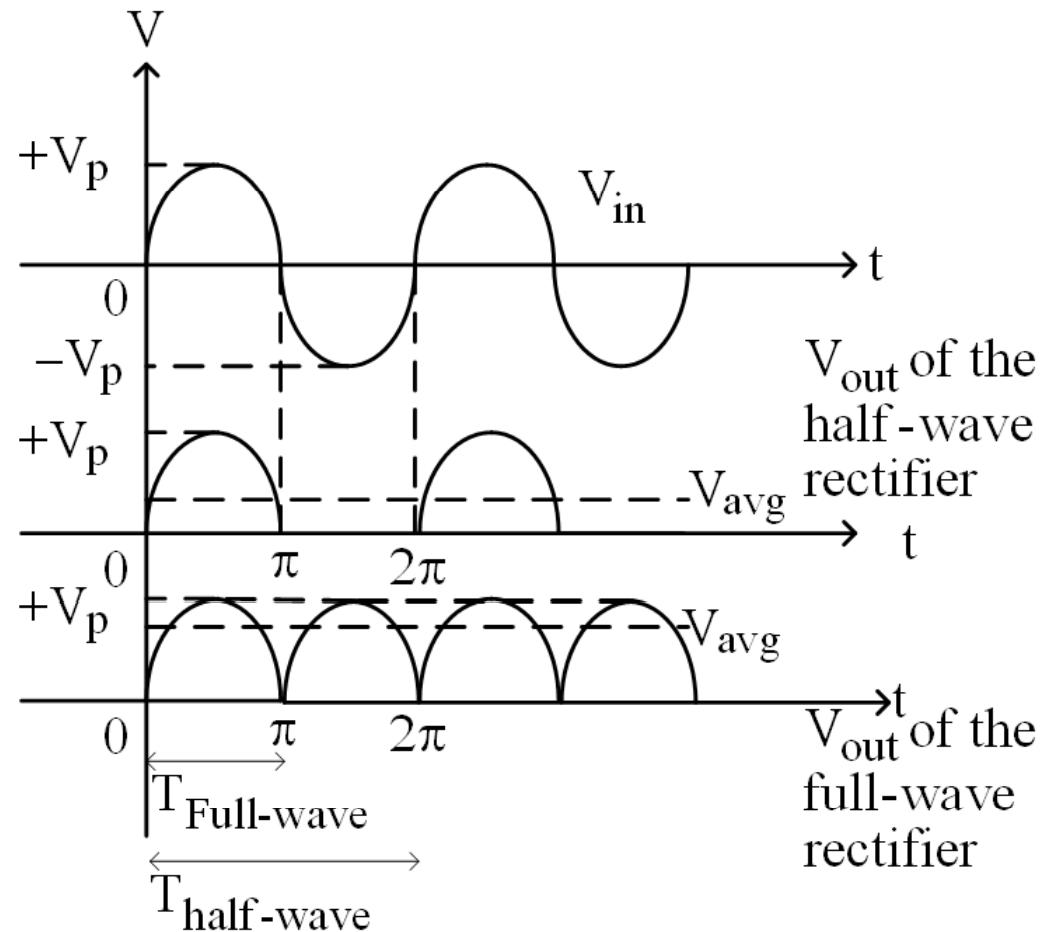
$$f_{\text{Full-wave}} = 2f_{\text{input}}$$




PIV_{D2} can be determined by analyzing the circuit when V_{in} is at its +ve half cycle.

$$\text{PIV}_{D2} = V_{\text{out}} - (-V_p/2)$$

$$V_{\text{out}} = (V_p/2) - V_o$$

$$\text{PIV}_{D2} = (V_p/2) - V_o - (-V_p/2)$$

$$\text{PIV}_{D2} = V_p - V_o$$

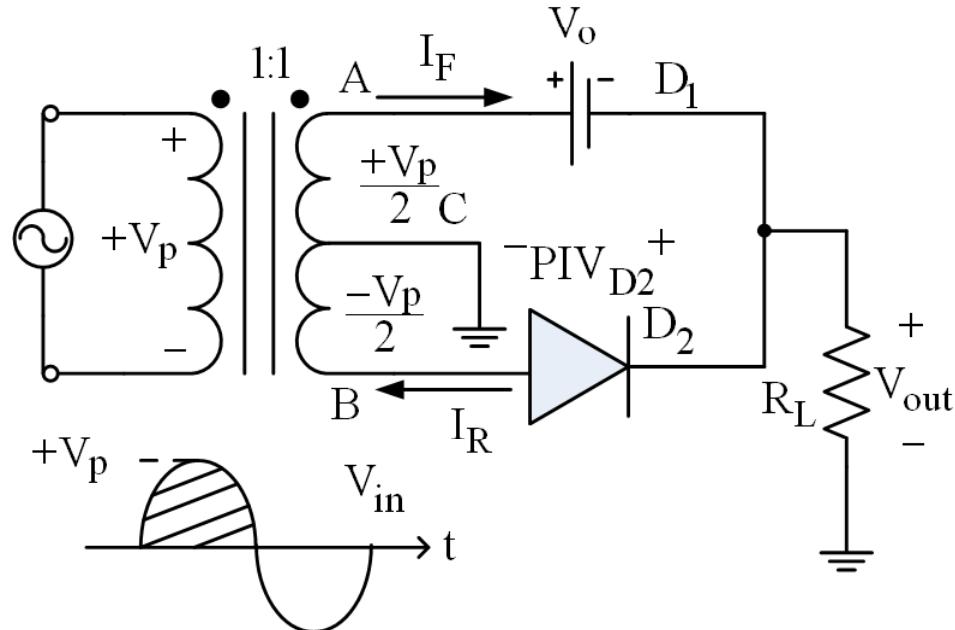


PIV_{D1} can be determined by analyzing the circuit when V_{in} is at its -ve half cycle.

$$PIV_{D1} = V_{out} - (-V_p/2)$$


$$V_{out} = (V_p/2) - V_o$$

$$PIV_{D1} = (V_p/2) - V_o - (-V_p/2)$$


$$PIV_{D1} = V_p - V_o$$

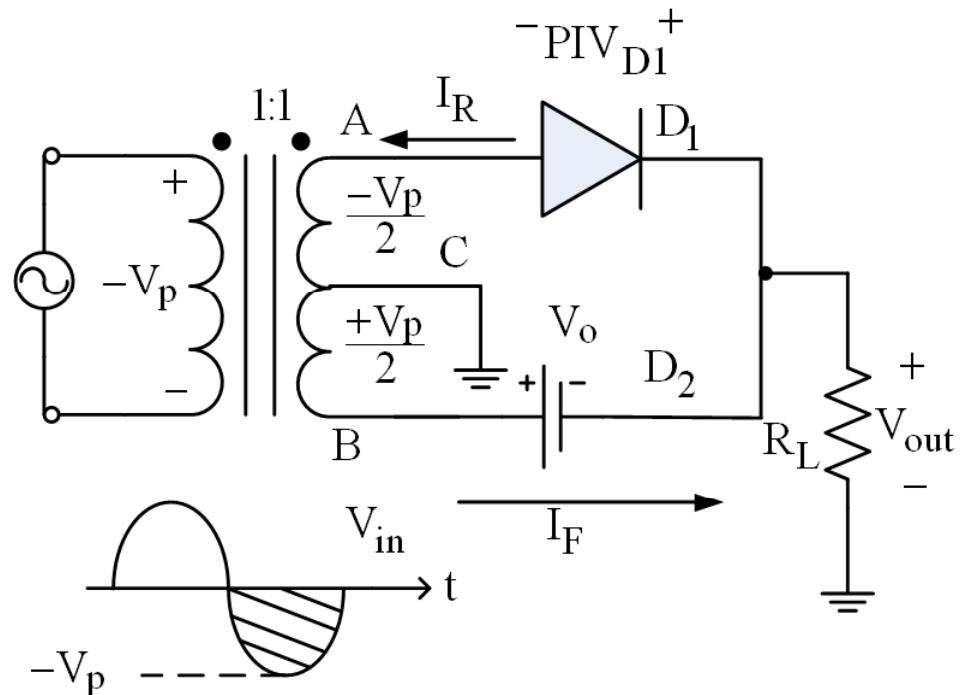

Bridge full-wave rectifier

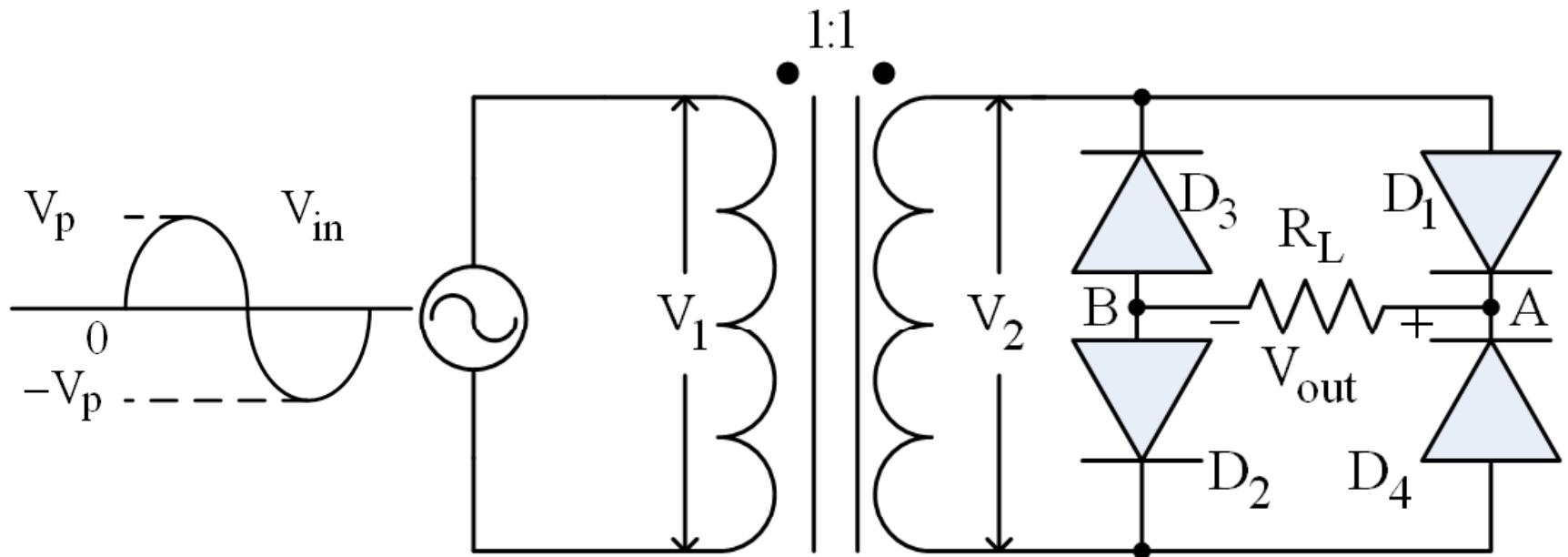

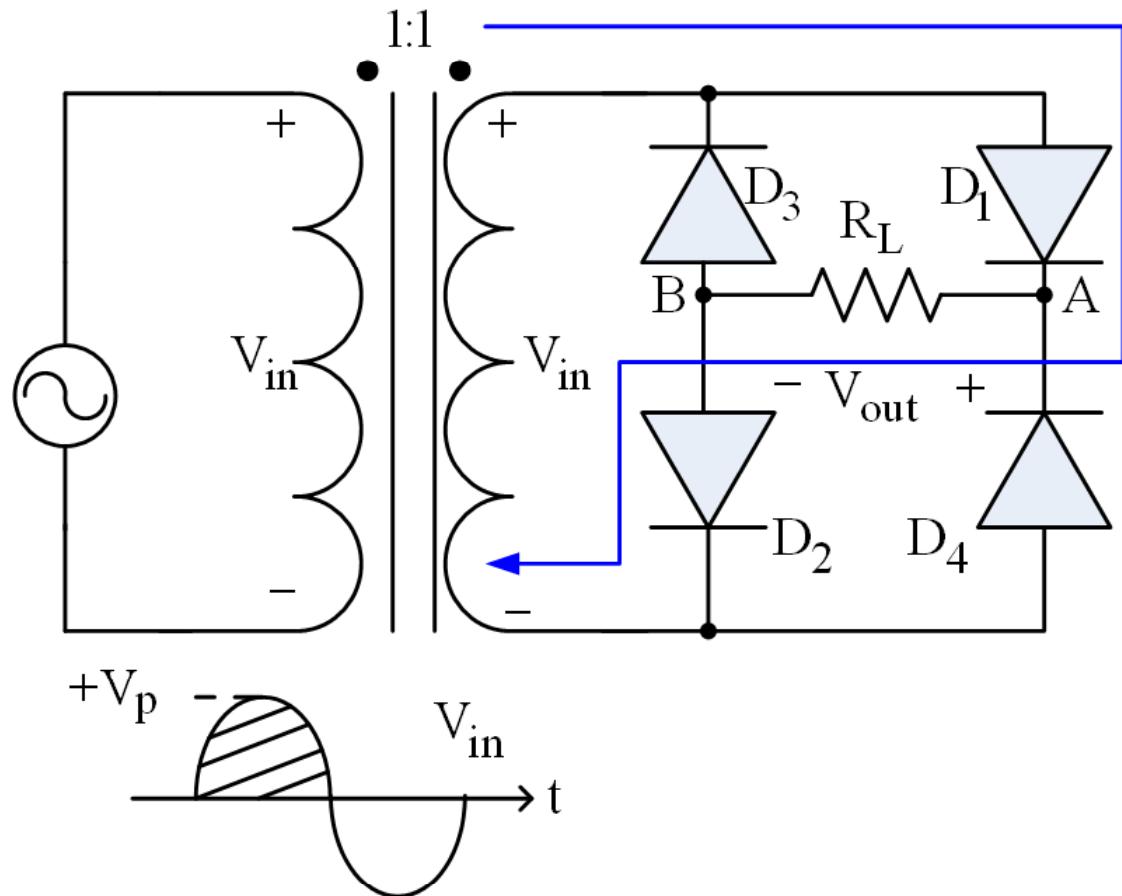
During +ve half cycle, D_1 and D_2 are fb. V_{out} is +ve at A and -ve at B.




$$V_{\text{out}} = V_{\text{in}}$$

$$\text{If } V_{\text{in}} = V_p,$$

$$V_{\text{out}} = V_p$$

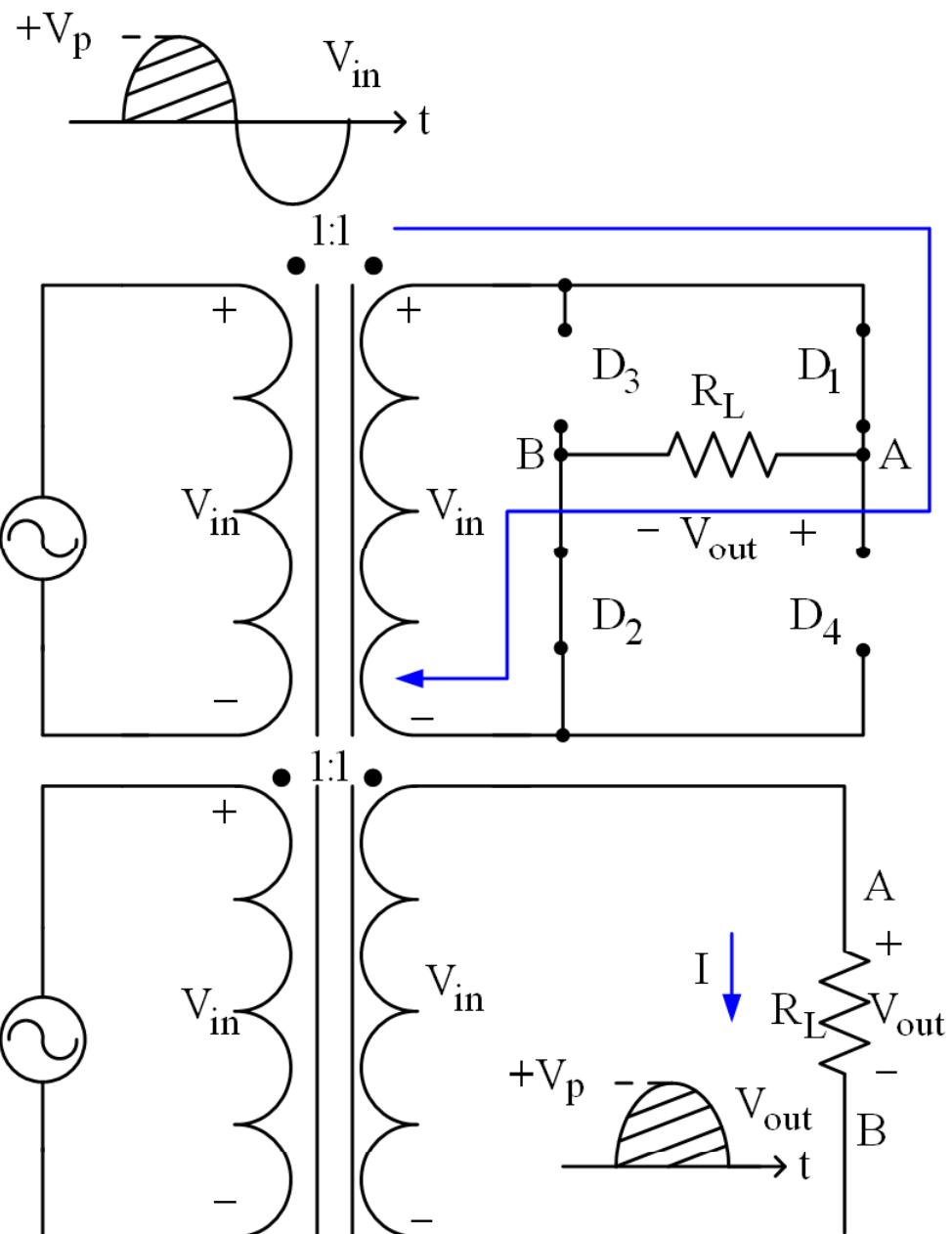

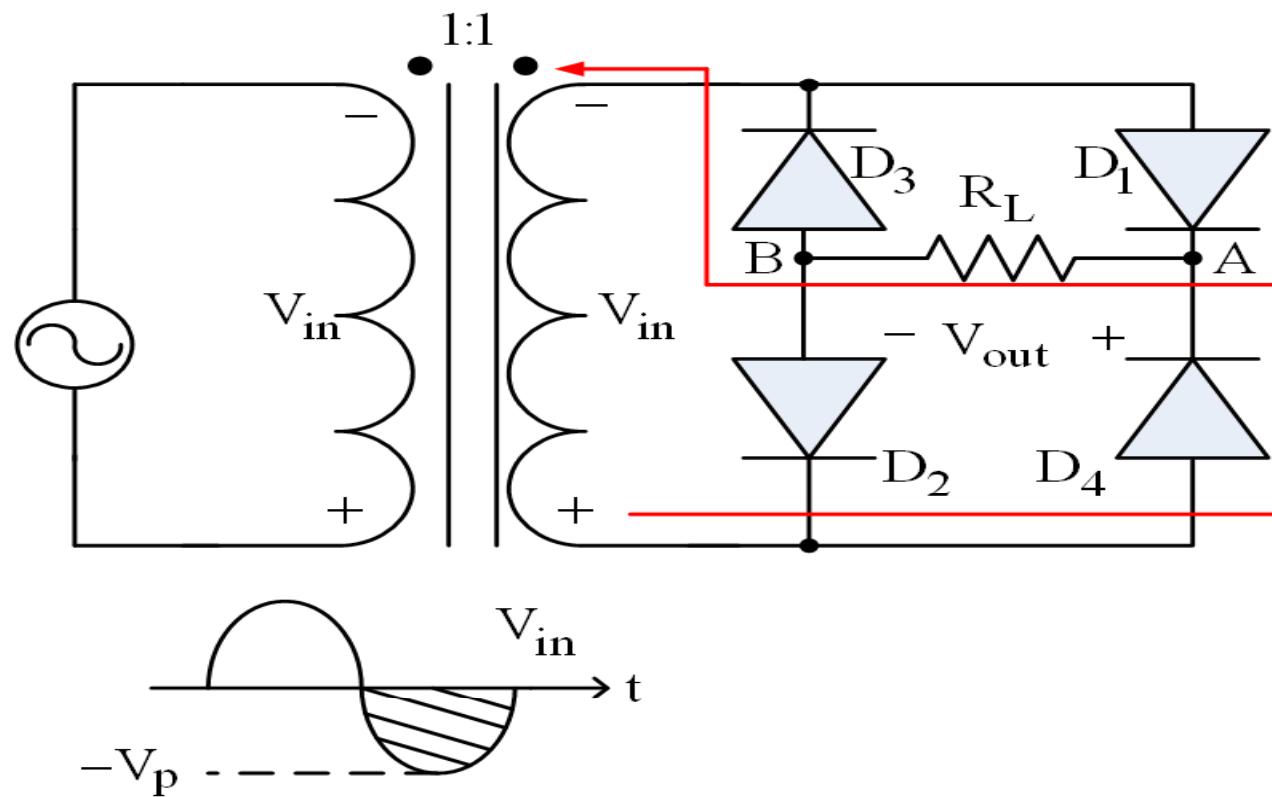
During -ve half cycle, D_3 and D_4 are fb. V_{out} is still +ve at A and -ve at B.




$$V_{\text{out}} = V_{\text{in}}$$

If $V_{in} = V_p$,

$$V_{out} = V_p$$

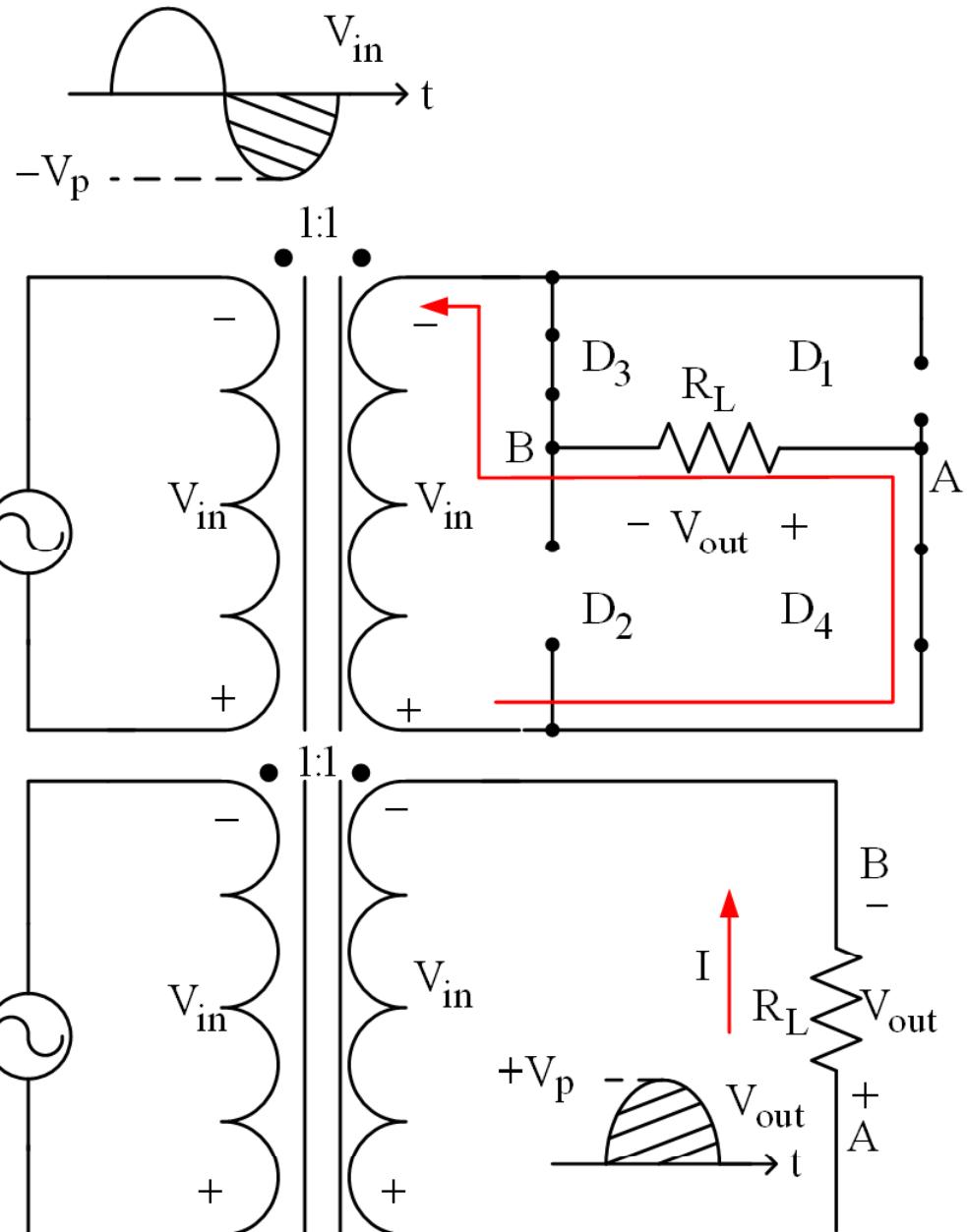

Overall performance


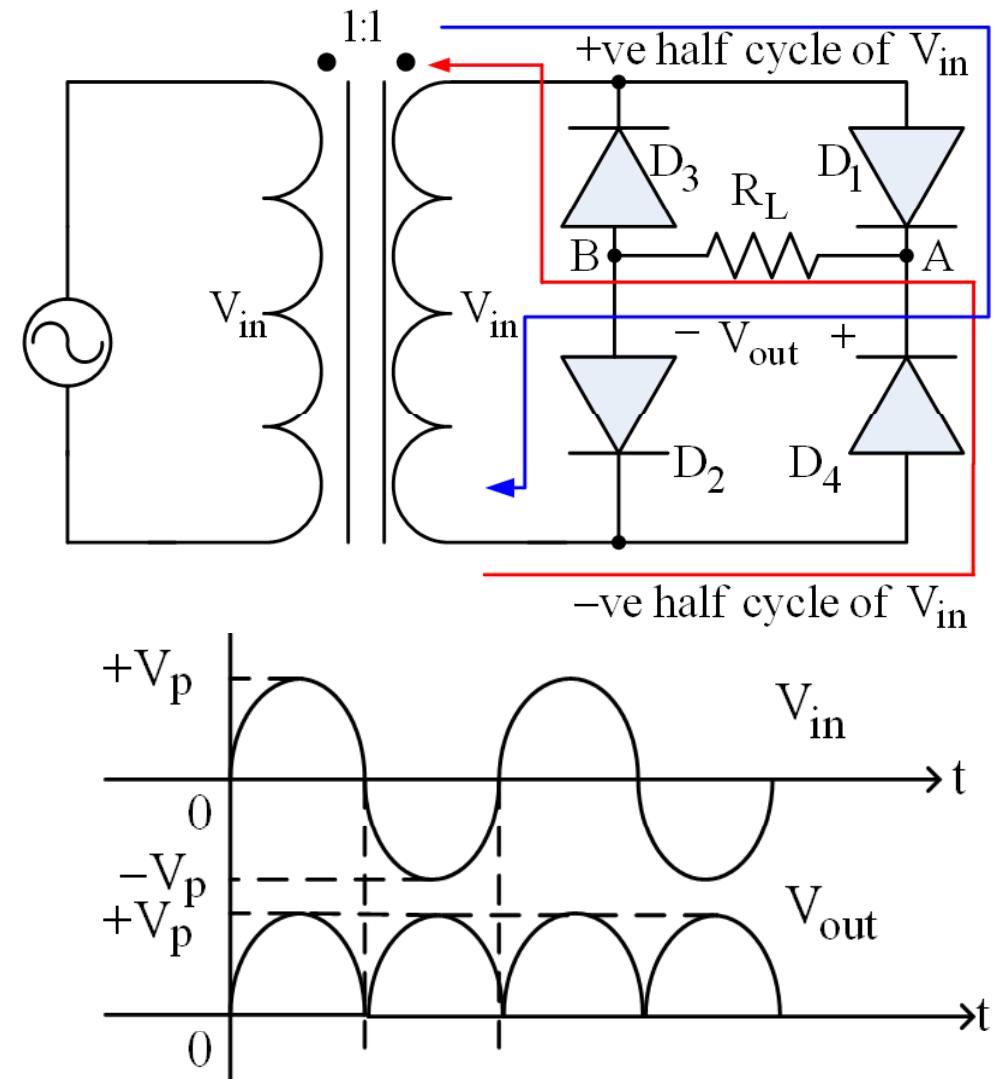


If potential barrier of the diode is considered:

$$V_{in} = 2V_o + V_{out}$$

$$V_{out} = V_{in} - 2V_o$$

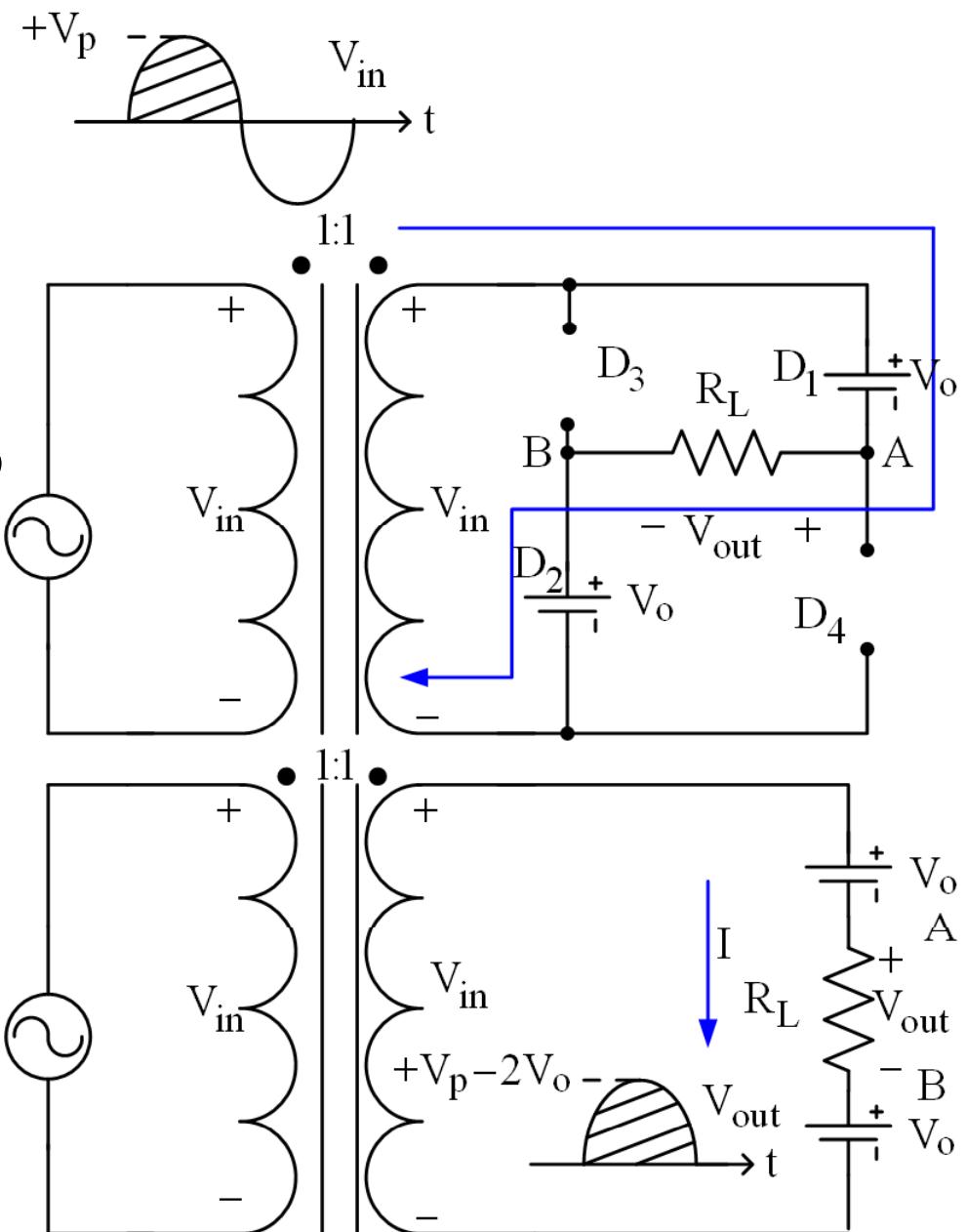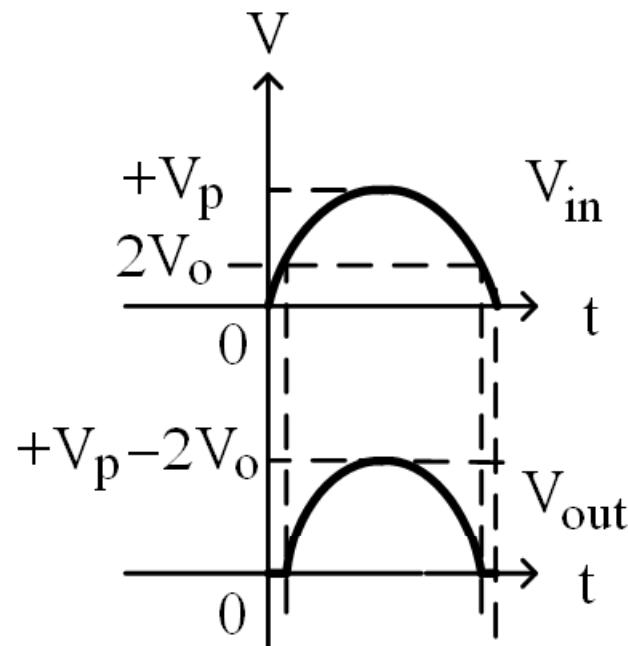D₁ and D₂ will only be fb if $V_{in} > 2V_o$





If potential barrier of the diode is considered:


$$V_{in} = 2V_o + V_{out}$$

$$V_{out} = V_{in} - 2V_o$$

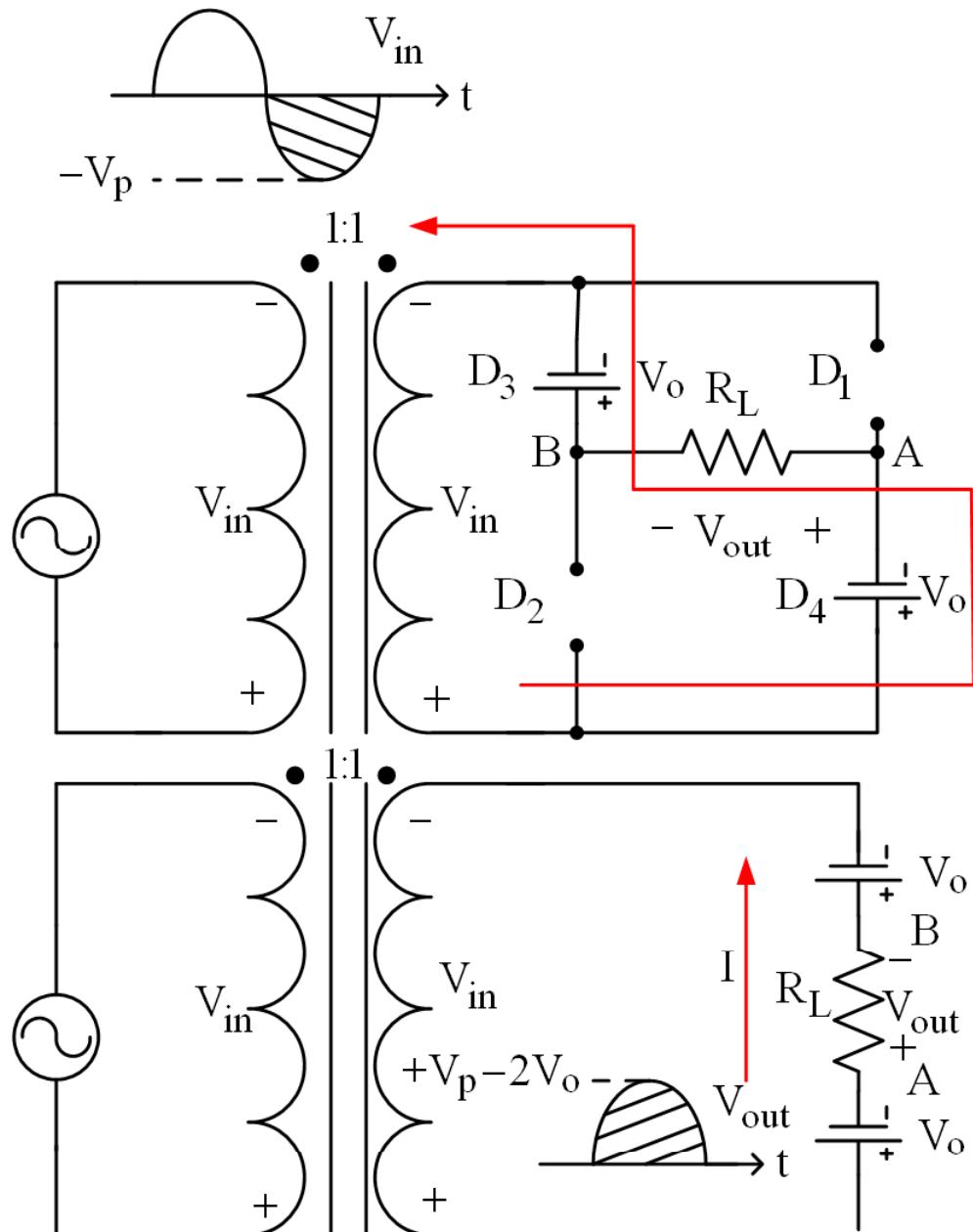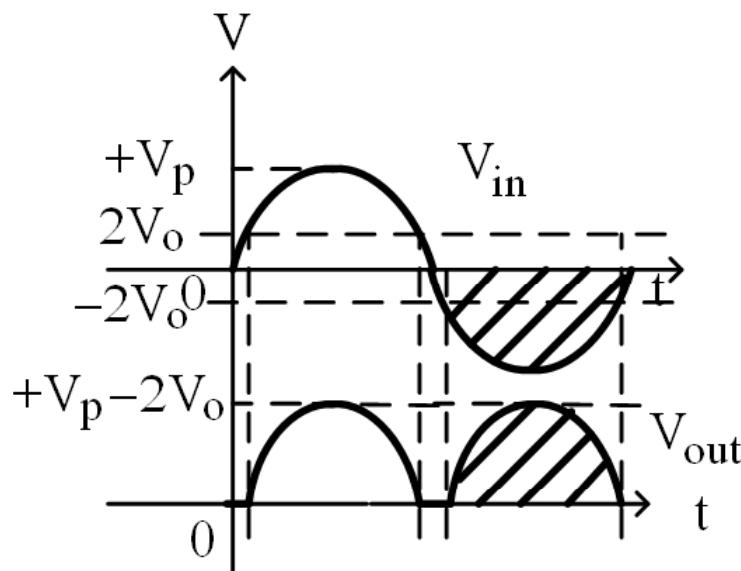D₃ and D₄ will only be fb if V_{in} > 2V_o



Overall performance:

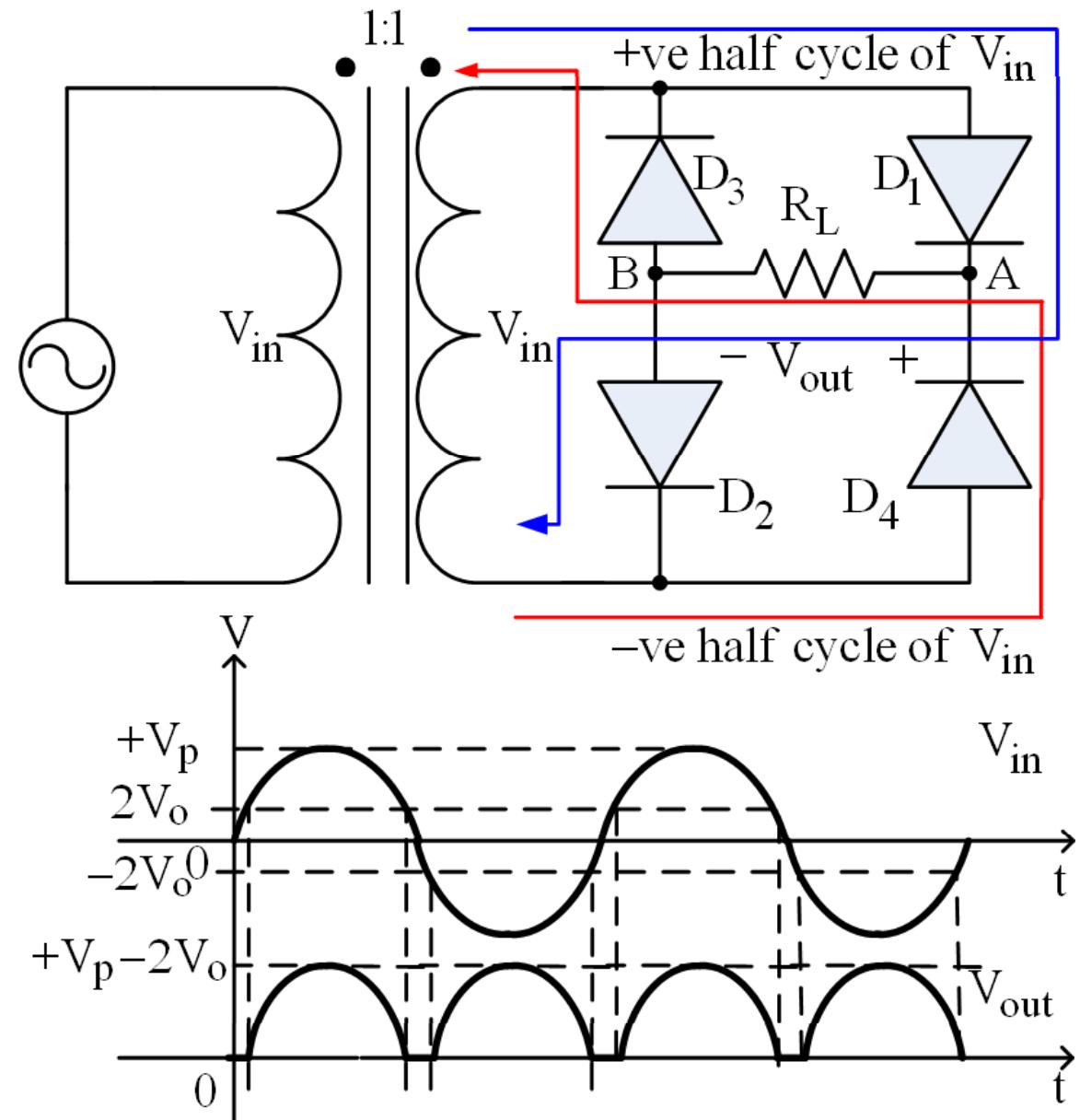

PIV of the diodes in the bridge full-wave rectifier

To determine PIV_{D1} and PIV_{D2} , analyze the circuit when V_{in} is at its negative half cycle.

When determining PIV of the diodes,

$$V_{in} = V_p$$

$$V_p - V_{out} = 0$$

$$PIV_{D2} - V_{out} + PIV_{D1} - V_p = 0$$


$$PIV_{D2} + PIV_{D1} - V_p = V_{out}$$

Assuming the diodes are identical and therefore $PIV_{D2} = PIV_{D1}$

$$V_p - (PIV_{D2} + PIV_{D1} - V_p) = 0$$

$$2V_p - 2PIV = 0$$

$$PIV = V_p$$

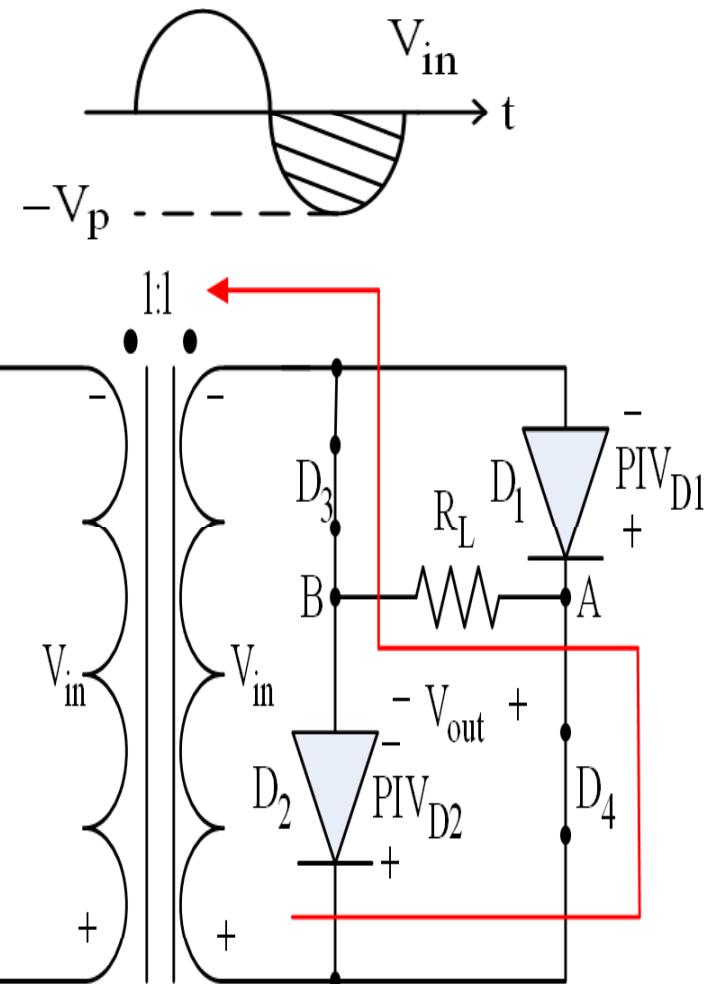

If the potential barrier of each diode is taken into consideration:

$$V_p - 2V_o - V_{out} = 0$$

$$PIV_{D2} - V_{out} + PIV_{D1} - V_p = 0$$

$$PIV_{D2} + PIV_{D1} - V_p = V_{out}$$

$$V_p - 2V_o - (PIV_{D2} + PIV_{D1} - V_p) = 0$$

Assuming the diodes are identical and therefore $PIV_{D2}=PIV_{D1}=PIV$

$$2V_p - 2V_o - 2PIV = 0$$

$$PIV = V_p - V_o$$

