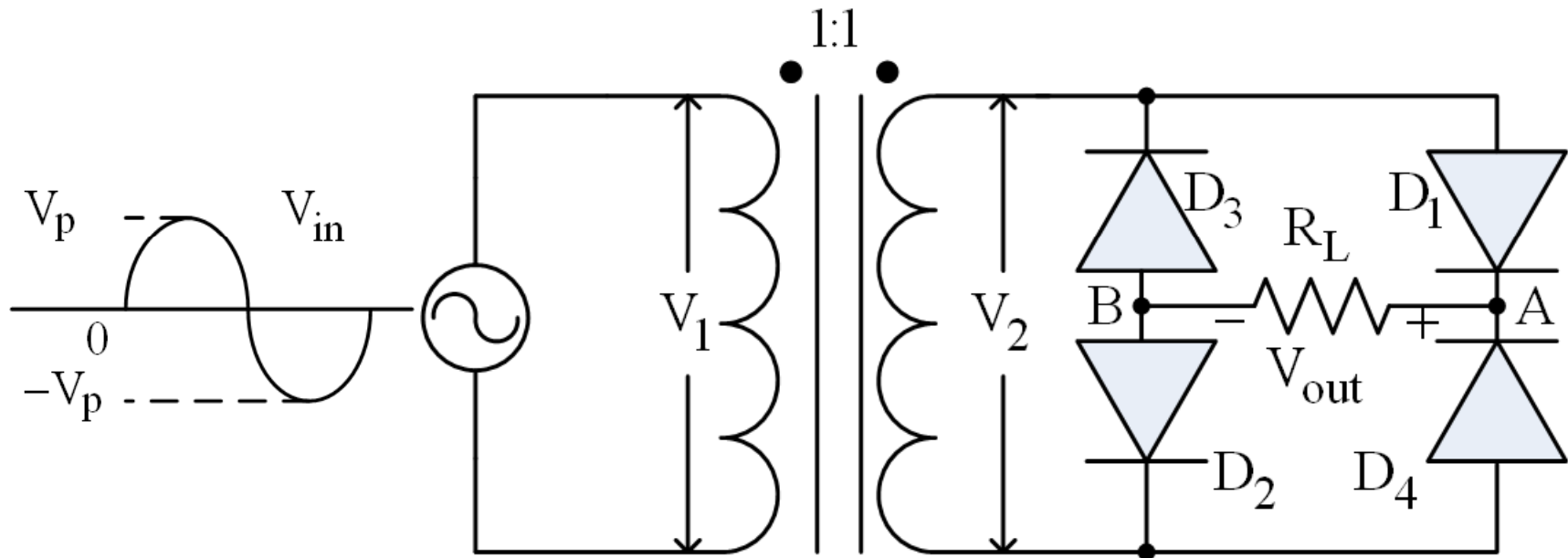



# CLASS 11

Bridge full-wave rectifier, rectifier-filter circuit, clipping/limiting and clamping diode circuits


# Bridge full-wave rectifier



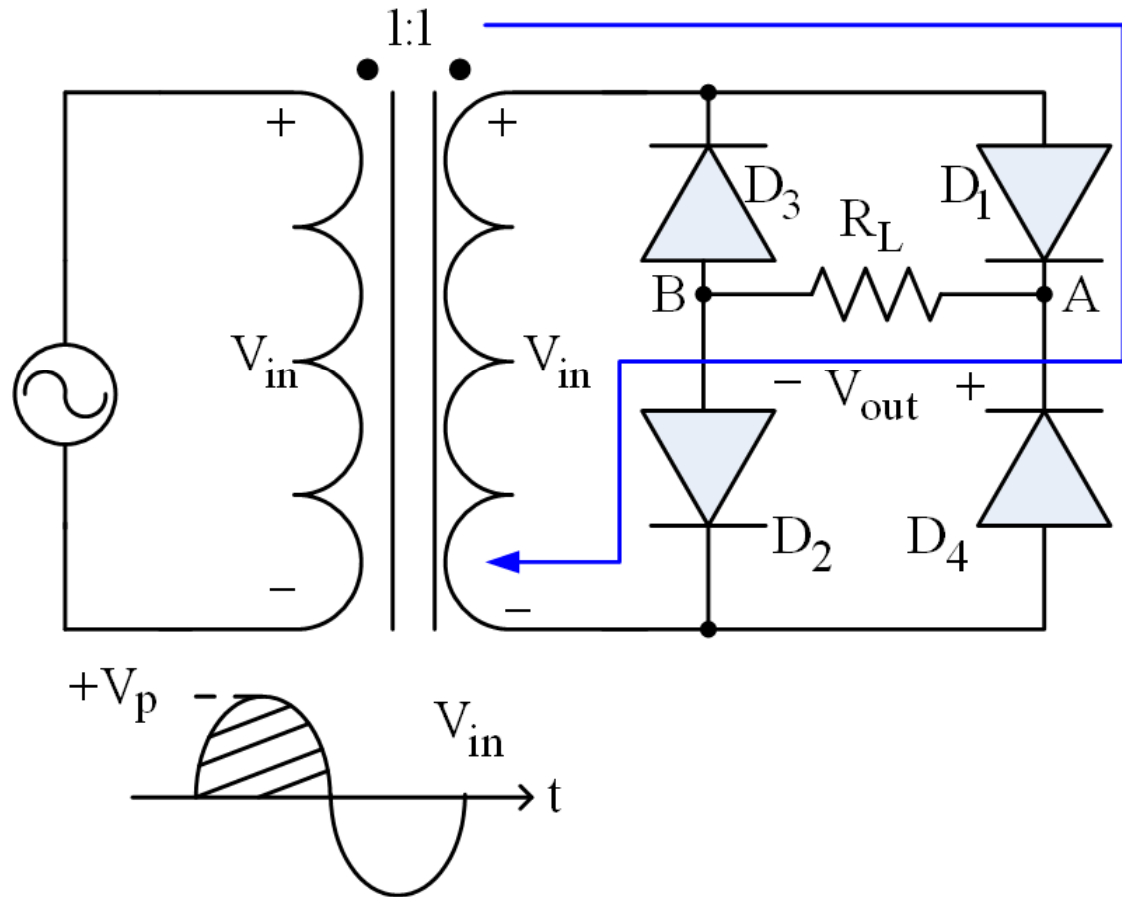
**During +ve half cycle,  $D_1$  and  $D_2$  are fb.  $V_{out}$  is +ve at A and -ve at B.**



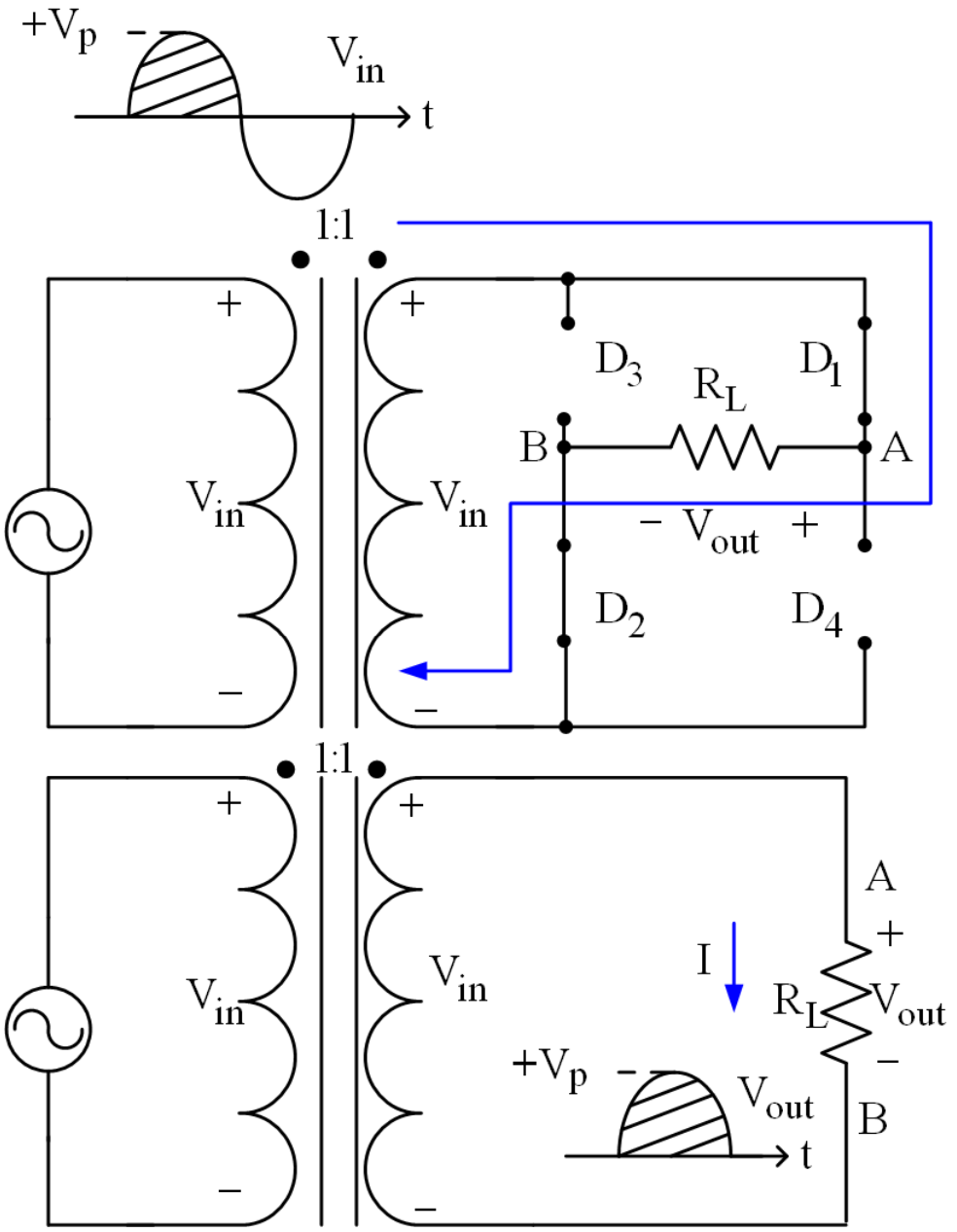
$V_{out} = V_{in}$   
**If  $V_{in} = V_p$ ,**  
 $V_{out} = V_p$




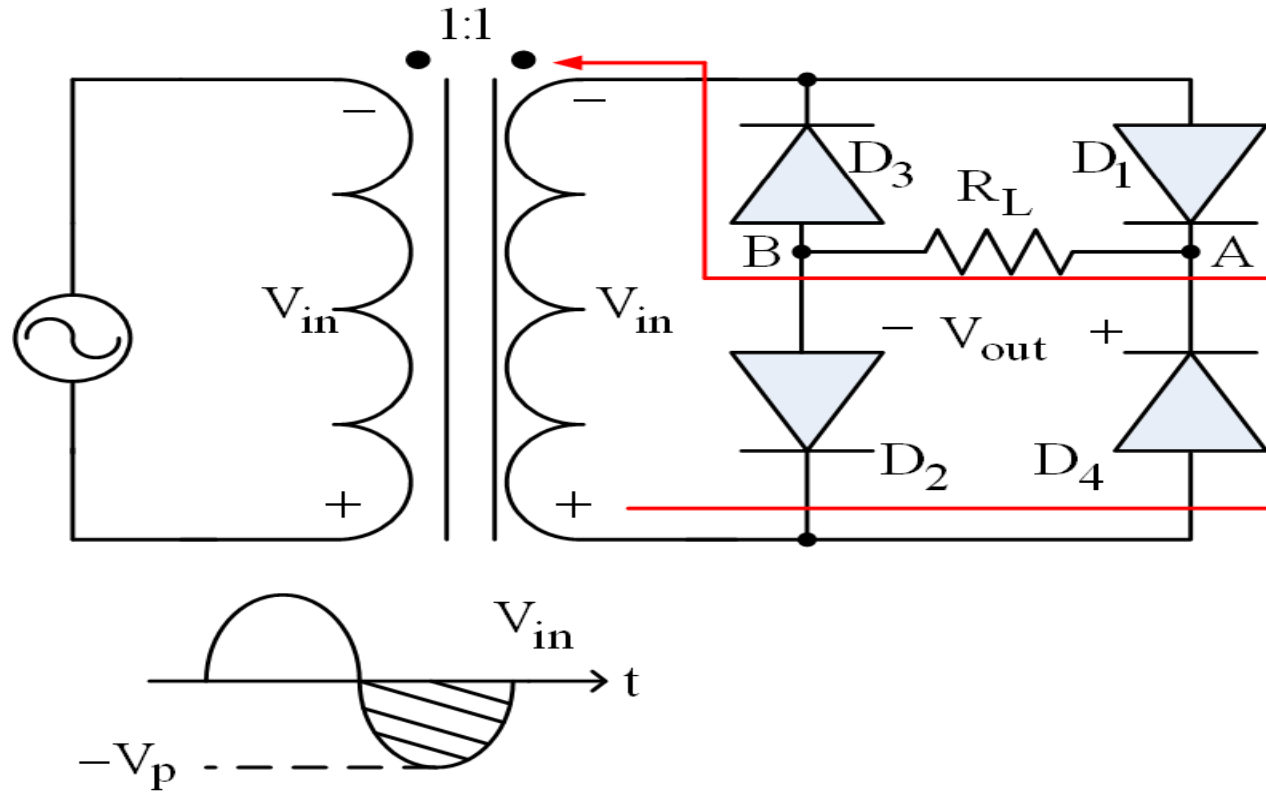
**During -ve half cycle,  $D_3$  and  $D_4$  are fb.  $V_{out}$  is still +ve at A and -ve at B.**



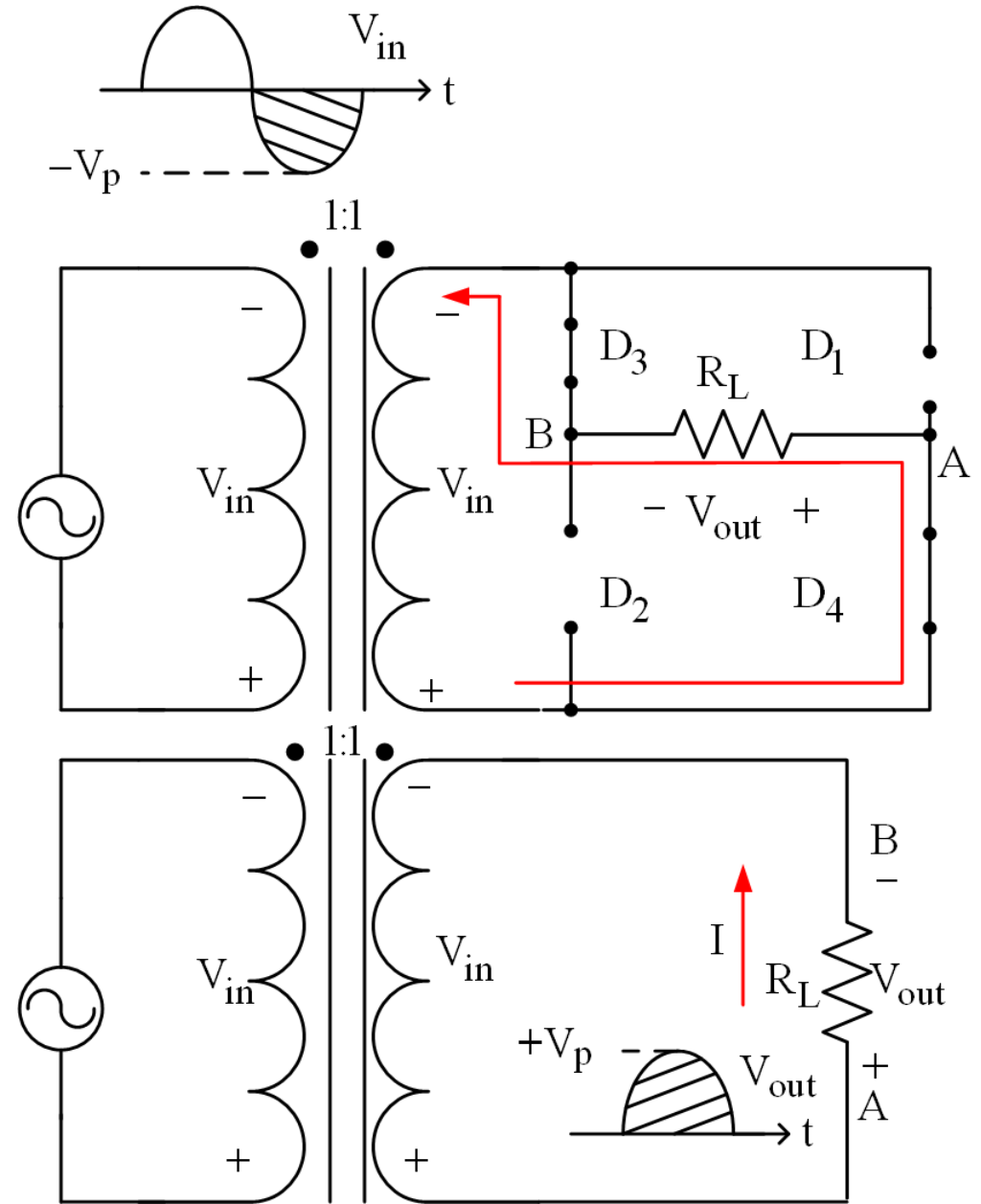$V_{out} = V_{in}$   
**If  $V_{in} = V_p$ ,**  
 $V_{out} = V_p$



# Overall performance

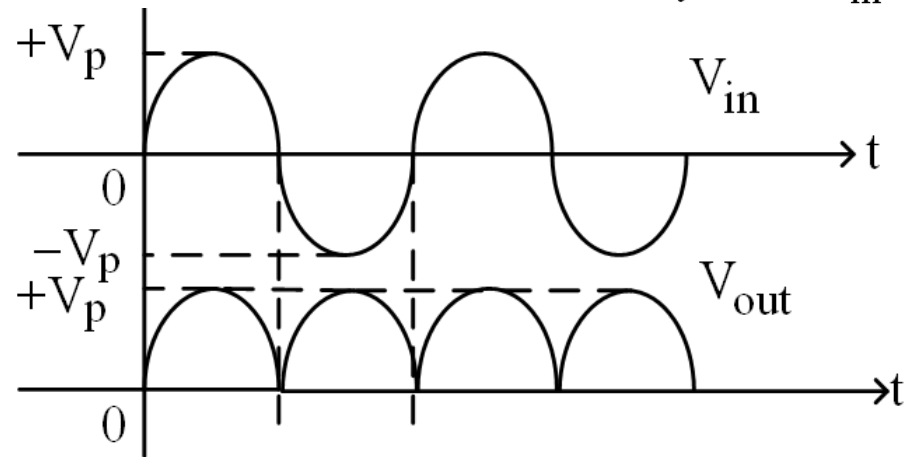
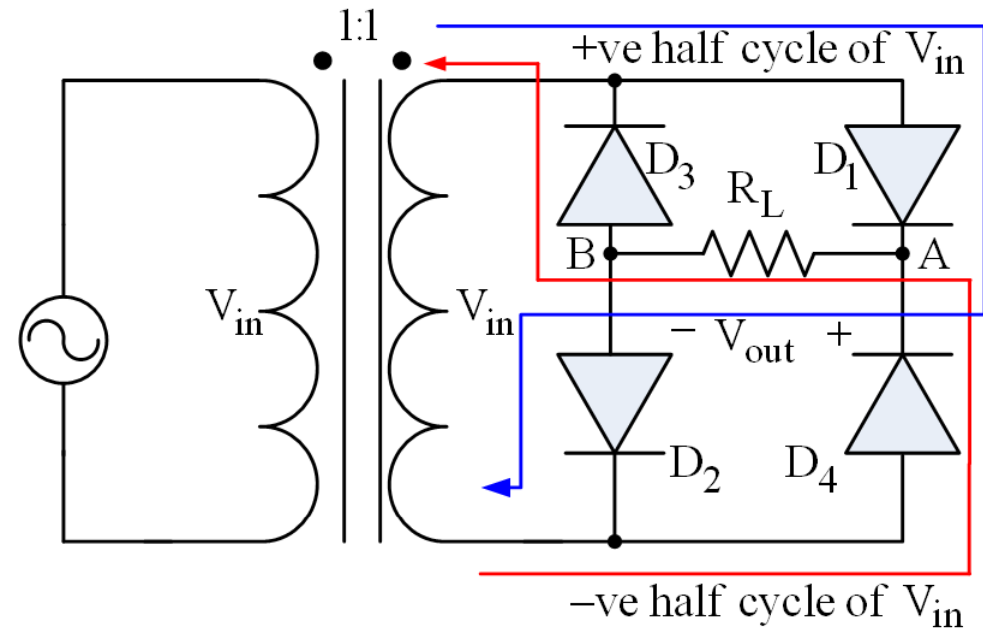


**If potential barrier of the diode is considered:**

$$V_{in} = 2V_o + V_{out}$$

$$V_{out} = V_{in} - 2V_o$$

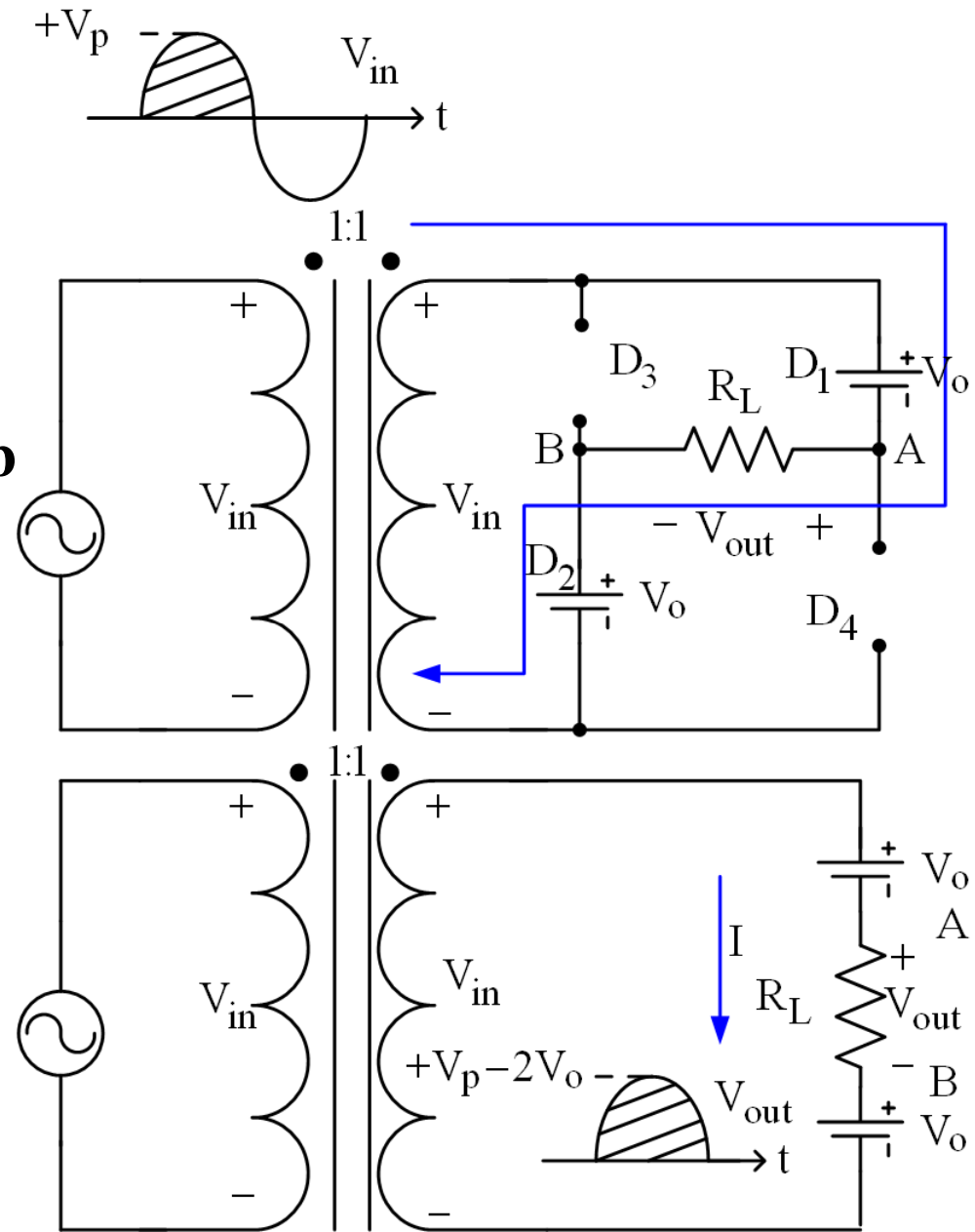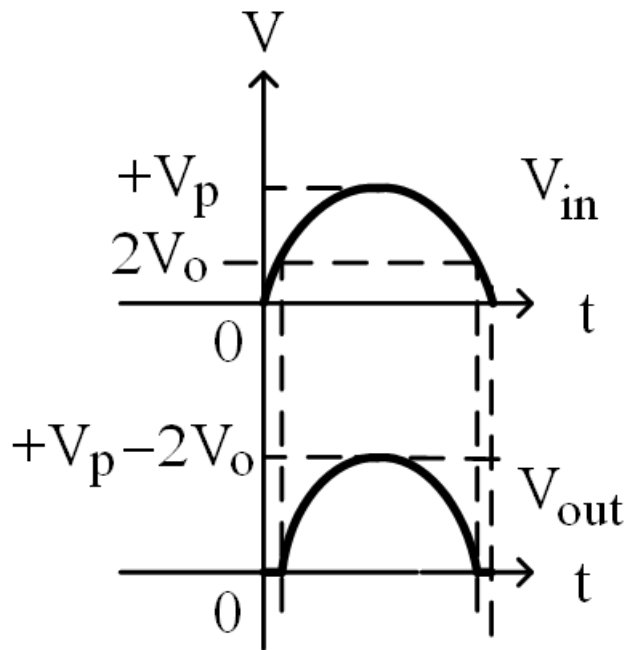**$D_1$  and  $D_2$  will only be fb if  $V_{in} > 2V_o$**







**If potential barrier of the diode is considered:**



$$V_{in} = 2V_o + V_{out}$$

$$V_{out} = V_{in} - 2V_o$$

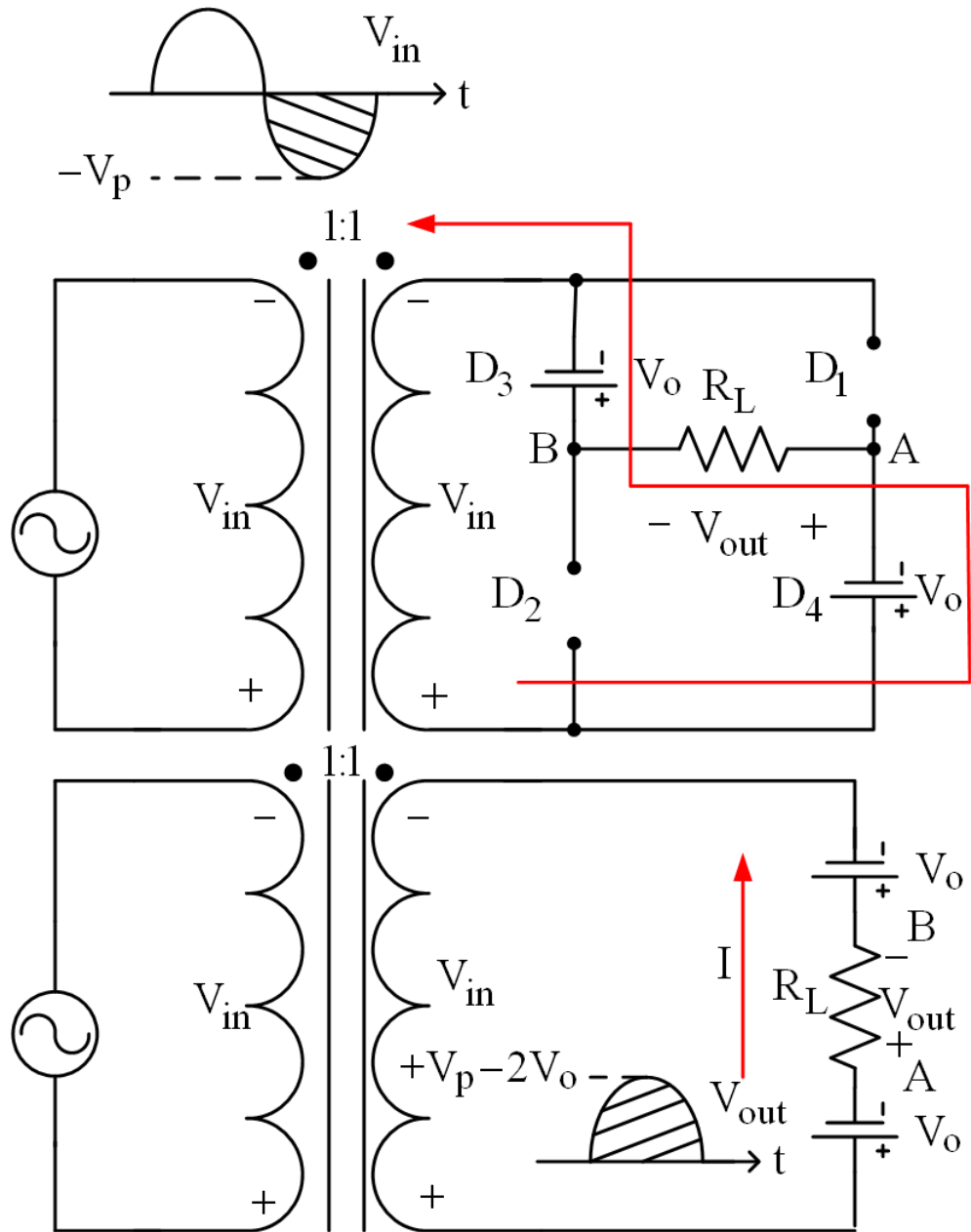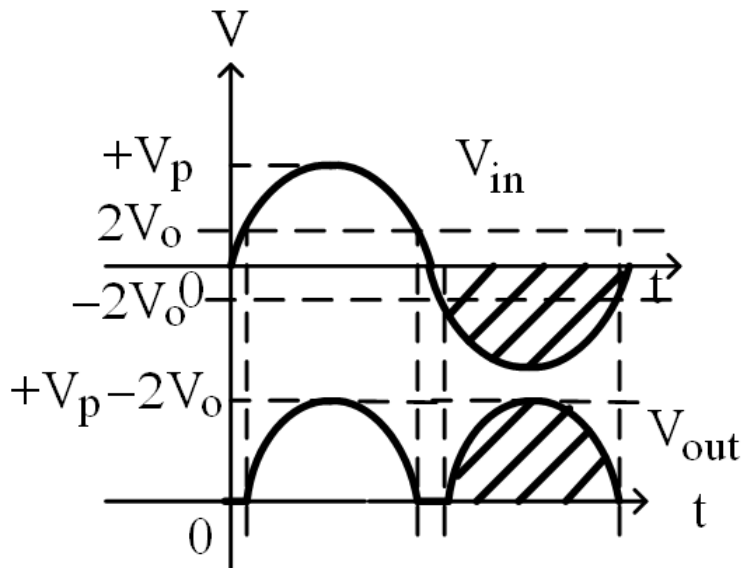**$D_3$  and  $D_4$  will only be fb if  $V_{in} > 2V_o$**



# Overall performance:

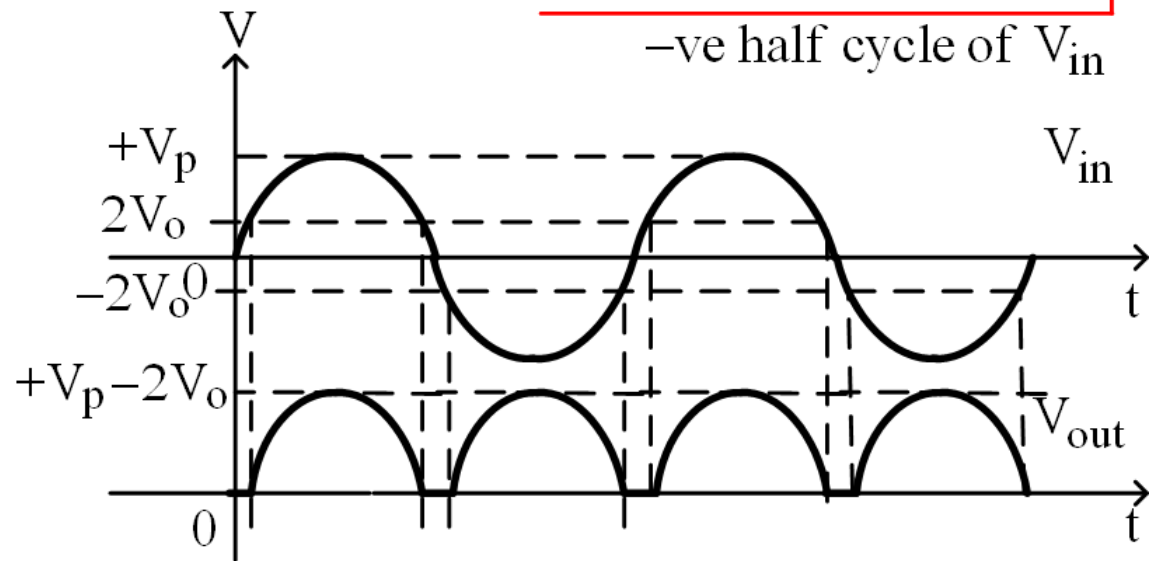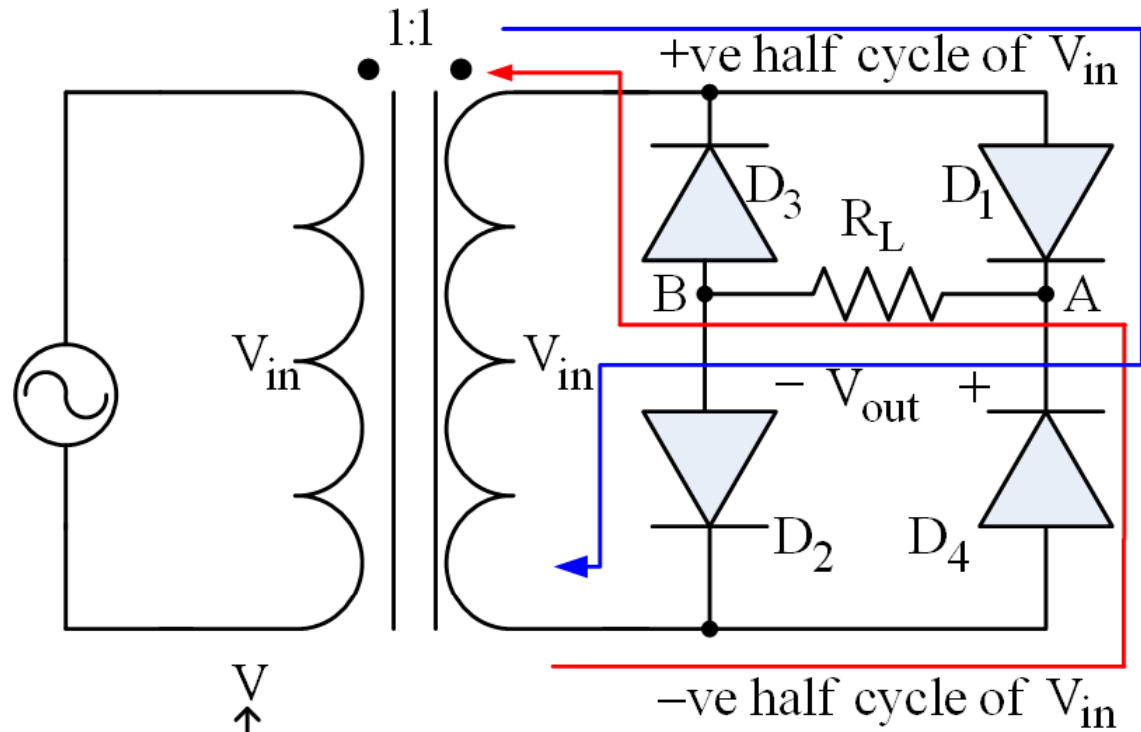

# PIV of the diodes in the bridge full-wave rectifier

To determine  $PIV_{D1}$  and  $PIV_{D2}$ , analyze the circuit when  $V_{in}$  is at its negative half cycle.

When determining PIV of the diodes,

$$V_{in} = V_p$$

$$V_p - V_{out} = 0$$

$$PIV_{D2} - V_{out} + PIV_{D1} - V_p = 0$$


$$PIV_{D2} + PIV_{D1} - V_p = V_{out}$$

Assuming the diodes are identical and therefore  $PIV_{D2} = PIV_{D1}$

$$V_p - (PIV_{D2} + PIV_{D1} - V_p) = 0$$

$$2V_p - 2PIV = 0$$

$$PIV = V_p$$


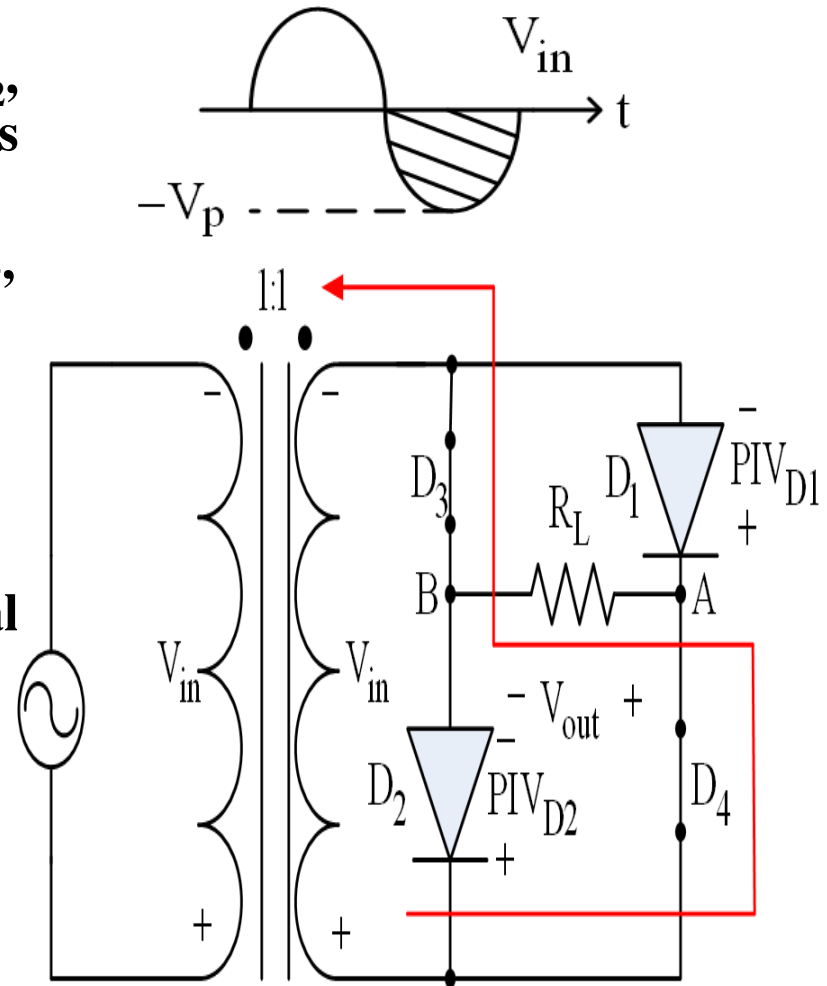




# Rectifier-filter circuit

- **This circuit reduces the rise and fall of the rectifier's output voltage. Hence, the dc voltage level is quite constant.**
- **The constant dc voltage and current sources are needed by electronic circuits for power and biasing purposes in order to operate.**
- **The rectifier-filter circuit is implemented using a capacitor or an inductor or the combination of both.**

### Rectifier-filter circuit

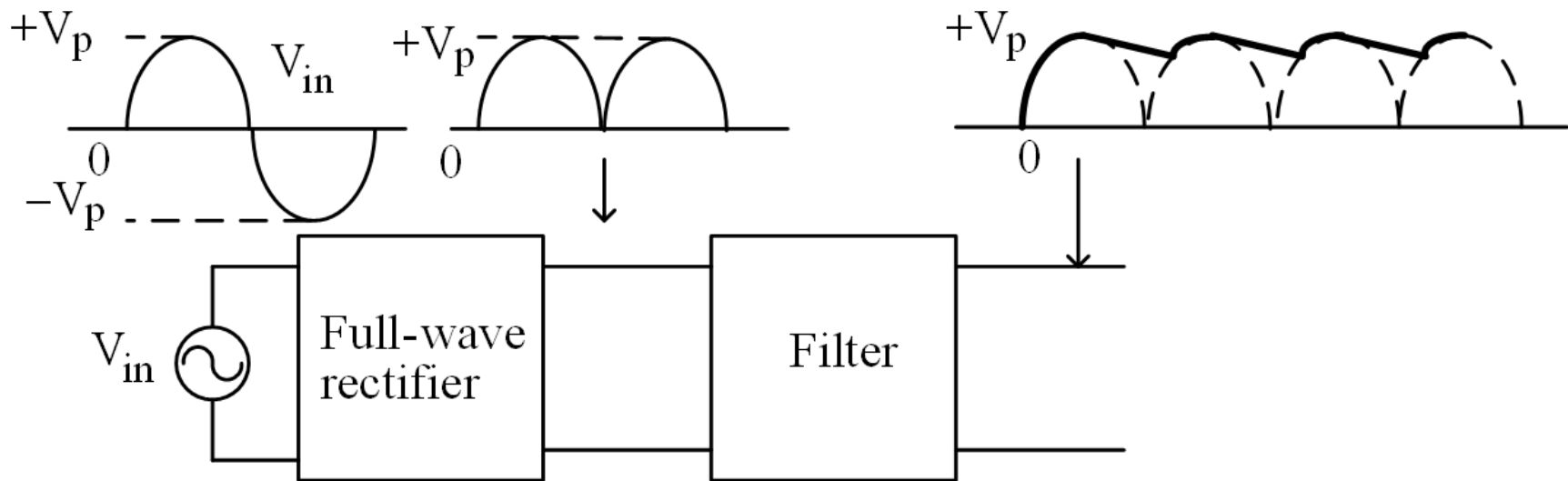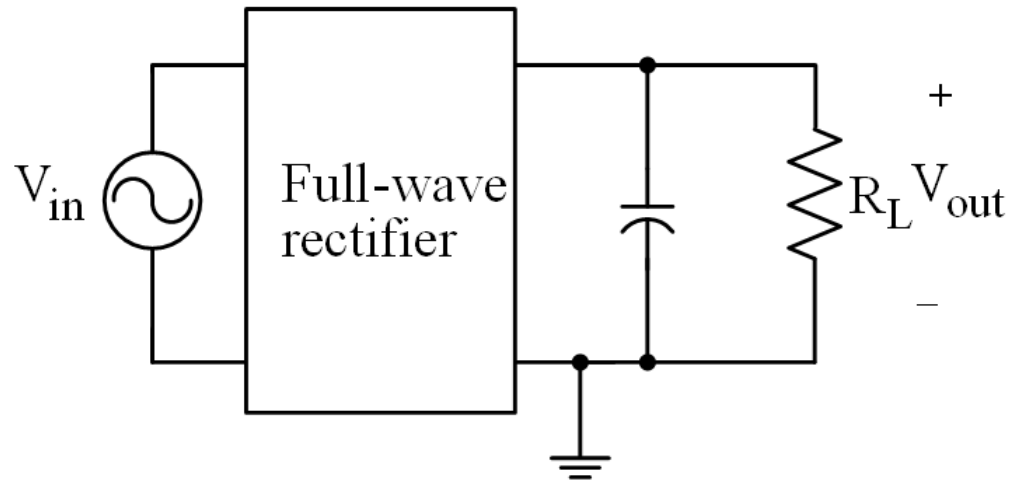


**For a rectifier-filter circuit with the rectifier from the half-wave type:**

**(1) Diode fb. C charged to  $V_p$ .  $V_C = V_{out}$  as C and  $R_L$  are in parallel.**

**(2) Diode rb. Diode is an o/c. C discharge through  $R_L$ .**

$$V_{out} = V_C = V_p e^{-t/(R_L C)}$$

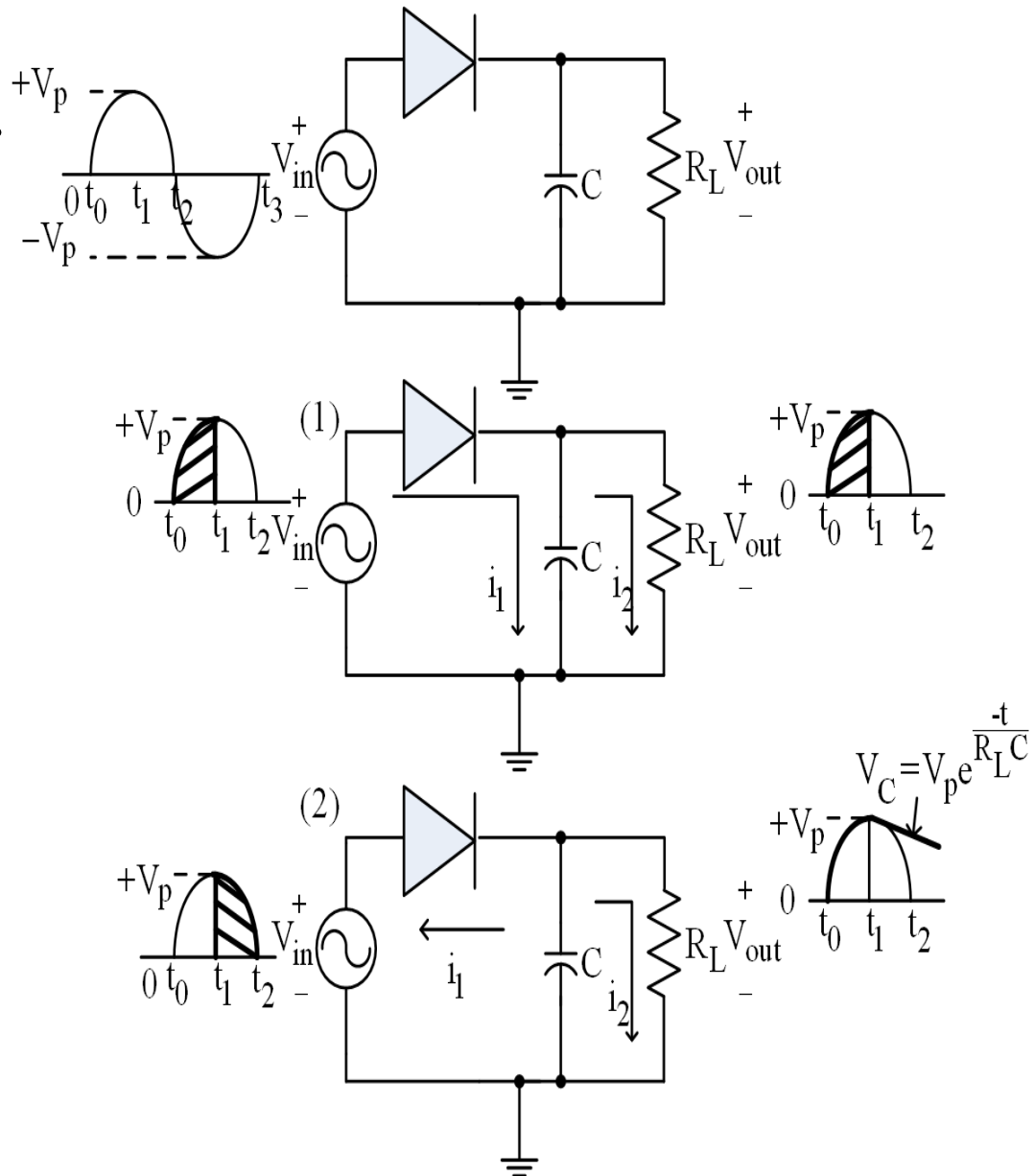


**(3)  $V_{out} = V_C = V_p e^{-t/(R_L C)}$**

**$t_3 \rightarrow t_4$ ,  $V_{in}$  is +ve but  $V_{in} < V_C$ .**


**Diode is still rb. C still discharging through  $R_L$ .**

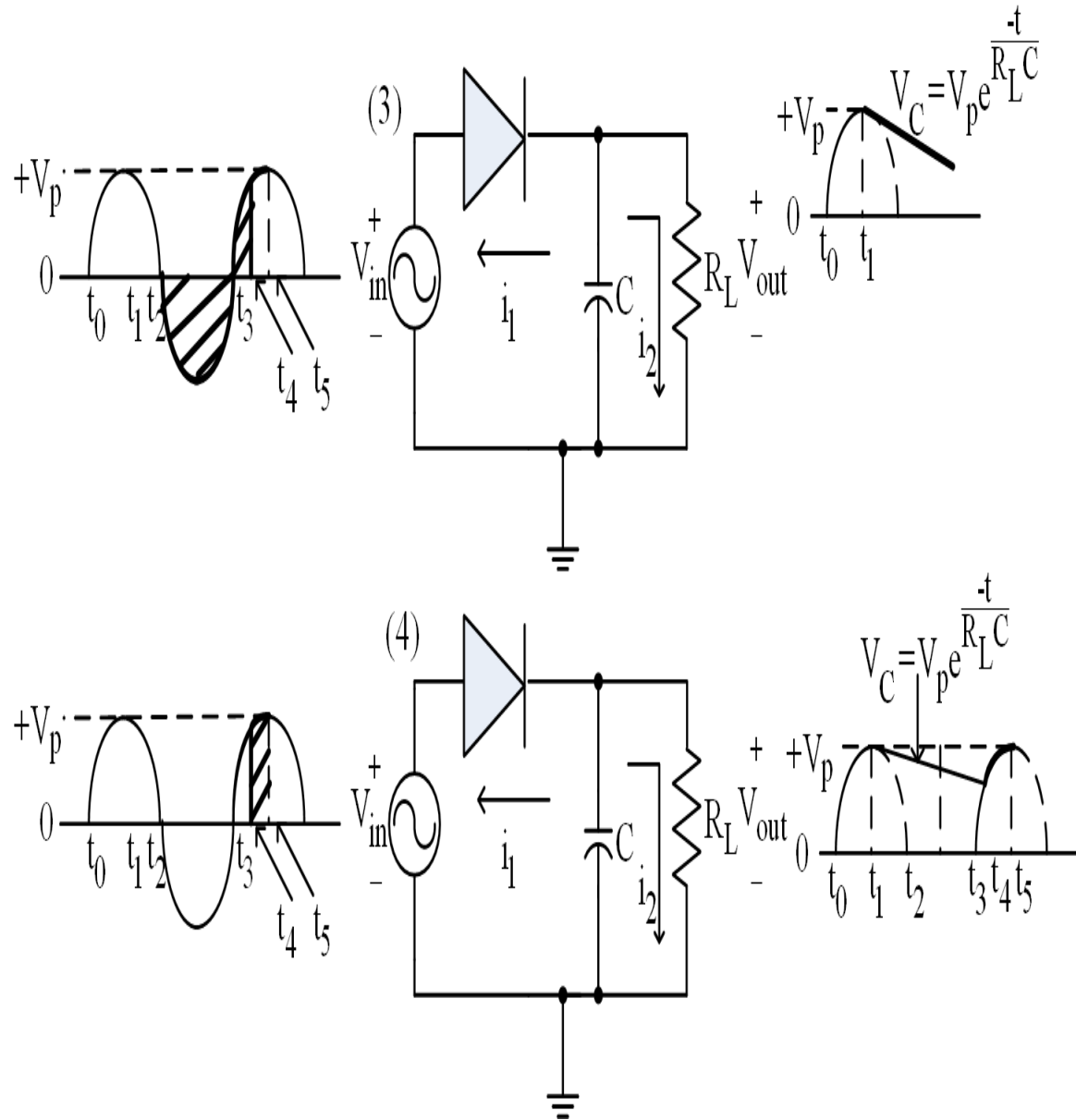**(4)  $t_4 \rightarrow t_5$ ,  $V_{in}$  is +ve and  $V_{in} > V_C$ . Diode is fb. Diode is s/c.  $V_{in}$  is charging C back to  $V_p$ .**





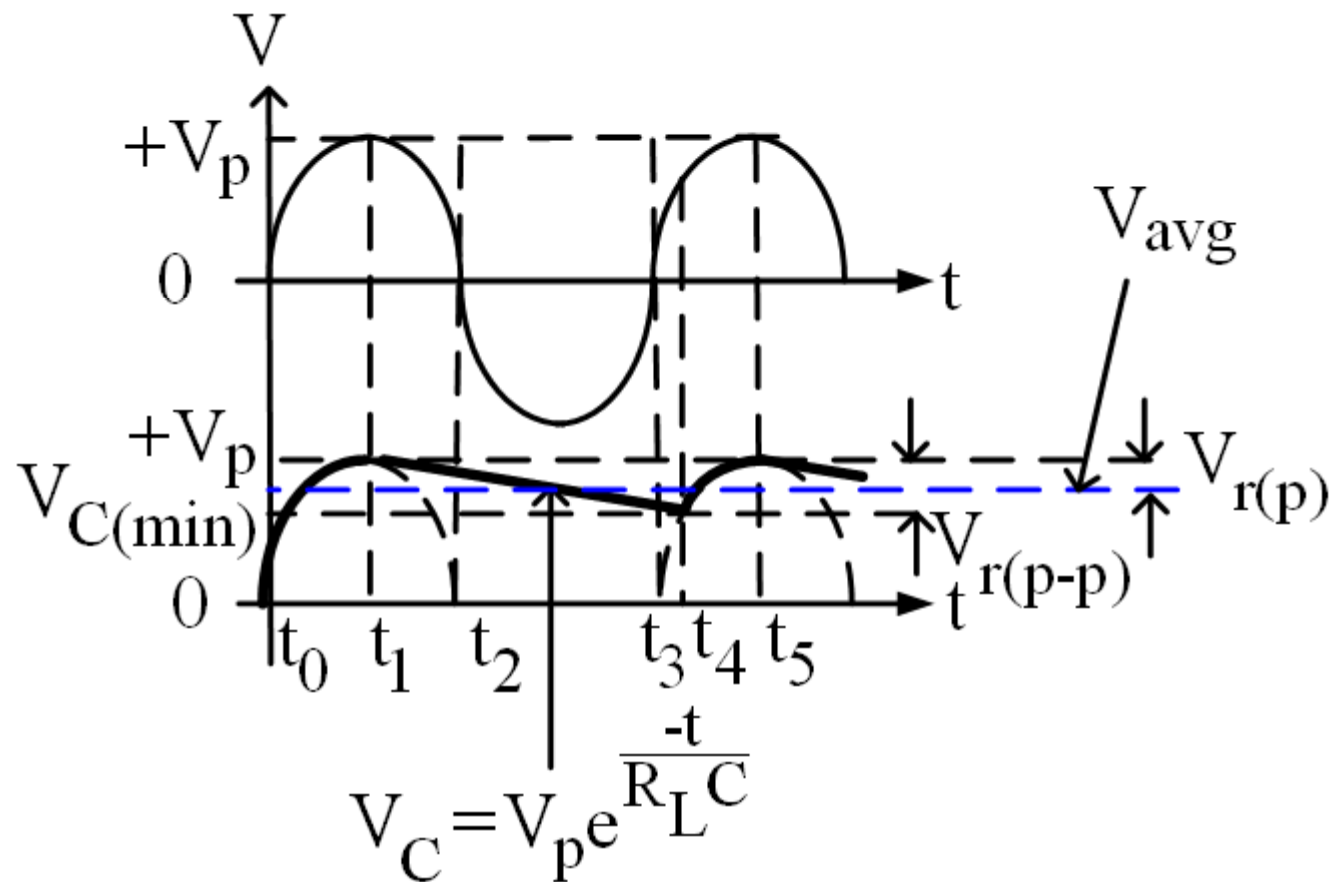
**Output of the rectifier-filter circuit with the rectifier from the half-wave type.  $V_{r(p-p)} = V_p - V_{C(\min)}$ . Smaller ripple voltage indicates that the rectifier-filter circuit is more efficient.**



(a) is the output of a rectifier-filter circuit with the rectifier of the half-wave type. C discharges from  $t_1$  to  $t_3$ .

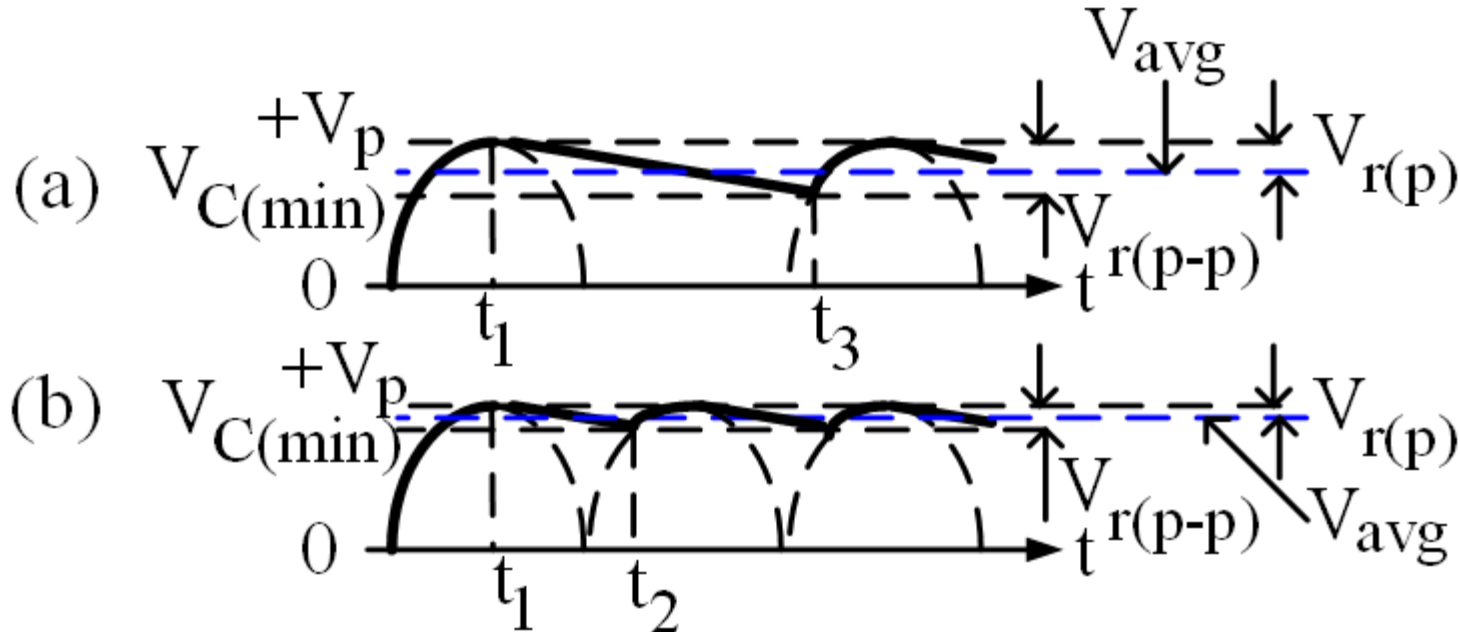(b) is the output of a rectifier-filter circuit with the rectifier of the full-wave type. C discharges from  $t_1$  to  $t_2$ .

**Discharging time is less for the full-wave rectifier-filter circuit.**  $V_{r(p-p)\_Full\text{-wave}} < V_{r(p-p)\_Half\text{-wave}}$



$V_C$  is min when  $t \approx T$

$$V_{C(\min)} = V_p e^{-\frac{T}{R_L C}}$$

Ripple voltage,  $V_{r(p-p)} = V_p - V_{C(\min)}$


$$V_{r(p-p)} = V_p - V_p e^{-\frac{T}{R_L C}}$$

$$= V_p \left( 1 - e^{-\frac{T}{R_L C}} \right)$$

$$= V_p \left( 1 - e^{-\frac{1}{R_L C f}} \right)$$

$$V_{r(p)} = \frac{V_p}{2} \left( 1 - e^{-\frac{1}{R_L C f}} \right)$$

$$V_{dc} = V_{avg} = V_p - V_{r(p)}$$

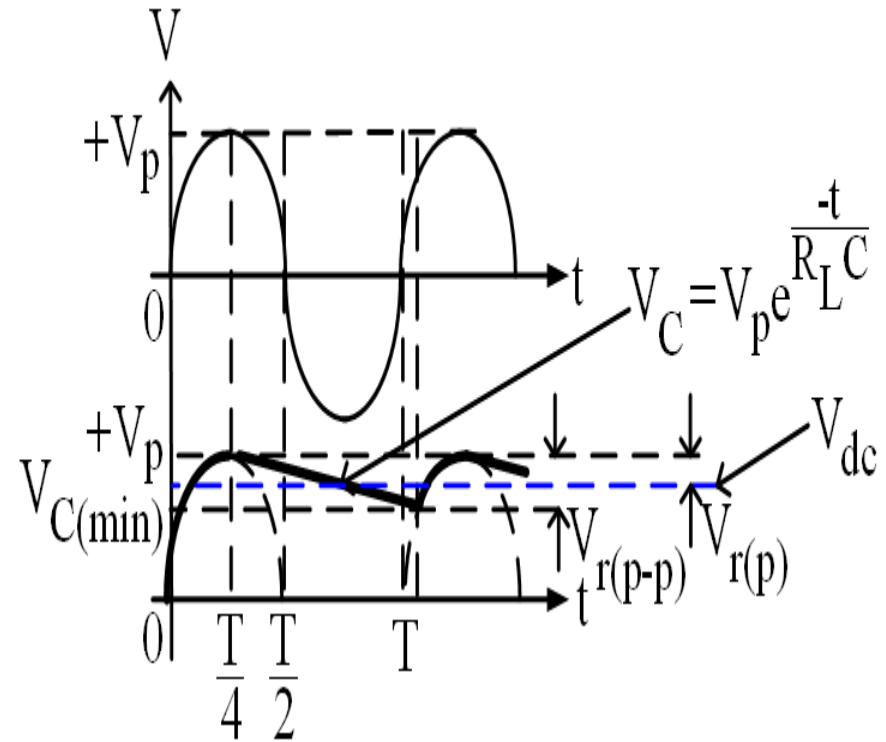

$$V_{dc} = V_p - \frac{V_p}{2} \left( 1 - e^{-\frac{1}{R_L C f}} \right)$$

$$V_{dc} = V_p \left[ 1 - \frac{1}{2} \left( 1 - e^{-\frac{1}{R_L C f}} \right) \right] = \frac{V_p}{2} \left[ 1 + e^{-\frac{1}{R_L C f}} \right]$$


$$\text{Ripple factor, } r = \frac{V_{r(p-p)}}{V_{dc}}$$

**Ripple factor,  $r$ , is a benchmark of the effectiveness of a filter. The smaller the  $r$  is, the better is the filter.  $r$  can be reduced by increasing the capacitance,  $C$ , or load resistance,  $R_L$ .**

# Clipping/Limiting Diode Circuit

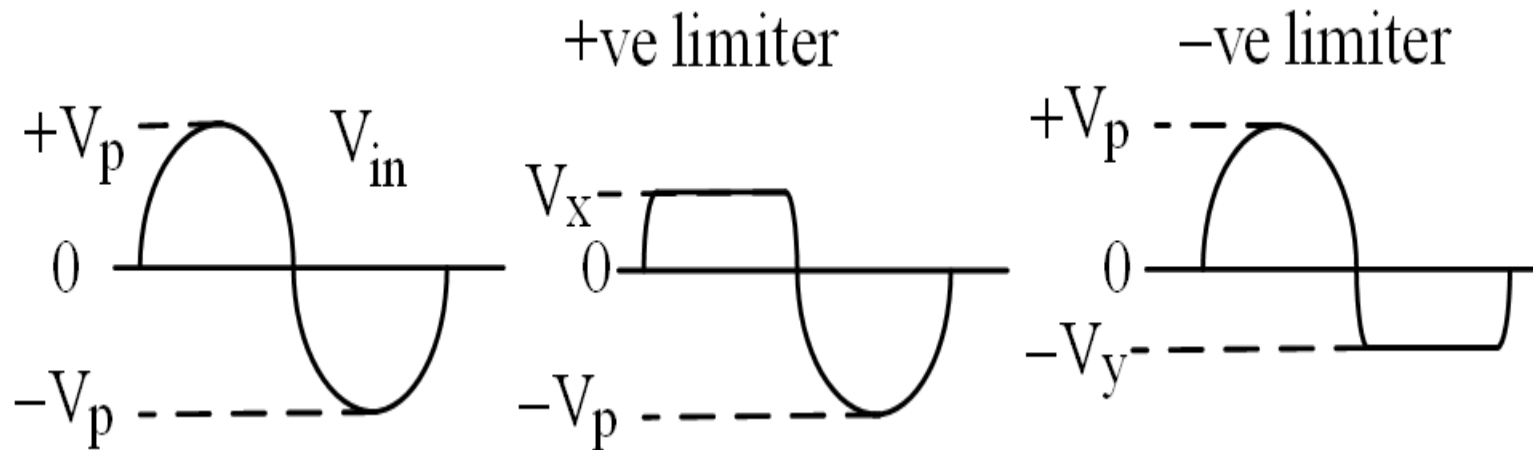
## Function:

To limit the output voltage from exceeding a certain desired value. This circuit can limit the output voltage from exceeding a certain +ve or -ve voltage.




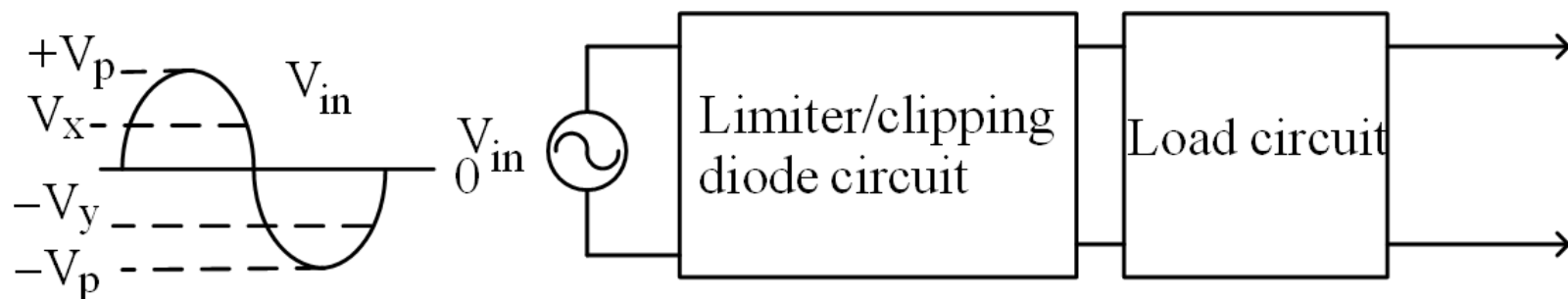
## Application:

A circuit (which in the diagram below is termed as the ‘Load circuit’) may not be able to process a voltage which is higher (or lower) than a certain value. If the source is unable to provide a signal that follows this requirement, a limiting/clipping diode circuit may need to be used.



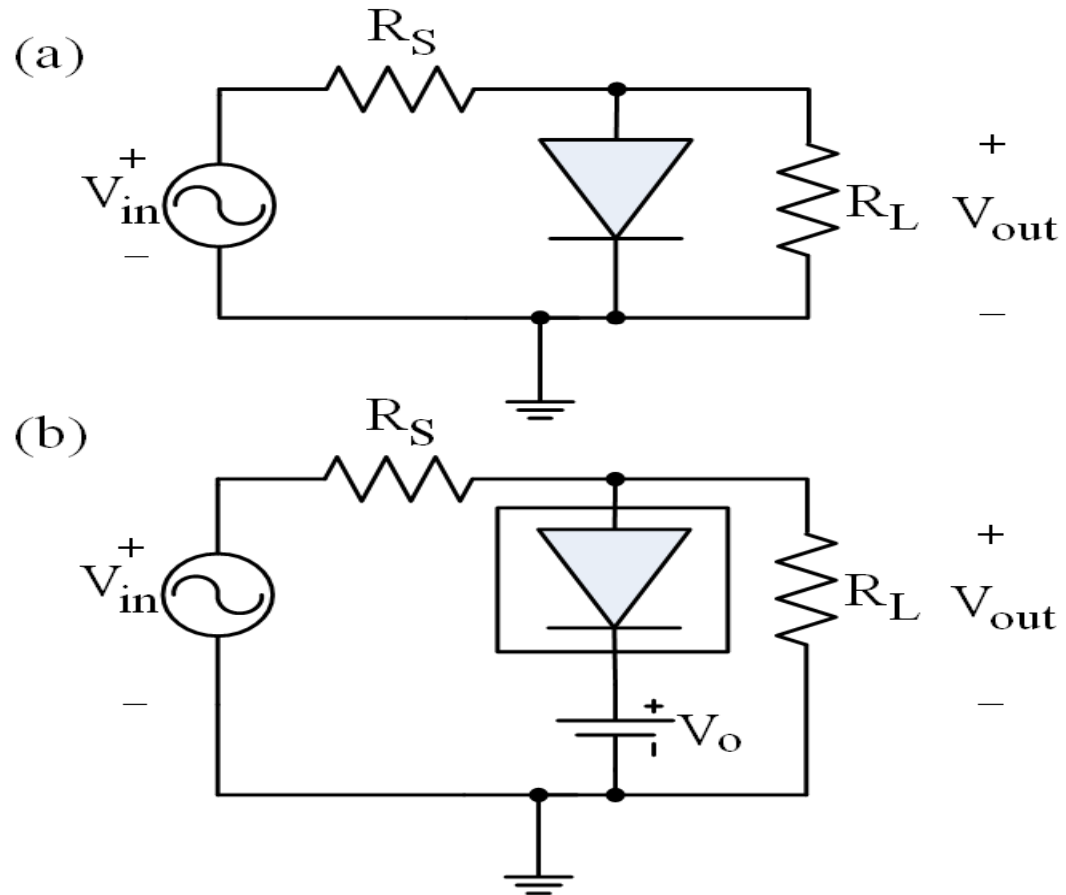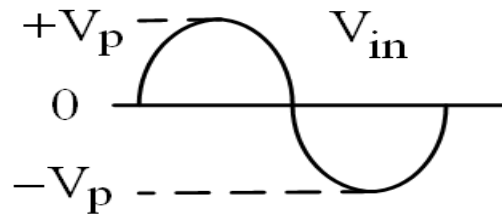- (a) is the limiting/clipping diode circuit with the potential barrier and forward resistor effects excluded.
- (b) is the limiting/clipping diode circuit with the potential barrier effect included.






**Ideal diode.**

**During the +ve half cycle, diode is fb.  
Hence,**

$$V_{out} = 0.$$

**During the -ve half cycle, diode is rb.  
Hence,**
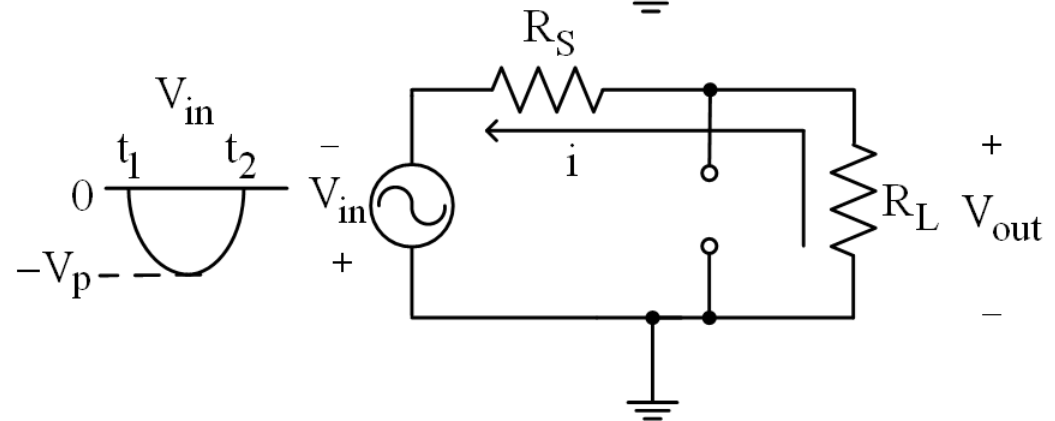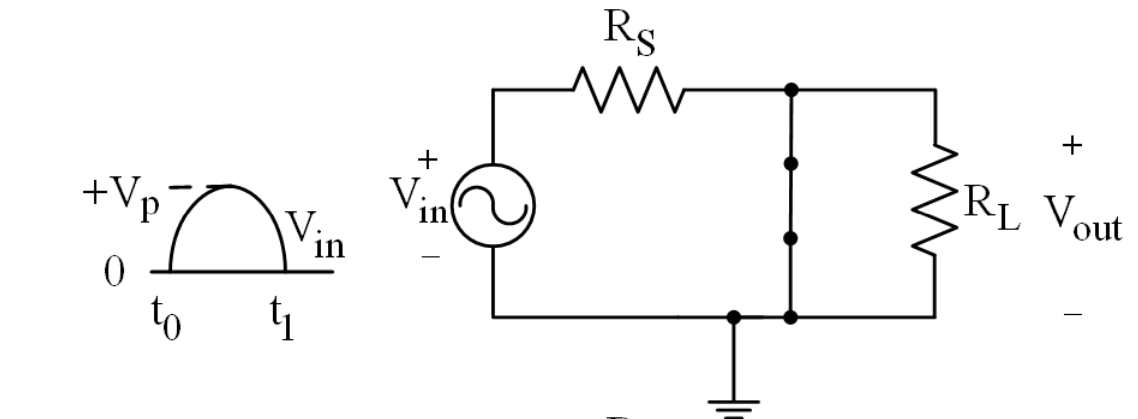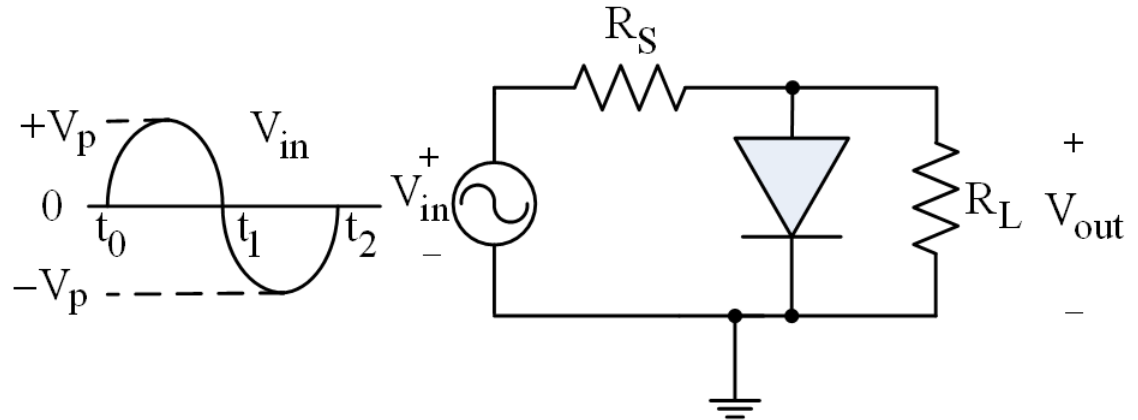
$$V_{out} = \frac{R_L}{R_L + R_S} (-V_{in})$$







**Overall performance:**

**+ve half cycle,**

**$V_{out} = 0$ .**

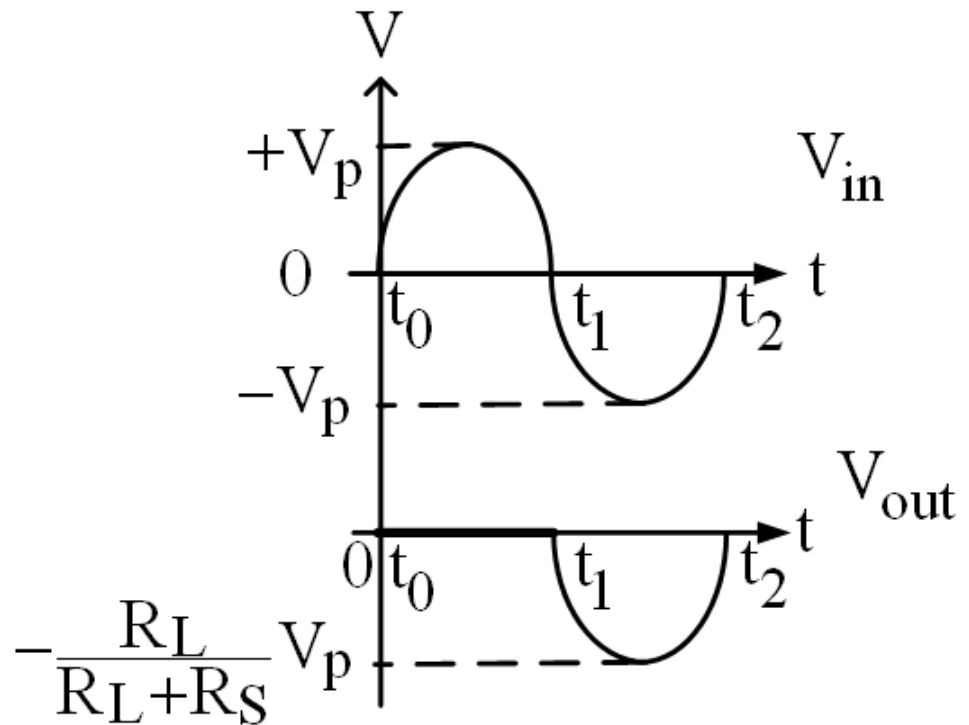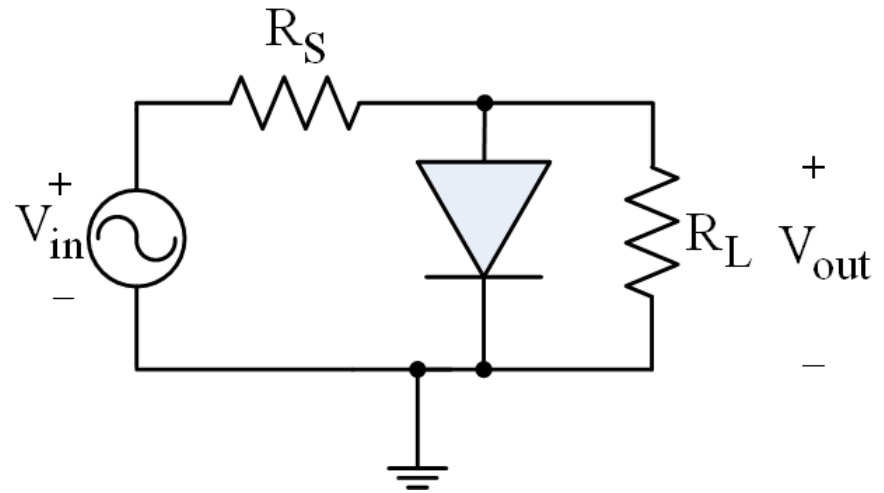**-ve half cycle,**


$$V_{out} = \frac{R_L}{R_L + R_S} (-V_{in})$$



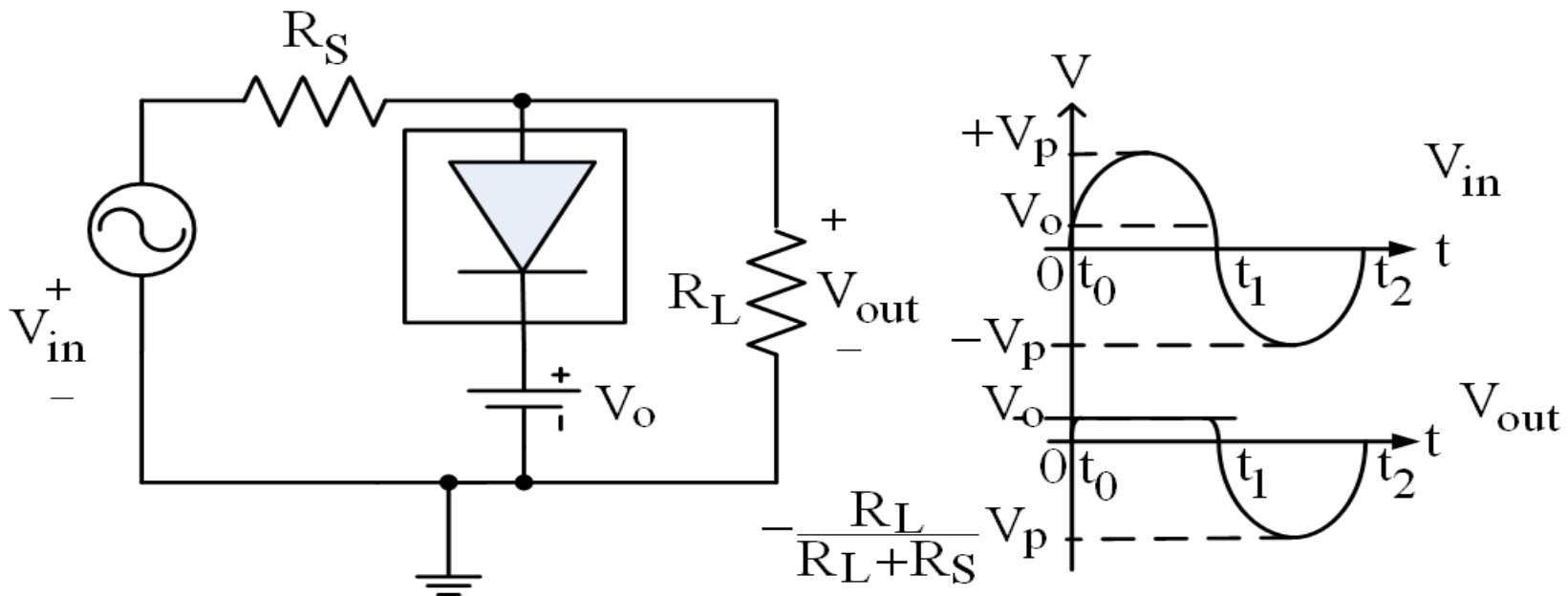**If potential barrier is considered: Diode fb (s/c) if  $V_{in} > V_o$ . Hence,  $V_{out} = V_o$ . If  $V_{in} < V_o$  or  $V_{in}$  is at its -ve half cycle, diode is rb (o/c). Hence,**

$$V_{out} = \frac{R_L}{R_L + R_S} (V_{in}) \text{ for } V_{in} < V_o \text{ and } V_{in} \text{ is +ve.}$$

$$V_{out} = \frac{R_L}{R_L + R_S} (-V_{in}) \text{ for } V_{in} \text{ during its -ve cycle.}$$





## Variable +ve clipper

**Diode fb (s/c) when  $V_{in} > V + V_o$ . Hence,  $V_{out} = V + V_o$ .**

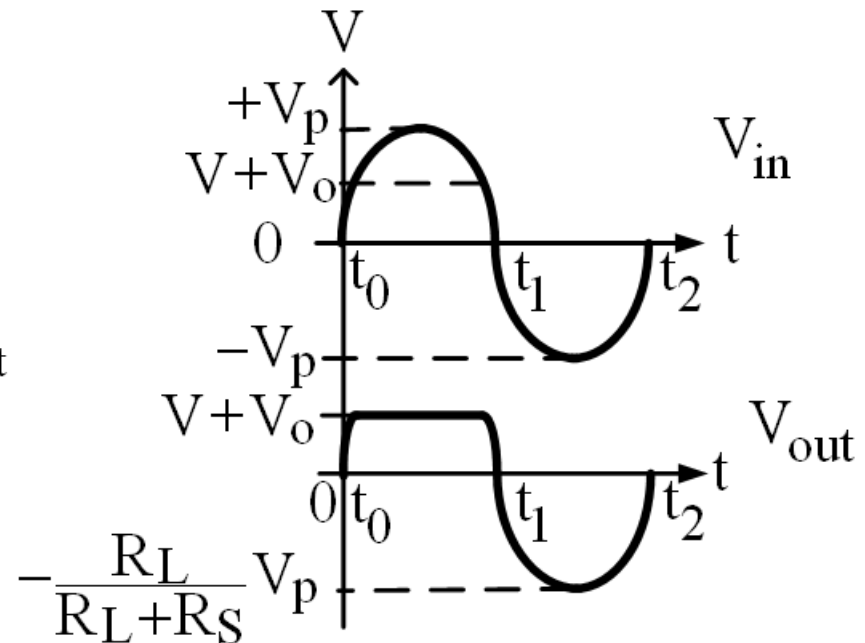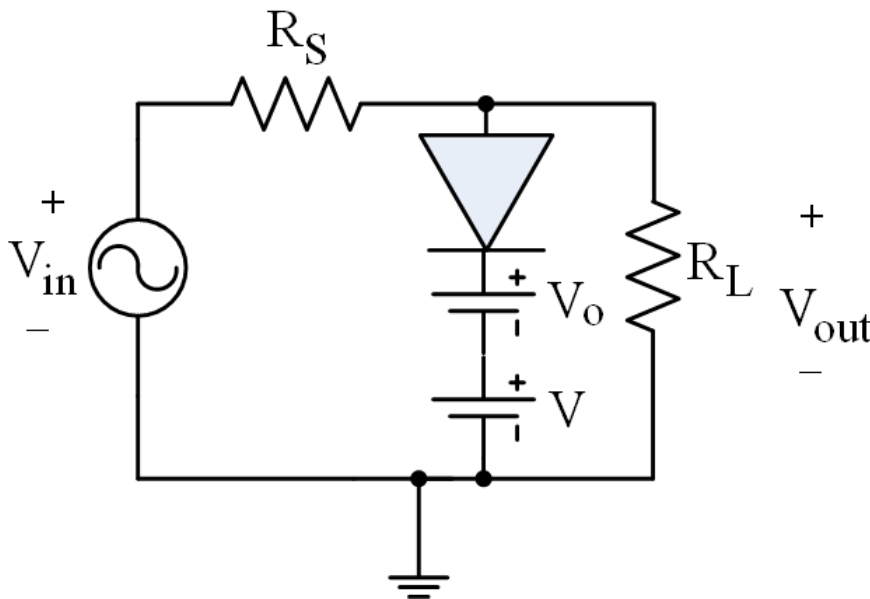**Diode rb (o/c) when  $V_{in} < V + V_o$ .**

$$V_{out} = \frac{R_L}{R_L + R_S} (V_{in}) \text{ for } V_{in} < V + V_o \text{ and } V_{in} \text{ is +ve.}$$

$$V_{out} = \frac{R_L}{R_L + R_S} (-V_{in}) \text{ for } V_{in} \text{ during its -ve cycle.}$$






# -ve clipper

During the +ve half cycle, diode is rb and o/c. Hence,

$$V_{out} = \frac{R_L}{R_L + R_S} (V_{in})$$

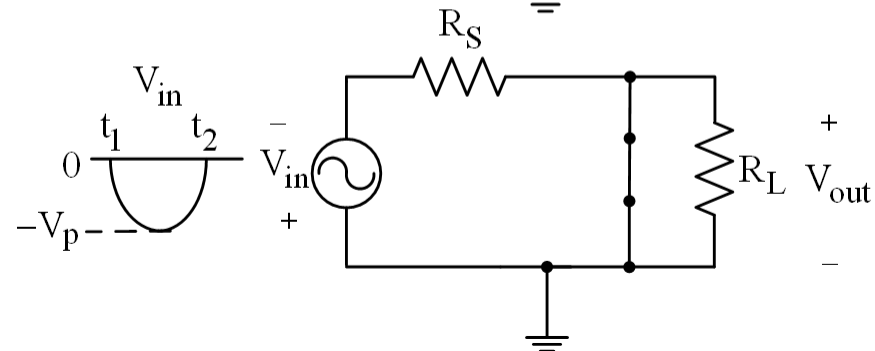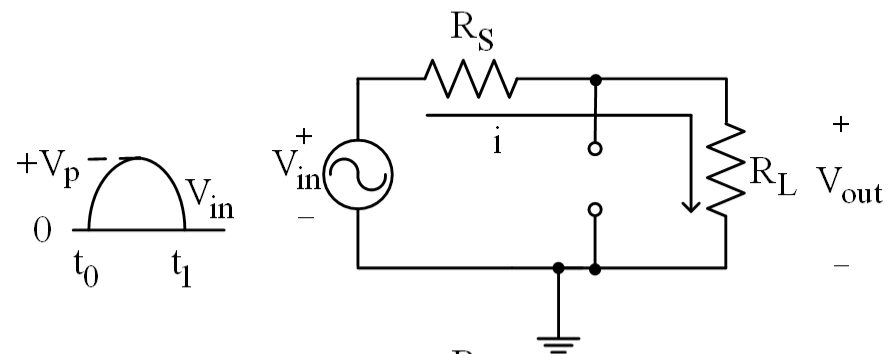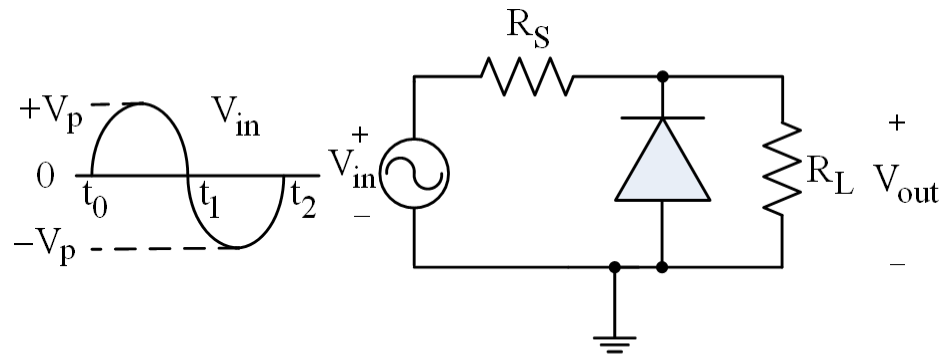During the -ve half cycle, diode is fb and s/c. Hence,  $V_{out} = 0$ .





**Overall performance:**

**+ve half cycle,**

$$V_{out} = \frac{R_L}{R_L + R_S} (V_{in})$$

**-ve half cycle,**


$$V_{out} = 0.$$

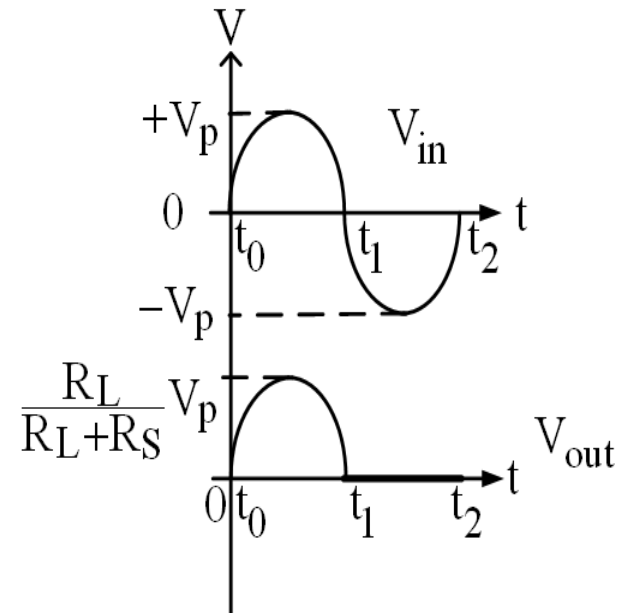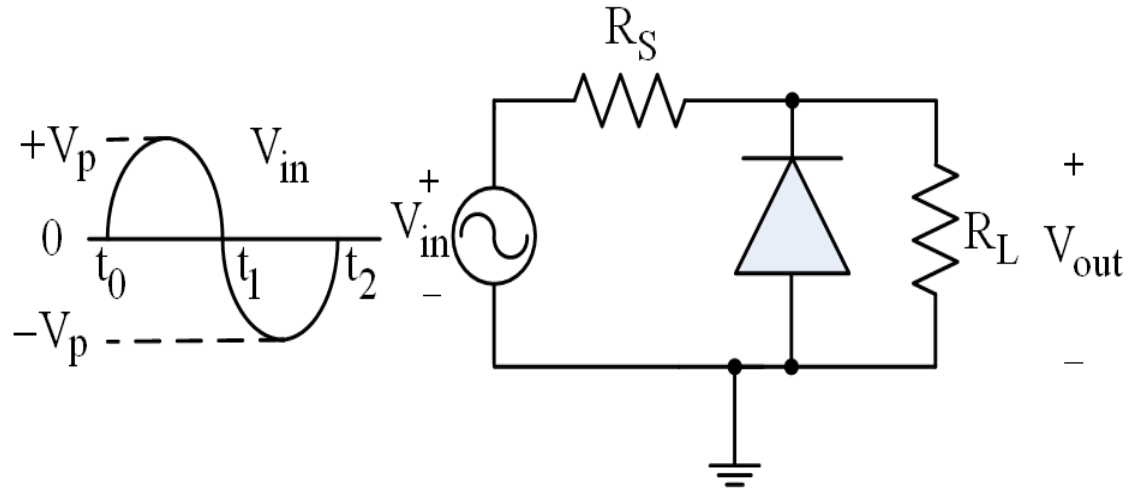

If potential barrier is considered: Diode fb (s/c) if  $V_{in}$  is -ve and  $V_{in}$  is more -ve than  $-V_o$ . Hence,  $V_{out} = -V_o$ . If  $V_{in}$  is -ve but  $V_{in}$  is more +ve than  $-V_o$ , diode is rb (o/c). Hence,

$$V_{out} = \frac{R_L}{R_L + R_S} (-V_{in})$$

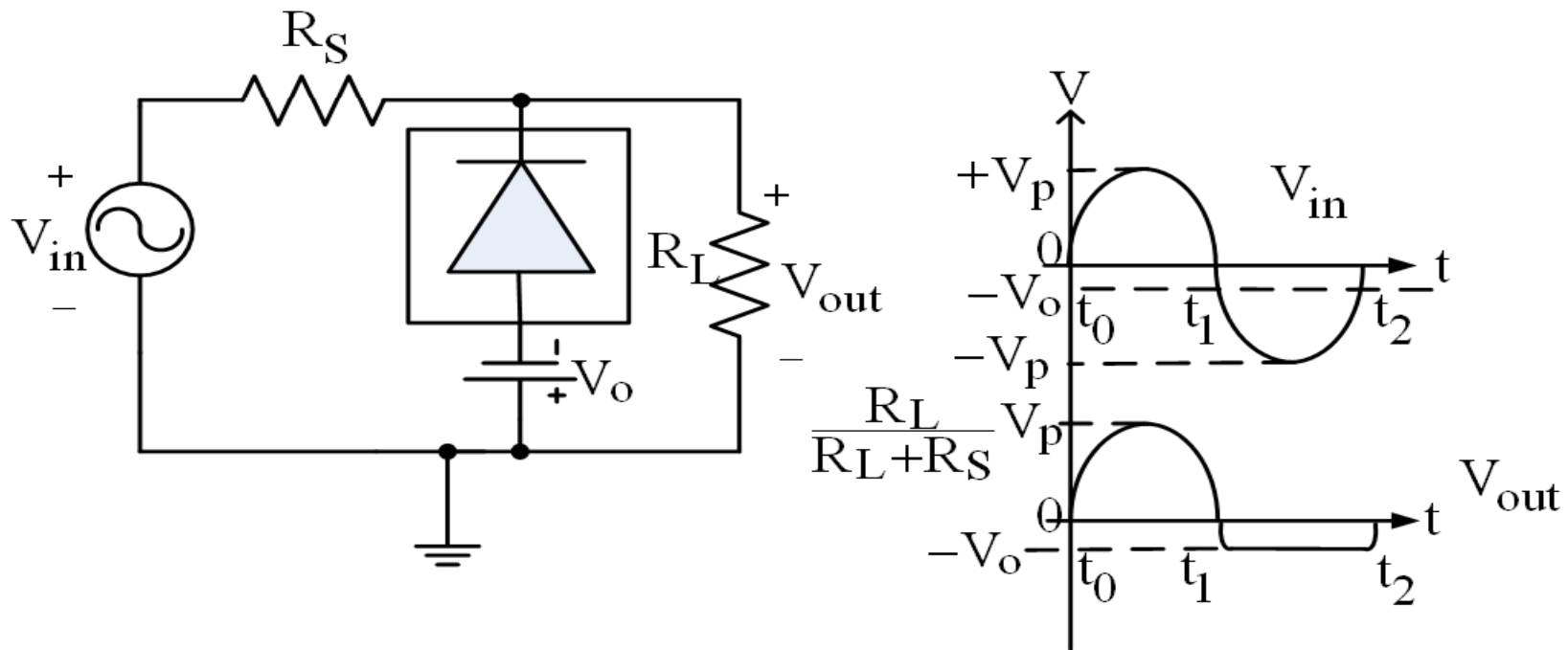For  $V_{in}$  during its +ve cycle,  $V_{out} = \frac{R_L}{R_L + R_S} (V_{in})$



# Variable -ve clipper



Diode fb (s/c) when  $V_{in} < -V - V_o$ . Hence,  $V_{out} = -V - V_o$ . Diode rb (o/c) when  $V_{in} > -V - V_o$  ( $V_{in}$  is more +ve than  $-V - V_o$ )

$$V_{out} = \frac{R_L}{R_L + R_S} (-V_{in})$$

for  $V_{in} > -V - V_o$  and  $V_{in}$  is -ve.

$$V_{out} = \frac{R_L}{R_L + R_S} (V_{in})$$

for  $V_{in}$  during its +ve cycle.

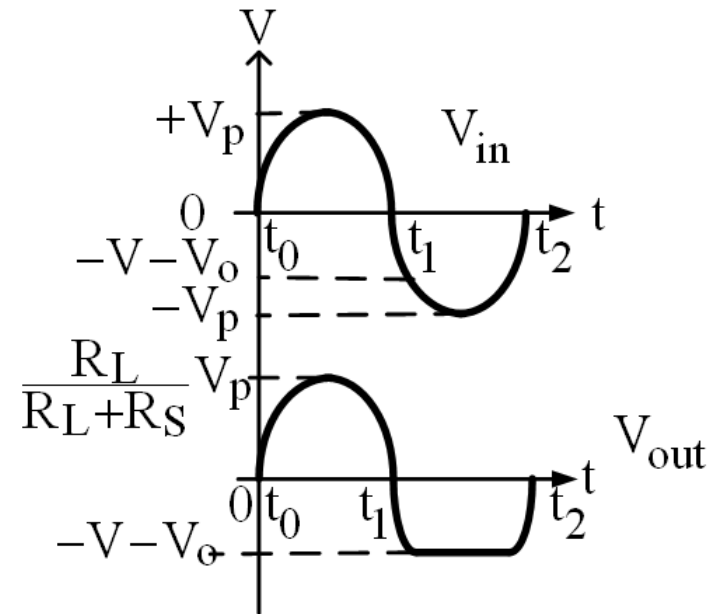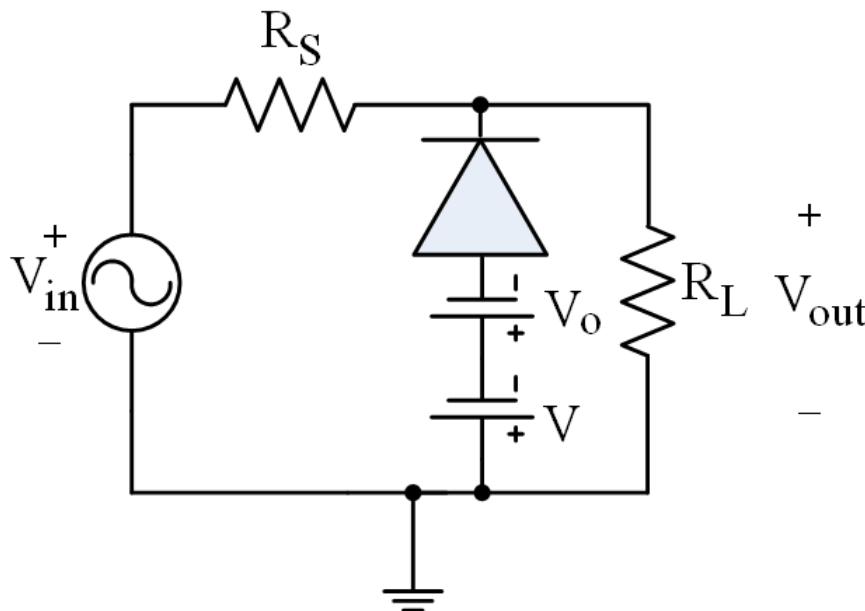

# Clamping diode

## Function:

To include a dc level into an ac signal.

Also known as a dc restorer.

Main application is in the TV receiver as a dc restorer.

