

CLASS 18&19

BJT CONFIGURATIONS AND I-V
CHARACTERISTICS

$$\begin{aligned}
\gamma &= \frac{I_{Ep}}{I_E} \\
&= \frac{\frac{qAD_p p_{no}}{W} e^{(qV_{EB})/kT}}{qA \left\{ \frac{D_p p_{no}}{W} e^{(qV_{EB})/kT} + \frac{D_E n_{Eo}}{L_E} \left[e^{(qV_{EB})/kT} - 1 \right] \right\}} \\
&= \frac{\frac{D_p p_{no}}{W}}{\left\{ \frac{D_p p_{no}}{W} + \frac{D_E n_{Eo}}{L_E} \right\}} \\
&= \frac{1}{\left\{ 1 + \frac{D_E n_{Eo} W}{D_p p_{no} L_E} \right\}} \\
n_{Eo} &= \frac{n_i^2}{N_E}, p_{no} = \frac{n_i^2}{N_B}, \therefore \gamma = \frac{1}{\left\{ 1 + \frac{D_E N_B W}{D_p N_E L_E} \right\}}
\end{aligned}$$

$$\gamma = \frac{1}{\left\{ 1 + \frac{D_E N_B W}{D_p N_E L_E} \right\}}$$

- **To increase the emitter efficiency, γ , N_B/N_E has to be low. This indicates that E has to be doped higher than B. This is the reason why E is represented by p^+ for the p^+ -n-p transistor.**
- **To increase γ , the width of the B, W , should be small as compared to the diffusion length of the electrons in the E.**

BJT CIRCUIT CONFIGURATIONS

3 basic configurations:

- 1. Common Emitter (CE)**
- 2. Common Collector (CC)**
- 3. Common Base (CB)**

All transistor circuits, no matter how complex they are, are based on either one or combinations of 2 or all of these configurations.

- **Common Emitter (CE)**


E is the common point for both the input and output signals. Input signal is applied to B and output is at C. E is AC ground.




- **Common Collector (CC)**

C is the common point for both the input and output signals. Input signal is applied to B and output is at E. C is AC ground.


- **Common Base (CB)**

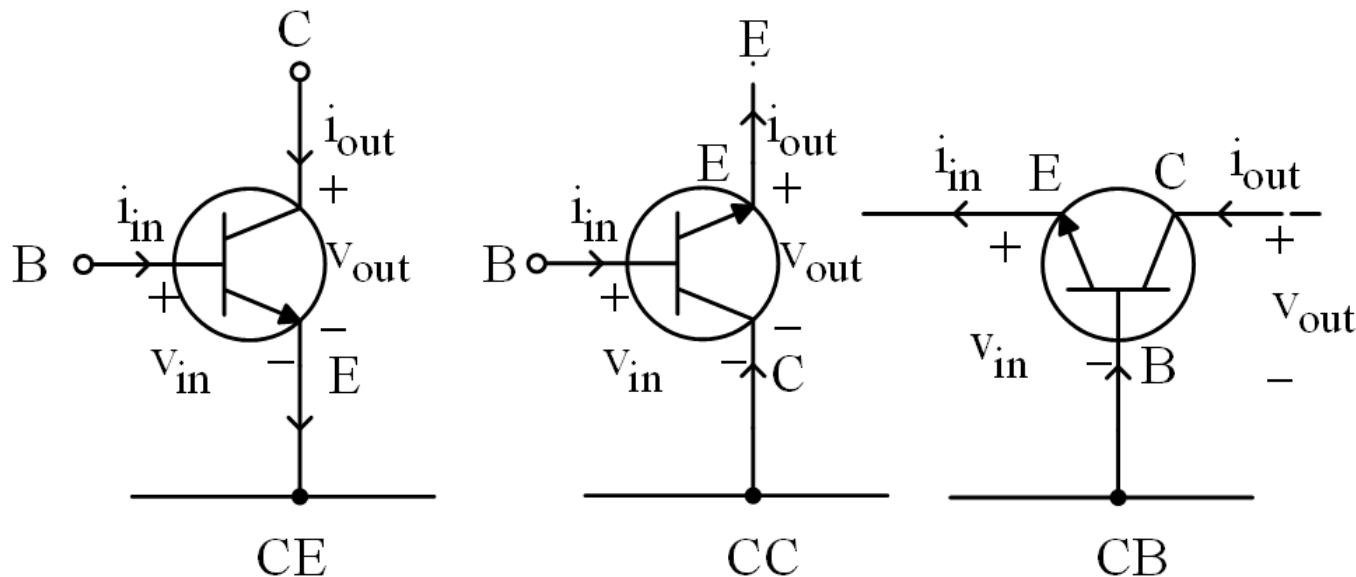B is the common point for both the input and output signals. Input signal is applied to E and output is at C. B is AC ground.



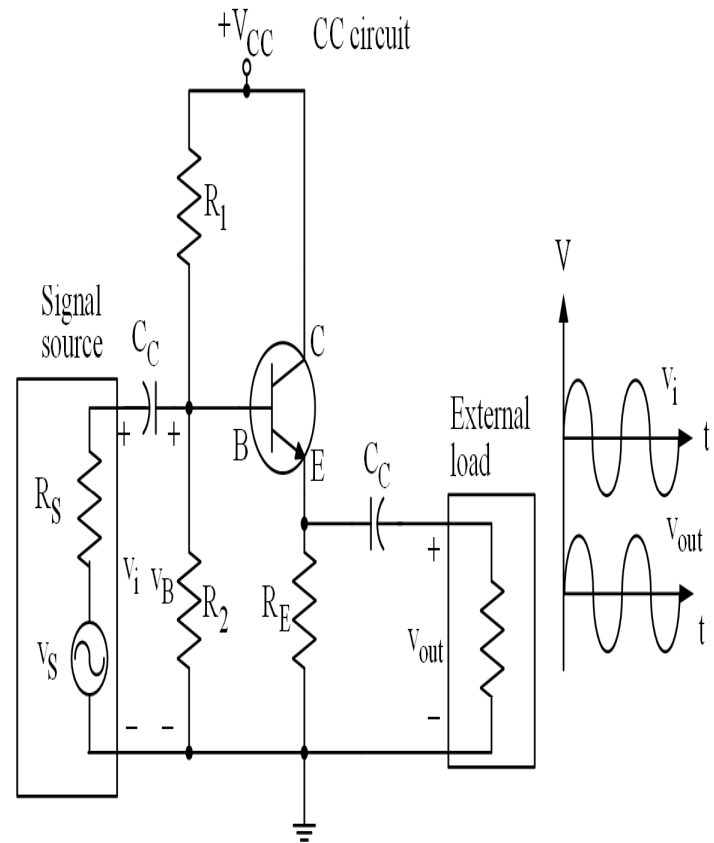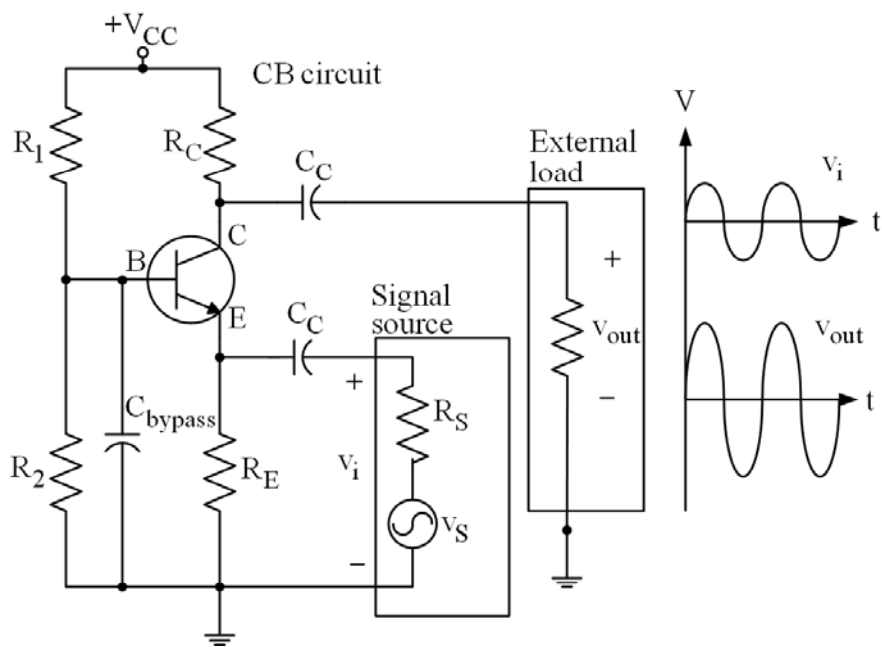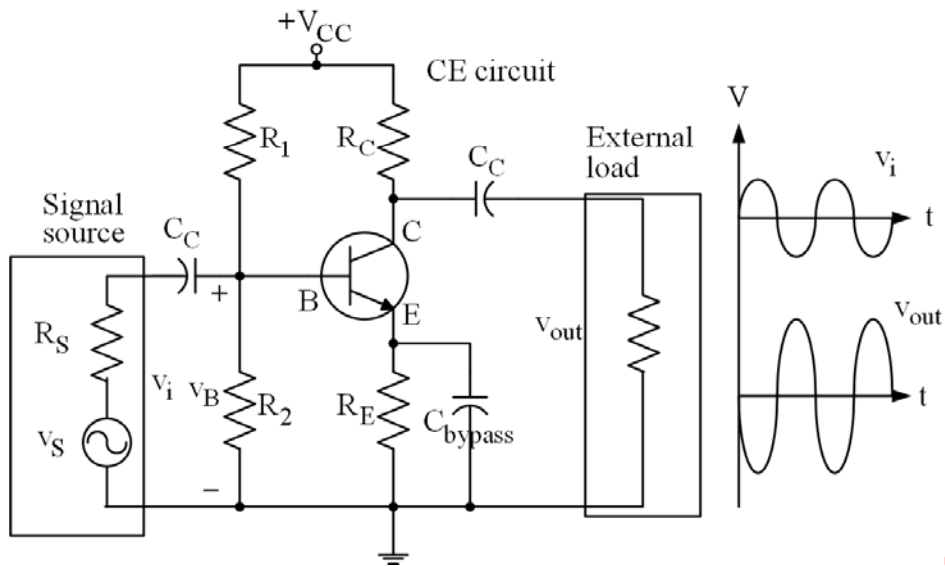

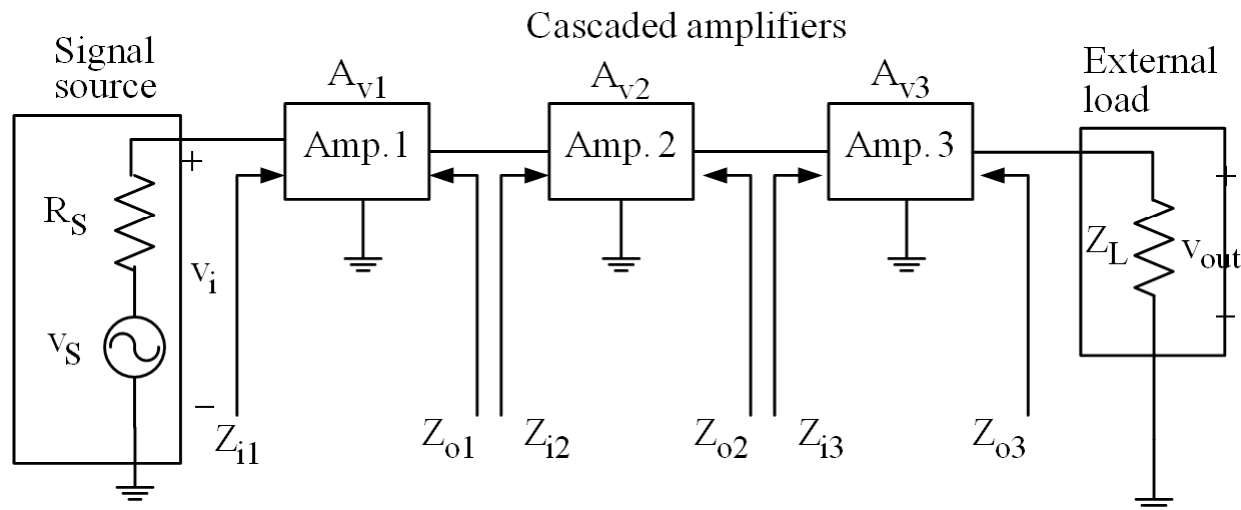- **CE is the most typical configuration used. For this configuration, the voltage gain, $A_v = V_{out}/V_i$, is high. A high A_v means the amplifier is efficient. The input impedance, Z_i , and output impedance, Z_o of CE are also high. A high Z_i is required to optimize the A_v of a cascaded amplifier circuit.**



- **CC (known also as emitter follower) has $A_v = 1$, a high Z_i and a low Z_o . CC is typically employed as a buffer or impedance transformer.**
- **CB has high A_v but smaller Z_i . This configuration is used for high frequency of operation.**


BJT MODE OF OPERATION

- **There are 4 modes of operation:**
 - 1. Active mode**
 - 2. Saturation mode**
 - 3. Cut-off mode**
 - 4. Inverted mode**

All the 4 modes are dependent on the biasing voltages, i.e. V_{EB} and V_{BC} .

Active mode:	E-B junction fb, B-C junction rb
Saturation mode:	E-B junction fb, B-C junction fb
Cut-off mode:	E-B junction rb, B-C junction rb
Inverted mode:	E-B junction rb, B-C junction fb

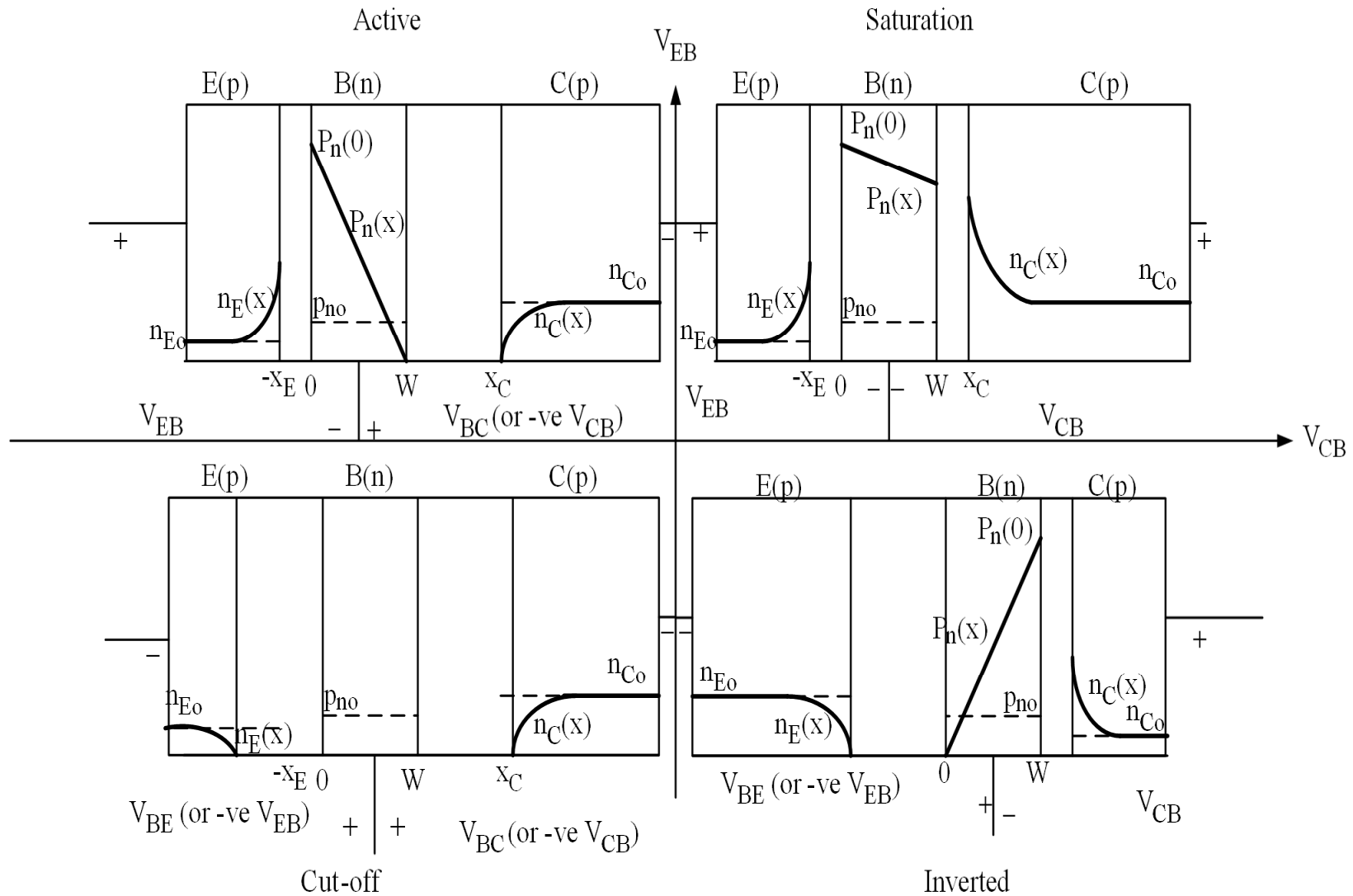Junction polarity and minority carrier distribution for a pnp transistor in 4 different modes of operation.



Observations:

1. Saturation Mode

Non-zero distribution of the minority carriers at the edges of both E-B and B-C depletion regions.

$$P_n(W) = p_{no} e^{(qV_{CB})/kT}$$

The bias voltage is small and the output current is large. The transistor is in the conducting state and function of the transistor is as a close (ON) switch.

2. Cut-off Mode

$P_n(0) = P_n(W) \approx 0$. The transistor functions as an open (OFF) switch.

$$I_E = I_B = I_C \approx 0$$

3. Inverted Mode

Known also as inverted active mode has C operating as E in the active mode and E operating as C in the active. The current gain for the inverted mode is normally lower than the active mode. This is because the “emitter efficiency” (in this case the C emits holes) is weaker since the doping of C is lower than the doping of B.

General equations for the currents in a BJT for all mode of operations:

$$I_E = qA \left[\frac{D_p p_{no}}{W} + \frac{D_E n_{Eo}}{L_E} \right] \left[e^{(qV_{EB})/kT} - 1 \right] - \left[\frac{qAD_p p_{no}}{W} \right] \left[e^{(qV_{CB})/kT} - 1 \right]$$

$$I_C = \frac{qAD_p p_{no}}{W} \left[e^{(qV_{EB})/kT} - 1 \right] - qA \left[\frac{D_p p_{no}}{W} + \frac{D_C n_{Co}}{L_C} \right] \left[e^{(qV_{CB})/kT} - 1 \right]$$



Equations for the BJT currents in the active mode:

$$I_E = \frac{qAD_p p_{no}}{W} e^{(qV_{EB})/kT} + \frac{qAD_E n_{Eo}}{L_E} \left[e^{(qV_{EB})/kT} - 1 \right]$$



$$I_C = \frac{qAD_p p_{no}}{W} e^{(qV_{EB})/kT} + \frac{qAD_C n_{Co}}{L_C}$$

INPUT AND OUTPUT I-V CHARACTERISTICS


- **Each BJT configuration has its own input and output I-V characteristics. From these characteristics, the appropriate voltages and currents that will enable the BJT to be operated as an amplifier (active mode) can be determined.**
- **The input and output characteristics of the BJT is different for each configuration.**
- **Remember that to operate the BJT as an amplifier, the BJT has to be in the active mode i.e. E-B is fb and B-C is rb.**

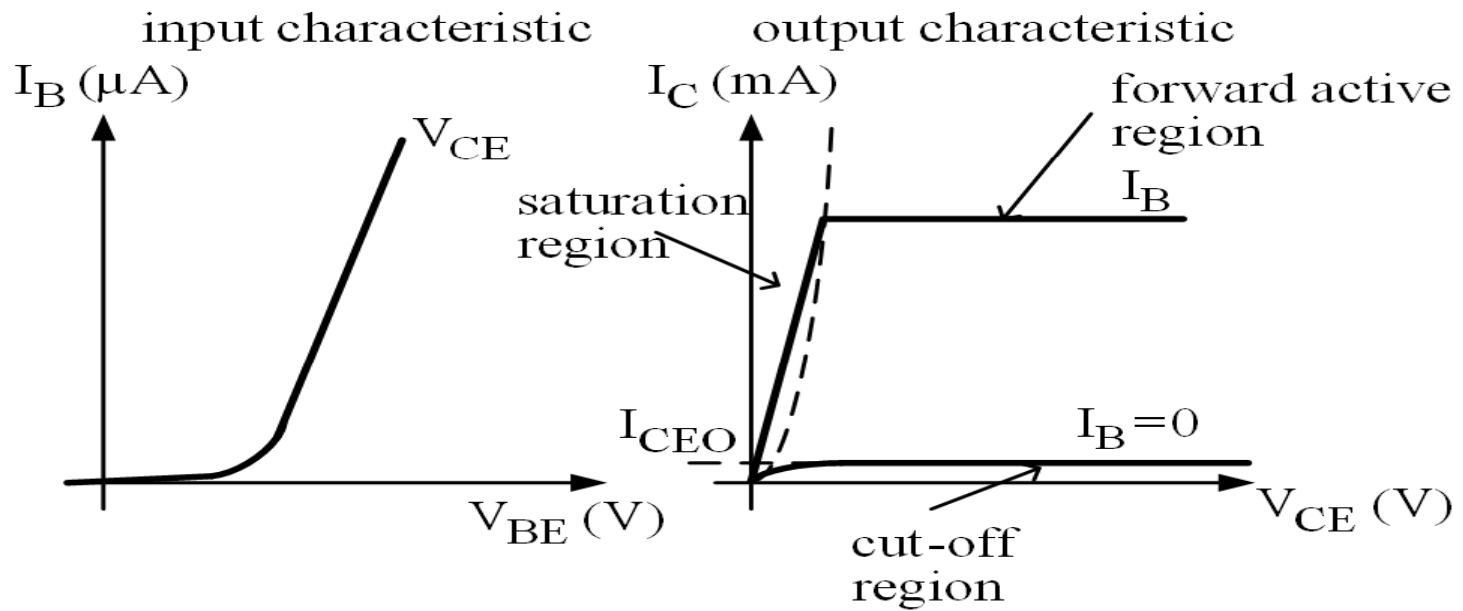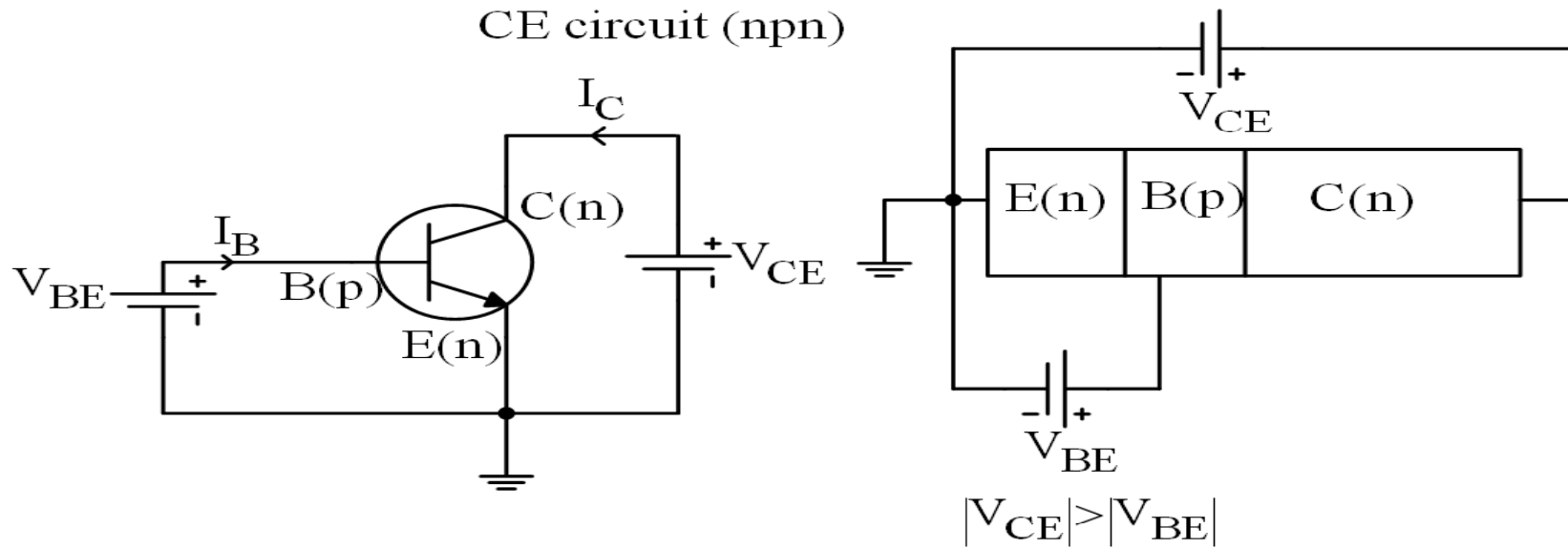


CE circuit (pnp)

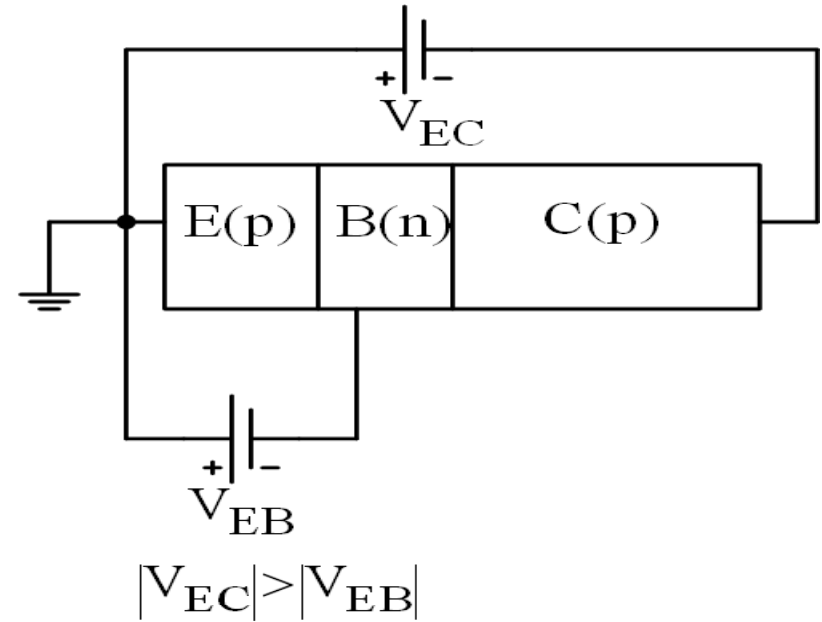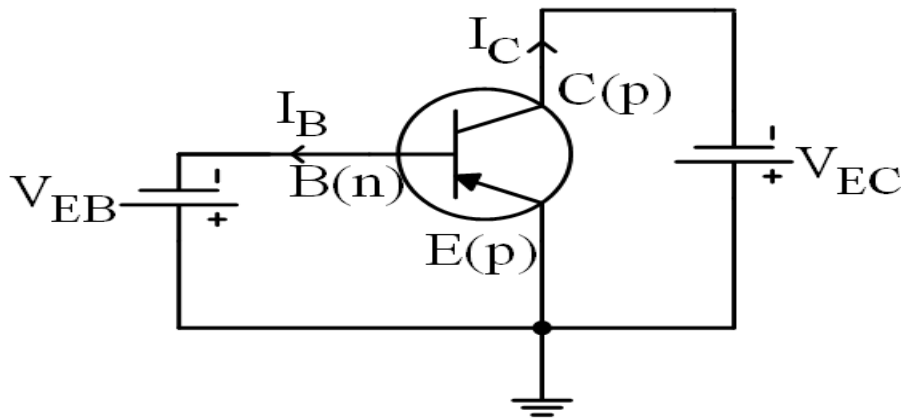

input characteristic


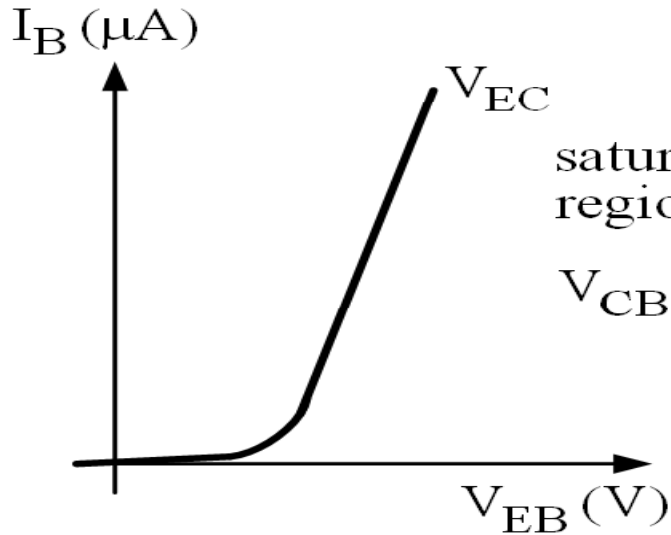


output characteristic



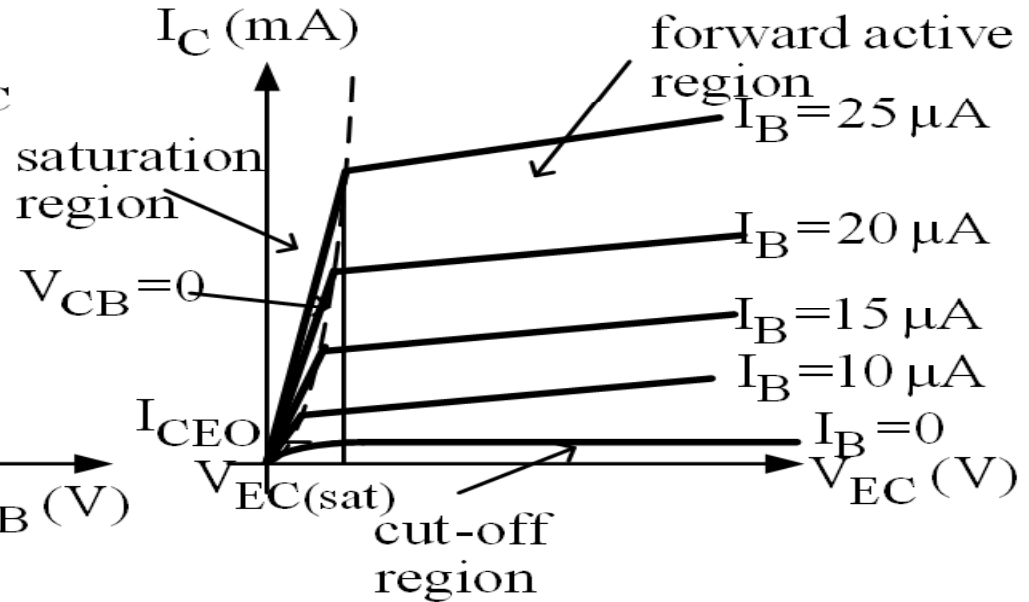


Observations:


- For an ideal transistor in the CE configuration, I_C for a fixed I_B is independent of V_{EC} for $V_{EC} > V_{EC(sat)}$. This condition is true if the effective width of the B is fixed.
- As the width of the depletion region in B of the B-C junction is dependent on V_{EC} , the effective width of B will also be dependent on V_{EC} . Therefore, I_C will be dependent on V_{EC} although $V_{EC} > V_{EC(sat)}$. For a fixed I_B and $V_{EC} > V_{EC(sat)}$, $I_C \uparrow$ when $V_{EC} \uparrow$. However, the increment is small when compared to the increment of I_C with the increase in V_{EC} when the transistor is in the saturation region.

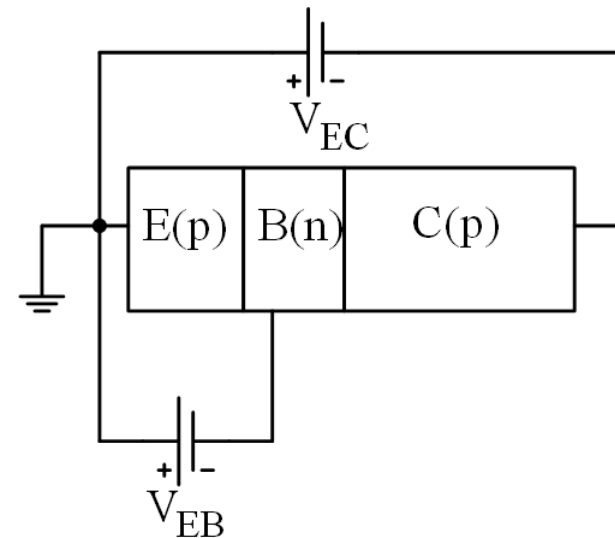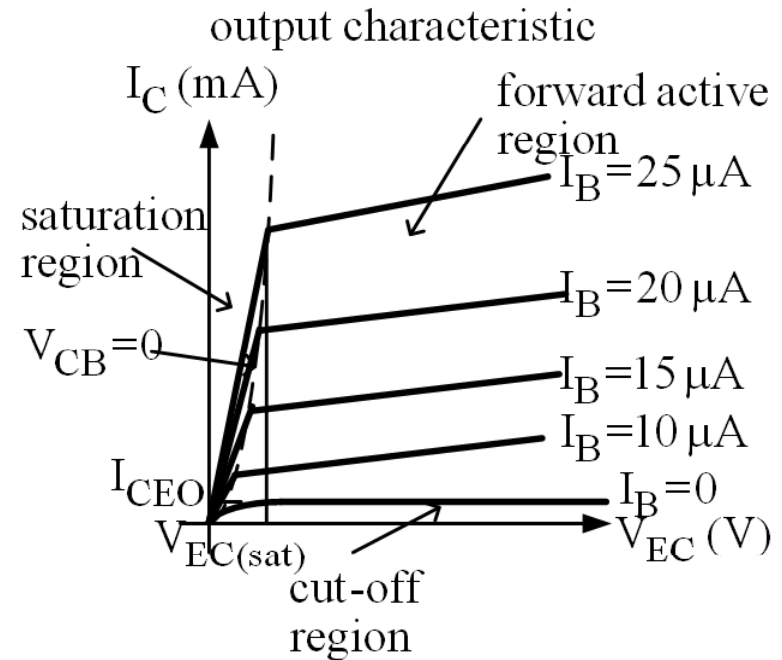

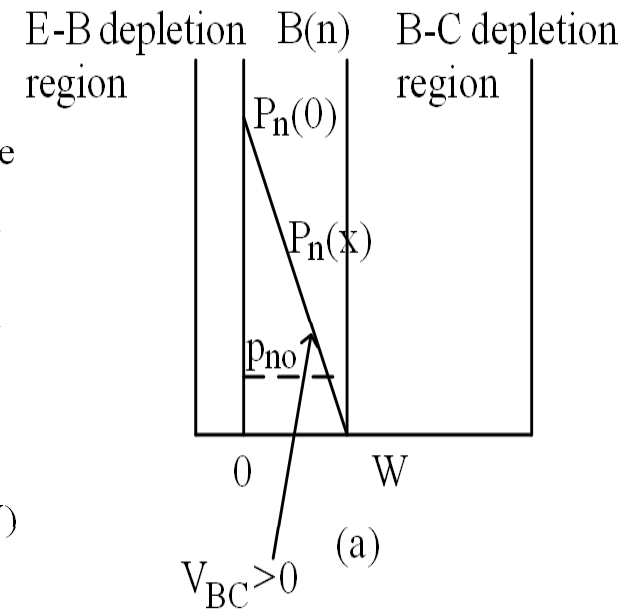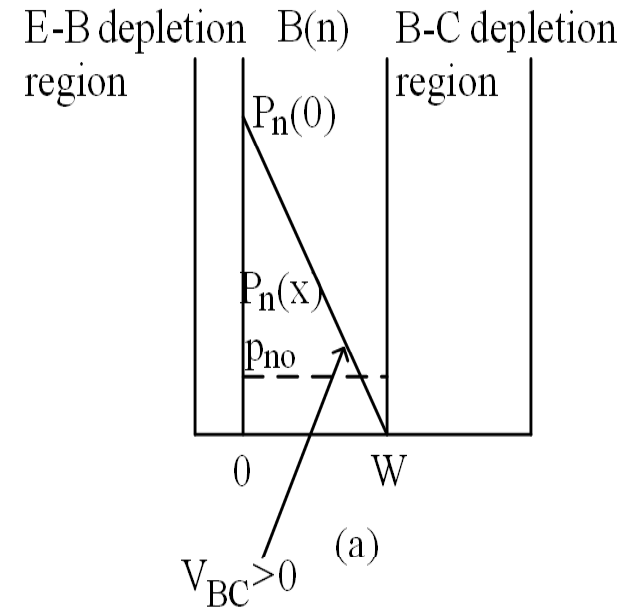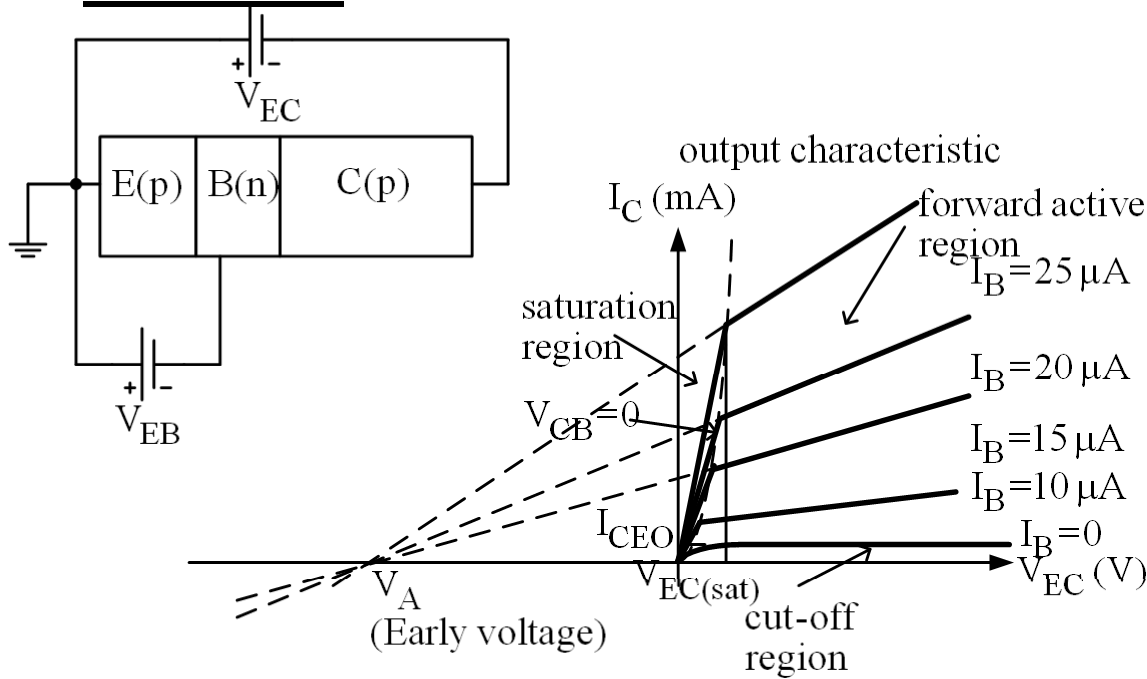
- When $V_{EC} \uparrow$, B-C junction becomes more rb, depletion region of B-C junction \uparrow , effective width of B \downarrow . Less recombination happen in B (or the slope of the hole density in B \uparrow), and therefore $I_C \uparrow$.
- The phenomena where $I_C \uparrow$ when $V_{EC} \uparrow$ is called the Early effect or base width modulation.




CB circuit (pnp)

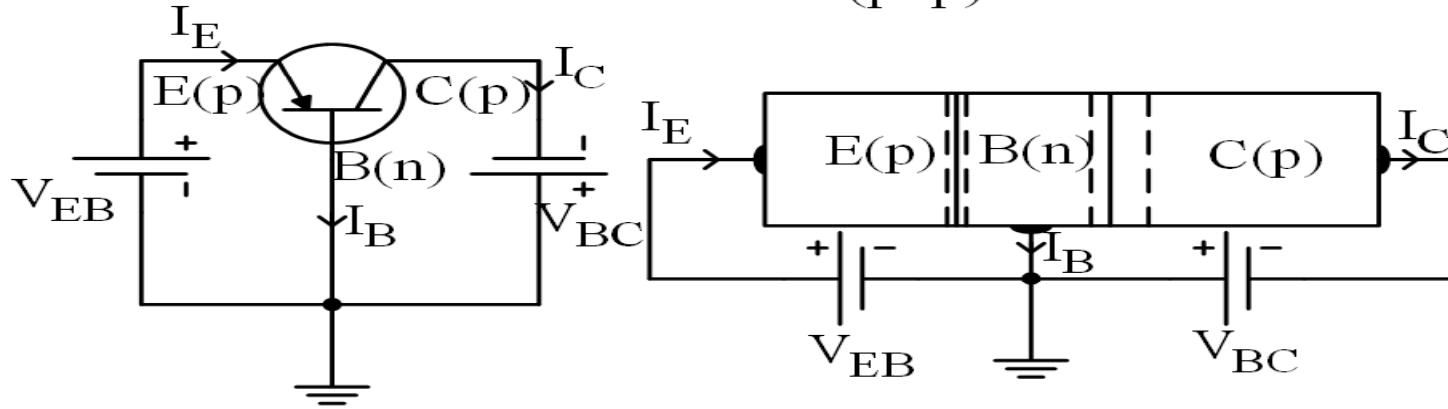

input characteristic
 I_E (mA)

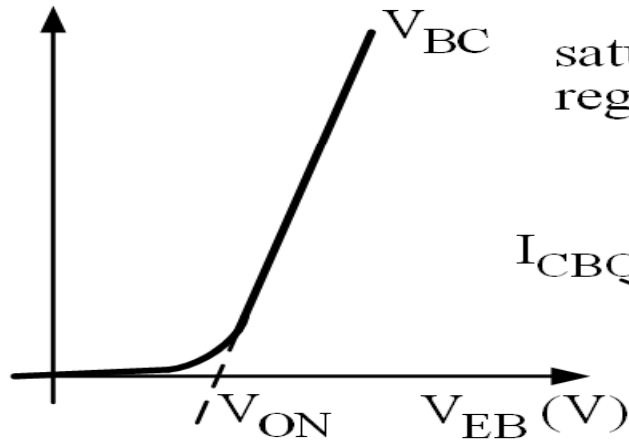

output characteristic

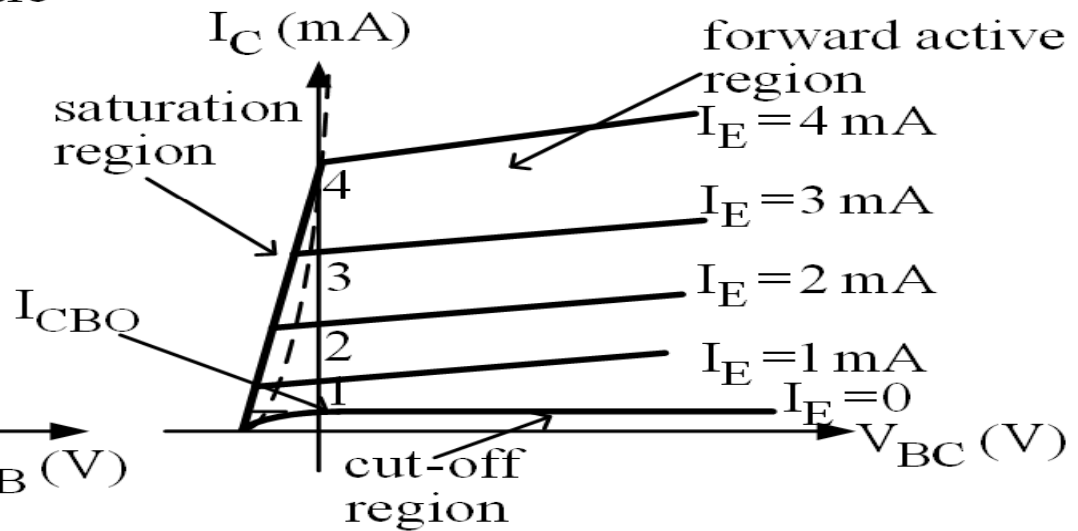

In the active region, $I_C \approx I_E$ and is independent of V_{BC} . $I_C \approx \alpha_o I_E$

Observations

- $V_{BC} \uparrow I_C \uparrow$ because when $V_{BC} \uparrow$, the B-C junction becomes more rb. The width of the effective B region (outside depletion) becomes smaller. Recombinations \downarrow . Hence, $I_C \uparrow$.
- At a fixed V_{BC} , if $I_E \uparrow I_C \uparrow$. As $I_C = \alpha_o I_E$ and $\alpha_o \approx 1$, $I_C \approx I_E$. Thus, $I_E \uparrow I_C \uparrow$.
- If $V_{BC} = 0$, there still exists a depletion region at the B-C junction. Fixed $-ve$ ions in the depletion region of the C can still manage to attract the holes from B to cross the B-C junction and enter C. I_C exists. If the V_{BC} becomes $-ve$ (i.e. V_C is more $+ve$ than V_B), the width of the depletion region \downarrow and $I_C \downarrow$. When $V_{CB} = V_{ON}$, the depletion region's width ≈ 0 . At this time, the B-C junction becomes fb and $I_C = 0$.

