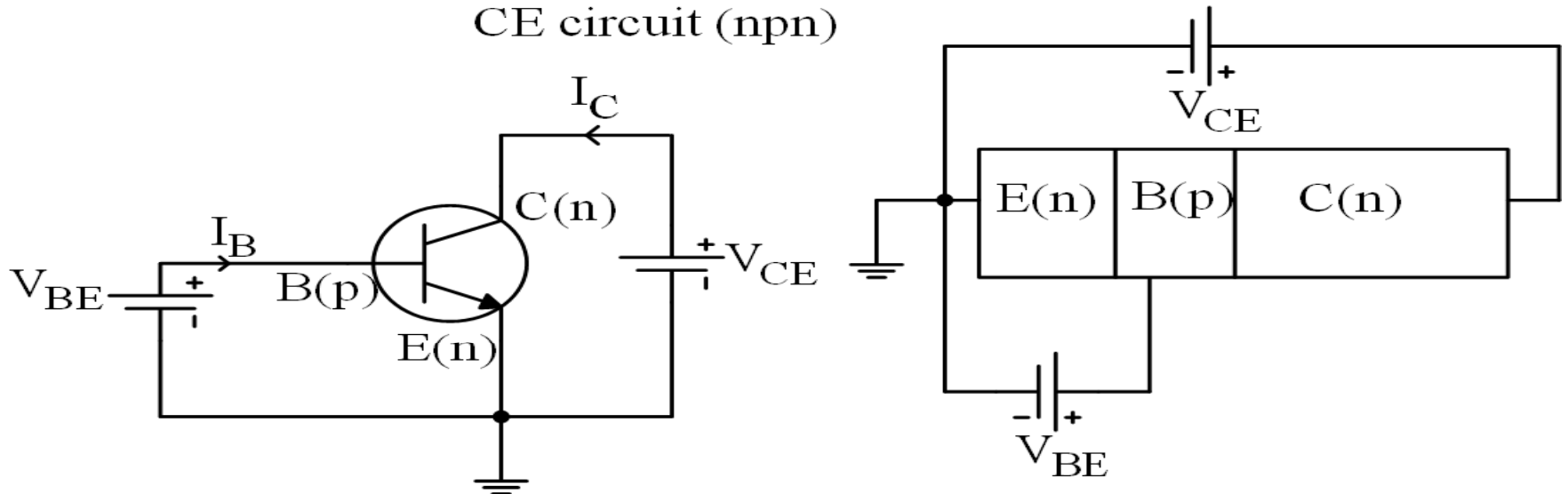


CLASS 6&7


BJT PARAMETERS AND BIASING

CE circuit (npn)




forward active region: $|V_{CE}| > |V_{BE}|$



input characteristic

 

output characteristic

 


CE circuit (pnp)

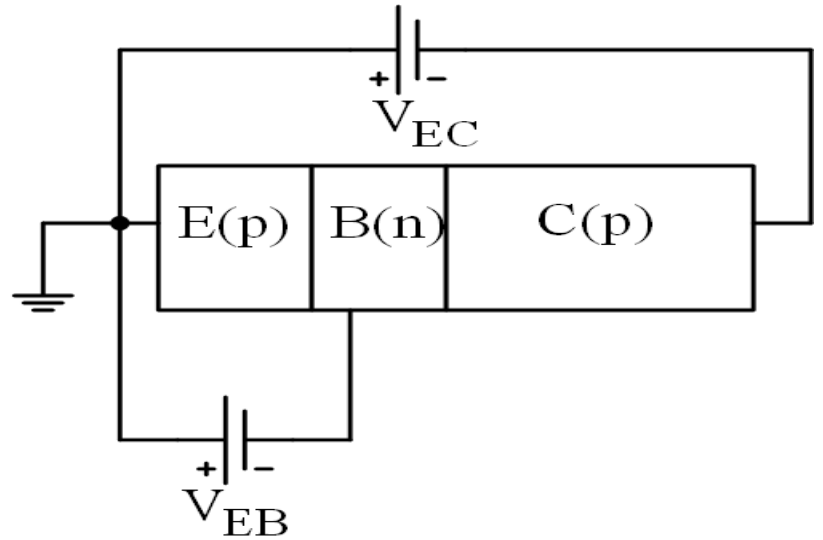 


forward active region: $|V_{EC}| > |V_{EB}|$

input characteristic


 


output characteristic



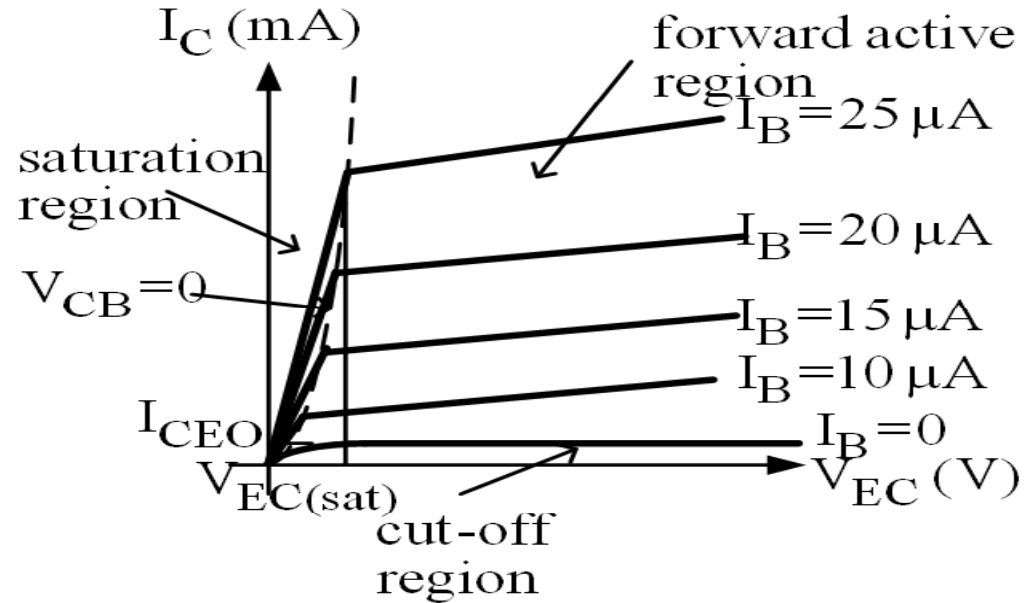


Observations:


- For an ideal transistor in the CE configuration, I_C for a fixed I_B is independent of V_{EC} for $V_{EC} > V_{EC(sat)}$. This condition is true if the effective width of the B is fixed.
- As the width of the depletion region in B of the B-C junction is dependent on V_{EC} , the effective width of B will also be dependent on V_{EC} . Therefore, I_C will be dependent on V_{EC} although $V_{EC} > V_{EC(sat)}$. For a fixed I_B and $V_{EC} > V_{EC(sat)}$, $I_C \uparrow$ when $V_{EC} \uparrow$. However, the increment is small when compared to the increment of I_C with the increase in V_{EC} when the transistor is in the saturation region.

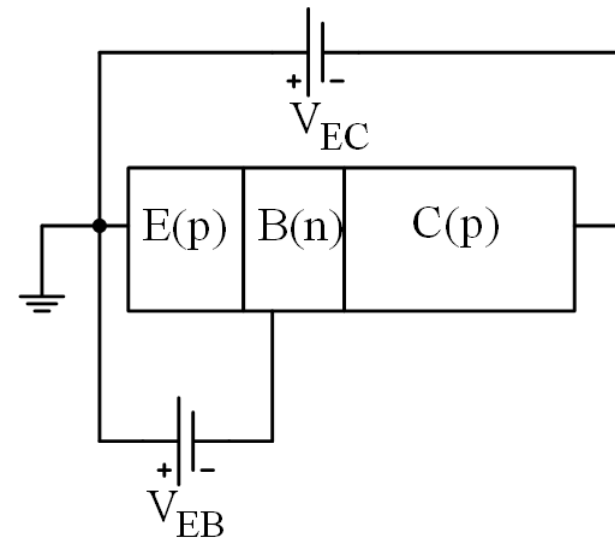 

  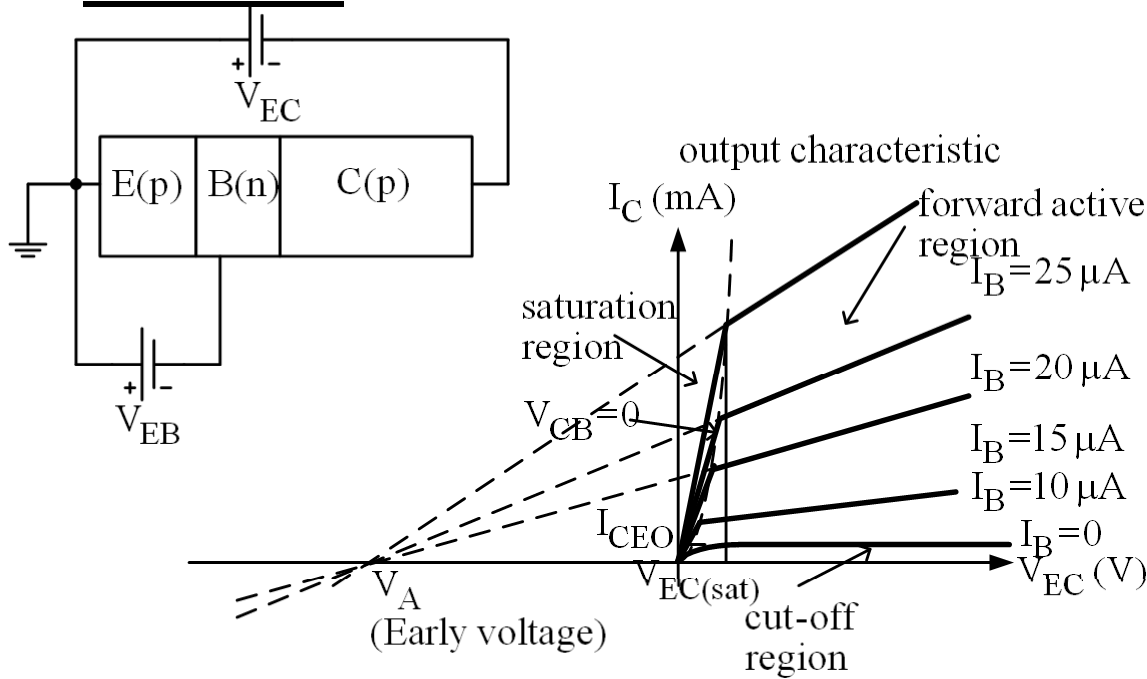
- When $V_{EC} \uparrow$, B-C junction becomes more rb, depletion region of B-C junction \uparrow , effective width of B \downarrow . Less recombination happen in B (or the slope of the hole density in B \uparrow), and therefore $I_C \uparrow$.
- The phenomena where $I_C \uparrow$ when $V_{EC} \uparrow$ is called the Early effect or base width modulation.




CB circuit (pnp)

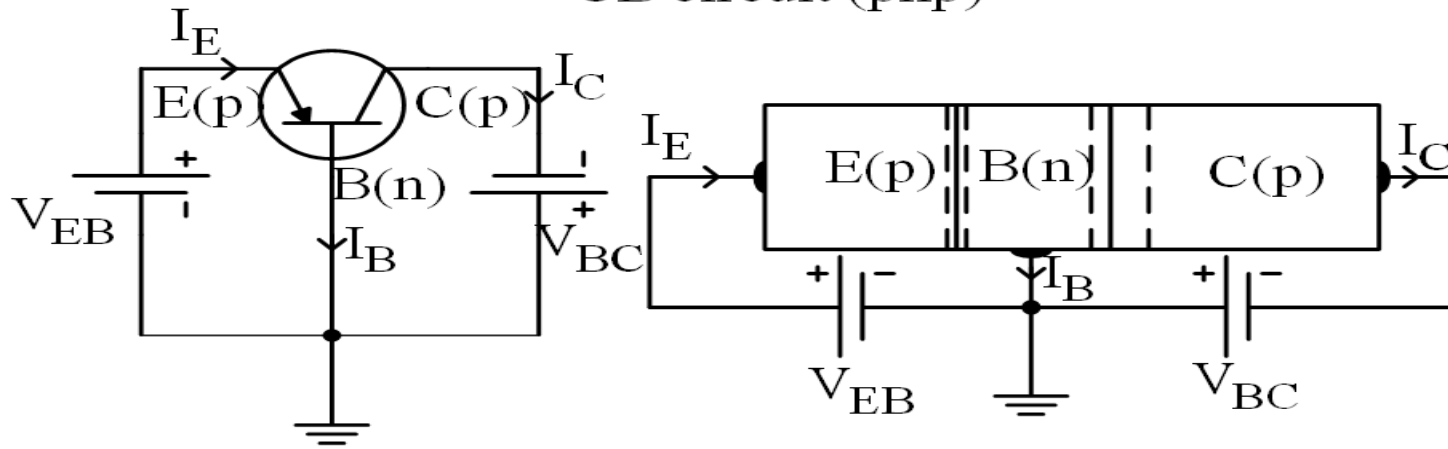

input characteristic
 I_E (mA)

 




output characteristic

 

In the active region, $I_C \approx I_E$ and is independent of V_{BC} . $I_C \approx \alpha_o I_E$
 α_o is the CB current gain.




Observations

- $V_{BC} \uparrow I_C \uparrow$ because when $V_{BC} \uparrow$, the B-C junction becomes more rb. The width of the effective B region (outside depletion) becomes smaller. Recombinations \downarrow . Hence, $I_C \uparrow$.
- At a fixed V_{BC} , if $I_E \uparrow I_C \uparrow$. This is because, $I_E \uparrow$ when $V_{EB} \uparrow$. As $I_C = \alpha_o I_E$ and $\alpha_o \approx 1$, $I_C \approx I_E$. Thus, $I_E \uparrow I_C \uparrow$.
- If $V_{BC} = 0$, there still exists a depletion region at the B-C junction. Fixed -ve ions in the depletion region of the C can still manage to attract the holes from B to cross the B-C junction and enter C. I_C exists. If the V_{BC} becomes -ve (i.e. V_C is more +ve than V_B), the width of the depletion region \downarrow and $I_C \downarrow$. When $V_{CB} \approx V_{ON}$, the depletion region's width ≈ 0 . At this time, the B-C junction becomes fb and $I_C = 0$.

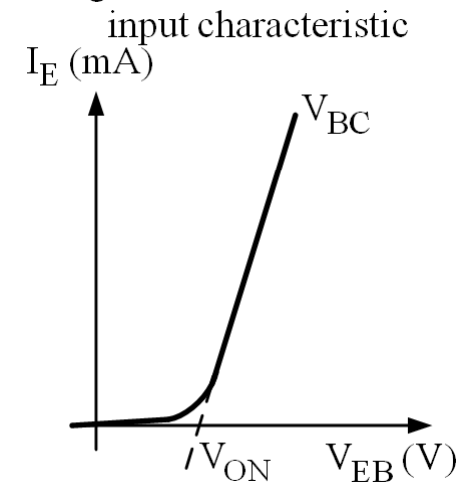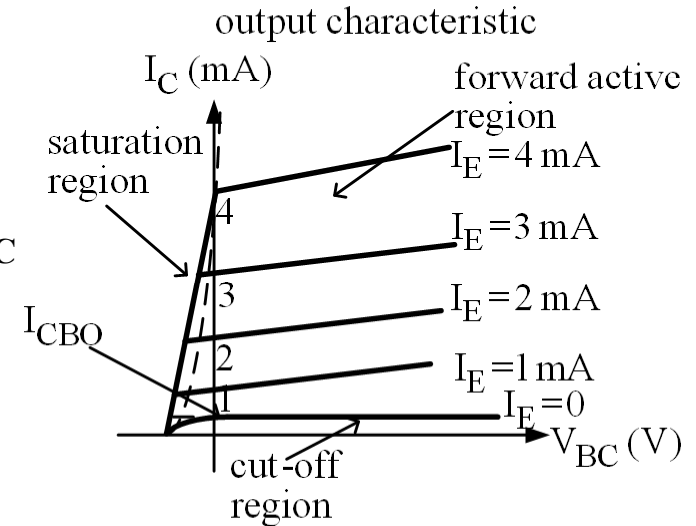 

Distribution of minority carriers in B for a pnp transistor.

- (a) Active mode for $|V_{BC}| \geq 0$.
- (b) Saturation mode with both E-B and B-C junctions fb.

 
 
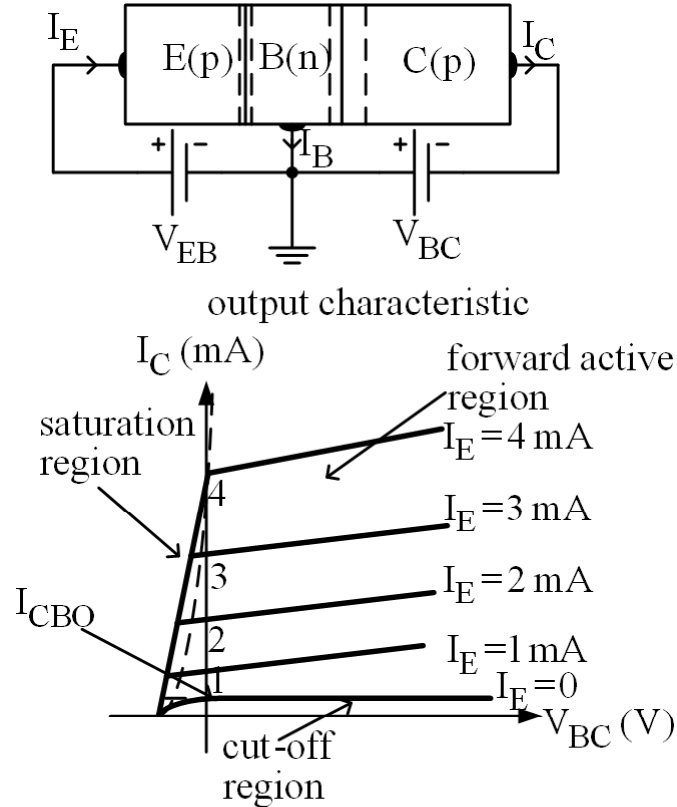


Observations

- Since the difference in the slope is not large when $V_{BC} > 0$ and $V_{BC} = 0$, I_C does not change much.
- $I_C = 0$ when one small forward voltage is supplied across the B-C junction ($V_{BC} \approx -1$ V for Silicon). Under this condition, the transistor is in the saturation region.
- The fb supplied to the B-C junction will increase the hole density at $x=W$ until it reaches a value equals to the hole density at $x=0$. This means that the hole gradient is 0 and consequently I_C will reduce to 0.

$$I_{Cp} = A \left[-qD_p \frac{dp_n}{dx} \Big|_{x=W} \right], \quad I_{Cn} = A \left[qD_C \frac{dn_C}{dx} \Big|_{x=x_C} \right]$$
 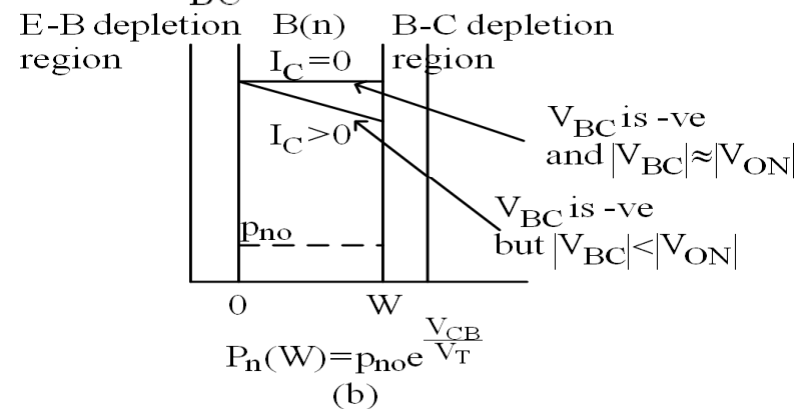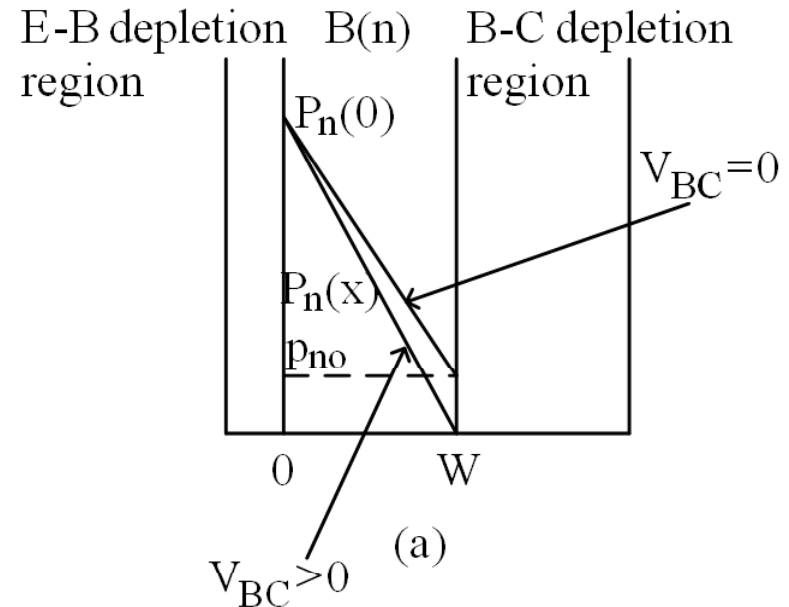
$$\approx \frac{qAD_p p_{no}}{W} e^{(qV_{EB})/kT} = \frac{qAD_C n_{Co}}{L_C}$$



Important observations:

$$I_E = I_B + I_C$$

For the CB,

$$I_C = \alpha_o I_E + I_{CBO}$$

where I_{CBO} is the C-B current when E is open ($I_E = 0$) and it is a minority carrier current.

$$I_C = \alpha_o (I_B + I_C) + I_{CBO}$$

$$I_C (1 - \alpha_o) = \alpha_o I_B + I_{CBO}$$

$$I_C = (\alpha_o I_B + I_{CBO}) / (1 - \alpha_o) = [\alpha_o I_B / (1 - \alpha_o)] + [I_{CBO} / (1 - \alpha_o)]$$


$$\alpha_o / (1 - \alpha_o) = \beta_{DC} = \text{CE DC current gain}$$

$$\beta_{DC} = \Delta I_C / \Delta I_B$$

$$I_{CEO} = I_{CBO} / (1 - \alpha_o)$$

where I_{CEO} is the leakage current when B is open ($I_B = 0$) and it is a minority carrier current.

$$I_C = \beta_{DC} I_B + I_{CEO}$$

 

$$\alpha_o / (1 - \alpha_o) = \beta_{DC}$$

$$\alpha_o = \beta_{DC} (1 - \alpha_o)$$

$$\alpha_o + \beta_{DC} \alpha_o = \beta_{DC}$$

$$\alpha_o (1 + \beta_{DC}) = \beta_{DC}$$

$$\alpha_o = \beta_{DC} / (1 + \beta_{DC})$$

$\beta_{DC} = \alpha_o / (1 - \alpha_o)$; this expression shows that $\beta_{DC} > 1$

$\alpha_o = \beta_{DC} / (1 + \beta_{DC})$; this expression shows that $\alpha_o < 1$



$\alpha_o \approx 1$. Thus, $\beta_{DC} \gg 1$.

If $\alpha_o = 0.99$, $\beta_{DC} = 0.99 / (1 - 0.99) = 99$.

If $\alpha_o = 0.998$, $\beta_{DC} = 0.998 / (1 - 0.998) = 499$.


These results show that a small change in I_B will cause a large difference in I_C .

  From the output characteristics of the CE, there is still output current, I_C , flowing although $I_B = 0$ and this is the I_{CEO} which is the leakage current when $I_B = 0$.




BIASING

- The BJT must be biased in order to operate it as an amplifier.
- A DC operating point must be set so that the signal at the input terminal can be amplified and reproduced without any distortion at the output terminal.
- For the CE amplifier, the DC operating point is I_C and V_{CE} (for npn or V_{EC} for pnp). The operating point must be in the active region in order for the BJT to operate as an amplifier.
- The DC operating point is known as the quiescent (Q) point. For the CE amplifier, the Q point is I_{CQ} and V_{CEQ} .
- With the correct biasing, the circuit need not be changed or redesign when another transistor from the same type is substituted or when the temperature changes. In other words, a biasing circuit needs to be stable.

 

To determine the operating point:

- The DC load line is drawn on the output characteristic to determine the operating current and voltage of the circuit. The intersection of the load line with the I and V axis depends on the circuit's schematic.
- A DC biasing point / quiescent (Q) point is determined from the load line in the active region. The Q point is a point on the load line that represents the current and voltage at the output of a transistor when there is no AC signal. The stability of a biasing point is influenced by the change in the parameters (as an example: β_{DC}) when the transistor is replaced by another transistor of the same type or by the change in temperature.

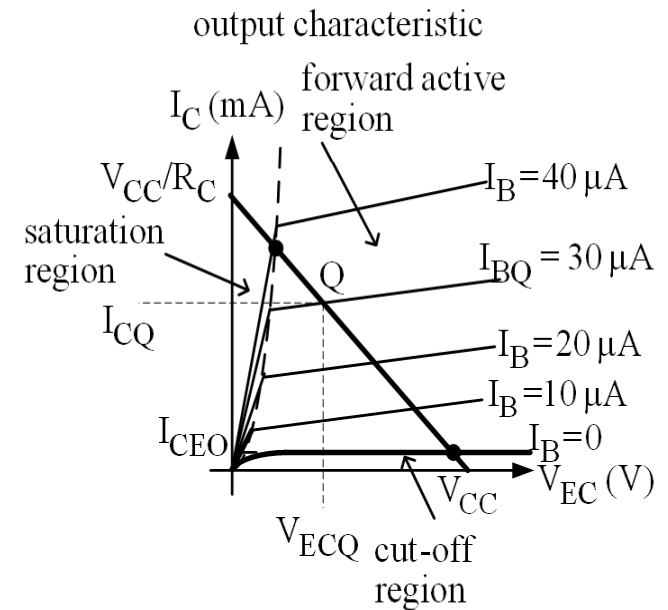


From Floyd, Electronic Devices, Sixth Edition.

Maximum Ratings

Rating	Symbol	Value	Unit
Collector-Emitter voltage	V_{CEO}	40	V dc
Collector-Base voltage	V_{CBO}	60	V dc
Emitter-Base voltage	V_{EBO}	6.0	V dc
Collector current — continuous	I_C	200	mA dc
Total device dissipation @ $T_A = 25^\circ\text{C}$ Derate above 25°C	P_D	625 5.0	mW mW/ $^\circ\text{C}$
Total device dissipation @ $T_C = 25^\circ\text{C}$ Derate above 25°C	P_D	1.5 12	Watts mW/ $^\circ\text{C}$
Operating and storage junction Temperature range	T_J, T_{stg}	-55 to +150	$^\circ\text{C}$

Thermal Characteristics

Characteristic	Symbol	Max	Unit
Thermal resistance, junction to case	$R_{\theta JC}$	83.3	$^\circ\text{C/W}$
Thermal resistance, junction to ambient	$R_{\theta JA}$	200	$^\circ\text{C/W}$

 

Electrical Characteristics ($T_A = 25^\circ\text{C}$ unless otherwise noted.)

Characteristic	Symbol	Min	Max	Unit
OFF Characteristics				
Collector-Emitter breakdown voltage ($I_C = 1.0$ mA dc, $I_B = 0$)	$V_{(BR)CEO}$	40	—	V dc
Collector-Base breakdown voltage ($I_C = 10$ μA dc, $I_E = 0$)	$V_{(BR)CBO}$	60	—	V dc
Emitter-Base breakdown voltage ($I_E = 10$ μA dc, $I_C = 0$)	$V_{(BR)EBO}$	6.0	—	V dc
Base cutoff current ($V_{CE} = 30$ V dc, $V_{EB} = 3.0$ V dc)	I_{BL}	—	50	nA dc
Collector cutoff current ($V_{CE} = 30$ V dc, $V_{EB} = 3.0$ V dc)	I_{CEX}	—	50	nA dc
ON Characteristics				
DC current gain ($I_C = 0.1$ mA dc, $V_{CE} = 1.0$ V dc)	h_{FE}	2N3903	20	—
		2N3904	40	—
($I_C = 1.0$ mA dc, $V_{CE} = 1.0$ V dc)		2N3903	35	—
		2N3904	70	—
($I_C = 10$ mA dc, $V_{CE} = 1.0$ V dc)		2N3903	50	150
		2N3904	100	300
($I_C = 50$ mA dc, $V_{CE} = 1.0$ V dc)	2N3903	30	—	
	2N3904	60	—	
($I_C = 100$ mA dc, $V_{CE} = 1.0$ V dc)	2N3903	15	—	
	2N3904	30	—	
Collector-Emitter saturation voltage ($I_C = 10$ mA dc, $I_B = 1.0$ mA dc) ($I_C = 50$ mA dc, $I_B = 5.0$ mA dc)	$V_{CE(sat)}$	—	0.2 0.3	V dc
Base-Emitter saturation voltage ($I_C = 10$ mA dc, $I_B = 1.0$ mA dc) ($I_C = 50$ mA dc, $I_B = 5.0$ mA dc)	$V_{BE(sat)}$	0.65	0.85 0.95	V dc

▲ FIGURE 4-19
Partial transistor data sheet.