

CLASS 8

p-n junction biasing, diode and
piecewise linear diode models

TUTORS

NAME	ROOM	TUTORIAL HOURS
NG YUN YANN	2.09	10-11, 11-12, 2-3 TUESDAY BT1 AEROANGKASA
TAN CHIY HOW	2.09	10-11, 11-12, 2-3 TUESDAY BT2 AEROANGKASA
NURUL NIETENI	2.09a	11-12, 2-3, 3-4 TUESDAY BK3 E&E

Hole current crosses the junction and enters the n as:

$$I_{pn} = \frac{AqD_p p_n}{L_p} \left(e^{V/V_T} - 1 \right)$$

Electron current crosses the junction and enters the p as:

$$I_{np} = \frac{AqD_n n_p}{L_n} \left(e^{V/V_T} - 1 \right)$$

where **A** = cross section area

L_p , **L_n** = hole, electron diffusion length in n,p

p_n , **n_p** = hole, electron density in n, p
(minority carriers)

q = electronic charge, 1.6×10^{-19} C

D_p , **D_n** = hole, electron diffusion coefficient


V = forward biasing voltage,

V_T = temperature equivalent voltage

$$= kT/q \approx 26 \text{ mV at } T = 300^\circ\text{K,}$$

k = Boltzmann constant = 1.38×10^{-23} J/°K

FORWARD CURRENT

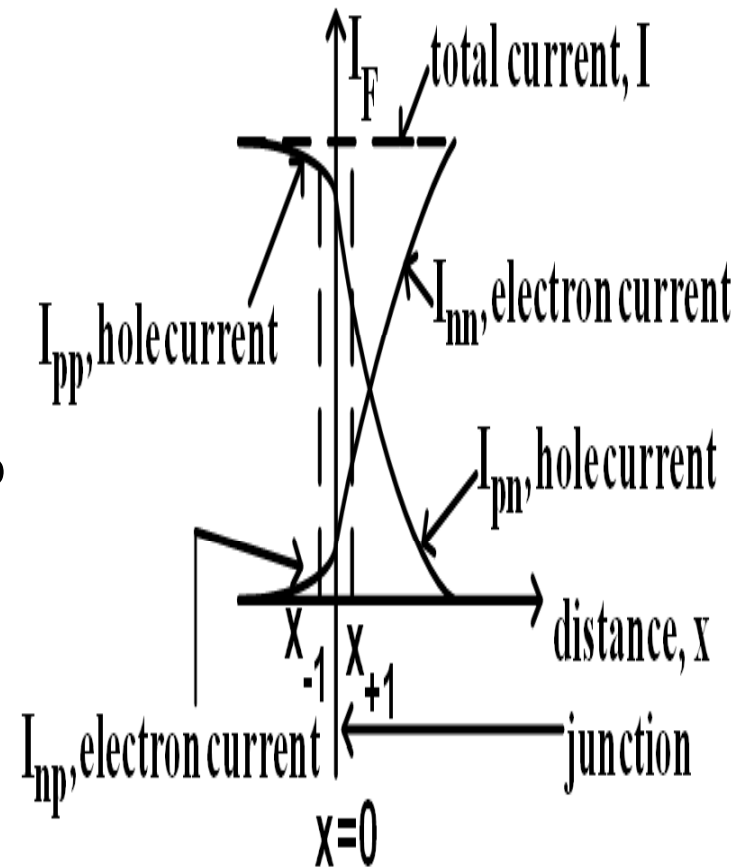


- **Hole diffusion length in n:**

$L_p = |x_1 - x_0|$ is the distance into the n before the hole recombines with an electron.

- **Electron diffusion length in p:**

$L_n = |x_2 - x_0|$ is the distance into the p before the electron recombines with a hole.

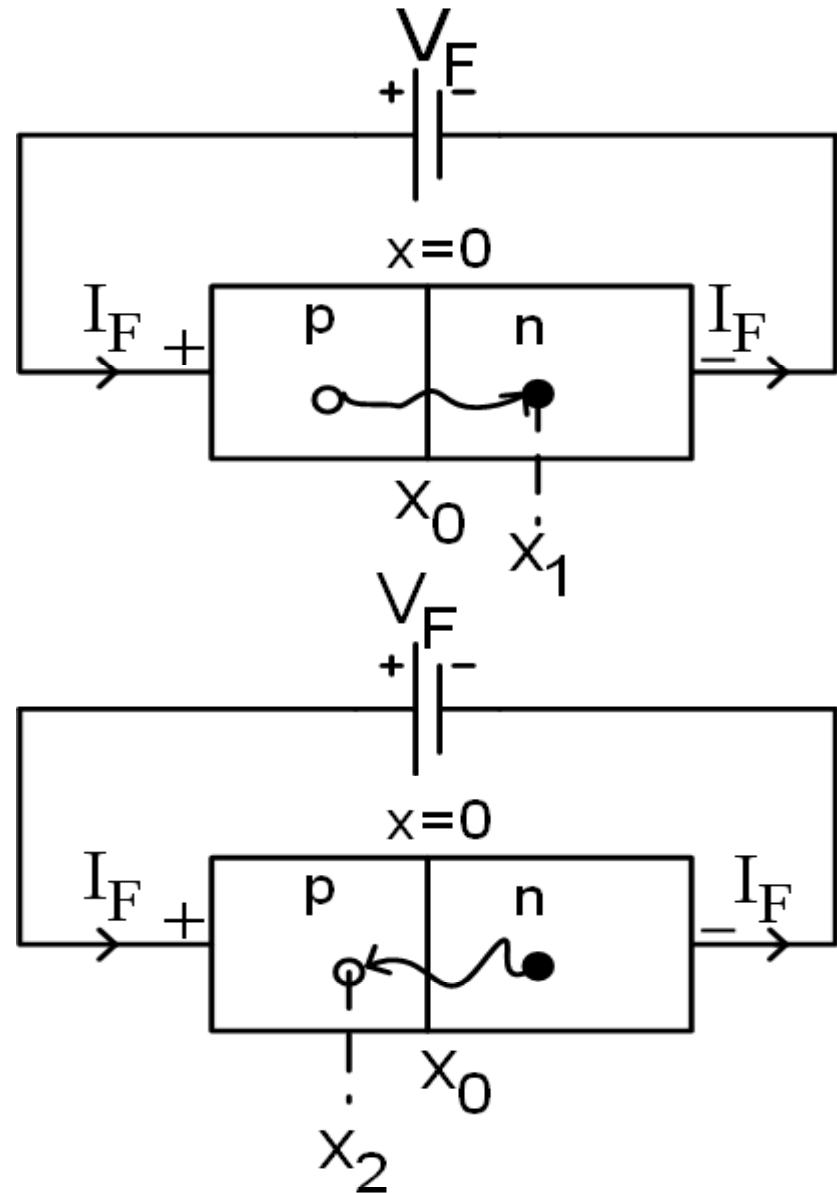

At $x = 0$, $I = I_{pn} + I_{np}$


$$I_{np} = \frac{AqD_n n_p}{L_n} \left(e^{V/V_T} - 1 \right)$$

$$I_{pn} = \frac{AqD_p p_n}{L_p} \left(e^{V/V_T} - 1 \right)$$

$$I = \left(\frac{AqD_p p_n}{L_p} + \frac{AqD_n n_p}{L_n} \right) \left(e^{V/V_T} - 1 \right)$$

$$= I_S \left(e^{V/V_T} - 1 \right)$$

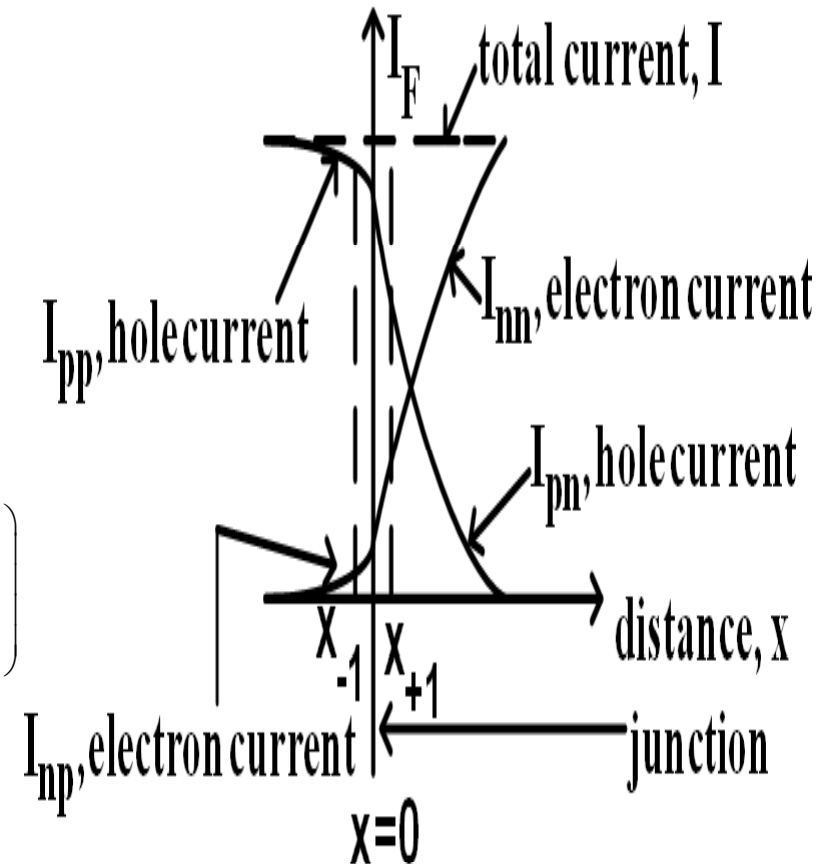where I_S is the reverse saturated current.



$$L_p = \sqrt{D_p \tau_p}$$

$$L_n = \sqrt{D_n \tau_n}$$

τ_p = Hole lifetime in n

τ_n = Electron lifetime in p

$$\tau_p = |t_1 - t_0|$$

$$\tau_n = |t_2 - t_0|$$




If l_p and l_n are the length of the p and n respectively, then

$$I = \left(\frac{AqD_p p_n}{L_p} + \frac{AqD_n n_p}{L_n} \right) \left(e^{V/V_T} - 1 \right)$$



is for the condition when $l_p \gg L_p$ and $l_n \gg L_n$.

If $l_p < L_p$ and $l_n < L_n$, then
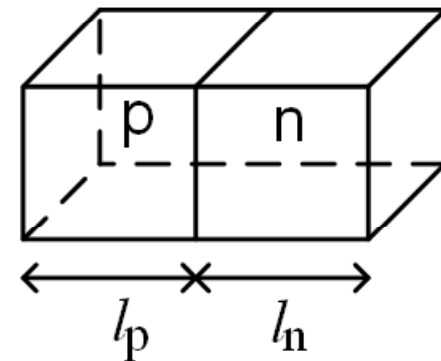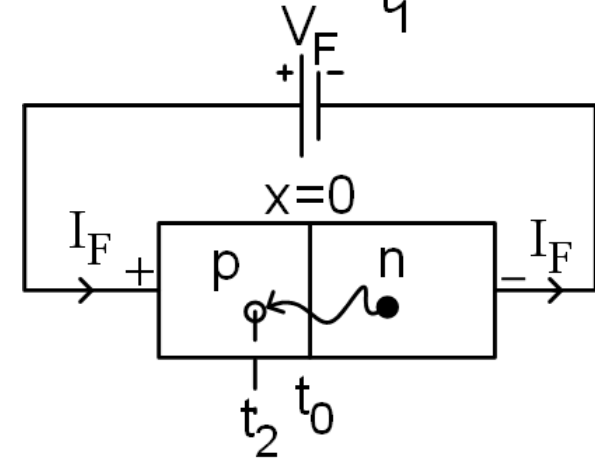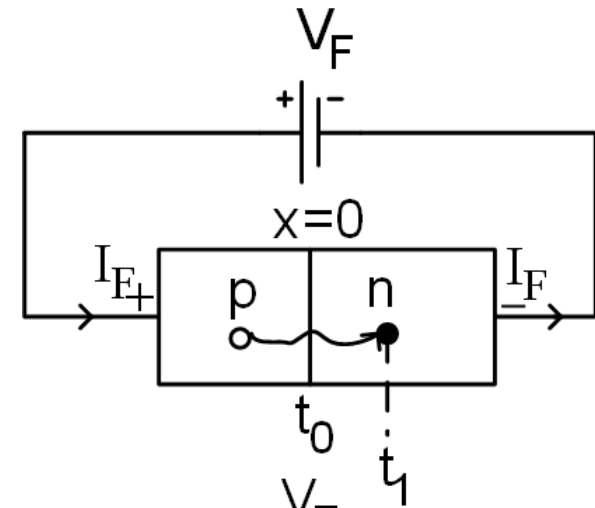
$$I = \left(\frac{AqD_p p_n}{l_p} + \frac{AqD_n n_p}{l_n} \right) \left(e^{V/V_T} - 1 \right)$$




DIODE

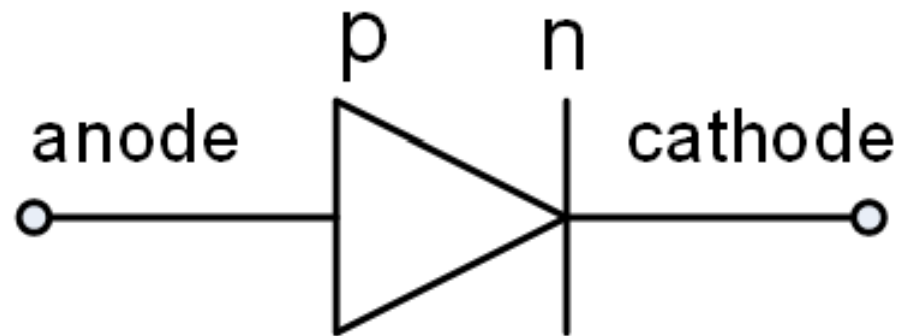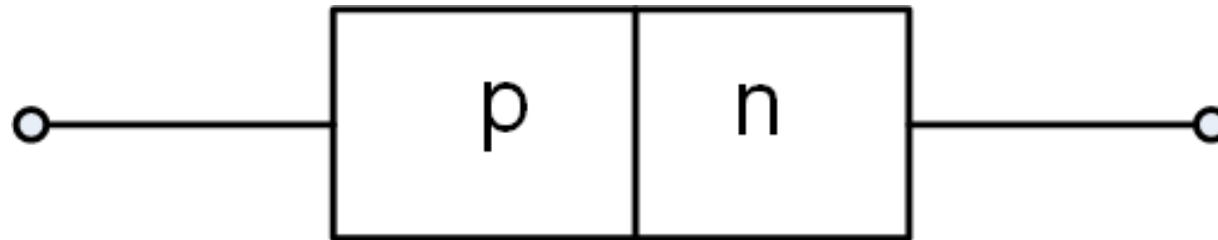

symbol for the diode

- In the fb region, the diode is a conductor and has low resistance towards current (provided $V_F > V_{ON}$). Diode can be replaced by a short.
- In the rb region, the diode is a weak conductor and has very high resistance towards current (condition before avalanche). Diode can be replaced by an open.
- The reverse avalanche region should be avoided as the diode may be damaged under this condition.

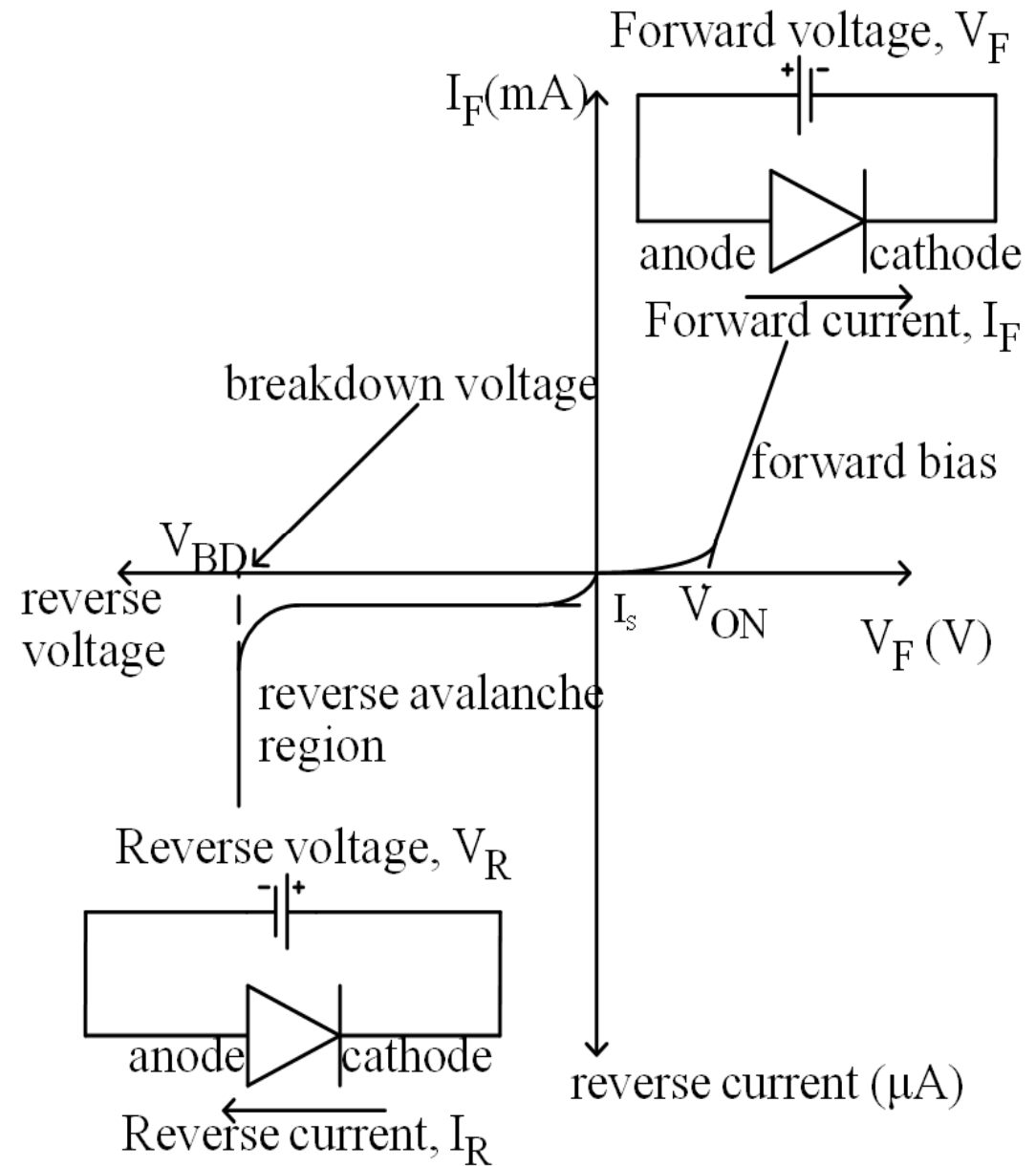

DIODE CURRENT

$$I = I_S \left(e^{\left(\frac{V}{\eta V_T} \right)} - 1 \right)$$

where I_S is the saturated current. For a small signal diode (small size diode for low power application), I_S is in the vicinity of 10^{-15} A. I_S is very dependent on temperature. For example, I_S in Ge may double for every 10°C increase in temperature.

$\eta = 1 \rightarrow 2$ depending on the material and the physical structure of the diode.

Diode fabricated through typical IC process $\eta = 1$ when operated under normal condition.


DIODE CIRCUITS

Piecewise linear diode model

Transistors are used in electronic circuits. Transistors are active devices that have non-linear characteristics.

A transistor is constructed of 2 p-n junctions. The p-n junction is having non-linear characteristics.

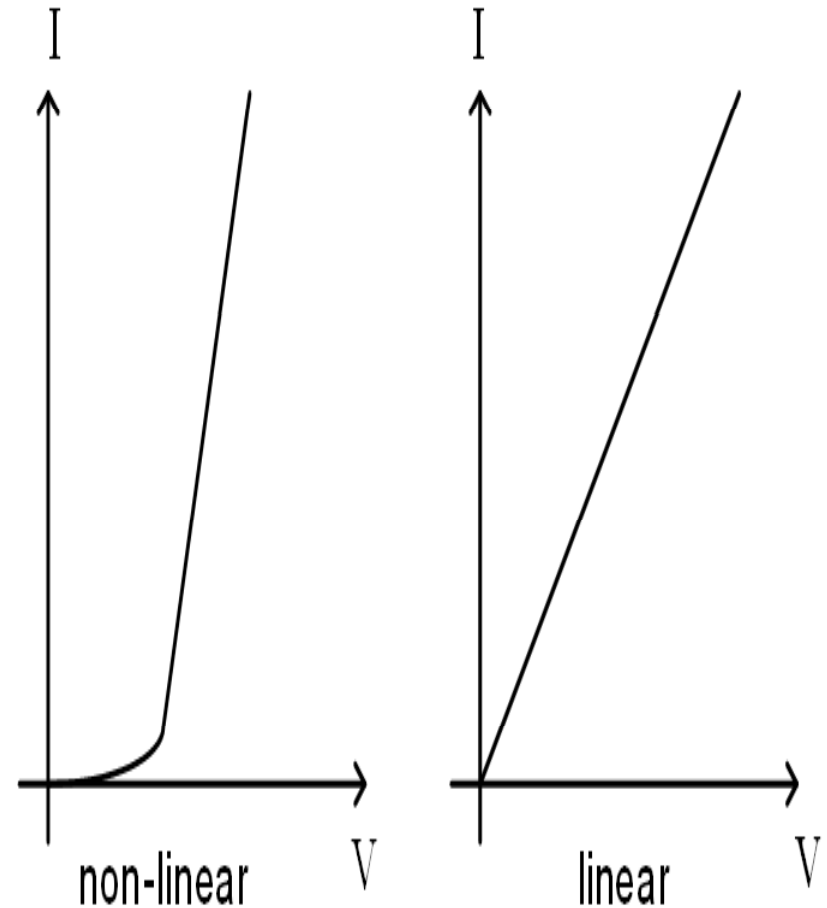Typical technique used in analyzing non-linear circuits is the graph technique. However, this technique is inappropriate if the circuit is complex, contains capacitors and inductors whose dynamic characteristic is more important than its static characteristic.



- **Diode is not an active device, but it has non-linear characteristics. Hence, the diode can be used as a model to analyze non-linear circuits.**
- **Piecewise linear diode model is in the form of a network that contains linear elements such as the resistor.**
- **The diode model technique can be used for other non-linear components. This is to simplify the analysis of non-linear circuits.**

Replacing junction diodes with piecewise linear diodes will:

- 1. reduce the problem of analyzing non-linear network as the network is converted to become linear. Consequently, typical method of analysis can be implemented.**
- 2. provide combined linear I-V relationships to give an approximation of the overall non-linear I-V characteristic.**

Diode characteristics:

- 1. Enable large current to flow in one direction (during forward bias) and only a very small current to flow in the opposite direction (during reverse bias).**
- 2. Enable large voltage drop across the diode terminals during reverse bias but a very small voltage during forward bias. The reverse voltage can reach hundreds of volts.**





IDEAL PIECEWISE LINEAR DIODE MODEL

$$I_F \gg I_R$$

$$V_R \gg V_d$$



Ideal piecewise linear diode model:

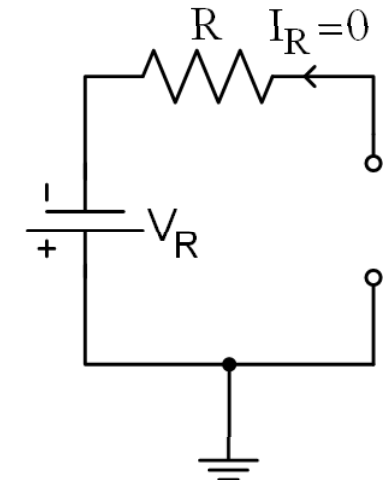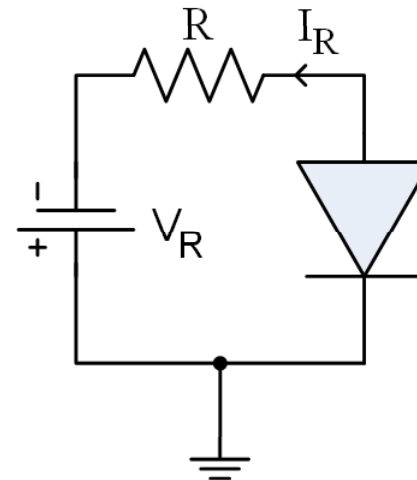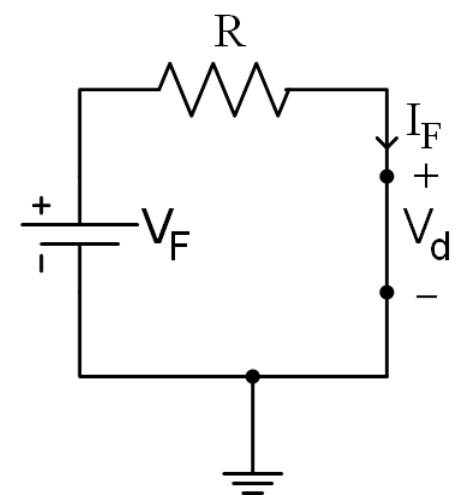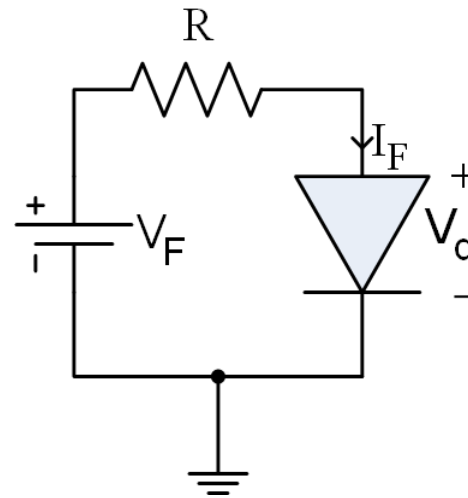1. Under the forward bias condition, $I_F > 0$ and $V_d = 0$. Diode is a s/c.
2. Under the reverse bias condition, $I_R = 0$ and $V_d < 0$. Diode is an o/c.
3. Potential barrier and reverse leakage current is neglected.




- **Conclusions:**

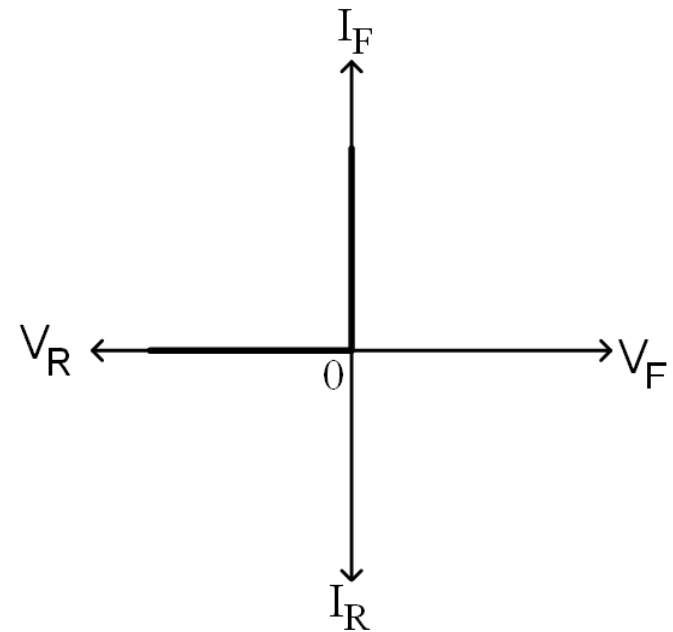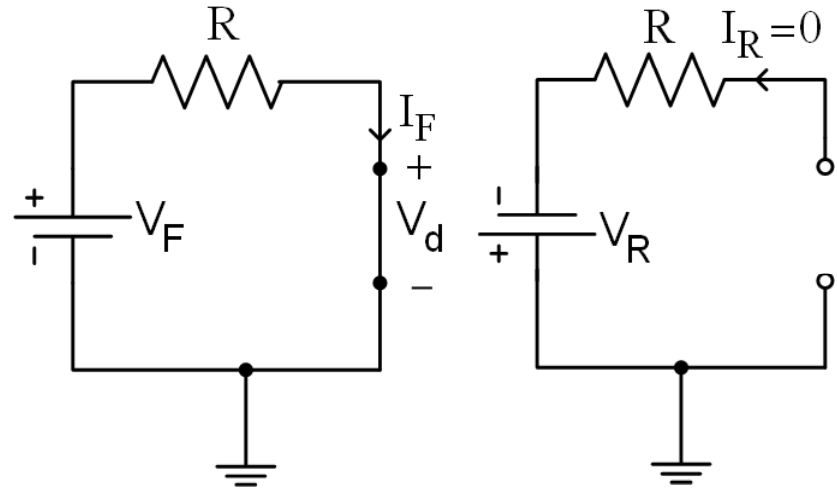
1. s/c when the current is +ve (as $V_d=0$). Under the fb condition, diode can be represented by a s/c.
2. o/c when the voltage is -ve (as $I_R=0$). Under the rb condition, diode can be represented by an o/c.
3. The ideal piecewise linear diode model is a rough approximation of the characteristics of a p-n junction diode but the precision is sufficient.
4. The ideal piecewise linear diode model is a 1st order model to estimate the general behavior of an unknown diode circuit.








Equivalent circuit for the diode in an ideal piecewise linear diode model.

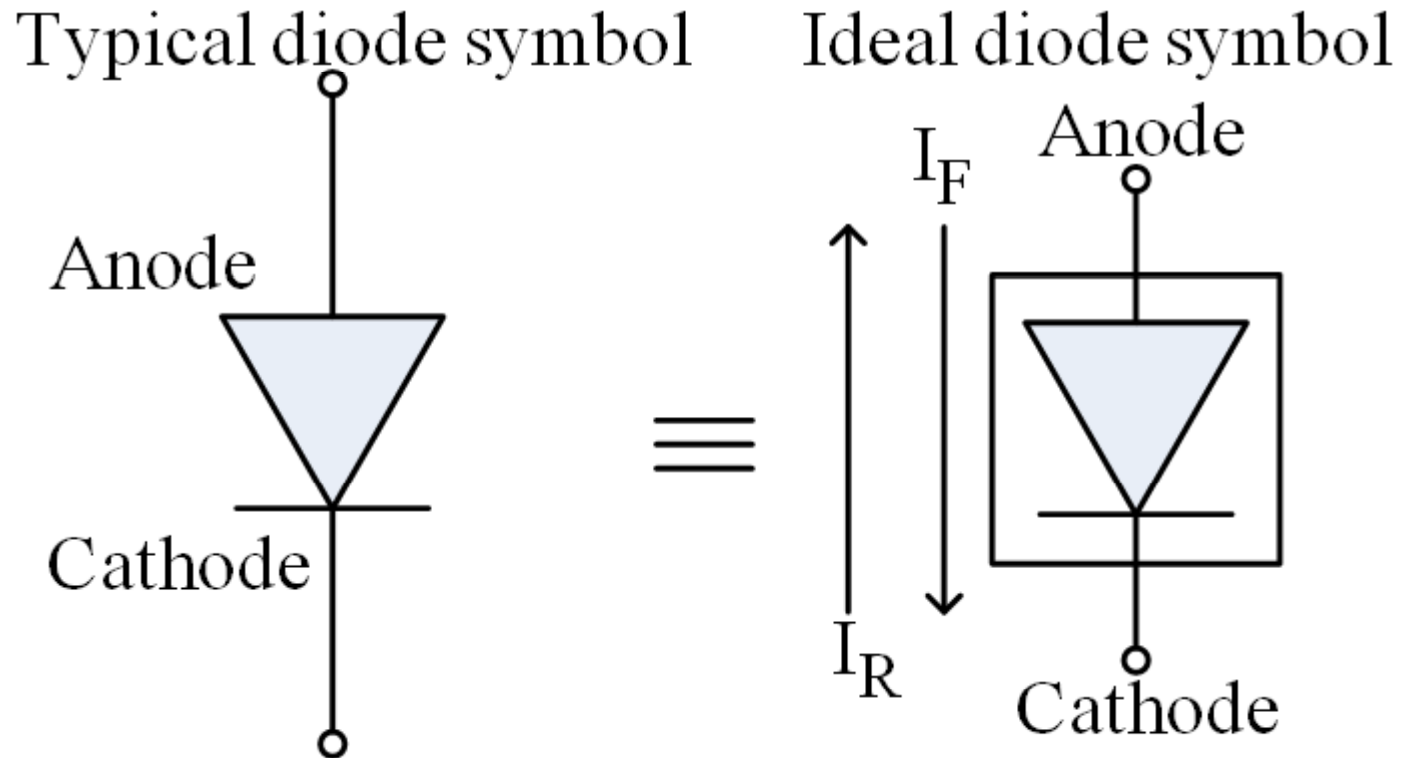


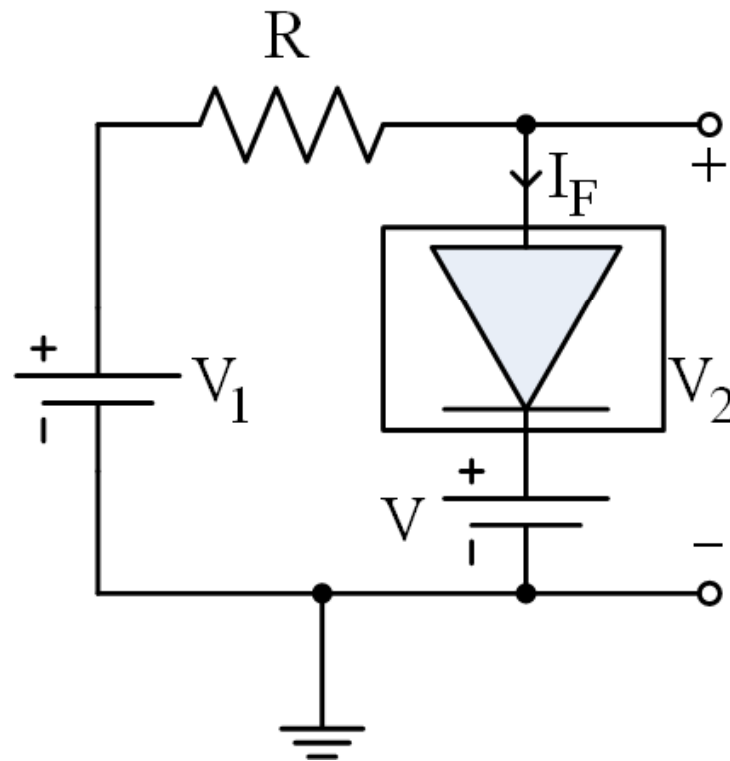Example 1: Draw the transfer characteristic of the following circuit using the ideal piecewise linear diode model.



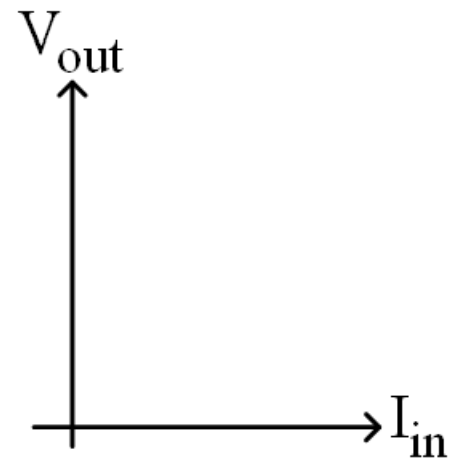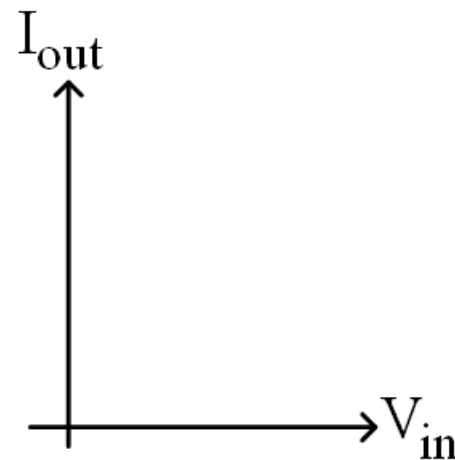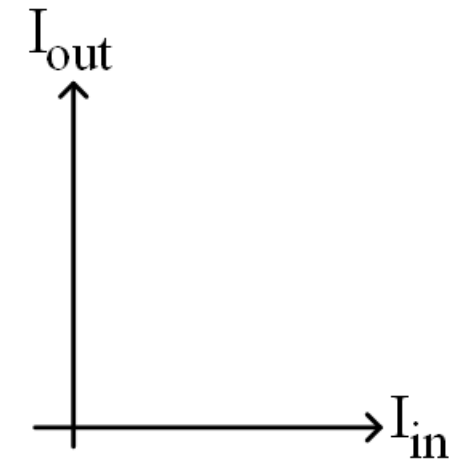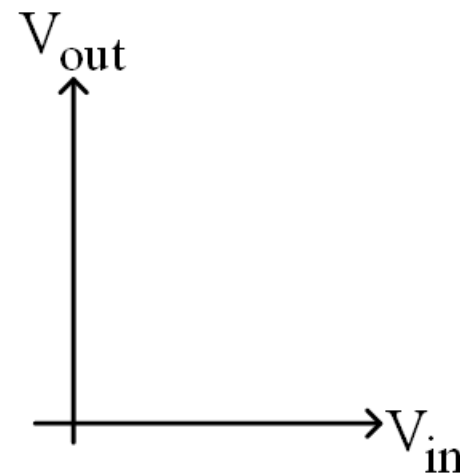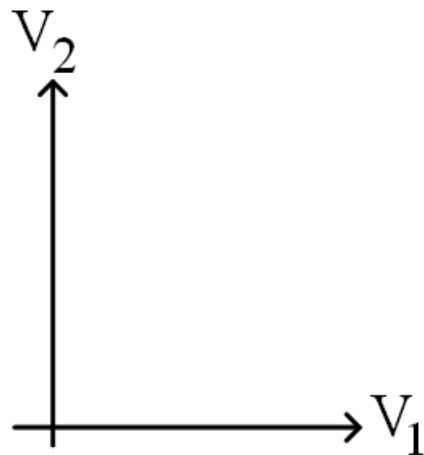- In general, transfer characteristic is the characterization of the o/p vs the i/p.
- In this Example 1, transfer characteristic is V_2 vs V_1 .



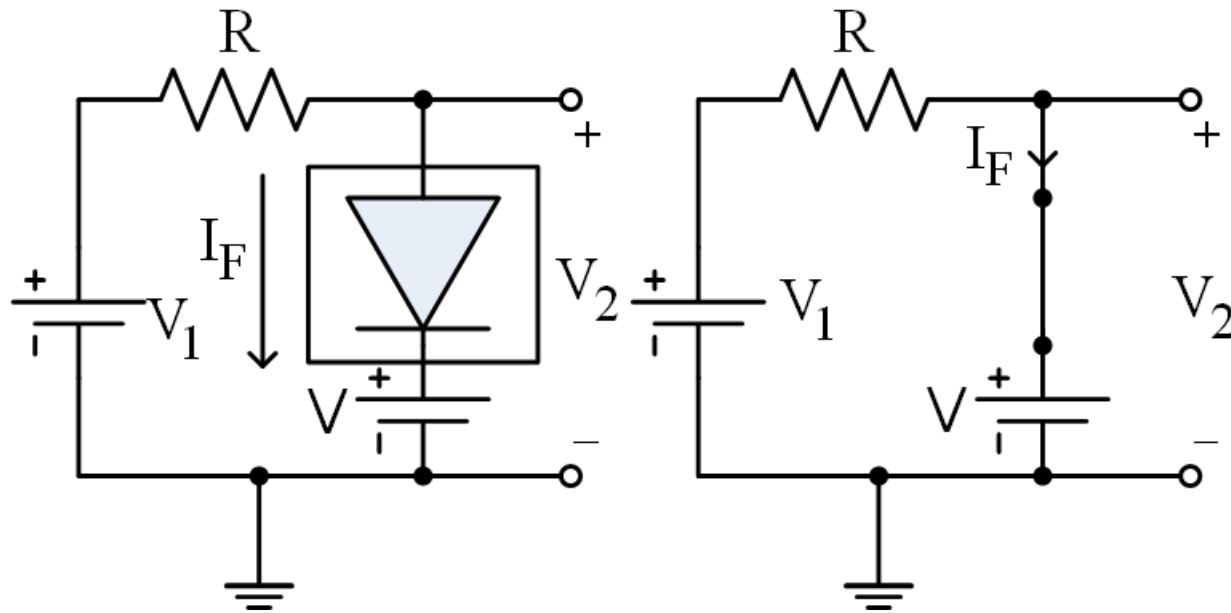


Solution:

Case 1 – What is the condition that will fb the diode?

Case 2 – What is the condition that will rb the diode?


Case 1

To fb the diode, $V_1 > V$. If the diode is ideal, it can be represented by a s/c. Hence, $V_2 > V$.

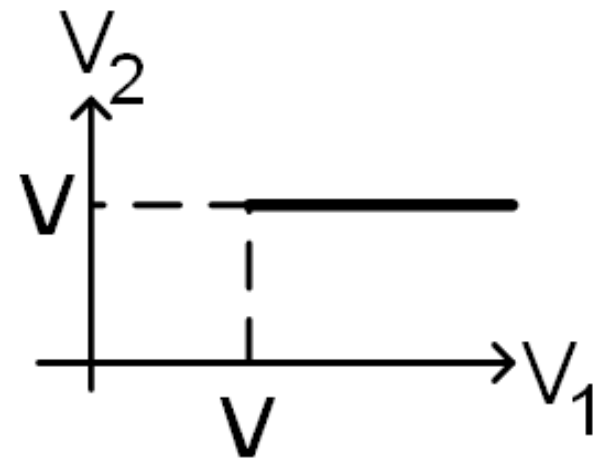


Case 2

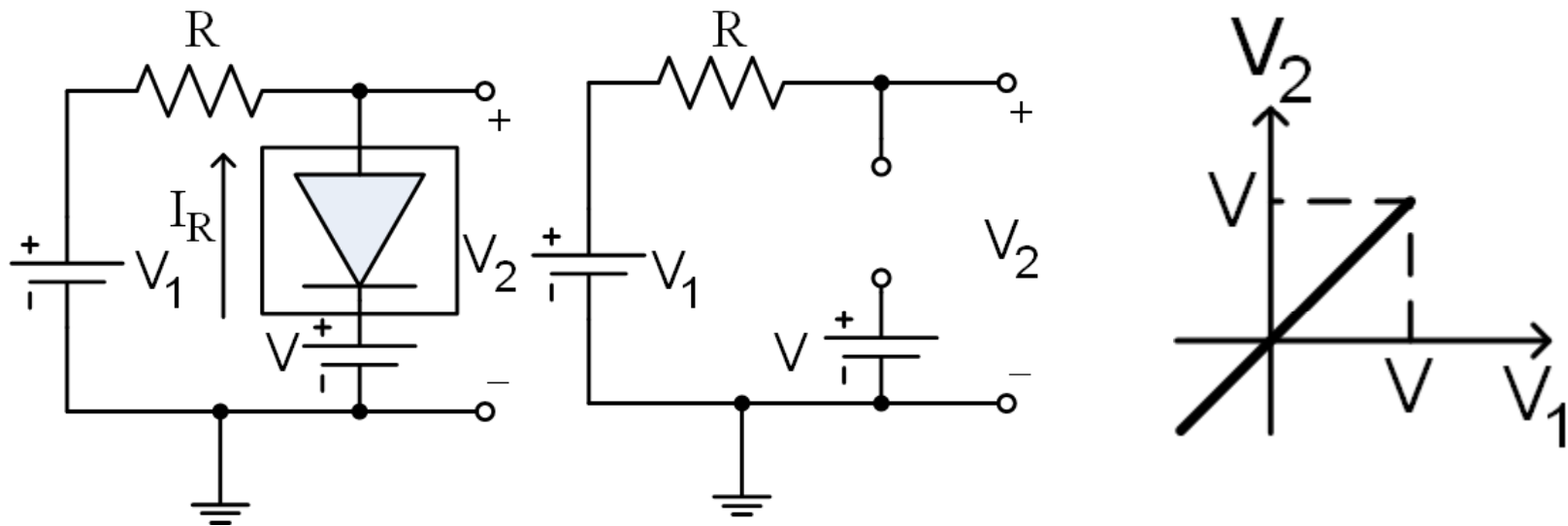To reverse bias the diode, $V_1 < V$. The ideal diode is represented by an o/c. Hence, $V_2 = V_1$.



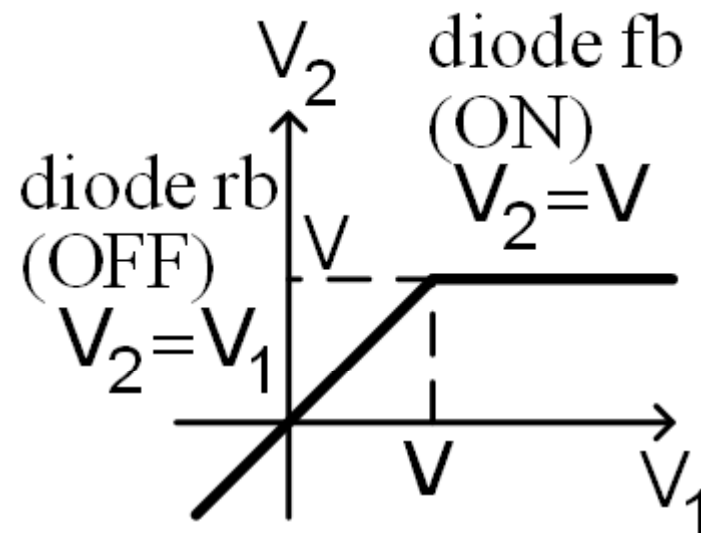The overall transfer characteristic of the diode circuit:



More accurate piecewise linear diode model

A more accurate representation of the diode's characteristic can be obtained by considering the forward voltage drop and resistance.

