## **CORRECTIONS TO Q2(b) and (c)**

## Q2 – Original solutions.

# (C) The diodes are Silicon based on the 0.7021 V across them when they are forward biased.

## Corrected solution to 2(b).

$$T = 300^{\circ}K$$

$$V_T = kT/q = 0.02589 \text{ V}.$$

From (a), 
$$I_{D1} / I_{D2} = 1/5$$

From the circuit,  $I_{D1} + I_{D2} = 3mA$ 

So, 
$$I_{D1} + 5I_{D1} = 3mA$$

$$I_{D1}=0.5\ mA$$

$$0.5 \text{ mA} = 10^{-15} (e^{V/V}_{T} - 1)$$

$$e^{V/V}_{T} = 5x10^{11}$$

$$V/V_T = 26.9379$$

Hence,  $V_T = 0.6974 \text{ V}$ .

## **Corrected solution to 2(c).**

The diodes are Silicon based on the approximately 0.7 V across them when they are forward biased.