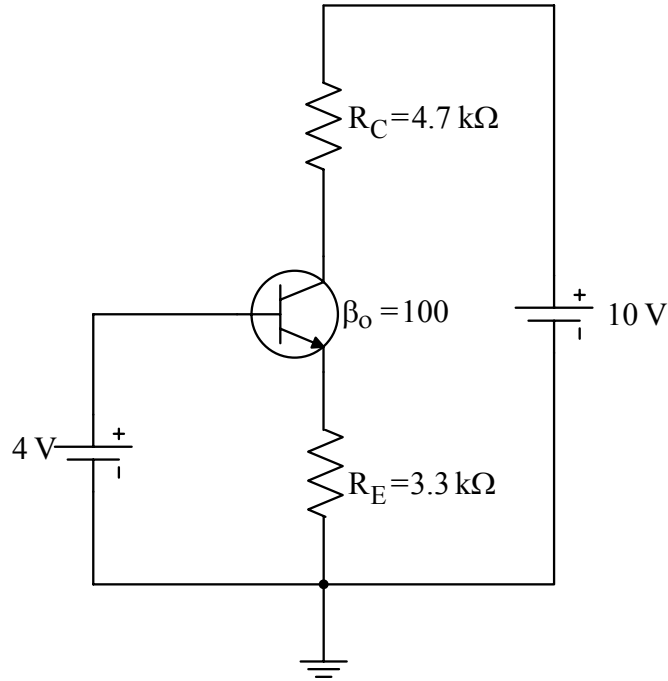



## TUTORIAL 6

1. Determine the voltage and current at the terminals B, E and C for each of the following circuit. The transistor is Silicon and  $V_{BE} = 0.7 \text{ V}$ . Determine the mode of operation of each transistor.  $V_{CE(\text{sat})} = 0.3 \text{ V}$ .


(a)




(b)

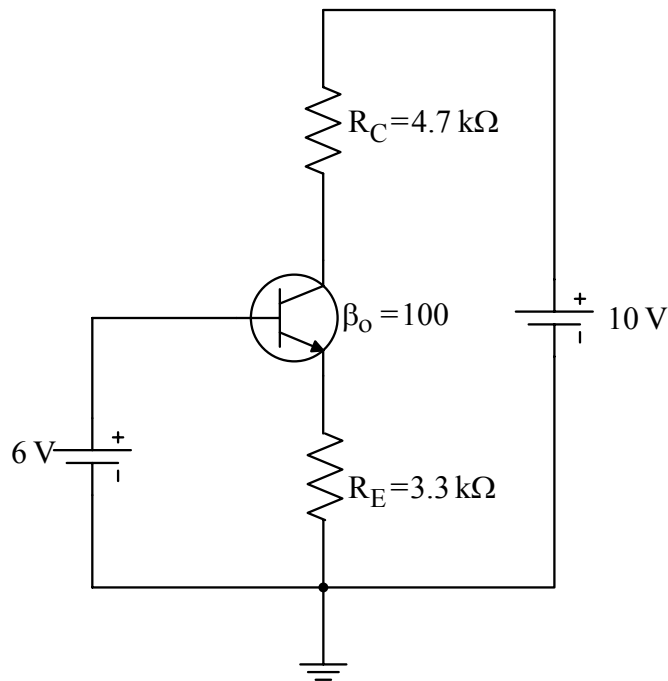

(c)

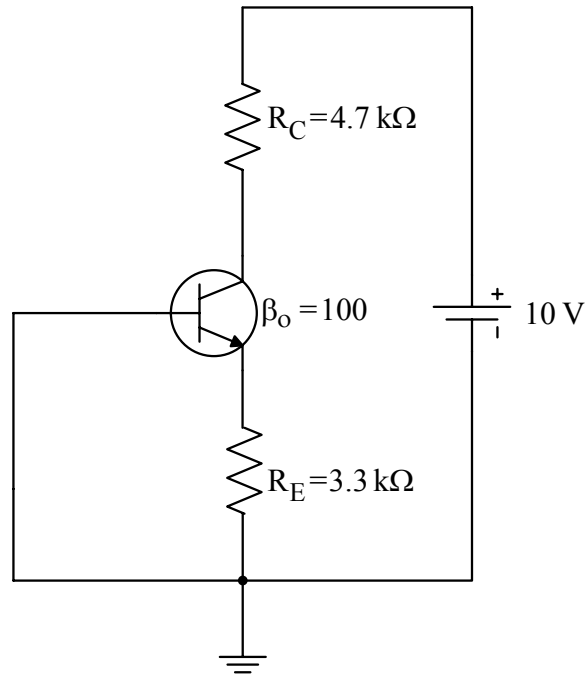

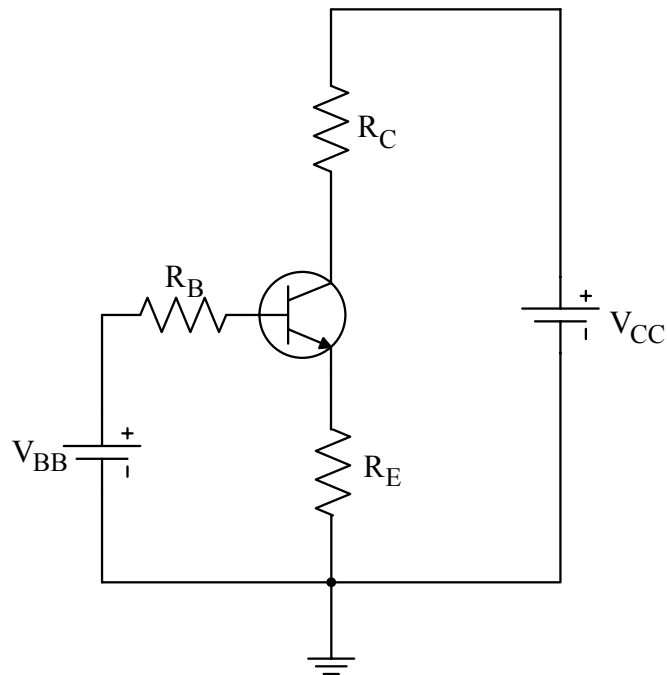
2. The following transistor is a Silicon with  $V_{BE} = 0.7 \text{ V}$ ,  $I_B = 40 \mu\text{A}$  and  $I_{CB0} = 0$ . If  $V_{BB} = 6 \text{ V}$ ,  $R_E = 1 \text{ k}\Omega$  and  $\beta = 80$ , determine
- $I_{EQ}$  and  $R_B$ .
  - $V_{CEQ}$  if  $V_{CC} = 15 \text{ V}$  and  $R_C = 3 \text{ k}\Omega$ .



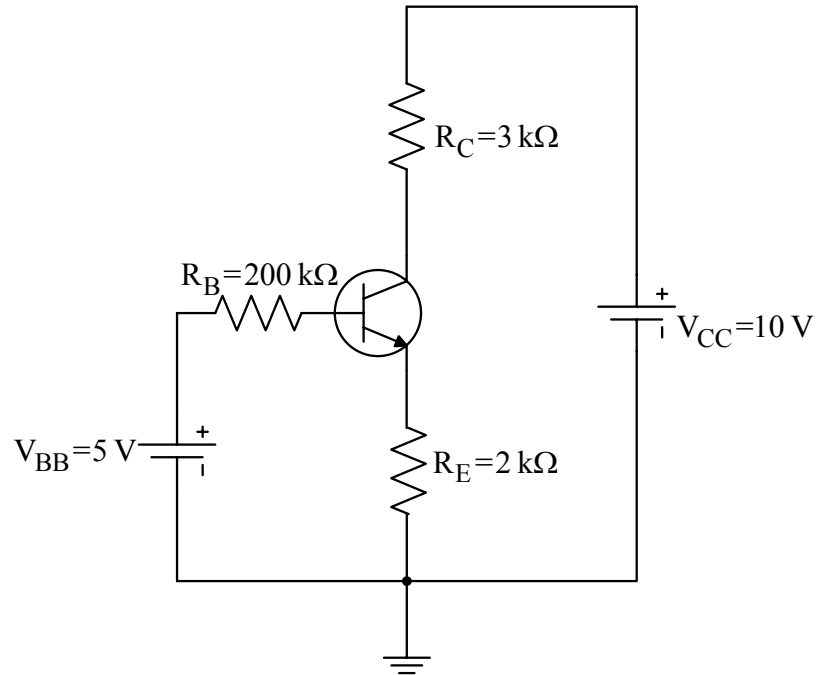- (iii) Draw the current components and the direction of their flow in an NPN BJT operating as an amplifier.

4(a). Sketch the output characteristic of a CE NPN transistor. Label the saturation, active and cut-off regions.


(b). Calculate the transistor's currents shown in the following diagram. Determine the Silicon transistor's operating region. Given  $\beta_0=120$  and  $I_{CB0}=20$  nA.



5(a). For the CB and CE Silicon NPN BJT amplifier, sketch:

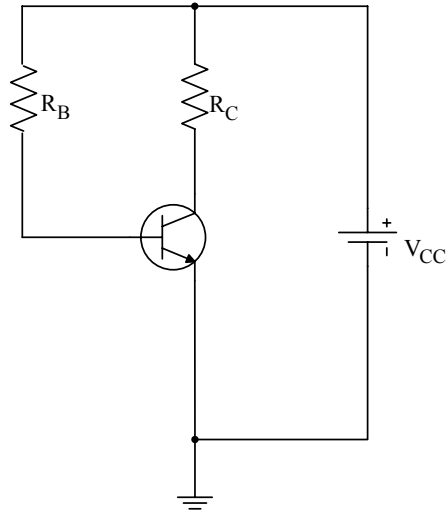- (i) the transistor's biasing diagram
- (ii) the input characteristic with the axis labeled
- (iii) the output characteristic with the axis and the typical input and leakage currents labeled


(b). A transistor is connected as a CE amplifier. If  $R_C=2.2$  k $\Omega$ ,  $V_{CC}=18$  V and  $I_B=40$   $\mu$ A, determine the biasing condition of the device and estimate the undistorted maximum output. Assume that the transistor is Silicon and  $V_{BE}=0.7$  V.



6(a). A Germanium transistor is operating as an amplifier (in its forward active mode). It has a leakage current  $I_{CB0} = 5 \mu\text{A}$  that has to be considered and  $\beta = 100$ . If the transistor is connected to operate as a CE, determine the collector current if:

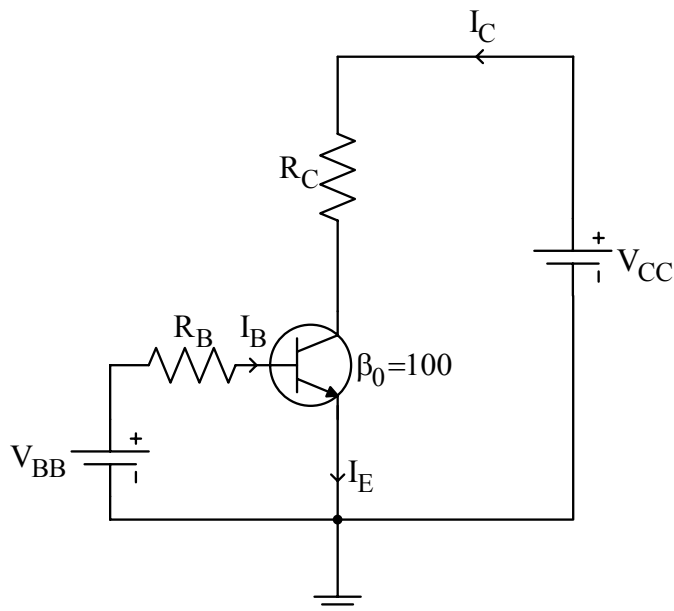- (i)  $I_B = 0$
- (ii)  $I_B = 40 \mu\text{A}$


(b). For the circuit below,  $\beta_0 = 100$ ,  $I_{BQ} = 20 \mu\text{A}$ ,  $V_{CC} = 15 \text{ V}$  and  $R_C = 3 \text{ k}\Omega$ . If  $I_{CB0} = 0$ , determine




- (i)  $I_{EQ}$
- (ii)  $V_{CEQ}$
- (iii)  $V_{CEQ}$  if  $R_C$  is increased to  $6 \text{ k}\Omega$

(c) Assume that the collector characteristic below is for the transistor in the circuit shown in (b). If  $I_{BQ} = 20 \mu\text{A}$ ,  $V_{CEQ} = 9 \text{ V}$ ,  $V_{CC} = 14 \text{ V}$  and the leakage current can be neglected, determine from the graph

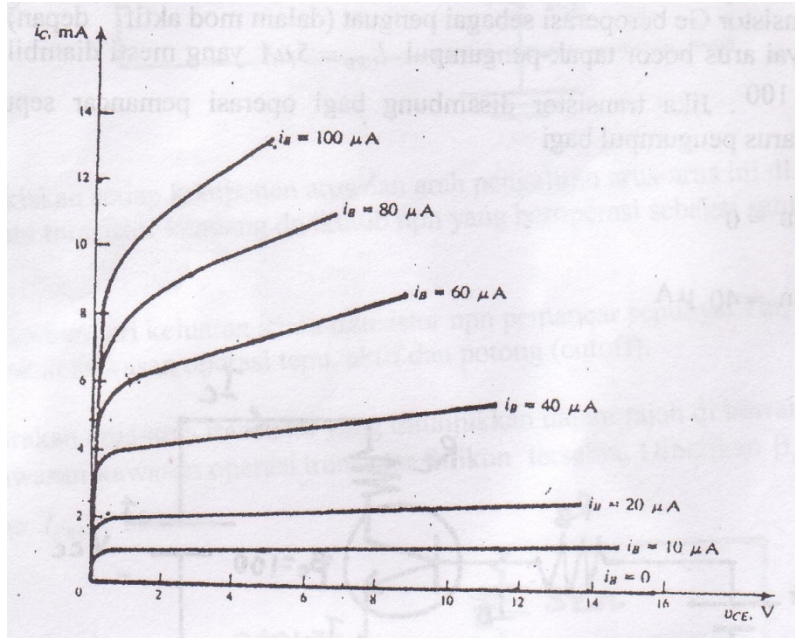- (i)  $I_{CQ}$
- (ii)  $R_C$
- (iii)  $I_{EQ}$
- (iv)  $\beta_0$



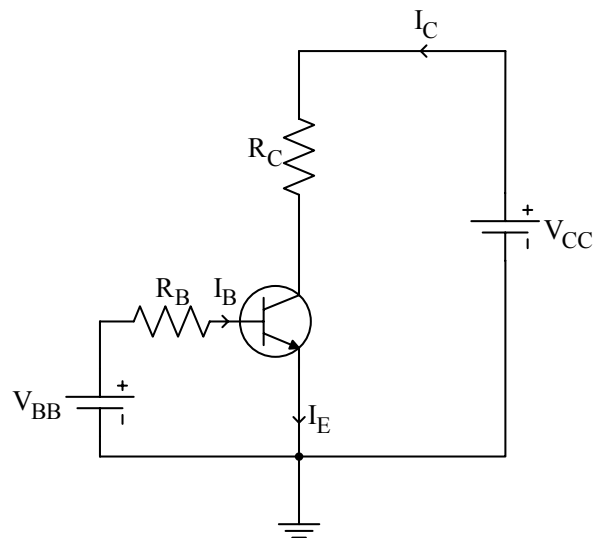7. Draw the transistor characteristic for the following circuit. Draw the load line of the circuit on the characteristic. What is the purpose of drawing the load line? If the circuit is to function as a switch, explain in detail the changes in  $I_E$ .




8. For the following 2 biasing BJT circuits, determine  $I_C$  and  $V_{CE}$  for

(i)  $h_{FE} = 50$

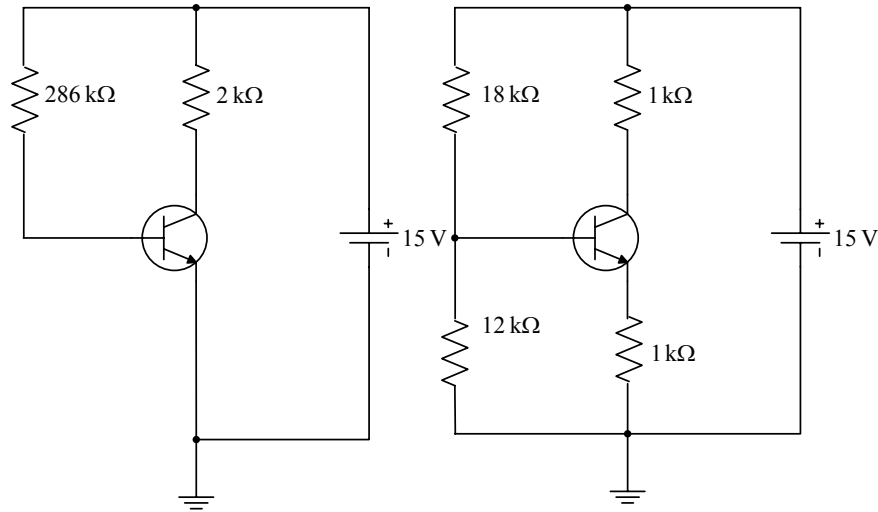(ii)  $h_{FE} = 150$


$V_{BE}$  for the transistors is 0.7 V. Reverse leakage current can be neglected. Comment on the performance (i.e. stability of the biasing point) for each circuit based on the results from (i) and (ii).



9. The Silicon transistor in the following circuit has  $I_{CB0} = 0$ ,  $h_{FE} = 100$  and  $V_{BE} = 0.7$  V.


(a) If  $R_C = 2$  kΩ and  $V_{CC} = 12$  V, determine  $R_F$  to obtain the maximum output signal swing.

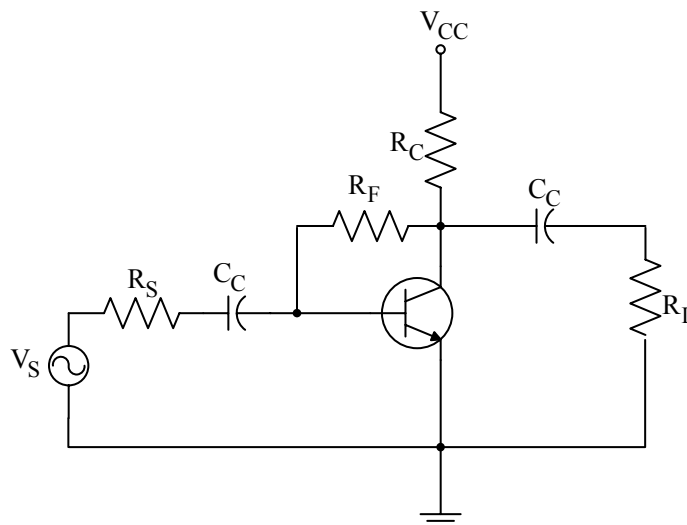(b) Determine the emitter resistance,  $R_E$ , which when added to the following Silicon transistor circuit will cause the circuit to operate with the following condition:  $V_{CEQ} = 5$  V,  $\beta_0 = 80$ ,  $I_{CB0} = 0$ ,  $V_{BE} = 0.7$  V,  $R_F = 220$  kΩ,  $R_C = 2$  kΩ and  $V_{CC} = 12$  V.




10. State whether the transistor in each circuit below is biased in the active, saturation or cut-off region. Give reasons for your answer.


(i)

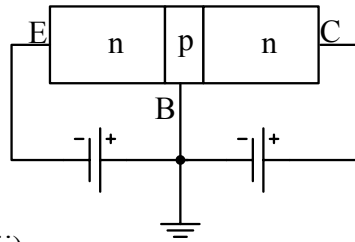

(ii)

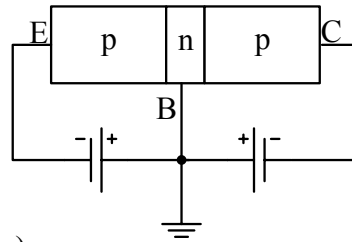

(iii)

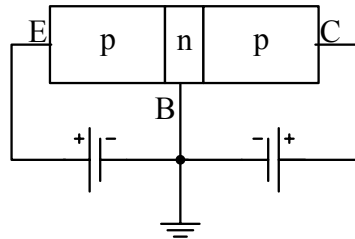

(iv)

