




UNIVERSITI SAINS MALAYSIA

EEE 241
ANALOG ELECTRONICS 1
Lecture 10&11

DR NORLAILI MOHD NOH

CE with Emitter Degeneration

To determine R_i :

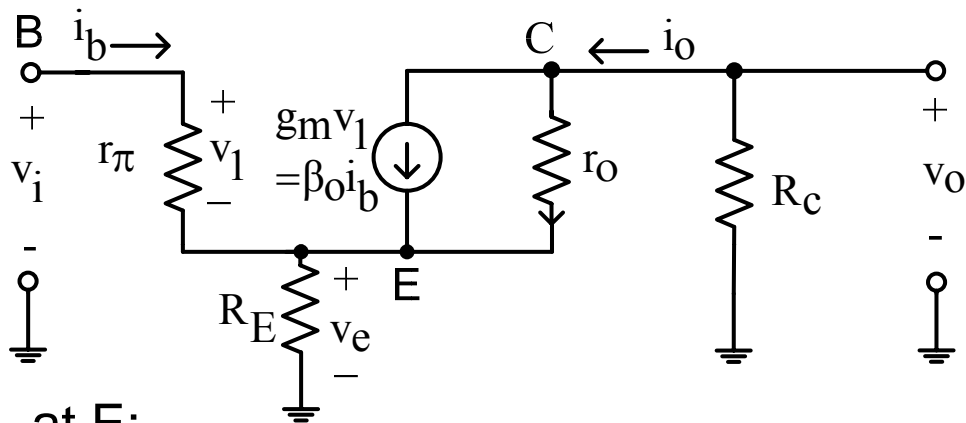


KCL at E:


$$i_b + \beta_0 i_b + \frac{v_o - v_e}{r_o} = \frac{v_e}{R_E}$$

$$(1 + \beta_0) i_b = \frac{v_e}{R_E} - \frac{-i_o R_C - v_e}{r_o} = \frac{v_e}{R_E} + \frac{i_o R_C + v_e}{r_o}$$

$$(1 + \beta_0) i_b = \frac{v_e}{R_E} + \frac{v_e}{r_o} + \frac{i_o R_C}{r_o}$$
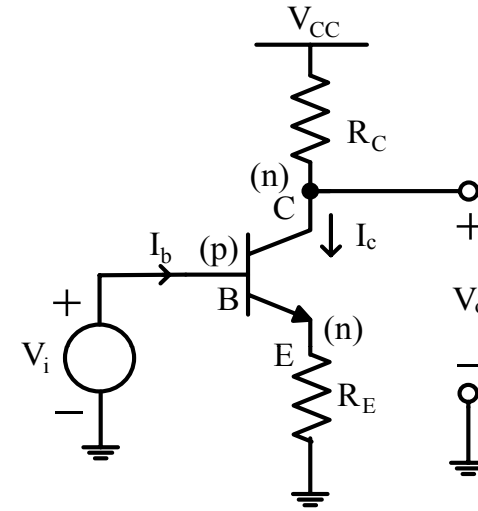
$$i_o = \left[(1 + \beta_0) i_b - \left(\frac{1}{R_E} + \frac{1}{r_o} \right) v_e \right] \frac{r_o}{R_C}$$



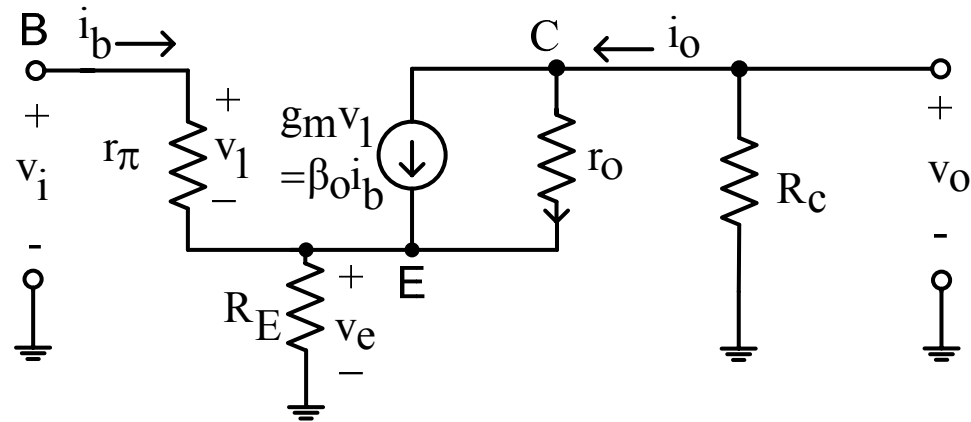

KCL at C:

$$i_o = \beta_o i_b + \frac{v_o - v_e}{r_o} = \beta_o i_b + \frac{-i_o R_C - v_e}{r_o}$$

Since KCL at E gives $i_o = \left[(1 + \beta_o) i_b - \left(\frac{1}{R_E} + \frac{1}{r_o} \right) v_e \right] \frac{r_o}{R_C}$ then,

$$\left[(1 + \beta_o) i_b - \left(\frac{1}{R_E} + \frac{1}{r_o} \right) v_e \right] \frac{r_o}{R_C} = \beta_o i_b + \frac{- \left[(1 + \beta_o) i_b - \left(\frac{1}{R_E} + \frac{1}{r_o} \right) v_e \right] \frac{r_o}{R_C} R_C - v_e}{r_o}$$

$$\left[(1 + \beta_o) \frac{r_o}{R_C} - \beta_o + (1 + \beta_o) \frac{r_o}{r_o R_C} R_C \right] i_b = \left\{ \left(\frac{1}{R_E} + \frac{1}{r_o} \right) \frac{r_o}{R_C} + \left(\frac{1}{R_E} + \frac{1}{r_o} \right) \frac{r_o}{r_o R_C} R_C - \frac{1}{r_o} \right\} v_e$$

$$\left[(1 + \beta_o) \frac{r_o}{R_C} - \beta_o + (1 + \beta_o) \right] i_b = \left\{ \left(\frac{1}{R_E} + \frac{1}{r_o} \right) \frac{r_o}{R_C} + \left(\frac{1}{R_E} + \frac{1}{r_o} \right) - \frac{1}{r_o} \right\} v_e$$

$$\left[(1+\beta_0)\frac{r_o}{R_C} - \beta_0 + (1+\beta_0) \right] i_b = \left\{ \left(\frac{1}{R_E} + \frac{1}{r_o} \right) \frac{r_o}{R_C} + \left(\frac{1}{R_E} + \frac{1}{r_o} \right) - \frac{1}{r_o} \right\} v_e$$

$$v_e = \left[\frac{(1+\beta_0)\frac{r_o}{R_C} + 1}{\frac{r_o}{R_E R_C} + \frac{1}{R_C} + \frac{1}{R_E}} \right] i_b$$


KVL of the input loop:

$$-v_i + v_1 + v_e = 0.$$

$$\text{Thus, } -v_i + i_b r_\pi + v_e = 0$$

$$v_i = r_\pi i_b + \left[\frac{(1+\beta_0)\frac{r_o}{R_C} + 1}{\frac{r_o}{R_E R_C} + \frac{1}{R_C} + \frac{1}{R_E}} \right] i_b$$
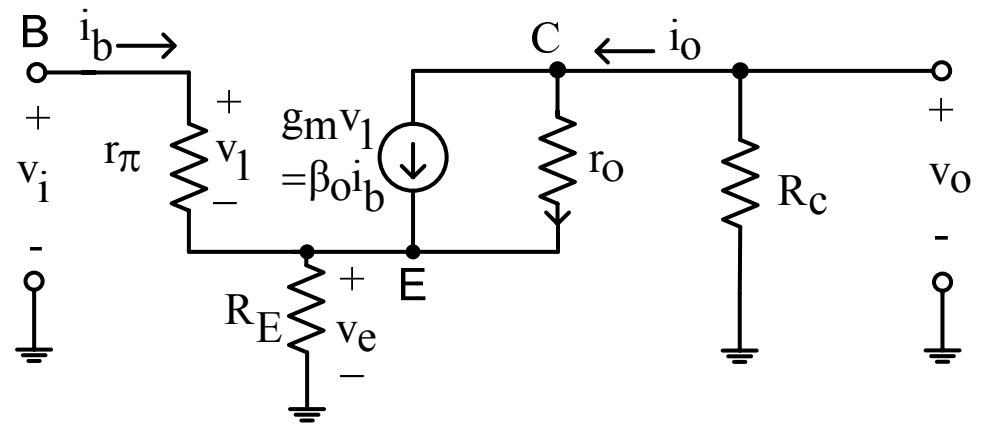
$$R_i = \frac{v_i}{i_b} = r_\pi + \left[\frac{(1+\beta_0)\frac{r_o}{R_C} + 1}{\frac{r_o}{R_E R_C} + \frac{1}{R_C} + \frac{1}{R_E}} \right] \leftarrow \text{enough}$$



$$\begin{aligned}
 R_i &= r_\pi + \left[\frac{(1+\beta_o)\frac{r_o}{R_C} + 1}{\frac{r_o}{R_E R_C} + \frac{1}{R_C} + \frac{1}{R_E}} \right] \\
 &= r_\pi + \frac{R_E R_C \left[1 + (1+\beta_o)\frac{r_o}{R_C} \right]}{r_o + R_C + R_E} \\
 &= r_\pi + \frac{(1+\beta_o)R_E \left[\frac{R_C}{(1+\beta_o)} + r_o \right]}{r_o + R_C + R_E}
 \end{aligned}$$

$$R_i = r_\pi + \frac{(1+\beta_0)R_E \left[\frac{R_C}{(1+\beta_0)} + r_o \right]}{r_o + R_C + R_E}$$

If $r_o \gg R_C$ and $r_o \gg R_E$ (in the case of $r_o \rightarrow \infty$), then

$$R_i = r_\pi + \frac{(1+\beta_0)R_E[r_o]}{r_o} = r_\pi + (1+\beta_0)R_E$$

For a finite r_o , $\frac{R_C}{r_o + R_C + R_E} < 1$.


Hence, a finite r_o will reduce the R_i when compared to the R_i when $r_o \rightarrow \infty$.

For a CE without degeneration, $R_i = \frac{v_i}{i_i} = r_\pi = \frac{\beta_0}{g_m}$.

Thus, a CE with degeneration will increase the R_i .

Normally, the R_i for a CE with emitter degeneration is taken as $r_\pi + (1+\beta_0)R_E$

To determine G_m :

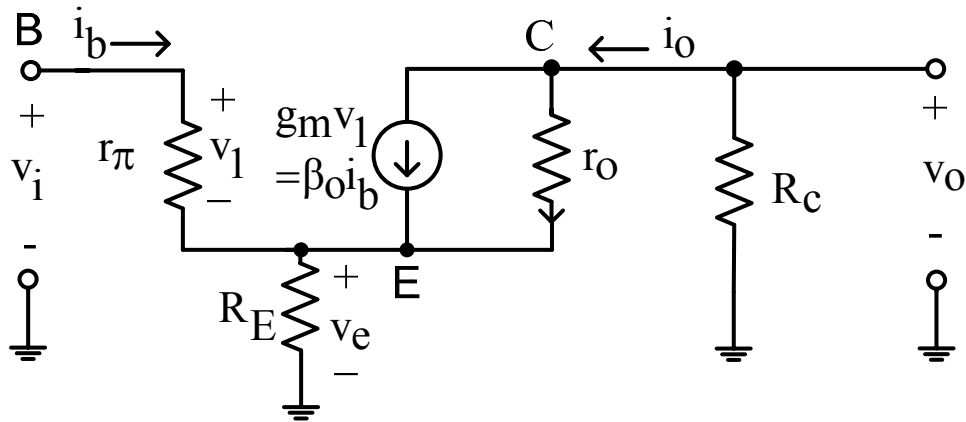

Transconductance,

$$G_m = \left. \frac{i_o}{v_i} \right|_{v_o=0}$$

At node E,

$$i_b + \beta_0 i_b = \frac{v_e}{R_E} + \frac{v_e}{r_o}$$

$$(1 + \beta_0) \frac{v_i - v_e}{r_\pi} = \left(\frac{1}{R_E} + \frac{1}{r_o} \right) v_e$$

$$v_e = \frac{(1 + \beta_0) v_i}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1 + \beta_0)}{r_\pi} \right]}$$


At node C,

$$i_o + \frac{(1+\beta_o)v_i}{r_o} = \beta_o i_b + \frac{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]}{r_o} (1+\beta_o)v_i$$

$$i_o + \frac{(1+\beta_o)v_i}{r_o} = \beta_o i_b + \frac{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]}{r_o} (1+\beta_o)v_i$$

$$= \beta_o \left\{ v_i - \frac{(1+\beta_o)v_i}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} \right\} = \beta_o \left\{ 1 - \frac{(1+\beta_o)}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} \right\} v_i$$
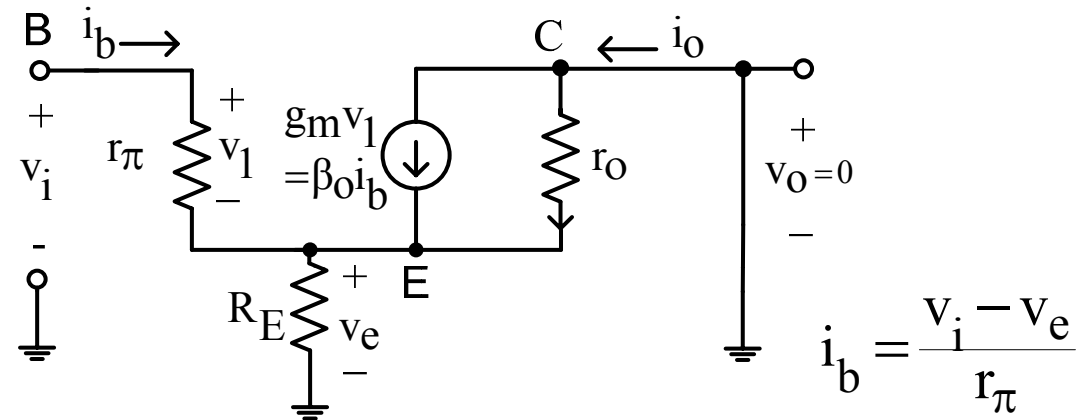
$$v_e = \frac{(1+\beta_o)v_i}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]}$$



$$i_o + \frac{(1+\beta_o)v_i}{r_o} = \beta_o \frac{\left\{ 1 - \frac{(1+\beta_o)}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} \right\} v_i}{r_\pi}$$

$$i_o = \beta_o \frac{\left\{ 1 - \frac{(1+\beta_o)}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} \right\} v_i}{r_\pi} - \frac{(1+\beta_o)v_i}{r_o}$$

$$i_o = \beta_o \left\{ \frac{\left[1 - \frac{(1+\beta_o)}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} \right]}{r_\pi} - \frac{(1+\beta_o)}{r_o \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} \right\} v_i$$

$$G_m = \frac{i_o}{v_i} = \beta_o \left\{ \frac{\left[1 - \frac{(1+\beta_o)}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} \right]}{r_\pi} - \frac{(1+\beta_o)}{r_o \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} \right\} \rightarrow \text{enough}$$


$$G_m = \frac{g_m \left[1 - \frac{R_E}{r_o \beta_o} \right]}{1 + g_m R_E \left(1 + \frac{1}{g_m r_o} + \frac{1}{\beta_o} \right)}$$

Practically, $\beta_o \gg 1$, $r_o \gg R_E$ and $g_m r_o \gg 1$

$$G_m = \frac{g_m}{1 + g_m R_E}$$

This expression is often used to calculate the transconductance of the CE with emitter degeneration amplifier. Practically, $G_{m_CE_emitter\ degen} < G_{m_CE}$ as $G_{m_CE} = g_m$.

To determine R_o :

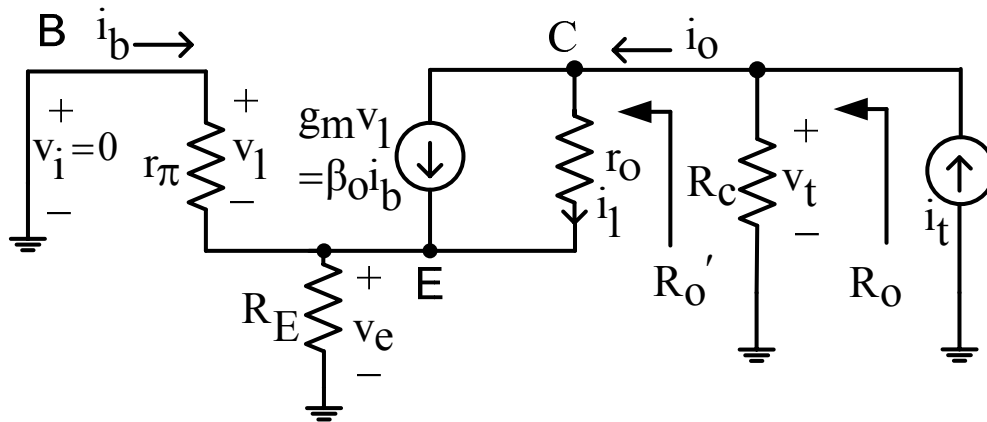

$$R_o = \left. \frac{v_t}{i_t} \right|_{v_i=0} = R_c // R_o'$$

$$v_1 = -v_e$$

$$v_1 = -i_o (r_\pi // R_E)$$

$$i_1 = i_o - g_m v_1 = i_o + g_m [i_o (r_\pi // R_E)]$$

$$-v_t + i_1 r_o + v_e = 0, \quad \therefore -v_t + i_1 r_o - v_1 = 0$$

$$-v_t + [1 + g_m (r_\pi // R_E)] i_o r_o + i_o (r_\pi // R_E) = 0$$

$$R_o' = \frac{v_t}{i_o} = [1 + g_m (r_\pi // R_E)] r_o + (r_\pi // R_E)$$

$$\therefore R_o = R_c // R_o' = R_c // \{ [1 + g_m (r_\pi // R_E)] r_o + (r_\pi // R_E) \} \rightarrow \text{enough}$$

$$R_o' = \frac{V_t}{i_t} = [1 + g_m(r_\pi // R_E)] r_o + (r_\pi // R_E)$$

$$(r_\pi // R_E) \ll [1 + g_m(r_\pi // R_E)] r_o$$

$$R_o' = [1 + g_m(r_\pi // R_E)] r_o = \left[1 + g_m \frac{r_\pi R_E}{r_\pi + R_E} \right] r_o$$

$$R_o' = \left[1 + \frac{g_m R_E}{\frac{1}{r_\pi} (r_\pi + R_E)} \right] r_o = \left[1 + \frac{g_m R_E}{1 + \frac{R_E}{r_\pi}} \right] r_o = \left[1 + \frac{g_m R_E}{1 + \frac{g_m R_E}{\beta_o}} \right] r_o$$

$$\text{If } g_m R_E \ll \beta_o, R_o' = [1 + g_m R_E] r_o$$

$$R_o = R_c // [1 + g_m R_E] r_o$$

$$\text{If } g_m R_E \gg \beta_o, R_o' = \left[1 + \frac{g_m R_E}{\frac{g_m R_E}{\beta_o}} \right] r_o = [1 + \beta_o] r_o$$

$$R_o' = \left[1 + \frac{g_m R_E}{\frac{g_m R_E}{\beta_o}} \right] r_o = [1 + \beta_o] r_o$$

$$R_{o_CE} = R_c // r_o. R_{o_CE_degen} > R_{o_CE}$$

CS with Source Degeneration






CS with S degeneration is not as typically implemented as the CE with E degeneration. The reasons are:

1. The transconductance of the MOS is far less than the transconductance of the BJT. When implementing S degeneration, the transconductance of the MOS will be reduced. This condition is undesired.
2. With E degeneration, R_i in CE is increased. However, $R_i \rightarrow \infty$ in the case of CS even without degeneration. Hence, the need for the degeneration circuit is not crucial.

CS with S degeneration is sometimes implemented to increase the R_o of the MOS.

CS with Source Degeneration

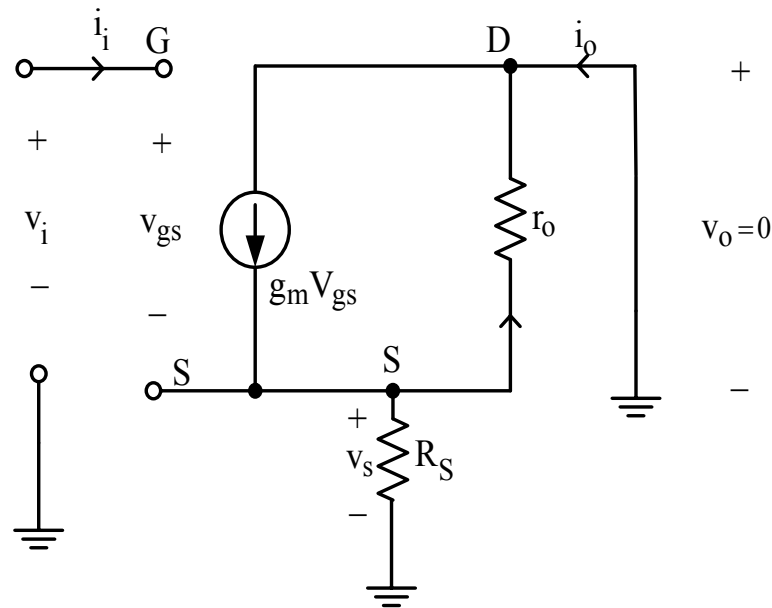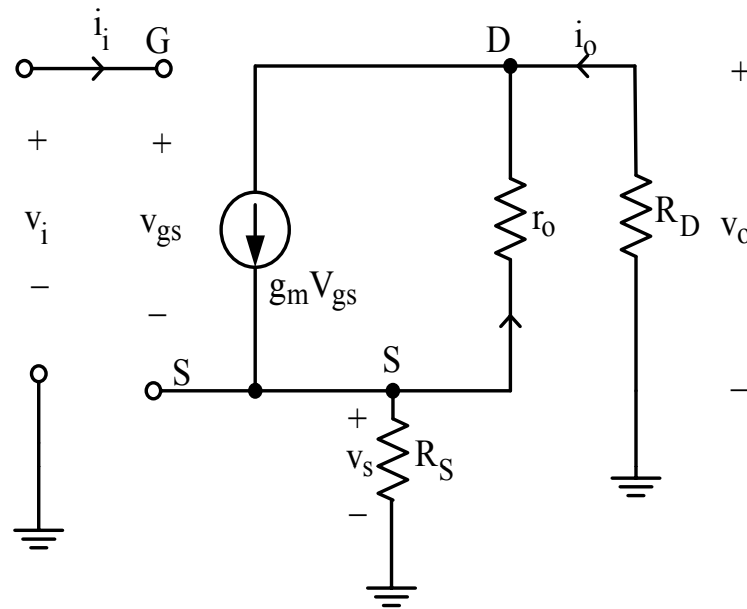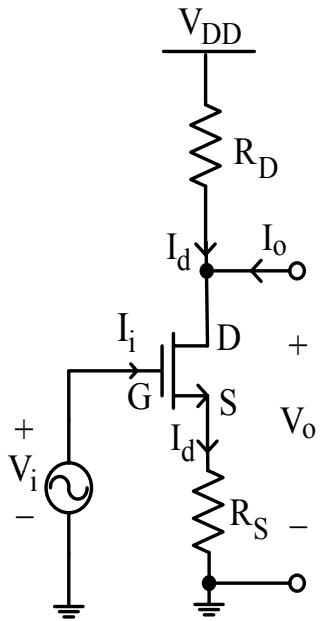

$$R_i = \frac{v_i}{i_i} = \infty$$

$$G_m = \left. \frac{i_o}{v_i} \right|_{v_o=0}$$

KCL at S when $v_o = 0$:

$$g_m v_{gs} = \frac{v_s}{r_o} + \frac{v_s}{R_s}$$

$$g_m (v_i - v_s) = \frac{v_s}{r_o} + \frac{v_s}{R_s}$$

$$g_m v_i = \frac{v_s}{r_o} + \frac{v_s}{R_s} + g_m v_s$$

$$g_m v_i = v_s \left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right)$$

$$g_m V_i = V_s \left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right)$$


$$V_s = \frac{g_m V_i}{\left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right)}$$

$$G_m = \frac{i_o}{V_i} \Big|_{v_o=0}$$

KCL at D when $v_o = 0$:

$$g_m V_{gs} = \frac{V_s}{r_o} + i_o$$

$$V_{gs} = V_i - V_s$$

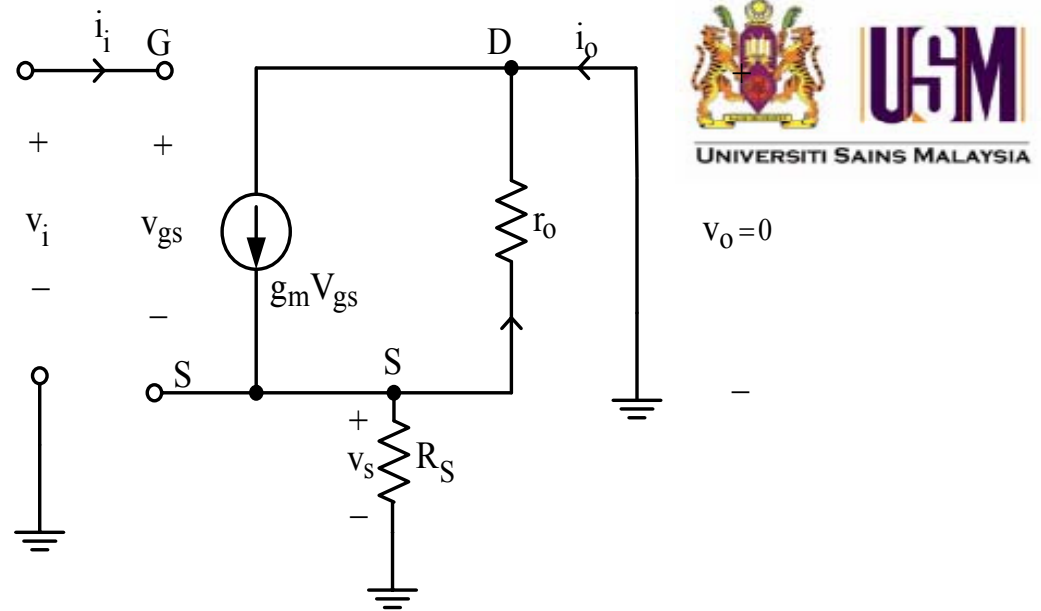

Therefore,

$$g_m \left\{ V_i - \left[\frac{g_m V_i}{\left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right)} \right] \right\} = \left[\frac{g_m V_i}{\left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right)} \right] + i_o$$

$$g_m \left\{ v_i - \left[\frac{g_m v_i}{\left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right)} \right] \right\} = \left[\frac{g_m v_i}{\left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right)} \right] + i_o$$

$$g_m \left\{ v_i - \left[\frac{g_m v_i}{\left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right)} \right] \right\} - \left[\frac{g_m v_i}{\left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right)} \right] = i_o$$

$$i_o = v_i \left\{ g_m \left\{ 1 - \left[\frac{g_m}{\left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right)} \right] \right\} - \frac{g_m}{r_o \left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right)} \right\}$$

$$i_o = v_i \left\{ g_m \left\{ 1 - \left[\frac{g_m}{g_m + \frac{1}{r_o} + \frac{1}{R_s}} \right] \right\} - \frac{g_m}{r_o \left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right)} \right\}$$

$$G_m = \frac{i_o}{v_i} = \left\{ \frac{g_m \left\{ \frac{g_m + \frac{1}{r_o} + \frac{1}{R_s}}{g_m + \frac{1}{r_o} + \frac{1}{R_s}} - \left[\frac{g_m}{g_m + \frac{1}{r_o} + \frac{1}{R_s}} \right] \right\}}{- \frac{g_m}{r_o \left(g_m + \frac{1}{r_o} + \frac{1}{R_s} \right)}} \right\}$$

$$G_m = \left\{ g_m \left\{ \frac{g_m + \frac{1}{r_o} + \frac{1}{R_s} - g_m - \frac{1}{r_o}}{g_m + \frac{1}{r_o} + \frac{1}{R_s}} \right\} \right\}$$

$$G_m = \left\{ g_m \left[\frac{\frac{1}{R_s}}{g_m + \frac{1}{r_o} + \frac{1}{R_s}} \right] \right\} = \frac{g_m}{R_s g_m + \frac{R_s}{r_o} + 1}$$

$$G_m = \frac{g_m}{R_s g_m + \frac{R_s}{r_o} + 1}$$

If $r_o \gg R_s$, $G_m = \frac{g_m}{R_s g_m + 1}$

If R_s is large, $G_m = \frac{g_m}{R_s g_m} = \frac{1}{R_s}$

Without S degeneration, $G_m = g_m$. This shows that with source degeneration, G_m has reduced. $G_{m_CS_degen} < G_{m_CS}$.

$$G_{m_CS_degen} = \frac{1}{R_s} \text{ and } G_{m_CE_degen} = \frac{g_m \left[1 - \frac{R_E}{r_o \beta_o} \right]}{1 + g_m R_E \left(1 + \frac{1}{g_m r_o} + \frac{1}{\beta_o} \right)}$$


If $r_o \gg R_E$, and $R_E \gg 1$, then

$$G_{m_CE_degen} = \frac{g_m [1]}{g_m R_E \left(1 + \frac{1}{\beta_o} \right)} = \frac{1}{R_E \left(1 + \frac{1}{\beta_o} \right)} = \frac{\beta_o}{R_E (1 + \beta_o)}$$

$$G_{m_CS_degen} = \frac{1}{R_S}$$

$$G_{m_CE_degen} = \frac{1}{R_E \left(1 + \frac{1}{\beta_o}\right)} = \frac{\beta_o}{R_E (1 + \beta_o)} \approx \frac{1}{R_E} \quad \text{if } \beta_o \gg 1$$

$$R_o = \left. \frac{v_t}{i_t} \right|_{v_i=0}$$

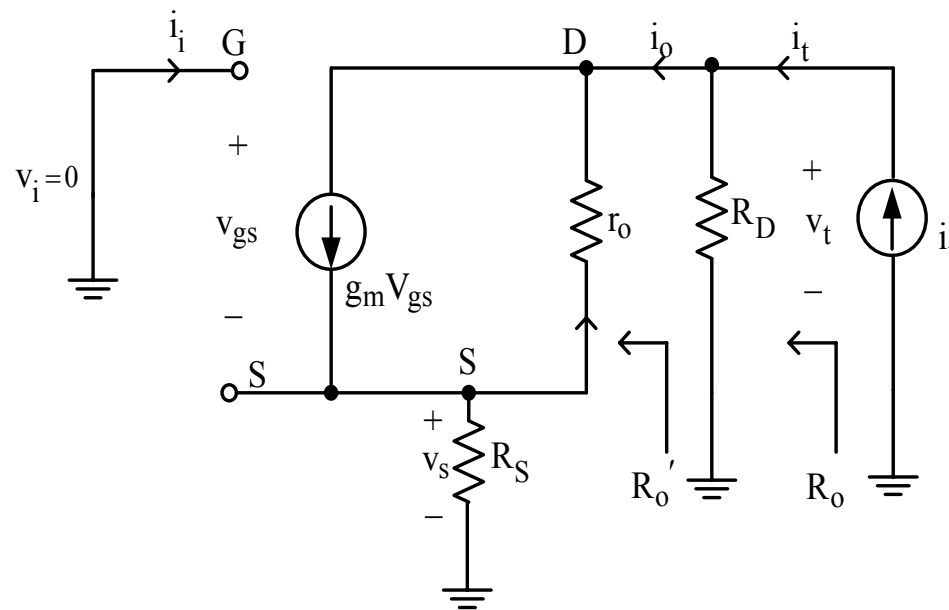

$$R_o = \left. \frac{v_t}{i_t} \right|_{v_i=0}, R_o' = \left. \frac{v_t}{i_o} \right|_{v_i=0}$$

$$v_{gs} = -v_s$$

KCL at node D:

$$i_o = -g_m v_s + \frac{v_t - v_s}{r_o}$$


KCL at node S:

$$g_m v_{gs} + \frac{v_t - v_s}{r_o} = \frac{v_s}{R_s}$$

$$-g_m v_s + \frac{v_t - v_s}{r_o} = \frac{v_s}{R_s}$$

$$\frac{v_s}{R_s} + g_m v_s + \frac{v_s}{r_o} = \frac{v_t}{r_o}$$
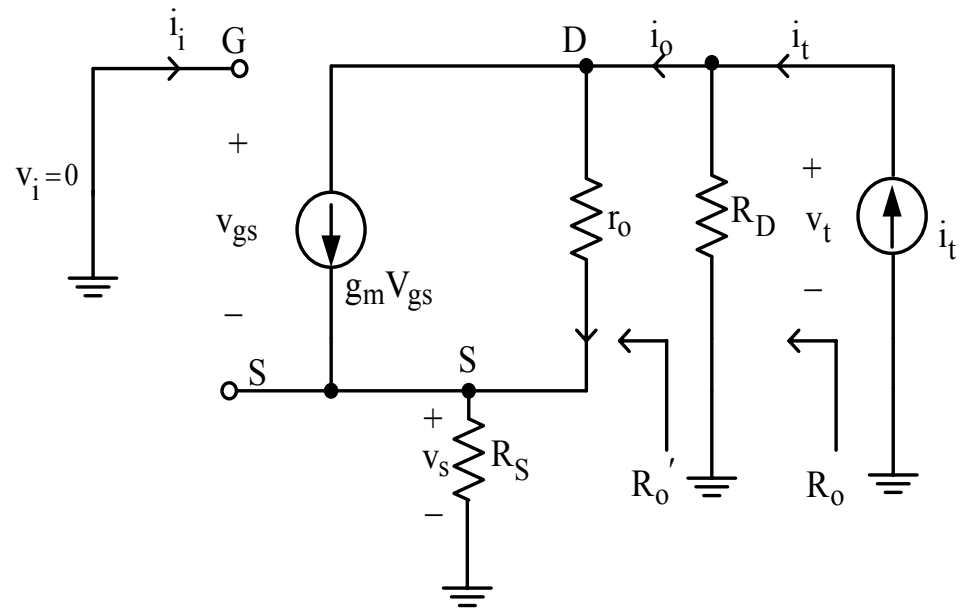
$$v_s = \frac{v_t}{\left(\frac{1}{R_s} + g_m + \frac{1}{r_o} \right) r_o}$$



$$i_o = -g_m v_s - \frac{v_s}{r_o} + \frac{v_t}{r_o}$$

$$= \left[\frac{\left(-g_m - \frac{1}{r_o} \right)}{\left(\frac{1}{R_s} + g_m + \frac{1}{r_o} \right) r_o} + \frac{1}{r_o} \right] v_t$$

$$i_o = -g_m v_s - \frac{v_s}{r_o} + \frac{v_t}{r_o}$$

$$= \left[\frac{\left(-g_m - \frac{1}{r_o}\right)}{\left(\frac{1}{R_s} + g_m + \frac{1}{r_o}\right)r_o} + \frac{1}{r_o} \right] v_t$$

$$R_o' = \frac{v_t}{i_o} = \frac{1}{\left[\frac{\left(-g_m - \frac{1}{r_o}\right)}{\left(\frac{1}{R_s} + g_m + \frac{1}{r_o}\right)r_o} + \frac{1}{r_o} \right]} = \frac{1}{\left[\frac{\left(-g_m - \frac{1}{r_o}\right) + \left(\frac{1}{R_s} + g_m + \frac{1}{r_o}\right)}{\left(\frac{1}{R_s} + g_m + \frac{1}{r_o}\right)r_o} \right]}$$

$$R_o' = \frac{1}{\left[\frac{\frac{1}{R_s}}{\left(\frac{1}{R_s} + g_m + \frac{1}{r_o}\right)r_o} \right]} = \frac{1}{\left[\frac{1}{R_s \left(\frac{1}{R_s} + g_m + \frac{1}{r_o}\right)r_o} \right]} = r_o + r_o R_s g_m + R_s$$

$$R_o' = r_o(1 + R_s g_m) + R_s$$

$$R_o' = r_o(1 + R_s g_m) + R_s$$

If $R_s \uparrow$, R_o' will also \uparrow .

For the CE with E degeneration:

$$R_o' = [1 + \beta_o] r_o.$$

Even though $R_E \rightarrow \infty$, R_o' will be limited to its maximum value of $r_o(1 + \beta_o)$.