

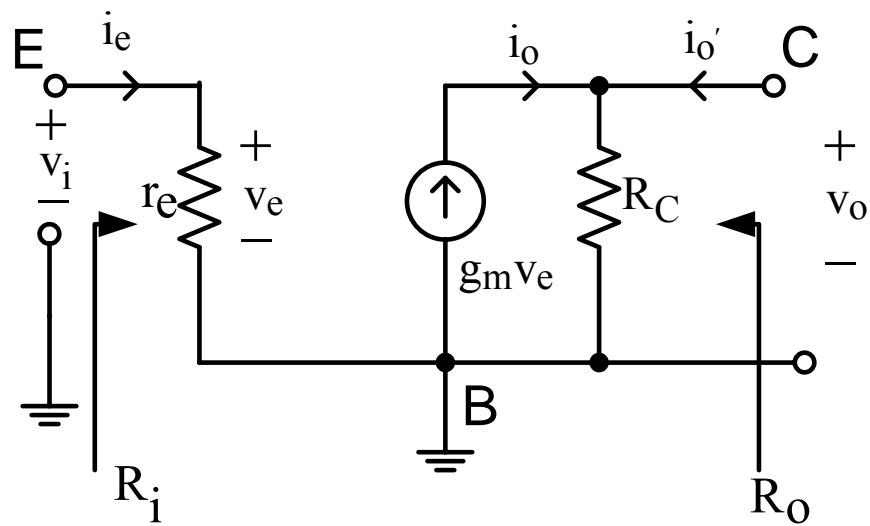
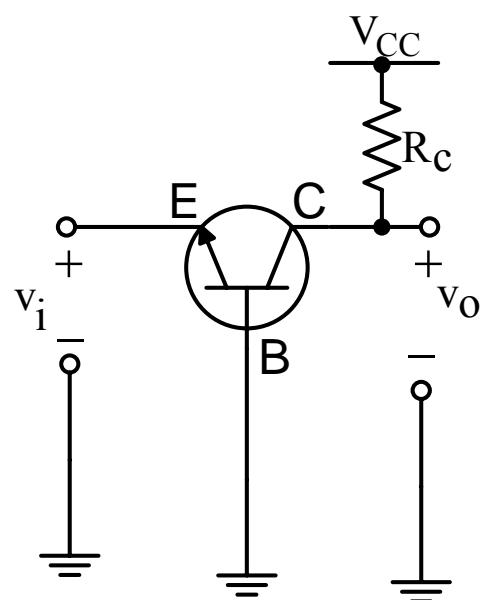


T-model:

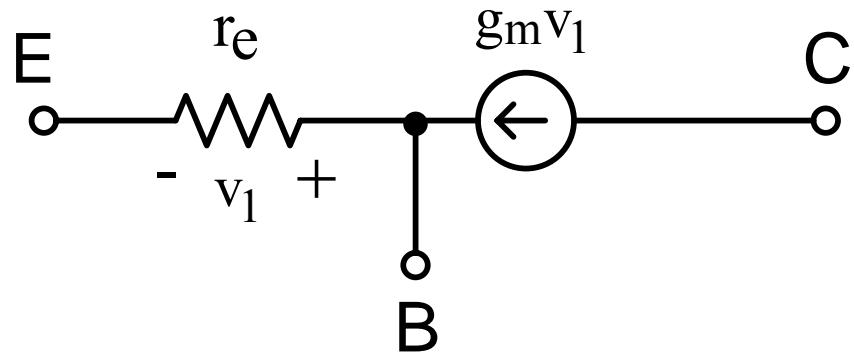

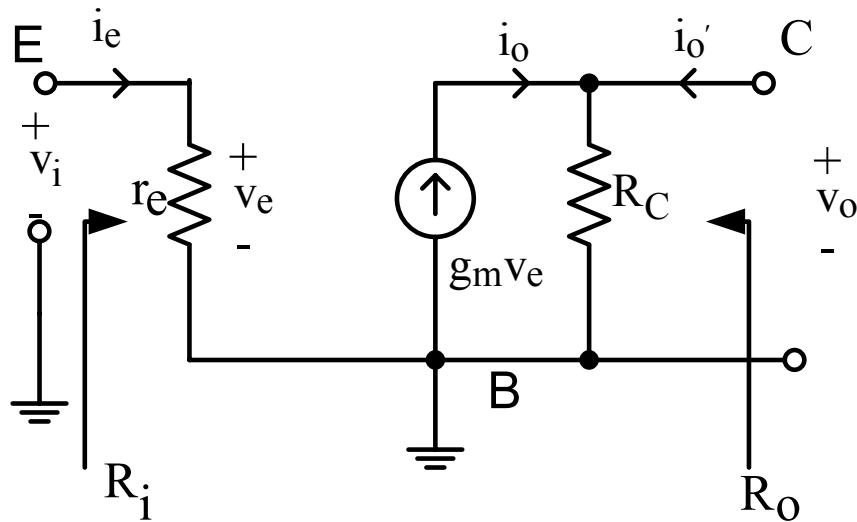

The s/c transconductance:

$$G_m = \frac{i_o}{v_i} \Big|_{v_o=0} = \frac{g_m v_e}{v_e} = g_m$$

The input resistance:

$$R_i = \frac{v_i}{i_e} = \frac{v_e}{i_e} = r_e$$

The output resistance:

$$R_o = \frac{v_o}{i_o'} \Big|_{v_i=0} = R_C$$

o/c or unloaded voltage gain,

$$a_v = \frac{v_o}{v_i} \Big|_{i_o'=0} = \frac{g_m v_e R_C}{v_e} = g_m R_C$$

$$a_i = \frac{i_o}{i_i} \Big|_{v_o=0} = \frac{g_m v_e}{v_e / r_e} = g_m r_e$$

$$a_i = \frac{i_o}{i_i} \Big|_{v_o=0} = \frac{g_m v_e}{v_e / r_e} = g_m r_e$$

Since,  $r_e = \frac{\alpha_o}{g_m}$ , then  $a_i = g_m \frac{\alpha_o}{g_m} \approx 1$

For the CE configuration:  $R_i = r_\pi = \frac{\beta_o}{g_m}$

For the CB configuration:  $R_i = r_e = \frac{\alpha_o}{g_m}$

$$R_{i\_CE} > R_{i\_CB}$$

$$R_{i\_CB} = \frac{\alpha_o}{\beta_o} R_{i\_CE} = \frac{1}{1+\beta_o} R_{i\_CE}$$


$$a_{i\_CB} \approx \alpha_o$$

$$a_{i\_CE} \approx \beta_o$$

$$a_{i\_CB} < a_{i\_CE}$$

$$a_{i\_CB} = \frac{\alpha_o}{\beta_o} a_{i\_CE} = \frac{1}{1+\beta_o} a_{i\_CE}$$

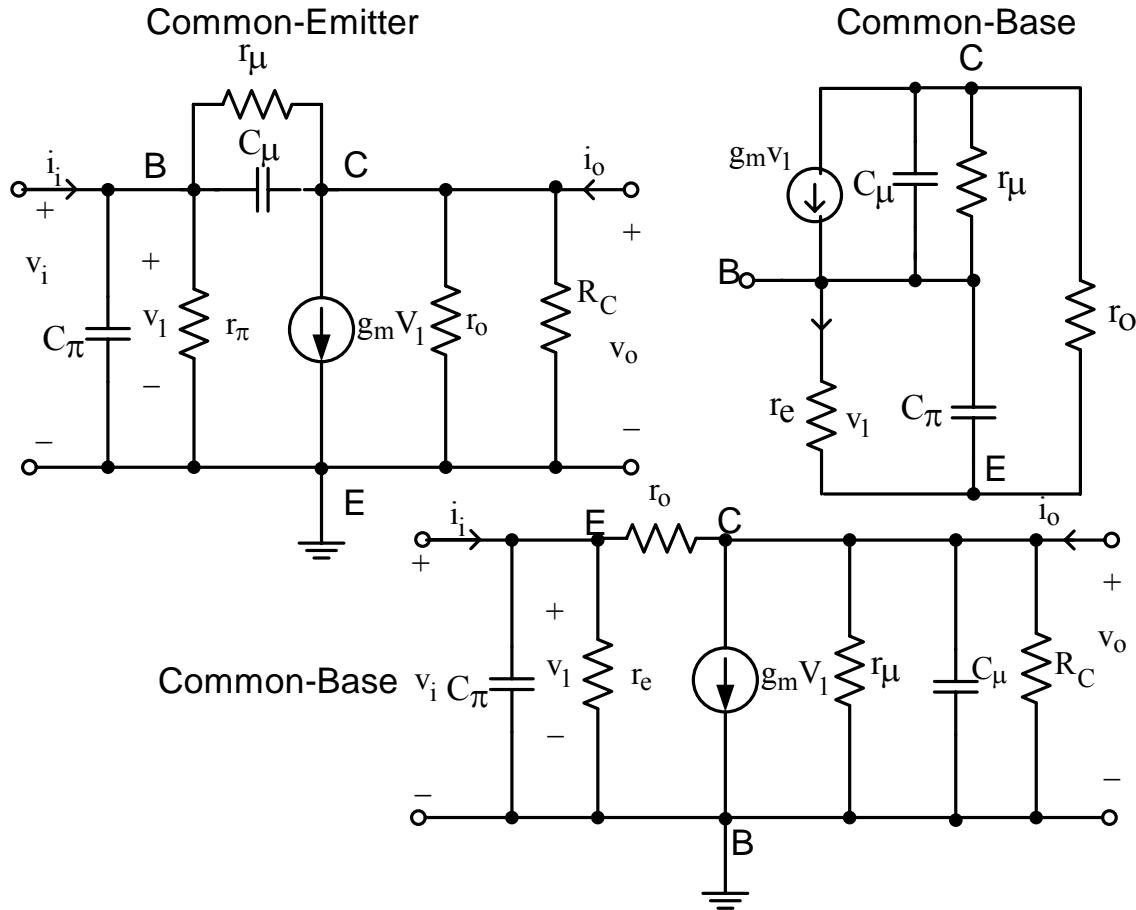In terms of i/p resistance and current gain, the CE amplifier performs better than CB.




$C_\mu$  is between B-C. At high freqs., capacitive components are dominant.

For CE,  $C_\mu$  is between i/p and o/p. Hence, at high-freqs., there will be a feedback from o/p to i/p.

For CB, i/p is at E and o/p is at C. Therefore,  $C_\mu$  will not cause a feedback at high-freqs. CB circuits are used for high-freq. application.

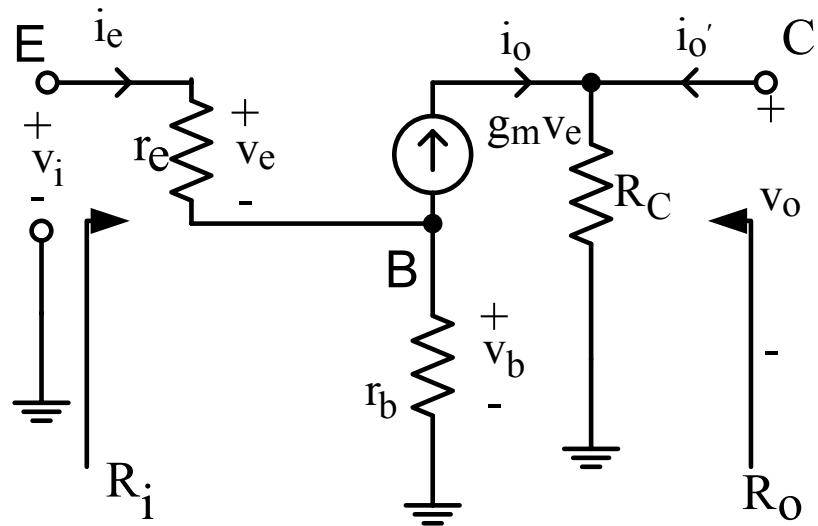Until now we have assumed that  $r_b$  is negligible. In practice,  $r_b$  has a significant effect on  $G_m$  and  $R_i$  when the CB stage is operated at sufficiently high current levels.



The s/c transconductance:

$$G_m = \frac{i_o}{v_i} \Big|_{v_o=0} = \frac{g_m v_e}{v_e + v_b}$$

KCL at B,

$$i_e = i_{rb} + g_m v_e$$

$$\frac{v_e}{r_e} = \frac{v_b}{r_b} + g_m v_e$$

$$v_b = \left( \frac{v_e}{r_e} - g_m v_e \right) r_b$$

$$G_m = \frac{g_m}{1 + \left( \frac{1}{r_e} - g_m \right) r_b}$$


From Equation (3.29),  $r_e = \frac{1}{g_m + \frac{1}{r_\pi}}$

$$\frac{1}{r_e} = g_m + \frac{1}{r_\pi}$$

$$G_m = \frac{g_m}{1 + \left( g_m + \frac{1}{r_\pi} - g_m \right) r_b}$$

$$= \frac{g_m}{1 + \frac{r_b}{r_\pi}}$$

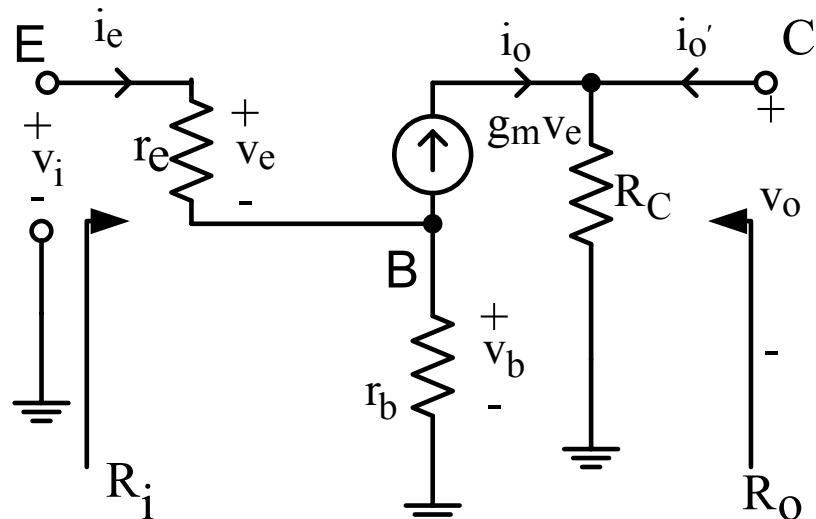Comparing this with the transconductance of the CB circuit if  $r_b$  is neglected (i.e.  $G_m = g_m$ ) shows that  $G_m$  becomes lower when  $r_b$  is included.



The input resistance:

$$R_i = \frac{v_i}{i_e} = \frac{v_b + v_e}{i_e} = \frac{\left( \frac{v_e}{r_e} - g_m v_e \right) r_b + v_e}{i_e} = \frac{\left( \frac{1}{r_e} - g_m \right) r_b + 1}{\frac{1}{r_e}}$$

$$R_i = \frac{v_i}{i_e} = \frac{v_b + v_e}{i_e} = \frac{\left(\frac{v_e}{r_e} - g_m v_e\right) r_b + v_e}{i_e} = \frac{\left(\frac{1}{r_e} - g_m\right) r_b + 1}{\frac{1}{r_e}}$$

$$R_i = \left[ \left( \frac{1}{r_e} - g_m \right) r_b + 1 \right] r_e$$

Since  $\frac{1}{r_e} = g_m + \frac{1}{r_\pi}$  and  $r_e = \frac{\alpha_o}{g_m}$ , then

$$R_i = \left[ \left( g_m + \frac{1}{r_\pi} - g_m \right) r_b + 1 \right] \frac{\alpha_o}{g_m} = \left[ \frac{r_b}{r_\pi} + 1 \right] \frac{\alpha_o}{g_m}$$

Comparing this with the input resistance of the CB circuit if  $r_b$  is neglected (i.e.  $R_i = \frac{\alpha_o}{g_m}$ ) shows that  $R_i$  becomes larger when  $r_b$  is included.

At high current level, i.e.  $I_C \uparrow$ ,  $r_\pi \downarrow$  as  $r_\pi = \frac{\beta_o}{g_m} = \frac{\beta_o V_T}{I_C}$ . So, if  $r_\pi$  is small enough that it is comparable with  $r_b$ , then  $r_b$  should be included in the analysis.

Example: If  $r_b = 100 \Omega$ ,  $\beta_o = 100$  and  $I_C = 26$  mA, then  $r_\pi = \frac{\beta_o}{g_m} = \frac{100 \times 26m}{26m} = 100 \Omega$ . Hence,  $r_\pi = r_b$  when  $I_C$  is high.

In CB configuration,  $R_o = R_C$


In CE configuration,  $R_o = R_C // r_o$


If  $R_C \rightarrow \infty$ ,  $R_{o\_CB} = \infty$  and  $R_{o\_CE} = r_o$

Under this condition,  $R_{o\_CB} > R_{o\_CE}$

Besides using the CB as high freq. amplifier, it can also be used as a current source whose current is nearly independent of the voltage across it (i.e.  $i_o = g_m v_e$ )

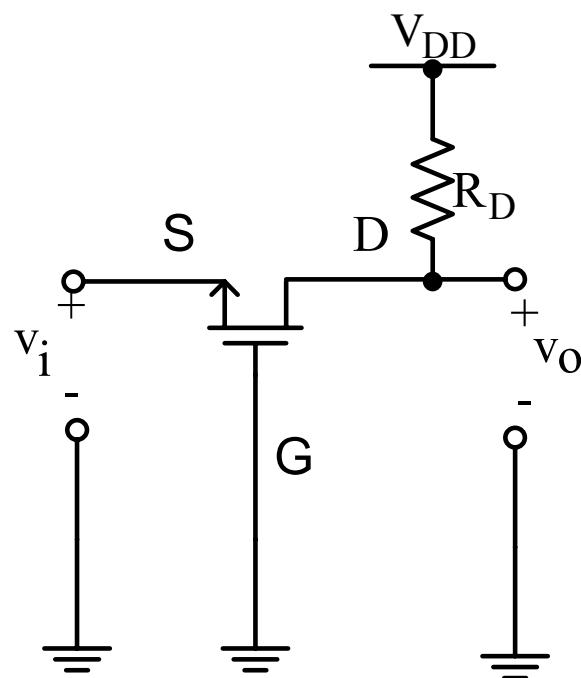
### 3.3.4 Common-gate (CG) configuration.



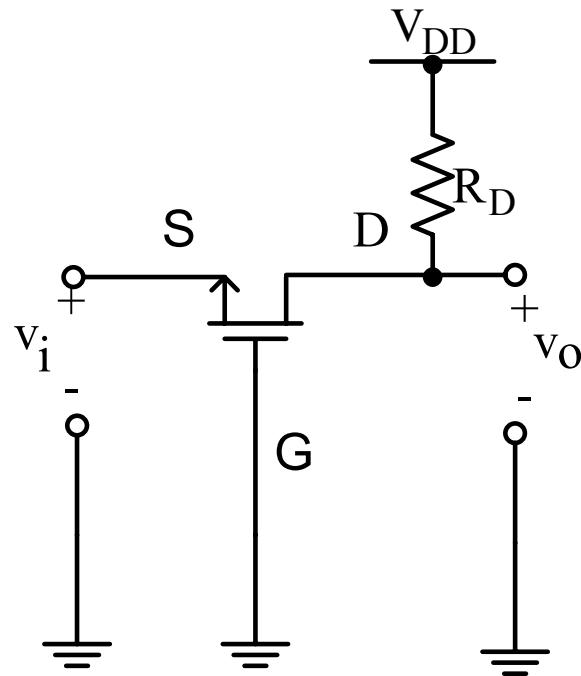

I/p signal is applied to the S. O/p is taken from the D. G is connected to the ac gnd.

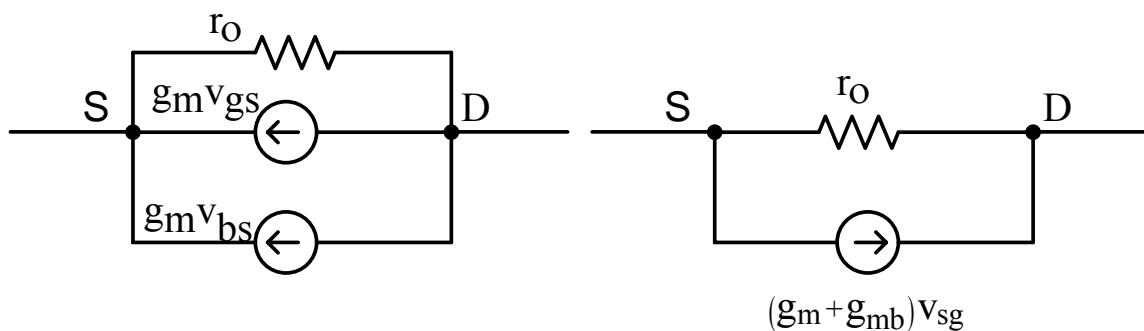The analysis of CG amplifiers can be simplified if the model is changed from a hybrid- $\pi$  to a T-model.



The body (B) is ac gnd,  $v_{bs} = v_{gs}$  because G is also at gnd.

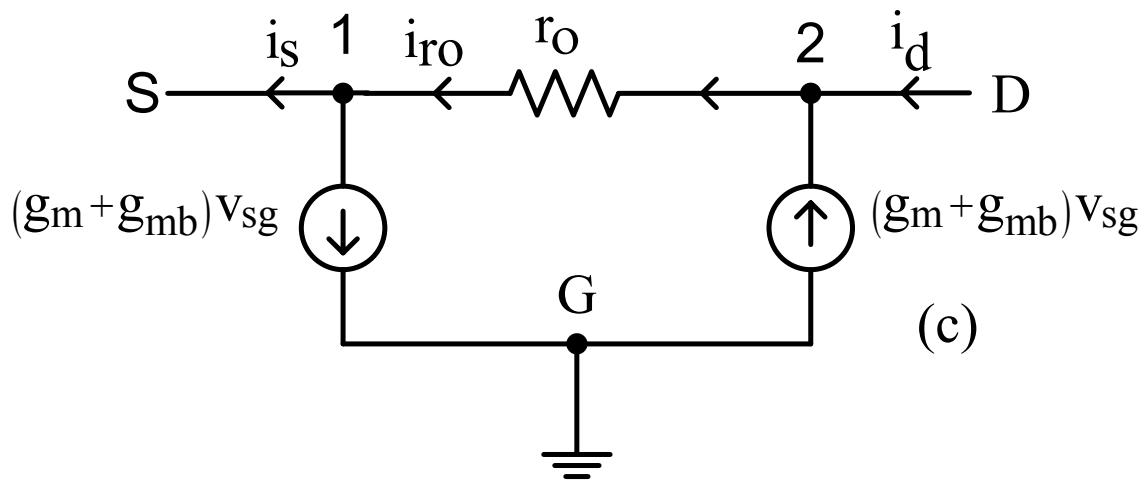
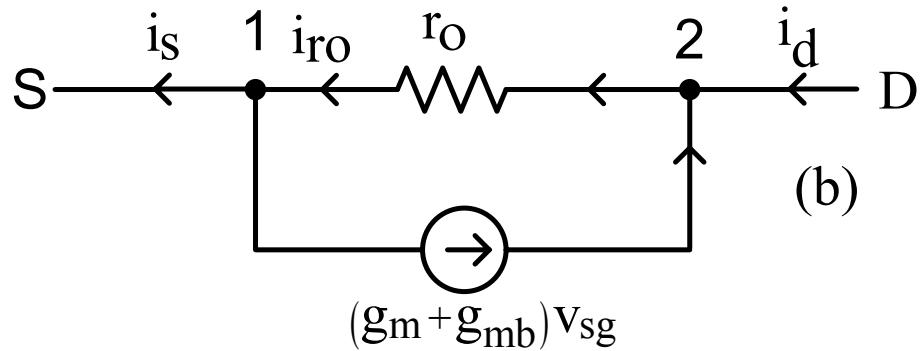


Figure (b):

$$\text{Node 1: } i_{ro} = i_s + (g_m + g_{mb})v_{sg}$$


$$\text{Node 2: } i_d + (g_m + g_{mb})v_{sg} = i_{ro}$$

Figure (c):

$$\text{Node 1: } i_{ro} = i_s + (g_m + g_{mb})v_{sg}$$


$$\text{Node 2: } i_d + (g_m + g_{mb})v_{sg} = i_{ro}$$

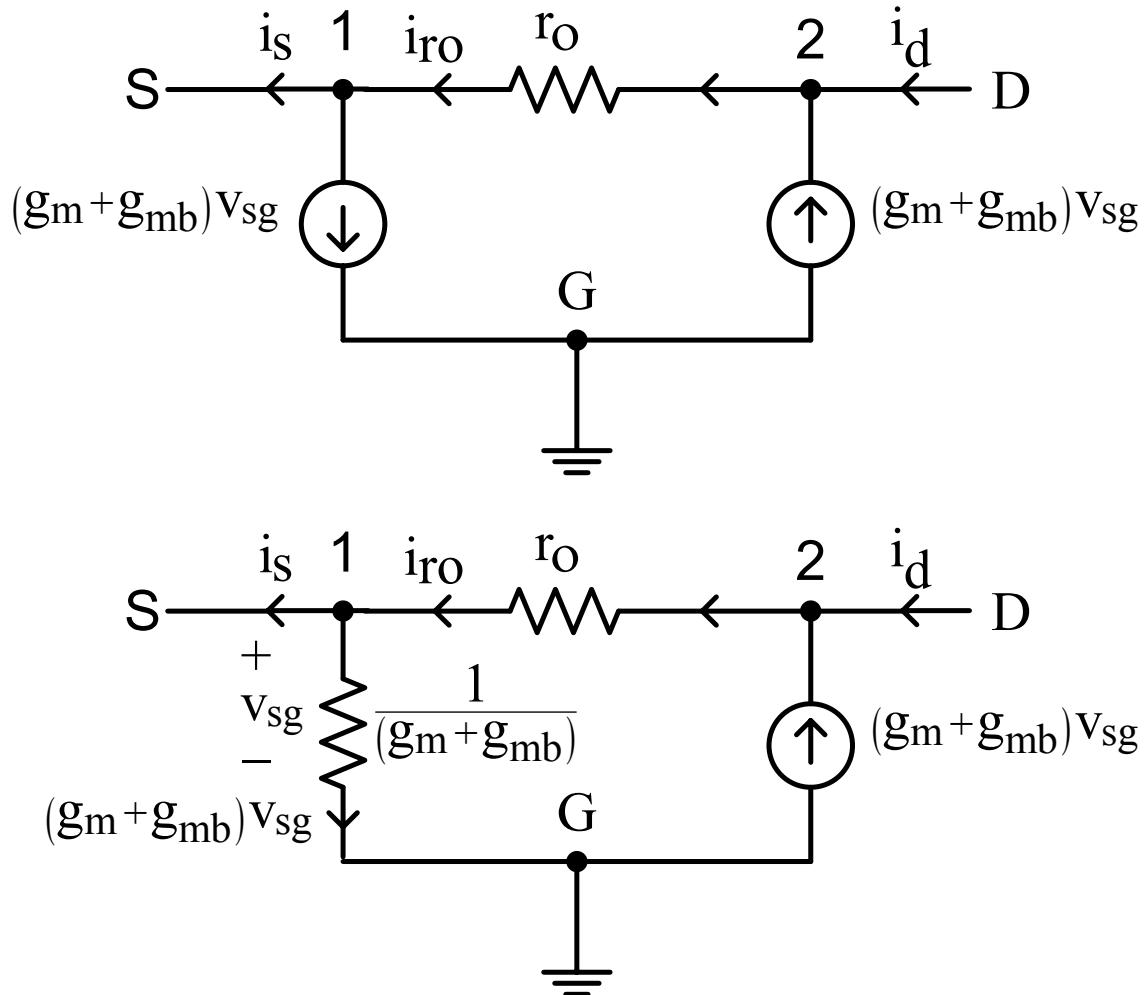
Equal currents are pushed into and pulled out of the  $G$  as the equations that describe the operation of the circuits are identical.



If  $r_o$  is finite, the circuit is bilateral because of the feedback. If  $r_o \rightarrow \infty$ , the cct. is unilateral.

For  $r_o \rightarrow \infty$ :

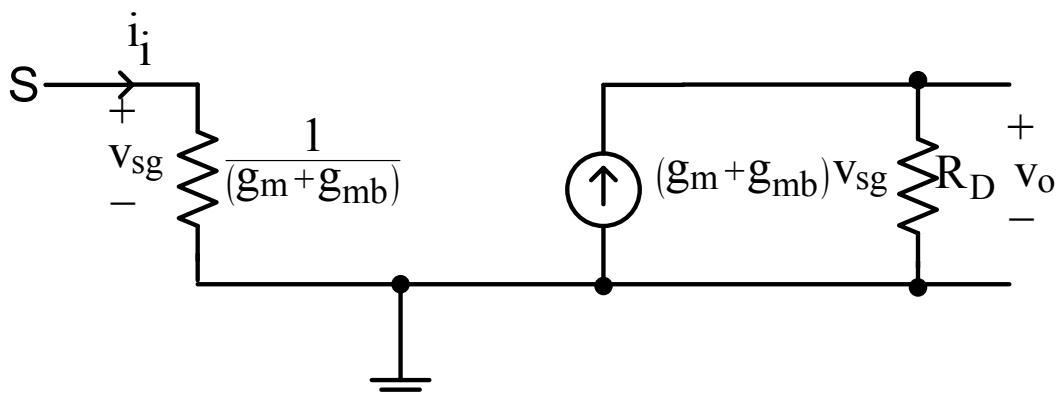

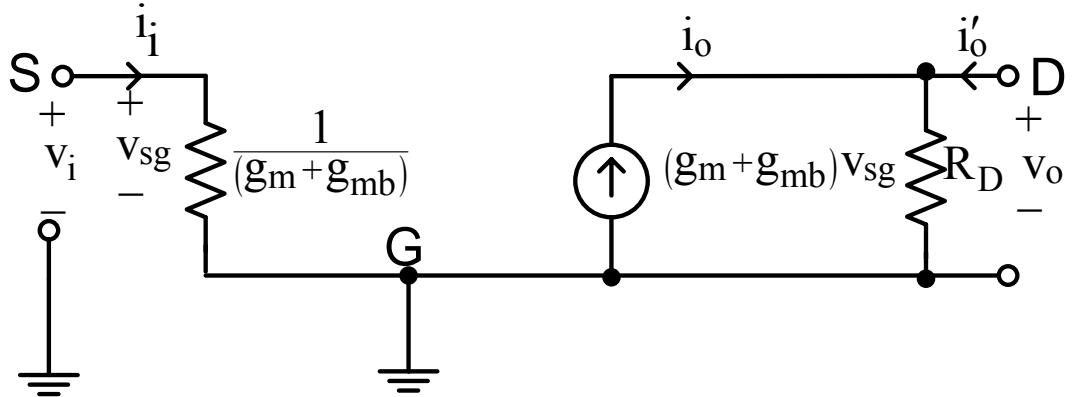

$$G_m = \left. \frac{i_o}{v_i} \right|_{v_o=0} = \frac{(g_m + g_{mb})v_{sg}}{v_{sg}} = g_m + g_{mb}$$



$$R_i = \frac{V_i}{i_i} = \frac{V_{sg}}{i_i} = \frac{1}{g_m + g_{mb}}$$

$$R_o = \left. \frac{v_o}{i_o'} \right|_{v_i=0} = R_D$$


$$a_v = \left. \frac{v_o}{v_i} \right|_{i_o' = 0} = \frac{(g_m + g_{mb})v_{sg}R_d}{v_{sg}} = (g_m + g_{mb})R_d$$

$$\begin{aligned} a_i &= \left. \frac{i_o}{i_i} \right|_{v_o=0} = \frac{(g_m + g_{mb})v_{sg}}{\frac{v_{sg}}{1}} \\ &= (g_m + g_{mb}) \left( \frac{1}{g_m + g_{mb}} \right) \\ &= 1 \end{aligned}$$
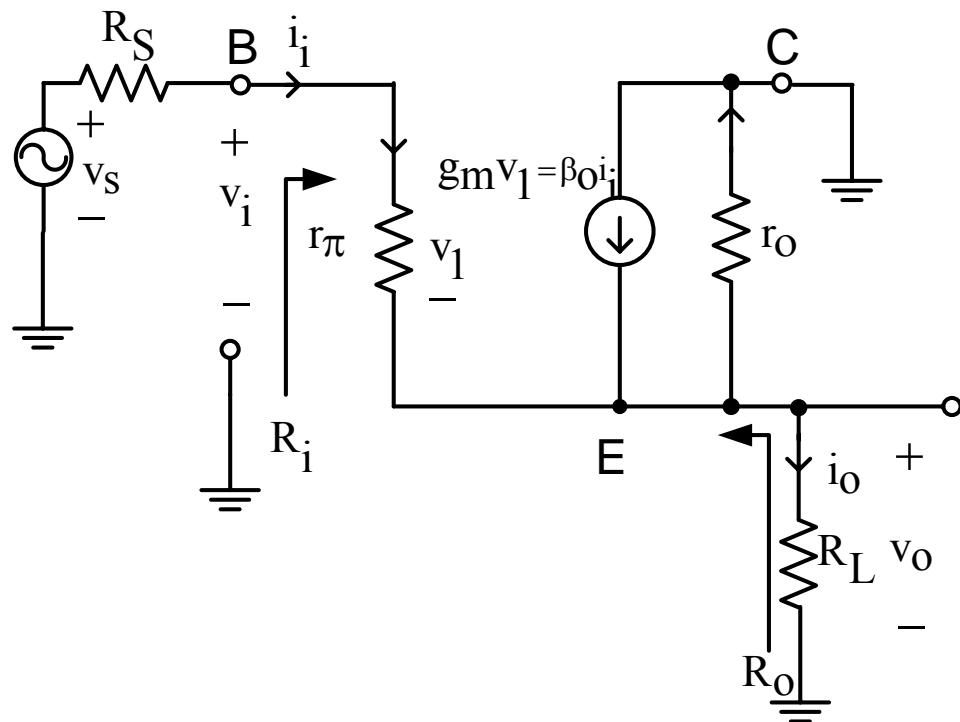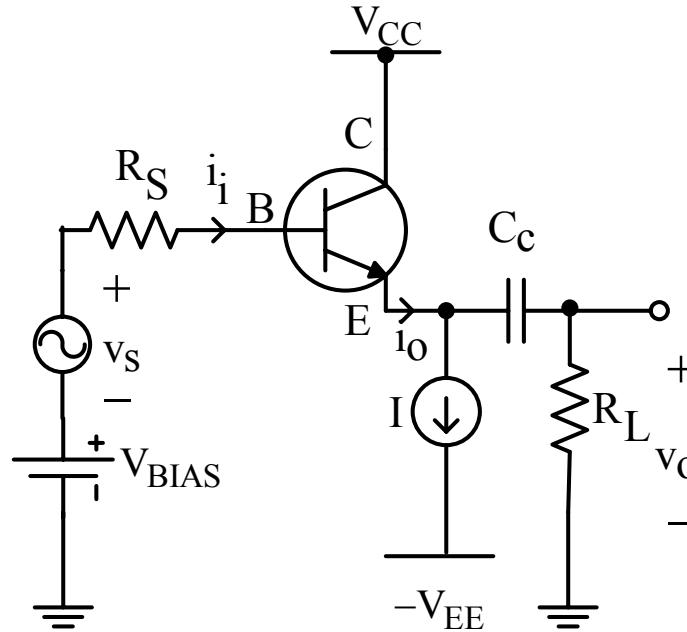
### 3.3.6 Common-collector (CC) configuration (Emitter follower)



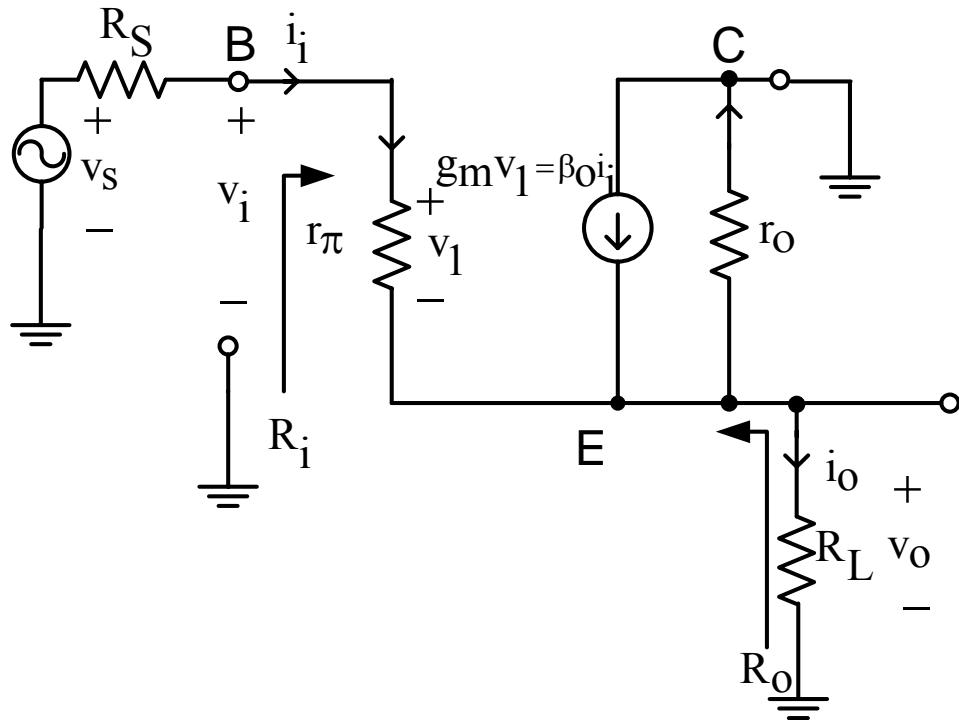I/p signal applied to the B.  
O/p signal taken from the E.



$$v_S = i_i (R_S + r_\pi) + v_o$$

$$v_i = i_i r_\pi + v_o$$


$$R_i = v_i / i_i$$

Hence, this circuit is not unilateral as the input resistance depends on the load resistor  $R_L$  and the output resistance depends on the source resistance  $R_S$ .

To determine  $R_i$ :

$$R_i = v_i / i_i$$
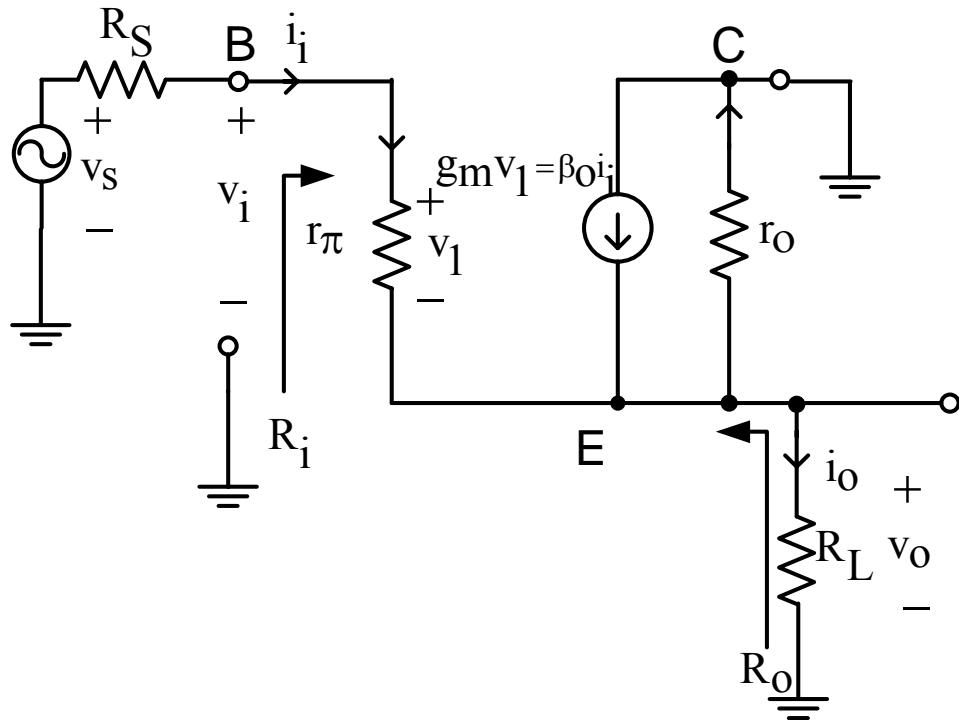
$$i_i + \beta_0 i_i = \frac{v_o}{R_L} + \frac{v_o}{r_o}$$



$$i_i + \beta_o i_i = \frac{v_o}{R_L} + \frac{v_o}{r_o}$$

$$i_i(1+\beta_o) = (v_i - i_i r_\pi) \left( \frac{1}{R_L} + \frac{1}{r_o} \right)$$

$$i_i \left[ 1 + \beta_o + r_\pi \left( \frac{1}{R_L} + \frac{1}{r_o} \right) \right] = v_i \left( \frac{1}{R_L} + \frac{1}{r_o} \right)$$

$$R_i = \frac{v_i}{i_i} = \left[ \frac{1 + \beta_o + r_\pi \left( \frac{1}{R_L} + \frac{1}{r_o} \right)}{\left( \frac{1}{R_L} + \frac{1}{r_o} \right)} \right] \quad \leftarrow \text{enough.}$$


$$R_i = \frac{1 + \beta_o + r_\pi \left( \frac{1}{R_L} + \frac{1}{r_o} \right)}{\left( \frac{1}{R_L} + \frac{1}{r_o} \right)}$$

$$= \frac{1 + \beta_o}{\left( \frac{1}{R_L} + \frac{1}{r_o} \right)} + r_\pi$$


For  $R_i$  with no load, i.e.  $R_i = \frac{V_i}{I_i} \Big|_{R_L=\infty}$ ,

$$R_i = (1 + \beta_o) r_o + r_\pi$$

To determine  $a_v$ :

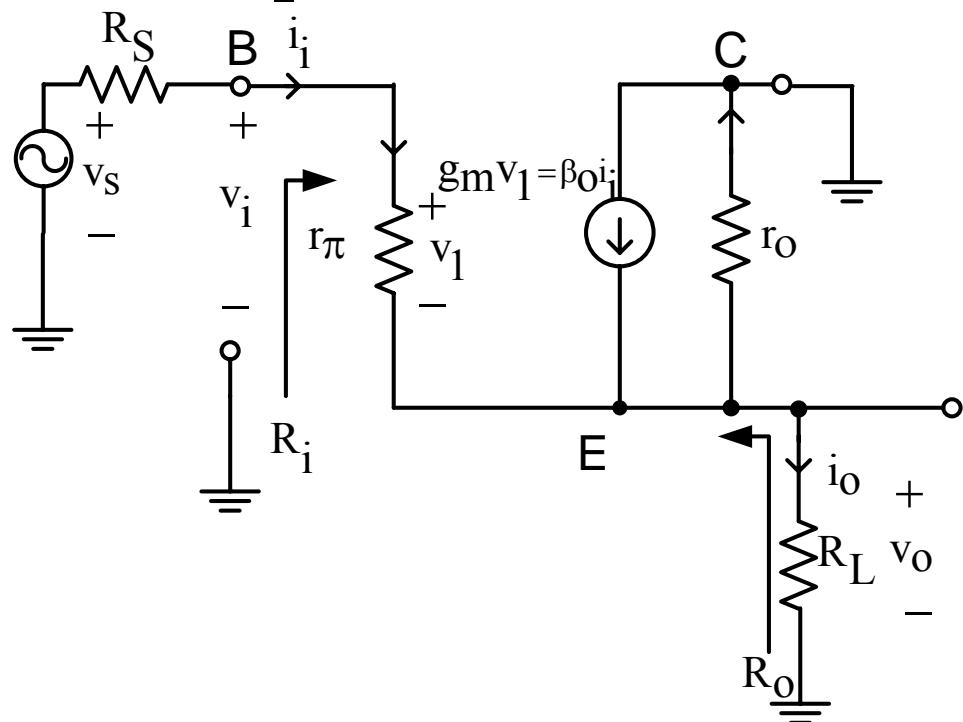

Overall voltage gain:  $a_v = v_o / v_s$

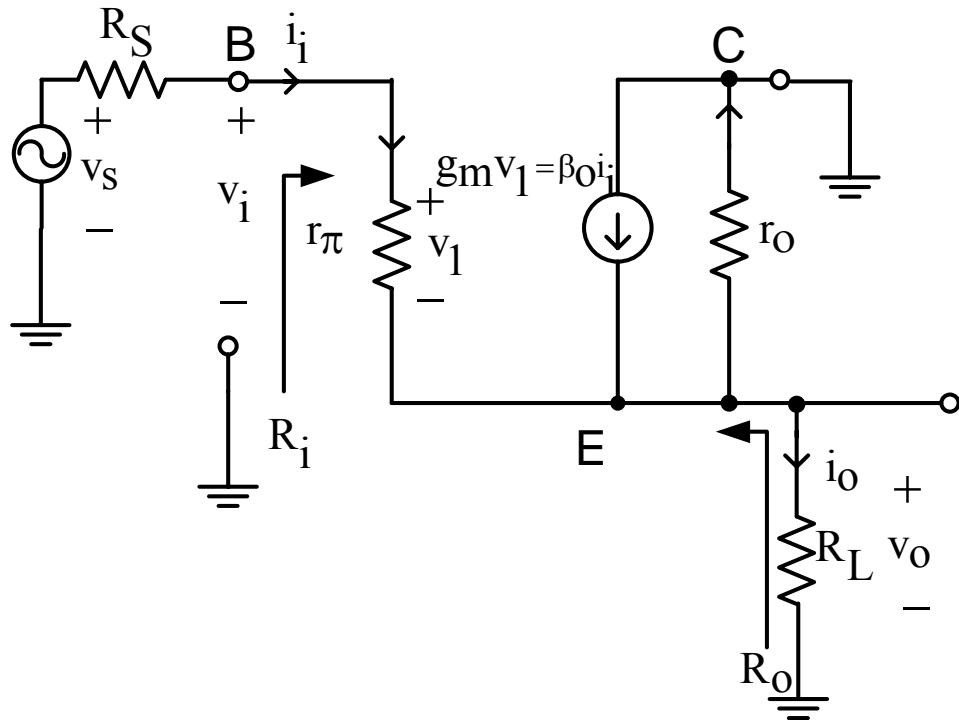

At node E,

$$\frac{v_s - v_o}{R_s + r_\pi} + g_m v_1 = v_o \left( \frac{1}{R_L} + \frac{1}{r_o} \right)$$

$$\frac{v_s}{R_s + r_\pi} + g_m \frac{r_\pi(v_s - v_o)}{R_s + r_\pi} = v_o \left( \frac{1}{R_L} + \frac{1}{r_o} + \frac{1}{R_s + r_\pi} \right)$$

Since  $g_m r_\pi = \beta_o$ ,

$$\frac{v_s}{R_s + r_\pi} + \frac{\beta_o(v_s - v_o)}{R_s + r_\pi} = v_o \left( \frac{1}{R_L} + \frac{1}{r_o} + \frac{1}{R_s + r_\pi} \right)$$

$$v_s \left( \frac{1}{R_s + r_\pi} + \frac{\beta_o}{R_s + r_\pi} \right) = v_o \left( \frac{1}{R_L} + \frac{1}{r_o} + \frac{1}{R_s + r_\pi} + \frac{\beta_o}{R_s + r_\pi} \right)$$

$$\begin{aligned}
a_v &= \frac{V_o}{V_s} = \frac{(1+\beta_o) \left( \frac{1}{R_s + r_\pi} \right)}{\left( \frac{1}{R_L} + \frac{1}{r_o} + \frac{1+\beta_o}{R_s + r_\pi} \right)} \quad \leftarrow \text{enough.} \\
&= \frac{1}{\frac{1}{(1+\beta_o) \left( \frac{1}{R_s + r_\pi} \right)} \left( \frac{1}{R_L} + \frac{1}{r_o} + \frac{1+\beta_o}{R_s + r_\pi} \right)} \\
&= \frac{1}{\left( \frac{R_s + r_\pi}{(1+\beta_o) R_L} + \frac{R_s + r_\pi}{(1+\beta_o) r_o} + 1 \right)} \\
&= \frac{1}{\left( \frac{r_o (R_s + r_\pi) + R_L (R_s + r_\pi)}{(1+\beta_o) R_L r_o} + 1 \right)} \\
&= \frac{1}{\left( \frac{(R_s + r_\pi)(r_o + R_L)}{(1+\beta_o) R_L r_o} + 1 \right)} \\
&= \frac{1}{\left( \frac{(R_s + r_\pi)}{(1+\beta_o) R_L // r_o} + 1 \right)}
\end{aligned}$$

Open-circuit overall voltage gain,

$$a_v = \frac{V_o}{V_s} \Big|_{R_L = \infty} = \frac{1}{\left( \frac{(R_s + r_\pi)}{(1+\beta_o) r_o} + 1 \right)}$$

$$a_v = \frac{1}{\left( \frac{(R_s + r_\pi)}{(1 + \beta_o) R_L // r_o} + 1 \right)}$$


If the B resistance,  $r_b$ , is significant, it can be simply be added to  $R_s$  in the expression. From the  $a_v$  expression,  $a_v$  will always be less than unity.

If  $\beta_o(R_L // r_o) \gg R_s + r_\pi$ , then  $a_v \approx 1$ . This means that the output signal follows the input signal. Hence, this topology is also known as the emitter follower.

If  $r_\pi \gg R_s$ ,  $\beta_o \gg 1$  and  $r_o \gg R_L$ , then

$$a_v = \frac{1}{\left( \frac{r_\pi}{(\beta_o) R_L} + 1 \right)}$$

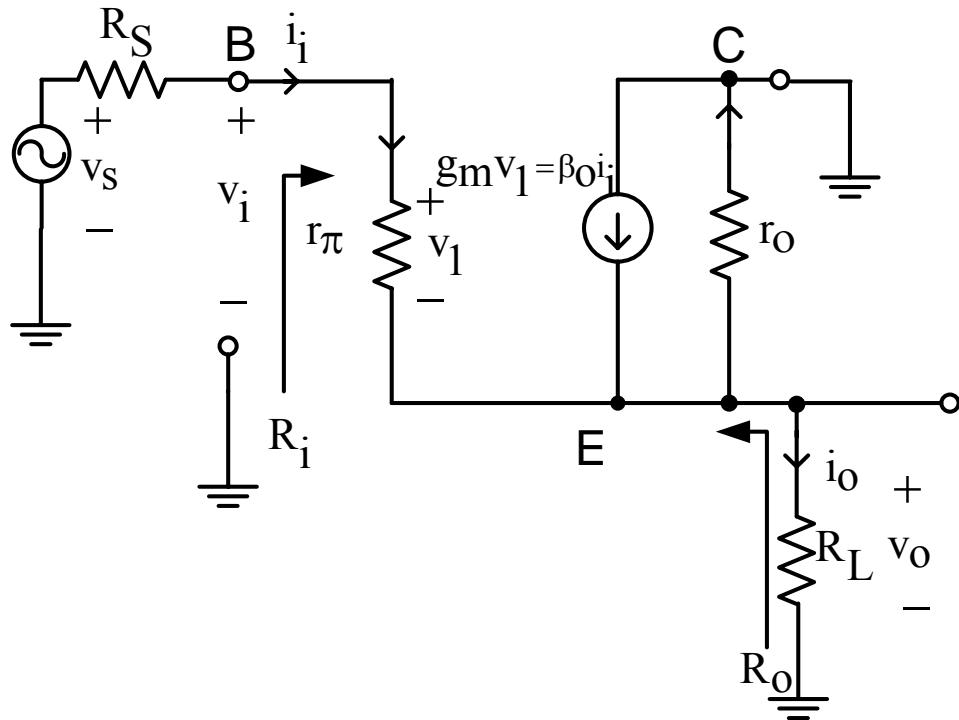Since  $g_m r_\pi = \beta_o$ , then  $a_v = \frac{1}{\left( \frac{1}{g_m R_L} + 1 \right)} = \frac{g_m R_L}{(1 + g_m R_L)}$



To determine the short circuit current gain,  $a_i$ :

$$a_i = \frac{i_o}{i_i} \Big|_{v_o=0}$$

$$i_o = i_i + g_m v_1$$

$$v_1 = i_i r_\pi$$

$$i_o = i_i + g_m i_i r_\pi$$

$$a_i = \frac{i_o}{i_i} = \frac{i_i (1 + g_m r_\pi)}{i_i} = 1 + g_m r_\pi = 1 + \beta_o$$

or

$$g_m v_1 = g_m i_i r_\pi = \beta_o i_i$$

$$i_o = i_i + \beta_o i_i = i_i (1 + \beta_o)$$

$$a_i = i_o / i_i = 1 + \beta_o$$