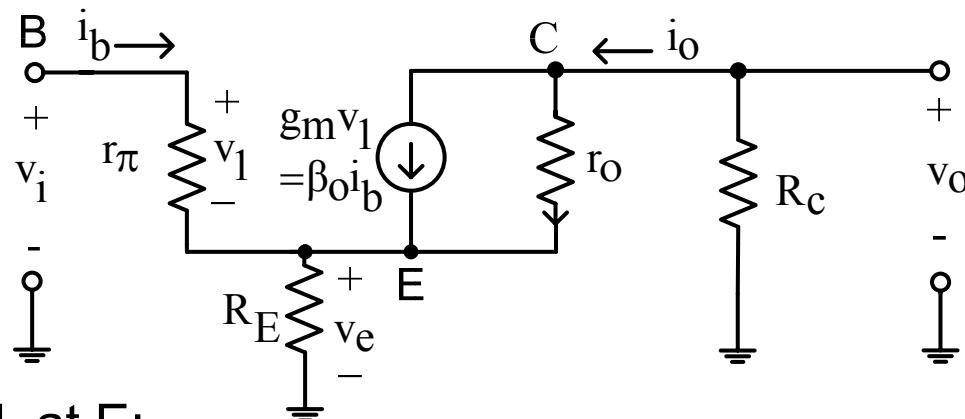




EEE 241
ANALOG ELECTRONICS 1
Lecture 16

DR NORLAILI MOHD NOH

CE with Emitter Degeneration




KCL at E:


$$i_b + \beta_o i_b + \frac{v_o - v_e}{r_o} = \frac{v_e}{R_E}$$

$$(1 + \beta_o) i_b = \frac{v_e}{R_E} - \frac{-i_o R_C - v_e}{r_o} = \frac{v_e}{R_E} + \frac{i_o R_C + v_e}{r_o}$$

$$(1 + \beta_o) i_b = \frac{v_e}{R_E} + \frac{v_e}{r_o} + \frac{i_o R_C}{r_o}$$
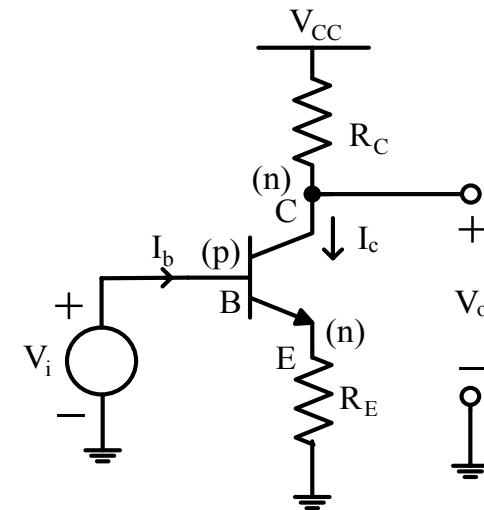
$$i_o = \left[(1 + \beta_o) i_b - \left(\frac{1}{R_E} + \frac{1}{r_o} \right) v_e \right] \frac{r_o}{R_C}$$



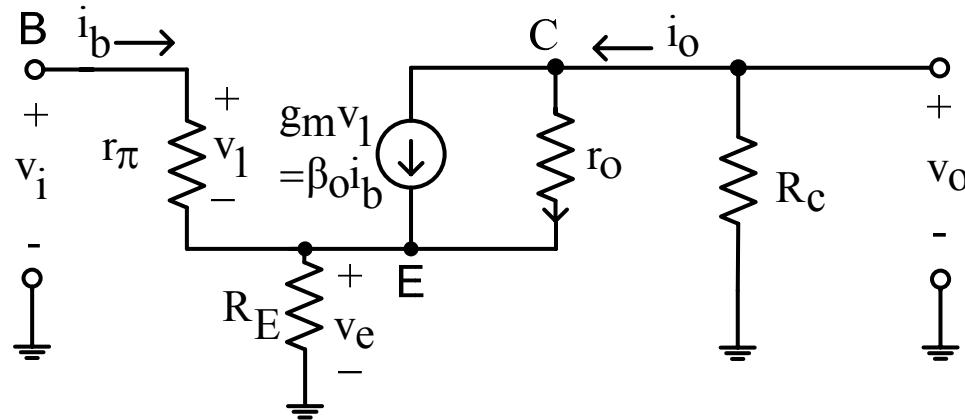


KCL at C:

$$i_o = \beta_o i_b + \frac{v_o - v_e}{r_o} = \beta_o i_b + \frac{-i_o R_C - v_e}{r_o}$$

$$\left[(1 + \beta_o) i_b - \left(\frac{1}{R_E} + \frac{1}{r_o} \right) v_e \right] \frac{r_o}{R_C} = \beta_o i_b + \frac{- \left[(1 + \beta_o) i_b - \left(\frac{1}{R_E} + \frac{1}{r_o} \right) v_e \right] \frac{r_o}{R_C} R_C - v_e}{r_o}$$
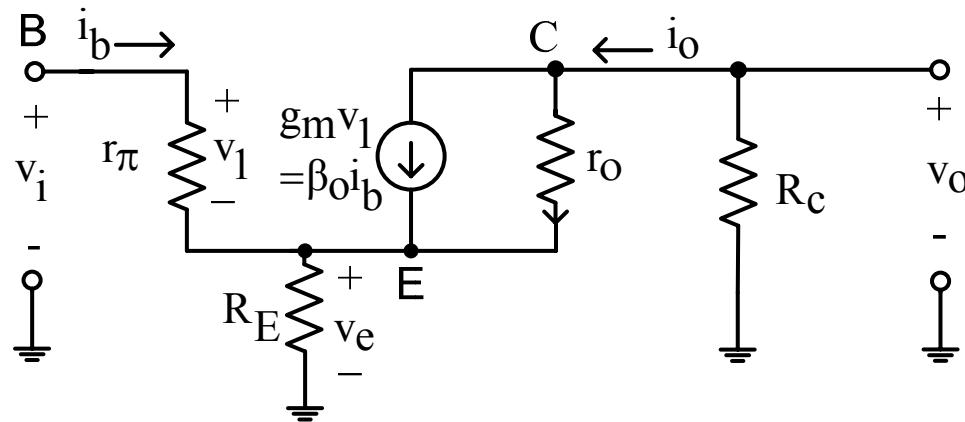
$$v_e = \left[\frac{\frac{(1 + \beta_o) r_o}{R_C} + 1}{\frac{r_o}{R_E R_C} + \frac{1}{R_C} + \frac{1}{R_E}} \right] i_b$$



KVL of the input loop: $-v_i + v_1 + v_e = 0$. Thus, $-v_i + i_b r_\pi + v_e = 0$

$$v_i = r_\pi i_b + \left[\frac{(1+\beta_0) \frac{r_o}{R_C} + 1}{\frac{r_o}{R_E R_C} + \frac{1}{R_C} + \frac{1}{R_E}} \right] i_b$$

$$R_i = \frac{v_i}{i_b} = r_\pi + \left[\frac{(1+\beta_0) \frac{r_o}{R_C} + 1}{\frac{r_o}{R_E R_C} + \frac{1}{R_C} + \frac{1}{R_E}} \right] \leftarrow \text{enough}$$

$$R_i = r_\pi + \frac{R_E R_C \left[1 + (1+\beta_0) \frac{r_o}{R_C} \right]}{r_o + R_C + R_E} = r_\pi + \frac{(1+\beta_0) R_E \left[\frac{R_C}{(1+\beta_0)} + r_o \right]}{r_o + R_C + R_E}$$

$$R_i = r_\pi + \frac{(1+\beta_o)R_E \left[\frac{R_C}{(1+\beta_o)} + r_o \right]}{r_o + R_C + R_E}$$

If $r_o \gg R_C$ and $r_o \gg R_E$ (in the case of $r_o \rightarrow \infty$), then

$$R_i = r_\pi + \frac{(1+\beta_o)R_E[r_o]}{r_o} = r_\pi + (1+\beta_o)R_E$$


$$\text{For a finite } r_o, \frac{\frac{R_C}{(1+\beta_o)} + r_o}{r_o + R_C + R_E} < 1.$$

Hence, a finite r_o will reduce the R_i when compared to the R_i when $r_o \rightarrow \infty$.

$$\text{For a CE without degeneration, } R_i = \frac{V_i}{I_i} = r_\pi = \frac{\beta_o}{g_m}.$$

Thus, a CE with degeneration will increase the R_i .

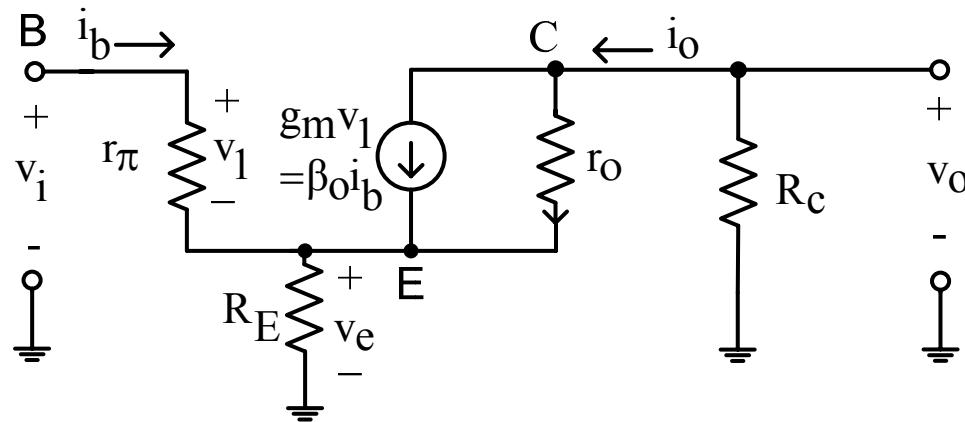Normally, the R_i for a CE with emitter degeneration is taken as $r_\pi + (1+\beta_o)R_E$



Transconductance,


$$G_m = \left. \frac{i_o}{v_i} \right|_{v_o=0}$$

At node E,

$$i_b + \beta_o i_b = \frac{v_e}{R_E} + \frac{v_e}{r_o}$$

$$(1 + \beta_o) \frac{v_i - v_e}{r_\pi} = \left(\frac{1}{R_E} + \frac{1}{r_o} \right) v_e$$
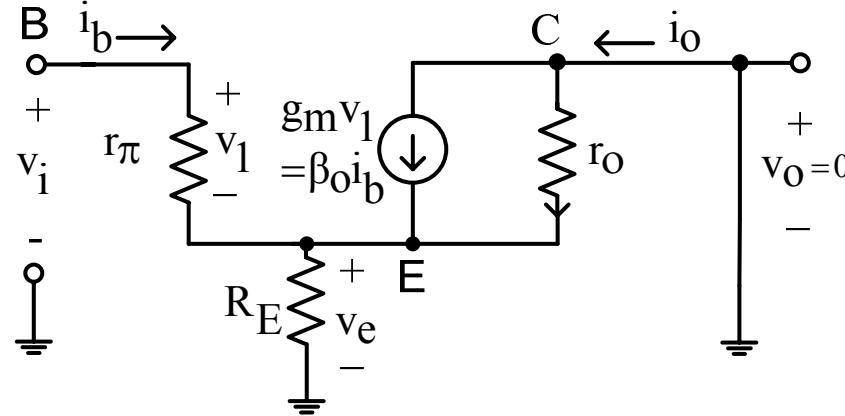
$$v_e = \frac{(1 + \beta_o) v_i}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1 + \beta_o)}{r_\pi} \right]}$$





At node C,

$$i_o + \frac{(1+\beta_o)v_i}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} = \beta_o i_b$$

$$i_o + \frac{(1+\beta_o)v_i}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} =$$
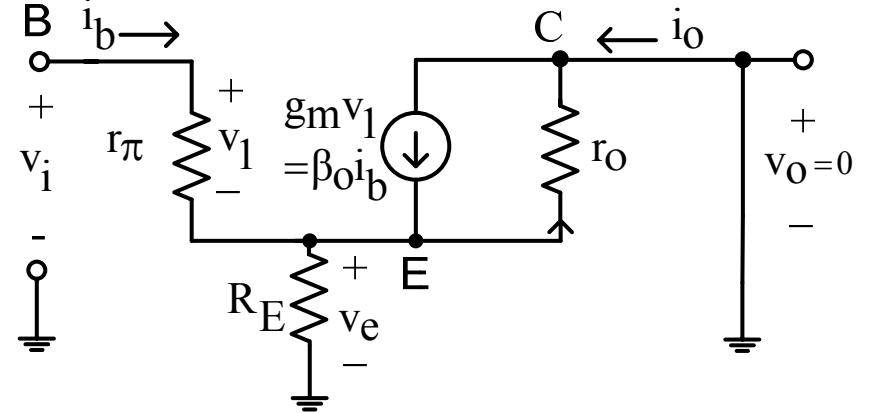
$$= \beta_o \left\{ v_i - \frac{(1+\beta_o)v_i}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} \right\} = \beta_o \frac{\left(1 - \frac{(1+\beta_o)}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} \right) v_i}{r_\pi}$$



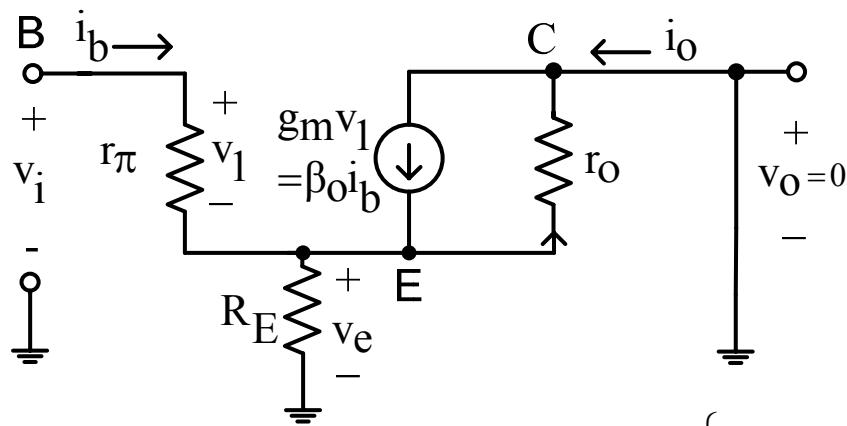

$$i_o + \frac{(1+\beta_o)v_i}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} = \beta_o \frac{\left\{ 1 - \frac{(1+\beta_o)}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} \right\} v_i}{r_\pi}$$

$$G_m = \left. \frac{i_o}{v_i} \right|_{v_o=0}$$

$$i_o + \frac{(1+\beta_o)v_i}{r_o r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} = \beta_o \frac{\left\{ 1 - \frac{(1+\beta_o)}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} \right\} v_i}{r_\pi}$$

$$i_o = \beta_o \frac{\left\{ 1 - \frac{(1+\beta_o)}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} \right\} v_i}{r_\pi} - \frac{(1+\beta_o)v_i}{r_o r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]}$$

$$i_o = \left\{ \beta_o \frac{\left\{ 1 - \frac{(1+\beta_o)}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} \right\}}{r_\pi} - \frac{(1+\beta_o)}{r_o r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} \right\} v_i$$

$$\frac{i_o}{v_i} = \left\{ \frac{\beta_o r_o \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right] \left\{ 1 - \frac{(1+\beta_o)}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} \right\}}{r_\pi r_o \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} - \frac{(1+\beta_o)}{r_o r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} \right\}$$

→ enough

$$\frac{\dot{i}_o}{v_i} = \left\{ \frac{\beta_o r_o \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right] (1+\beta_o)}{r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} - \frac{r_\pi r_o \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]}{r_o r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} - \frac{(1+\beta_o)}{r_o r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} \right\}$$

$$\frac{i_o}{v_i} = \left\{ \frac{\left\{ \beta_o r_o \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right] - \frac{\beta_o r_o (1+\beta_o)}{r_\pi} \right\}}{r_\pi r_o \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} - \frac{(1+\beta_o)}{r_o r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]} \right\}$$

$$\frac{i_o}{V_i} = \frac{\beta_o r_o \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right] - \frac{\beta_o r_o (1+\beta_o)}{r_\pi} - (1+\beta_o)}{r_o r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]}$$

$$\frac{i_o}{V_i} = \frac{\beta_o r_o \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right] - \frac{\beta_o r_o (1+\beta_o)}{r_\pi} - (1+\beta_o)}{r_o r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]}$$

$$G_m = \frac{g_m r_\pi r_o \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right] - \frac{\beta_o r_o (1+\beta_o)}{r_\pi} - (1+\beta_o)}{r_o r_\pi \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)}{r_\pi} \right]}$$

$$\begin{aligned}
G_m &= \frac{g_m \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)g_m}{\beta_o} \right] - \frac{g_m(1+\beta_o)g_m}{\beta_o} - \frac{g_m}{r_o\beta_o}(1+\beta_o)}{\left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)g_m}{\beta_o} \right]} \\
&= \frac{g_m \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)g_m}{\beta_o} - \frac{(1+\beta_o)g_m}{\beta_o} - \frac{1}{r_o\beta_o}(1+\beta_o) \right]}{\left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)g_m}{\beta_o} \right]} \\
&= \frac{g_m \left[\frac{1}{R_E} + \frac{1}{r_o} - \frac{(1+\beta_o)}{r_o\beta_o} \right]}{\left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)g_m}{\beta_o} \right]}
\end{aligned}$$

$$\begin{aligned}
 G_m &= \frac{g_m \left[\frac{1}{R_E} + \frac{1}{r_o} - \frac{(1+\beta_o)}{r_o \beta_o} \right]}{\left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)g_m}{\beta_o} \right]} \\
 &= \frac{g_m \left[\frac{r_o \beta_o}{R_E} + \beta_o - (1+\beta_o) \right]}{r_o \beta_o \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)g_m}{\beta_o} \right]} \\
 &= \frac{g_m \left[\frac{r_o \beta_o}{R_E} - 1 \right]}{r_o \beta_o \left[\frac{1}{R_E} + \frac{1}{r_o} + \frac{(1+\beta_o)g_m}{\beta_o} \right]}
 \end{aligned}$$

$$G_m = \frac{g_m \left[\frac{r_o \beta_o}{R_E} - 1 \right]}{\left[\frac{r_o \beta_o}{R_E} + \beta_o + (1 + \beta_o) g_m r_o \right]} = \frac{g_m \left[\frac{r_o \beta_o}{R_E} - 1 \right]}{\frac{1}{R_E} \left[r_o \beta_o + R_E \beta_o + (1 + \beta_o) g_m r_o R_E \right]}$$

$$G_m = \frac{g_m \left[\frac{r_o \beta_o - R_E}{R_E} \right]}{\frac{1}{R_E} \left[r_o \beta_o + R_E \beta_o + (1 + \beta_o) g_m r_o R_E \right]} = \frac{g_m \left[r_o \beta_o - R_E \right]}{\left[r_o \beta_o + R_E \beta_o + (1 + \beta_o) g_m r_o R_E \right]}$$

$$G_m = \frac{g_m \left[r_o \beta_o - R_E \right]}{r_o \beta_o + R_E \beta_o + g_m r_o R_E + \beta_o g_m r_o R_E} = \frac{g_m \left[r_o \beta_o - R_E \right]}{r_o \beta_o \left(1 + \frac{R_E}{r_o} + \frac{g_m R_E}{\beta_o} + g_m R_E \right)}$$


$$G_m = \frac{g_m \left[1 - \frac{R_E}{r_o \beta_o} \right]}{1 + g_m R_E \left(1 + \frac{1}{g_m r_o} + \frac{1}{\beta_o} \right)}$$

$$G_m = \frac{g_m \left[1 - \frac{R_E}{r_o \beta_o} \right]}{1 + g_m R_E \left(1 + \frac{1}{g_m r_o} + \frac{1}{\beta_o} \right)}$$

Practically, $\beta_o \gg 1$, $r_o \gg R_E$ and $g_m r_o \gg 1$

$$G_m = \frac{g_m}{1 + g_m R_E}$$

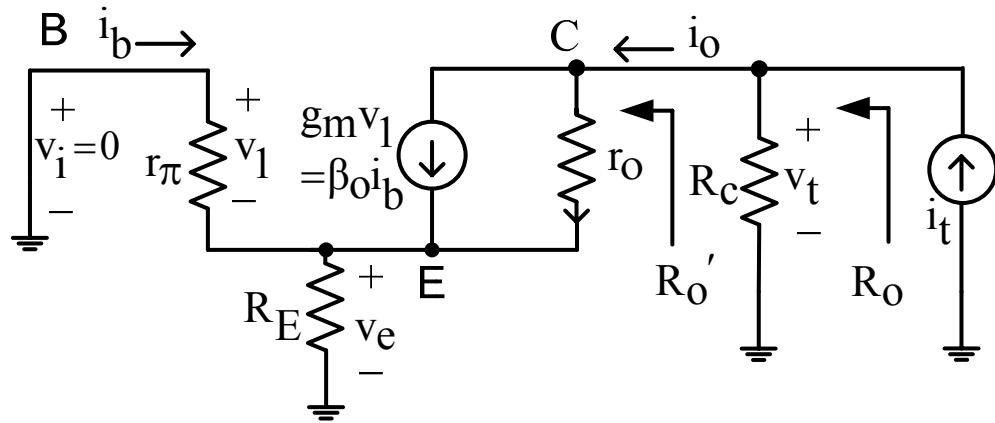This expression is often used to calculate the transconductance of the CE with emitter degeneration amplifier. Practically, $G_{m_CE_emitter\ degen} < G_{m_CE}$ as $G_{m_CE} = g_m$.



$$R_o = \left. \frac{v_t}{i_t} \right|_{v_i=0} = R_c // R_o'$$

$$v_1 = -i_t (r_\pi // R_E)$$

$$i_1 = i_t - g_m v_1 = i_t + g_m [i_t (r_\pi // R_E)]$$

$$-v_t + i_1 r_o - v_1 = 0$$

$$-v_t + [1 + g_m (r_\pi // R_E)] i_t r_o + i_t (r_\pi // R_E) = 0$$

$$R_o' = \left. \frac{v_t}{i_t} \right|_{v_i=0} = [1 + g_m (r_\pi // R_E)] r_o + (r_\pi // R_E)$$

$$(r_\pi // R_E) \ll [1 + g_m (r_\pi // R_E)] r_o$$

$$R_o' = \frac{V_t}{i_t} = [1 + g_m(r_\pi // R_E)] r_o + (r_\pi // R_E)$$

$$(r_\pi // R_E) \ll [1 + g_m(r_\pi // R_E)] r_o$$

$$R_o' = [1 + g_m(r_\pi // R_E)] r_o = \left[1 + g_m \frac{r_\pi R_E}{r_\pi + R_E} \right] r_o$$

$$R_o' = \left[1 + \frac{g_m R_E}{\frac{1}{r_\pi} (r_\pi + R_E)} \right] r_o = \left[1 + \frac{g_m R_E}{1 + \frac{R_E}{r_\pi}} \right] r_o = \left[1 + \frac{g_m R_E}{1 + \frac{g_m R_E}{\beta_o}} \right] r_o$$

If $g_m R_E \ll \beta_o$, $R_o' = [1 + g_m R_E] r_o$

$$R_o = R_c // [1 + g_m R_E] r_o$$

If $g_m R_E \gg \beta_o$, $R_o' = \left[1 + \frac{g_m R_E}{\frac{g_m R_E}{\beta_o}} \right] r_o = [1 + \beta_o] r_o$

$$R_o' = \left[1 + \frac{g_m R_E}{\frac{g_m R_E}{\beta_o}} \right] r_o = [1 + \beta_o] r_o$$

$$R_{o_CE} = R_c // r_o \cdot R_{o_CE_degen} > R_{o_CE}$$

CS with Source Degeneration






CS with S degeneration is not as typically implemented as the CE with E degeneration. The reasons are:

1. The transconductance of the MOS is far less than the transconductance of the BJT. When implementing S degeneration, the transconductance of the MOS will be reduced. This condition is undesired.
2. With E degeneration, R_i in CE is increased. However, $R_i \rightarrow \infty$ in the case of CS even without degeneration. Hence, the need for the degeneration circuit is not crucial.

CS with S degeneration is sometimes implemented to increase the R_o of the MOS.

CS with Source Degeneration

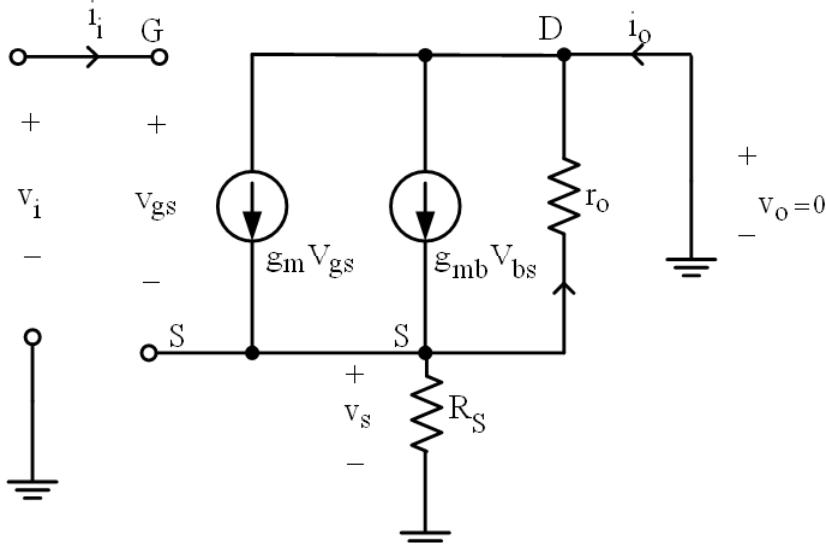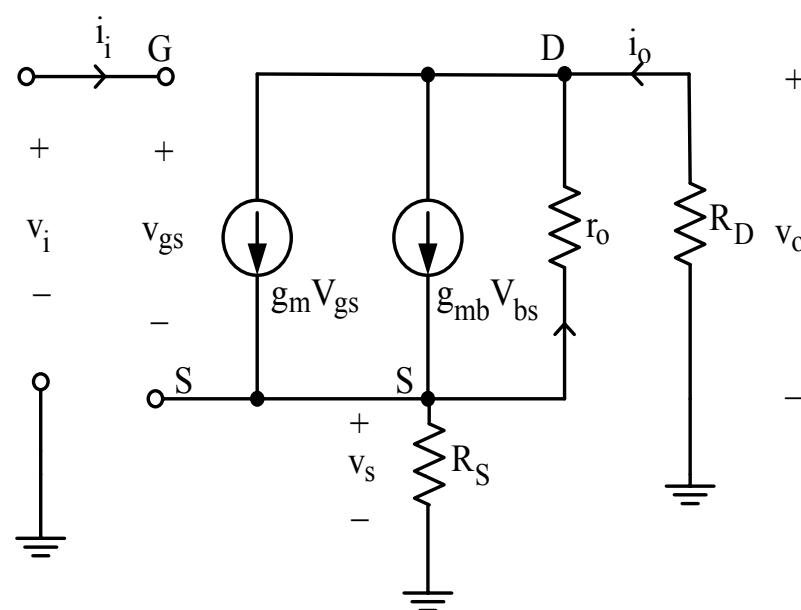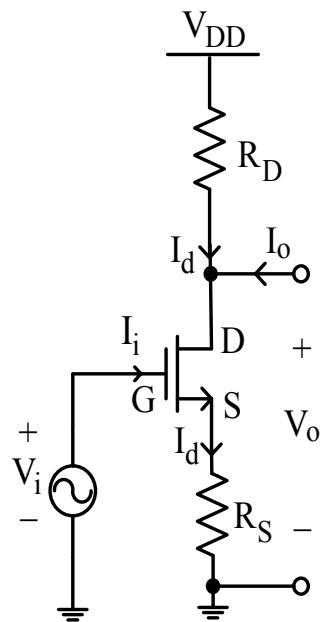

$$R_i = \frac{V_i}{I_i} = \infty$$

Now, S is not at ac gnd. Thus,
 $v_{bs} \neq 0$. g_{mb} generator cannot be omitted.

$$G_m = \left. \frac{i_o}{v_i} \right|_{v_o=0}$$

$$v_b = 0, v_{bs} = -v_s$$

KCL at S when $v_o=0$:

$$g_m v_{gs} - g_{mb} v_s = \frac{v_s}{r_o} + \frac{v_s}{R_s}$$

$$g_m(v_i - v_s) - g_{mb} v_s = \frac{v_s}{r_o} + \frac{v_s}{R_s}$$

$$g_m v_i = \frac{v_s}{r_o} + \frac{v_s}{R_s} + g_m v_s + g_{mb} v_s$$

$$g_m v_i = v_s \left(g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s} \right)_{21}$$

$$g_m v_i = v_s \left(g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s} \right)$$

$$v_s = \frac{g_m v_i}{\left(g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s} \right)}$$

$$G_m = \frac{i_o}{v_i} \Big|_{v_o=0}$$

$$v_b = 0, v_{bs} = -v_s$$

KCL at D when $v_o = 0$:

$$g_m v_{gs} - g_{mb} v_s = \frac{v_s}{r_o} + i_o$$

Therefore,

$$\begin{aligned} & g_m \left\{ v_i - \left[\frac{g_m v_i}{\left(g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s} \right)} \right] \right\} - g_{mb} \left[\frac{g_m v_i}{\left(g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s} \right)} \right] \\ &= \left[\frac{g_m v_i}{\left(g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s} \right)} \right] + i_o \end{aligned}$$

$$g_m \left\{ V_i - \left[\frac{g_m V_i}{\left(g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s} \right)} \right] \right\} - g_{mb} \left[\frac{g_m V_i}{\left(g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s} \right)} \right] \\ - \left[\frac{\frac{g_m V_i}{\left(g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s} \right)}}{r_o} \right] = i_o$$

$$i_o = V_i \left\{ g_m \left\{ 1 - \left[\frac{g_m}{\left(g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s} \right)} \right] \right\} - \frac{g_{mb} g_m}{\left(g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s} \right)} \right\} \\ - \frac{g_m}{r_o \left(g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s} \right)}$$

$$G_m = \frac{i_o}{v_i} = \left\{ g_m \left\{ \frac{g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s}}{g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s}} - \left[\frac{g_m}{\left(g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s} \right)} \right] \right\} - \frac{g_{mb} g_m}{\left(g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s} \right)} \right\} - \frac{g_m}{r_o \left(g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s} \right)}$$

$$G_m = \left\{ g_m \left\{ \frac{g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s} - g_m - g_{mb} - \frac{1}{r_o}}{g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s}} \right\} \right\}$$

$$G_m = \left\{ g_m \left[\frac{\frac{1}{R_s}}{g_m + g_{mb} + \frac{1}{r_o} + \frac{1}{R_s}} \right] \right\} = \frac{g_m}{R_s(g_m + g_{mb}) + \frac{R_s}{r_o} + 1}$$

$$G_m = \frac{g_m}{R_s(g_m + g_{mb}) + \frac{R_s}{r_0} + 1}$$

If $r_0 \gg R_s$, $G_m = \frac{g_m}{R_s(g_m + g_{mb}) + 1}$

If R_s is large, $G_m = \frac{g_m}{R_s(g_m + g_{mb})} = \frac{1}{R_s\left(1 + \frac{g_{mb}}{g_m}\right)} = \frac{1}{R_s(1 + \chi)}$

$$\chi = 0.1 \rightarrow 0.3$$

Without S degeneration, $G_m = g_m$. This shows that with source degeneration, G_m has reduced. $G_{m_CS_degen} < G_{m_CS}$.

$$G_{m_CS_degen} = \frac{1}{R_s(1 + \chi)} \text{ and } G_{m_CE_degen} = \frac{g_m \left[1 - \frac{R_E}{r_0 \beta_o} \right]}{1 + g_m R_E \left(1 + \frac{1}{g_m r_0} + \frac{1}{\beta_o} \right)}$$

If $r_0 \gg R_E$, and $R_E \gg 1$, then


$$G_{m_CE_degen} = \frac{1}{R_E \left(1 + \frac{1}{\beta_o} \right)} = \frac{\beta_o}{R_E (1 + \beta_o)}$$

$$G_{m_CS_degen} = \frac{1}{R_s(1+\chi)}$$

$$G_{m_CE_degen} = \frac{1}{R_E \left(1 + \frac{1}{\beta_o}\right)} = R_E \left(1 + \beta_o\right)$$

This shows that the G_m of the CS with S degeneration is more dependent on the device parameter when compared to the G_m of the CE with E degeneration.

$$R_o = \frac{v_t}{i_t} \Big|_{v_i=0}$$

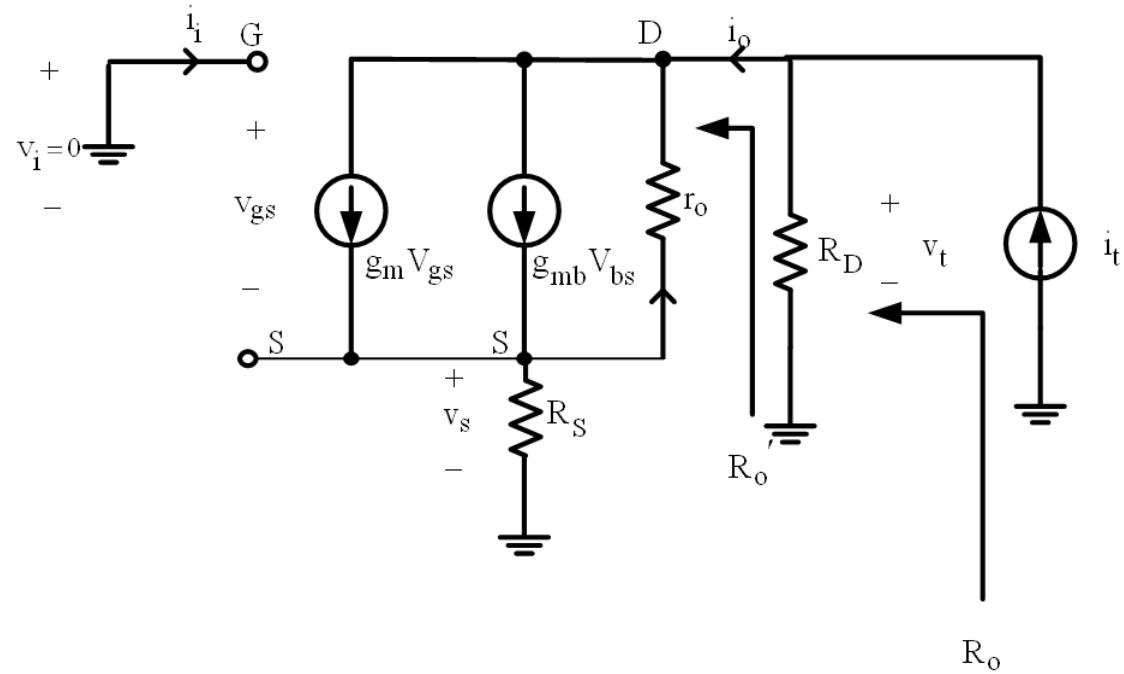

$$R_o = \left. \frac{V_t}{i_t} \right|_{V_i=0}, R_o' = \left. \frac{V_t}{i_t} \right|_{V_i=0}$$

$$v_{gs} = -v_s$$

KCL at node D:

$$i_t' = -g_{mb}v_s - g_m v_s + \frac{V_t - V_s}{r_o}$$


KCL at node S:

$$\frac{V_s}{R_s} + g_{mb}v_s + g_m v_s + \frac{V_s}{r_o} = \frac{V_t}{r_o}$$

$$v_s = \frac{V_t}{\left(\frac{1}{R_s} + g_{mb} + g_m + \frac{1}{r_o} \right) r_o}$$

$$i_t' = -g_{mb}v_s - g_m v_s - \frac{V_s}{r_o} + \frac{V_t}{r_o}$$
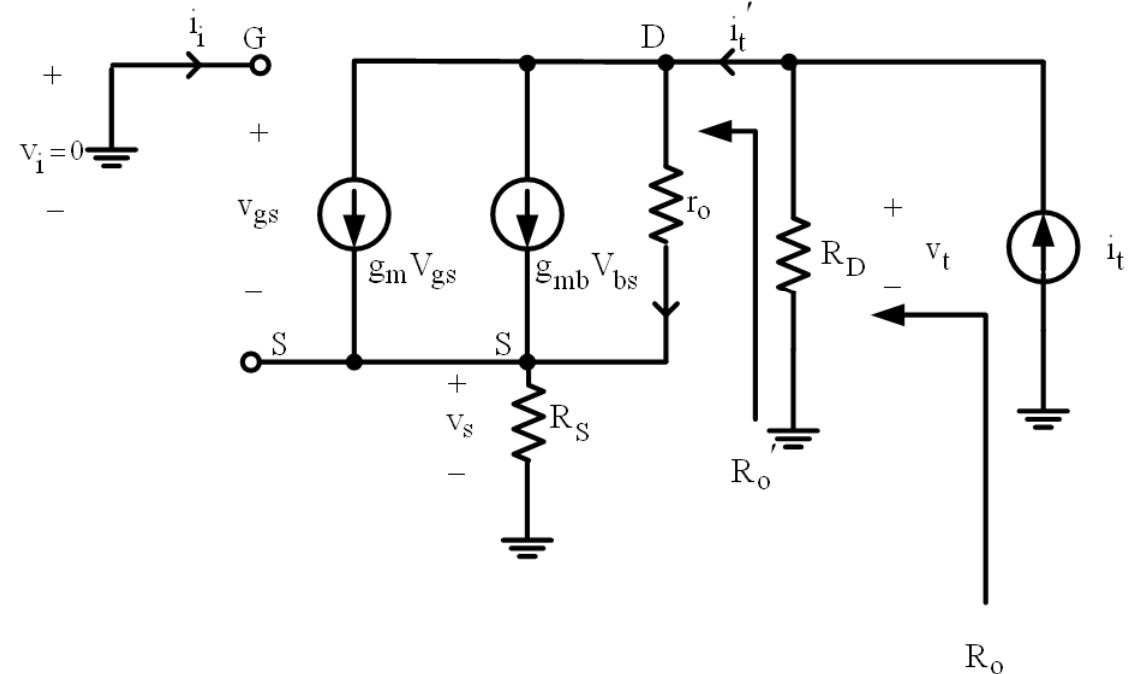
$$= \left[\frac{\left(-g_{mb} - g_m - \frac{1}{r_o} \right)}{\left(\frac{1}{R_s} + g_{mb} + g_m + \frac{1}{r_o} \right) r_o} + \frac{1}{r_o} \right] V_t$$



$$i_t' = -g_{mb}v_s - g_m v_s - \frac{v_s}{r_o} + \frac{v_t}{r_o}$$

$$= \left[\frac{\left(-g_{mb} - g_m - \frac{1}{r_o} \right)}{\left(\frac{1}{R_s} + g_{mb} + g_m + \frac{1}{r_o} \right) r_o} + \frac{1}{r_o} \right] v_t$$

$$R_o' = \frac{v_t'}{i_t'} = \frac{1}{\left[\frac{\left(-g_{mb} - g_m - \frac{1}{r_o} \right)}{\left(\frac{1}{R_s} + g_{mb} + g_m + \frac{1}{r_o} \right) r_o} + \frac{1}{r_o} \right]} = \frac{1}{\left[\left(-g_{mb} - g_m - \frac{1}{r_o} \right) + \left(\frac{1}{R_s} + g_{mb} + g_m + \frac{1}{r_o} \right) \right]}$$

$$R_o' = \frac{1}{\left[\frac{1}{R_s} \right]} = \frac{1}{\left[R_s \left(\frac{1}{R_s} + g_{mb} + g_m + \frac{1}{r_o} \right) r_o \right]} = r_o + r_o R_s g_{mb} + r_o R_s g_m + R_s$$

$$R_o' = r_o (1 + R_s (g_{mb} + g_m)) + R_s$$

$$R_o' = r_o(1 + R_s(g_{mb} + g_m)) + R_s$$

If $R_s \uparrow$, R_o' will also \uparrow .

For the CE with E degeneration:

$$R_o' = [1 + \beta_o] r_o$$

Even though $R_E \rightarrow \infty$, R_o' will be limited to its maximum value of $r_o(1 + \beta_o)$.