



EEE 241

ANALOG ELECTRONICS I


**Lectures 2&3 – Single
Transistor Amplifiers**

DR NORLAILI MOHD NOH


3.3 Basic Single-Transistor Amplifier Stages

3 different configurations :

1. Common-emitter

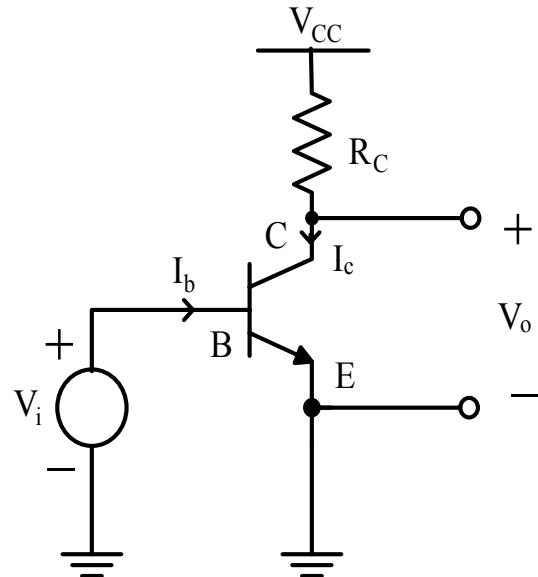

Common-source

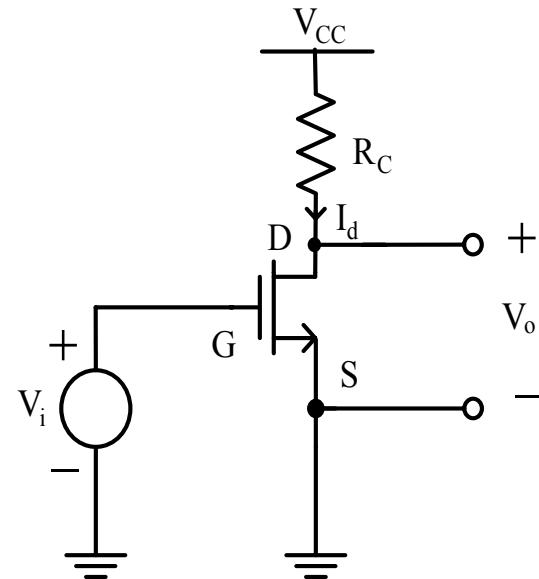

Signal applied to : B

Amplified output


taken from :

C


G

D

2. Common-collector (emitter follower)

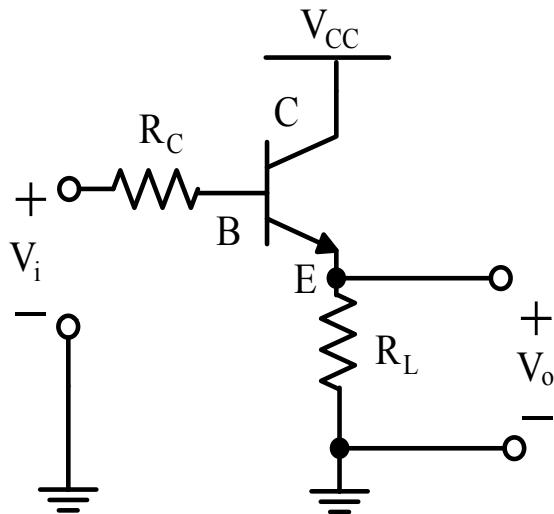

Common-drain (source follower)

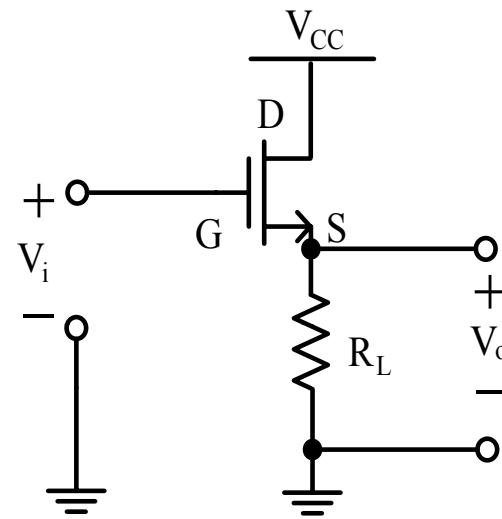

Signal applied to : B

G


Amplified output

taken from :


E

S

3. Common-base

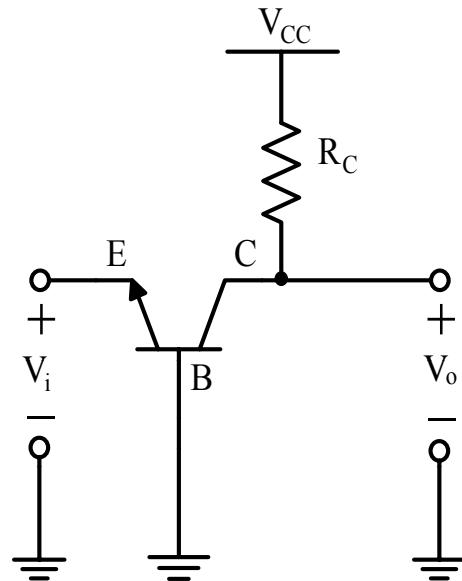

Common-gate

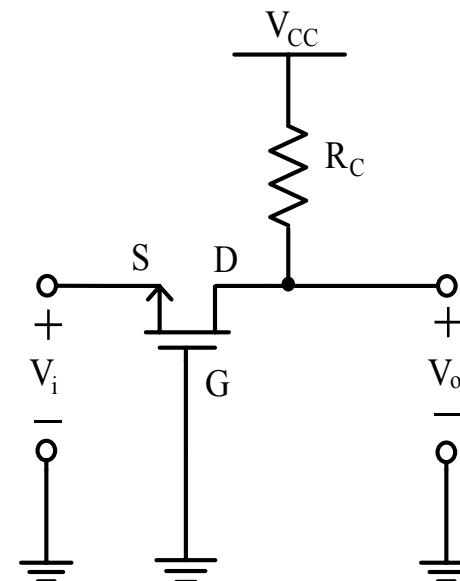

Signal applied to : E

S

Amplified output


taken from :

C

D

Common-emitter configuration

In forward active :

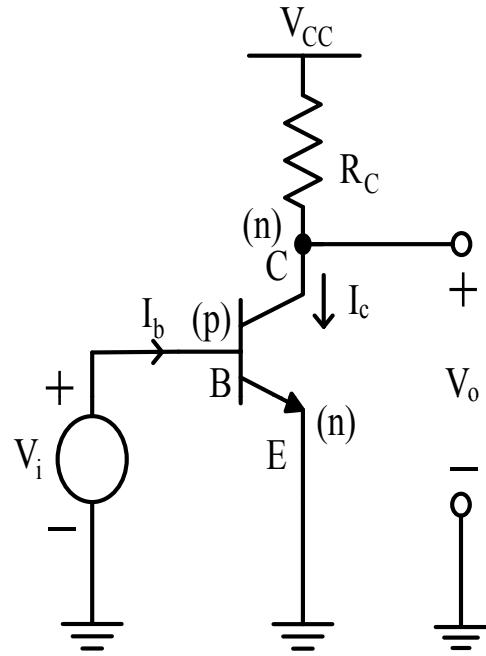

$$I_c = I_s \exp \frac{V_i}{V_T}$$


I_s = saturated current

$$I_b = \frac{I_c}{\beta_F} = \frac{I_s}{\beta_F} \exp \frac{V_i}{V_T}$$

β_F = forward current gain

$$V_o = V_{CC} - I_c R_C$$


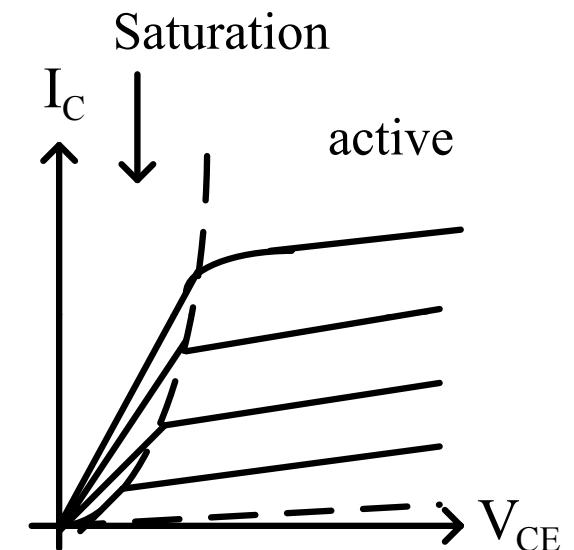
$$= V_{CC} - R_C I_s \exp \frac{V_i}{V_T}$$



When V_o approaches 0 (i.e. V_{ce} approaches 0), the C-B junction becomes forward biased and the device enters saturation. Once the transistor becomes saturated, the output voltage and collector current take on nearly constant values :

$$V_o = V_{CE(sat)}$$
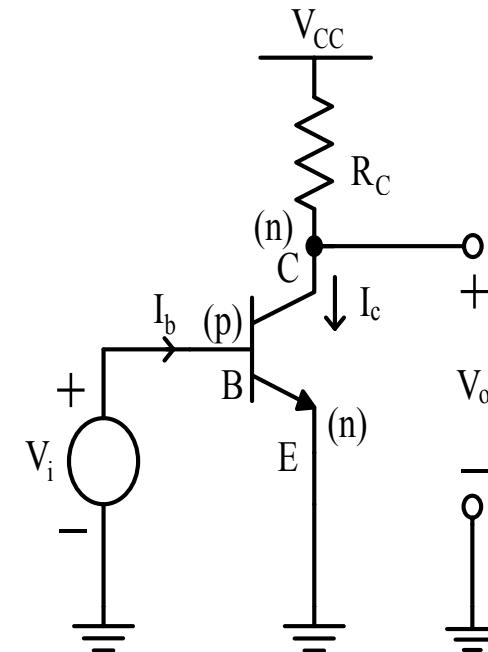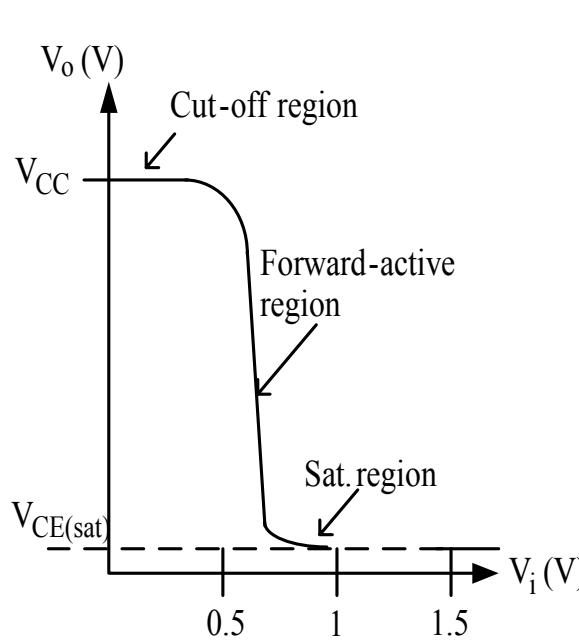
$$I_c = \frac{V_{CC} - V_{CE(sat)}}{R_C}$$



When V_o approaches 0 (i.e. V_{ce} approaches 0), the C-B junction becomes forward-biased and the device enters saturation. Once the transistor becomes saturated, the output voltage and collector current take on nearly constant values :

$$V_o = V_{CE(sat)}$$


$$I_c = \frac{V_{CC} - V_{CE(sat)}}{R_C}$$

When $V_i = 0$, the transistor operates in the cut off state (as B-E and B-C junctions are both reverse bias) and no current flows other than leakage current I_{CO} .

In saturation :

$$V_o = V_{CE(sat)}$$

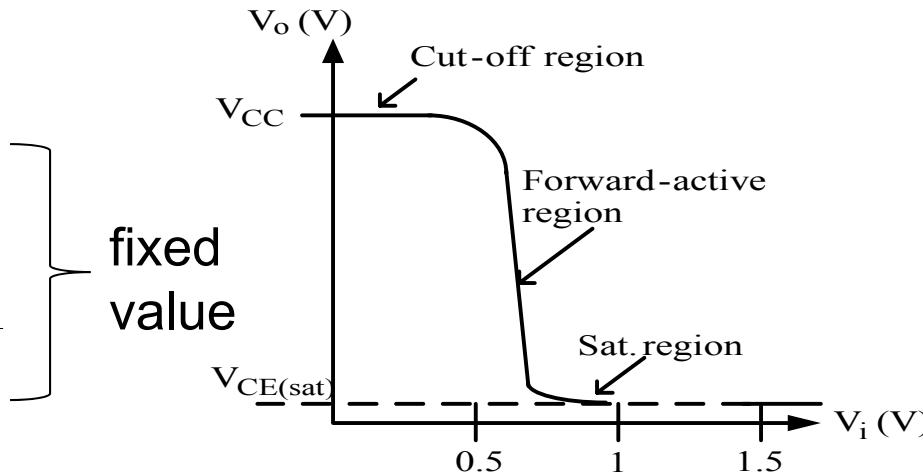
$$I_c = \frac{V_{CC} - V_{CE(sat)}}{R_C}$$




When V_i is high and $> V_o$, the C-B junction is forward bias. Thus, device is in the saturation region. As V_i is high, I_b is also high. Forward current gain $\beta_F = I_c / I_b$. Forward current gain β_F reduces as transistor leaves the forward-active region of operation and moves into saturation.

In the forward-active region, small changes in the input voltage can give rise to large changes in the output voltage. The circuit thus provides voltage gain.

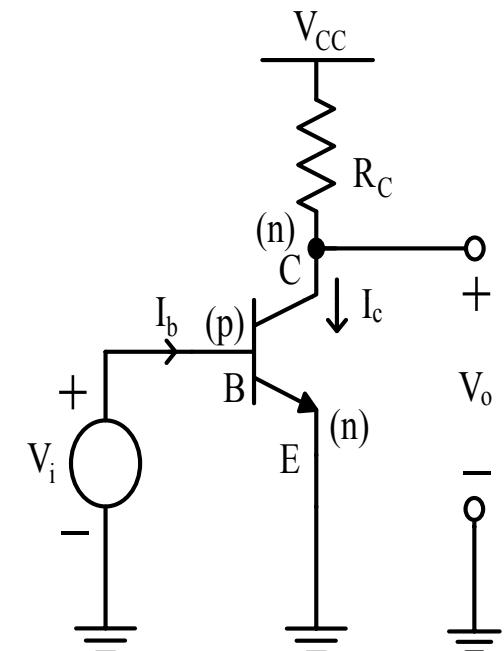When $V_i = 0$, $I_b = 0$ and $I_c = 0$. $V_{CC} = I_c R_C + V_o$ and since $I_c = 0$, $V_o = V_{CC}$. This is the device operating in the cut off region.



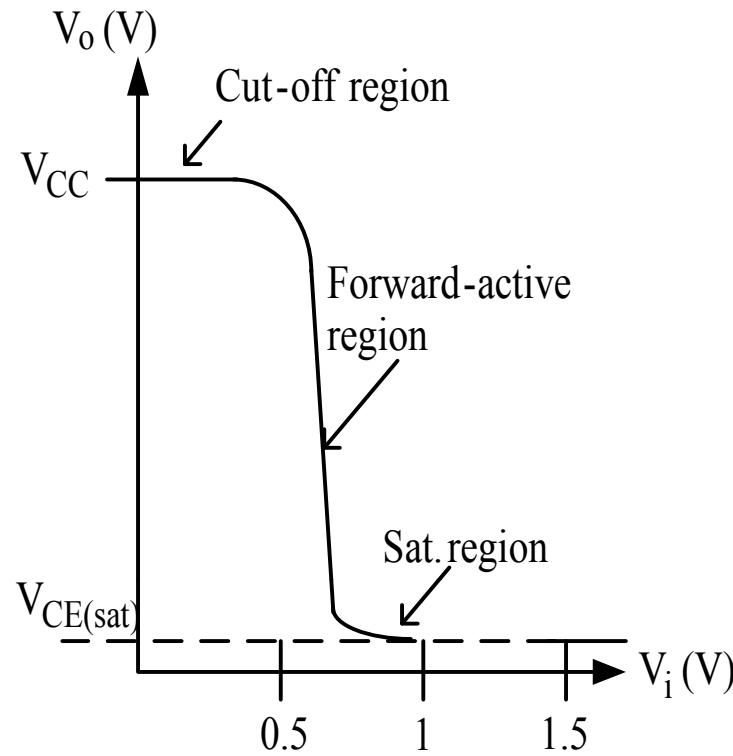

In the forward active region,


$$I_c = I_s \exp \frac{V_i}{V_T}$$

$$I_b = \frac{I_c}{\beta_F}$$



$$\begin{aligned} V_o &= V_{CC} - I_c R_C \\ &= V_{CC} - R_C I_s \exp \frac{V_i}{V_T} \end{aligned}$$

When $V_i \downarrow, I_c \downarrow \therefore V_o \rightarrow V_{CC}$

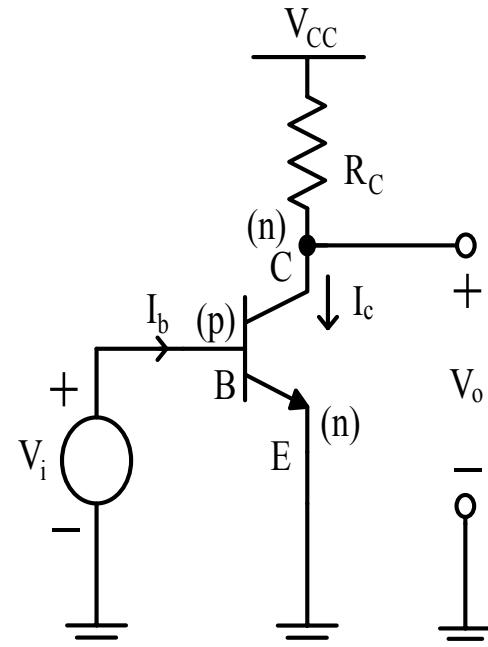When $V_i \uparrow, I_c \uparrow \therefore V_o \rightarrow 0$






Small-signal circuit of Common-Emitter

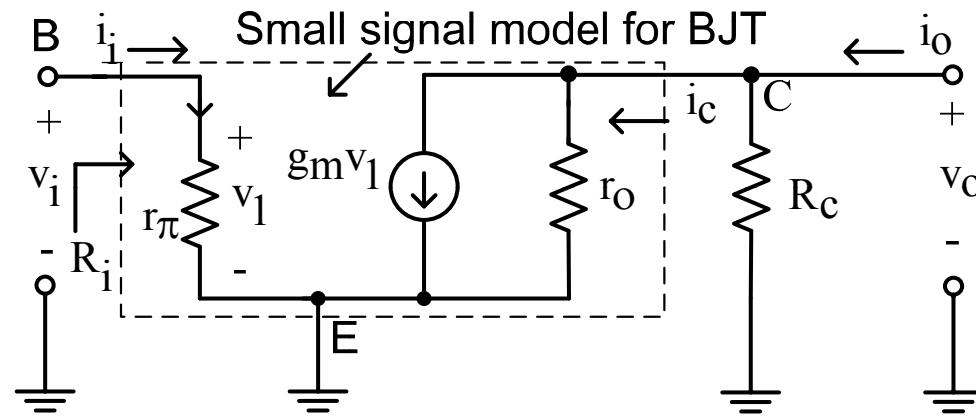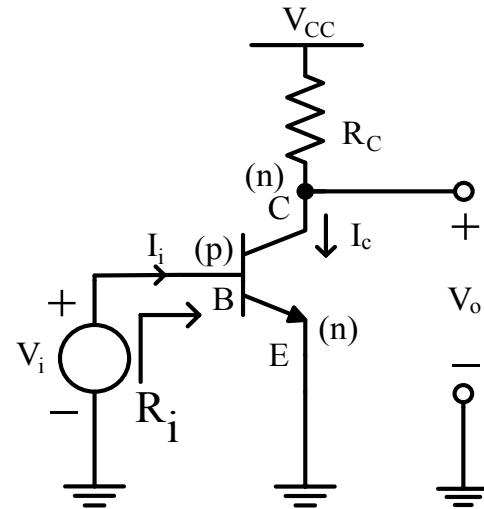

$$\text{Input resistance } R_i = \frac{V_i}{i_i} = r_\pi = \frac{\beta_0}{g_m}$$

$$\text{Transconductance, } G_m = \left. \frac{i_o}{v_i} \right|_{v_o=0} = \frac{g_m v_1}{v_i} = \frac{g_m v_i}{v_i} = g_m$$

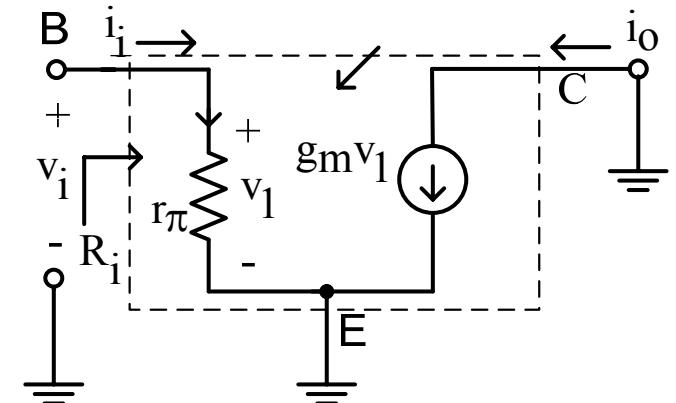

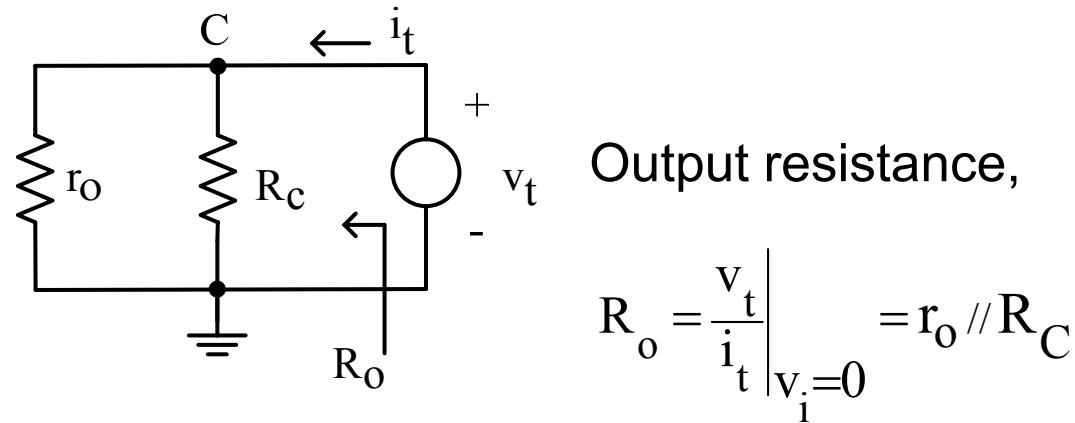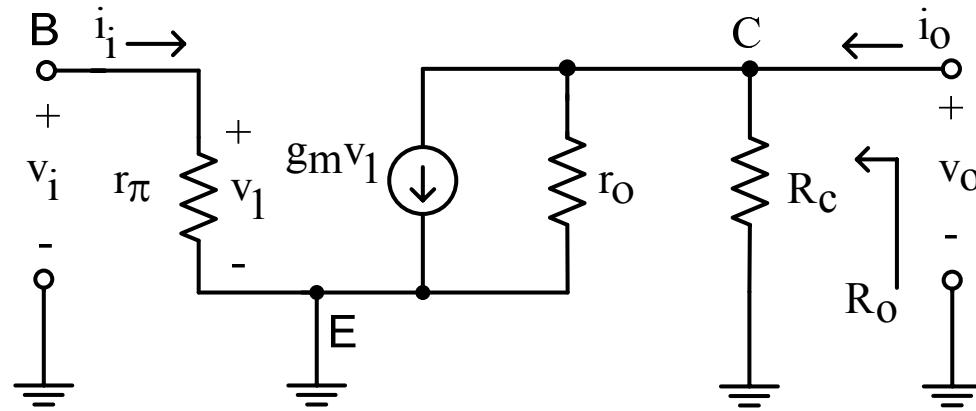

Open-circuit or unloaded voltage gain,

$$a_v = \left. \frac{v_o}{v_i} \right|_{i_o=0} = -\frac{g_m v_1 r_o // R_C}{v_i}$$

Since $V_1 = V_i$, then $a_v = -g_m r_o // R_C$.


If $R_C \uparrow\uparrow$, then $\lim_{R_C \rightarrow \infty} a_v = -g_m r_o = -\frac{I_C}{V_T} \frac{V_A}{I_C} = -\frac{V_A}{V_T} = -\frac{1}{\eta}$

I_c = dc collector current at the operating point

V_T = thermal voltage

V_A = Early voltage


$$\eta = \frac{kT}{qV_A}$$

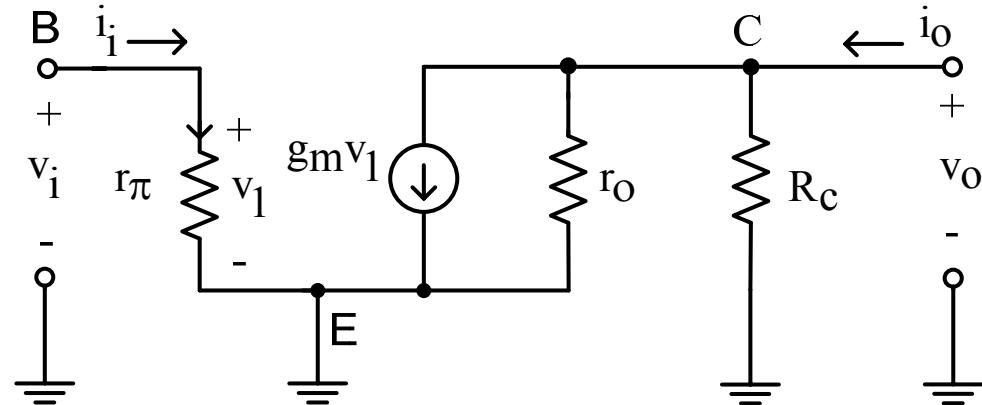

$$\lim_{R_C \rightarrow \infty} a_v = -g_m r_o = -\frac{V_A}{V_T} = -\frac{1}{\eta}$$

represents the max. low-freq. voltage gain obtainable from the transistor. It is independent of the C bias current for BJT and the magnitude is ≈ 5000 for typical npn devices.



s/c current gain: $a_i = \frac{i_o}{i_i} \Big|_{v_o=0} = \frac{g_m v_1}{r_\pi} = g_m r_\pi = \beta_o$

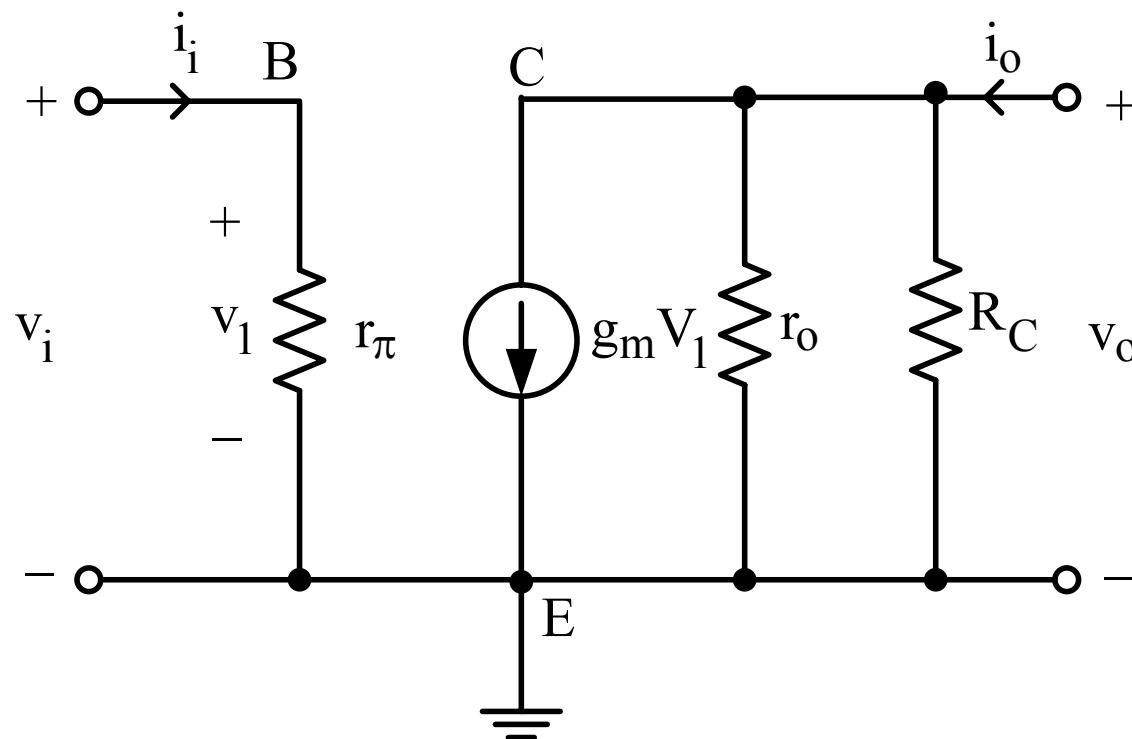


Do example on pg. 178.

Comparison between the MOS and BJT small signal models :

	BJT	MOS
1	r_π input resistance	∞ input resistance from G to S
2	g_m of BJT is higher than that of MOS biased with the same current. Hence, high-gain amplifiers with BJTs are easier to obtain than with MOS.	

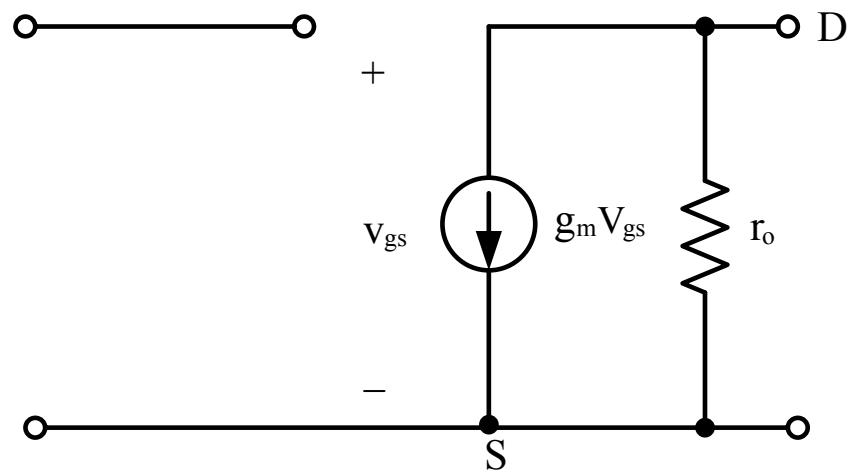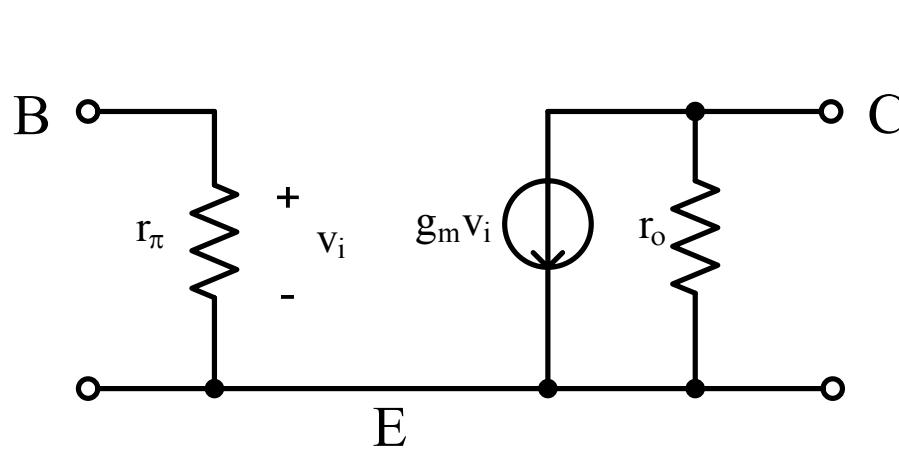


3.3.2 Common-Source (CS) configuration

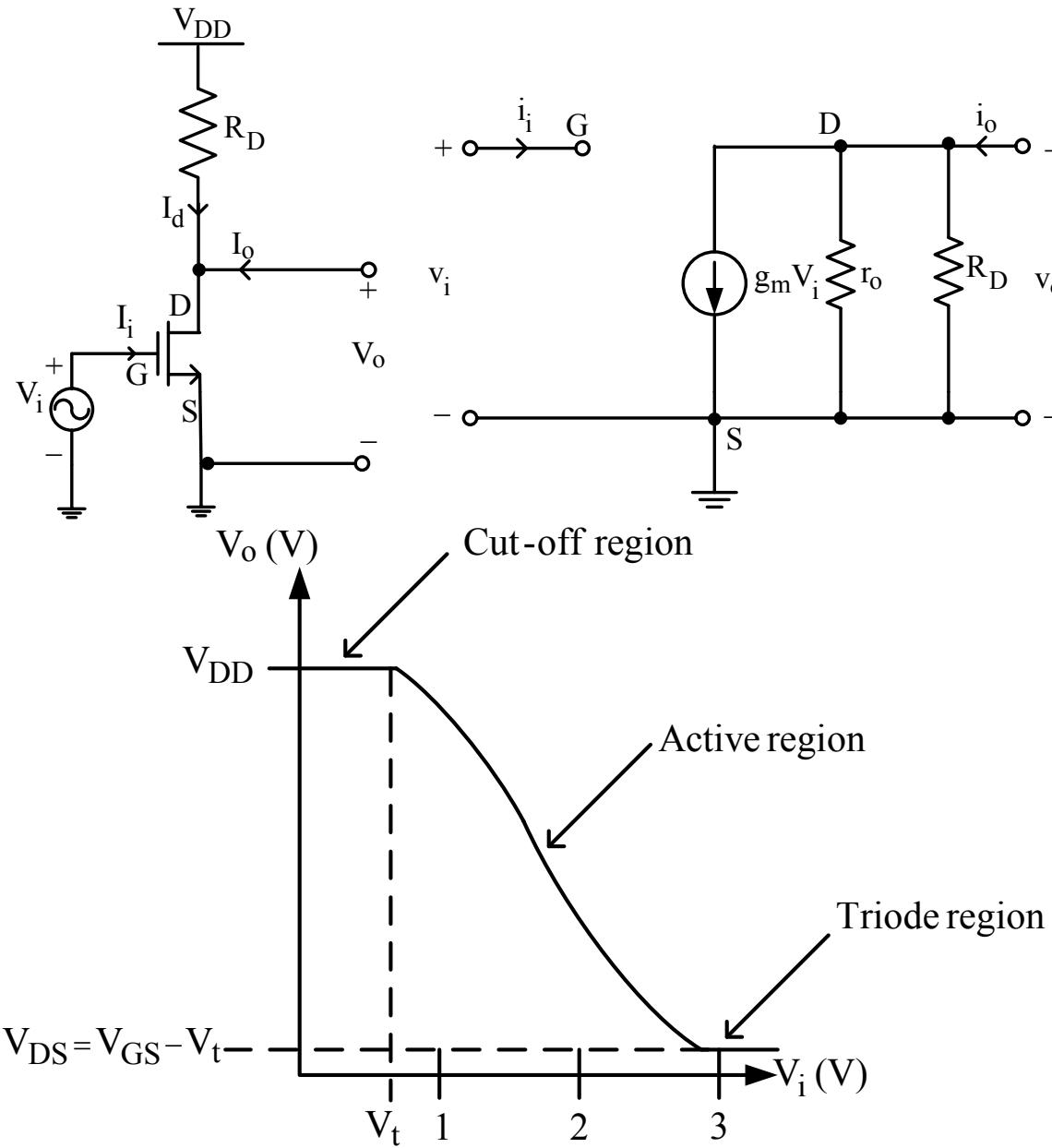

$$V_i = 0, I_d = 0 \rightarrow \text{cutoff operation}$$

$$V_o = V_{DD} - I_d R_d = V_{DD}$$

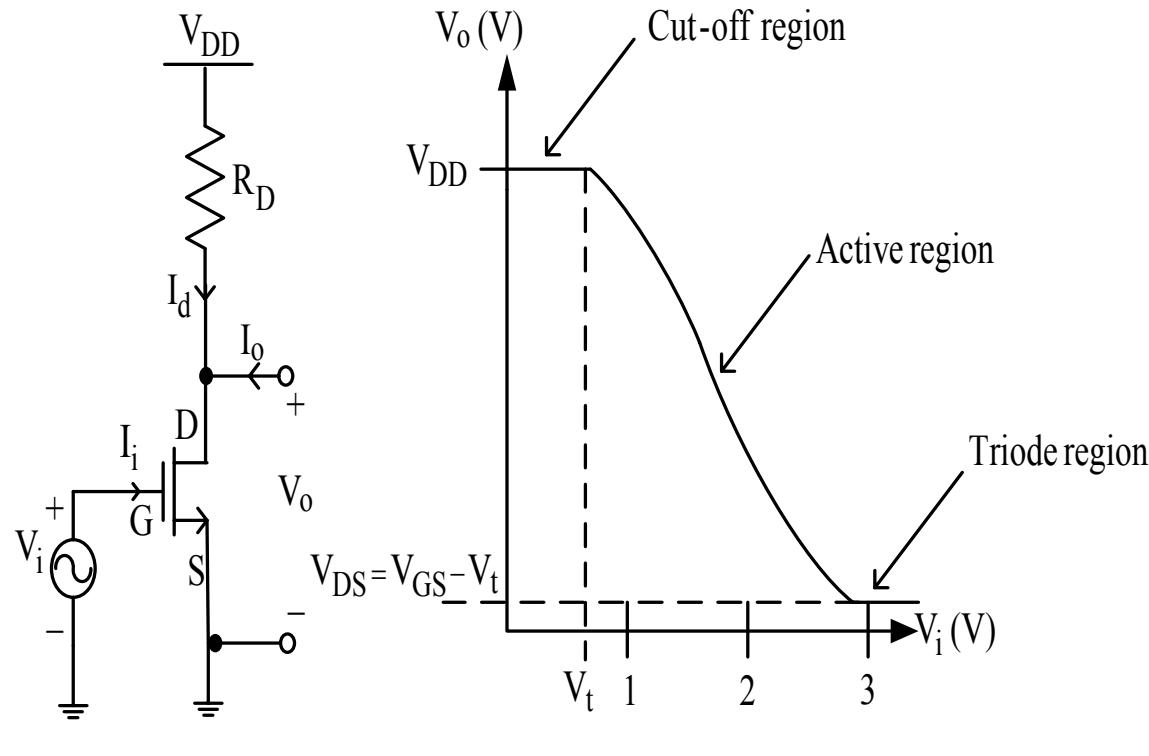

$V_i > V_t$, I_d flows
 → active/sat. operation
 $V_o = V_{DS}$ and $V_{DS} > V_{GS} - V_t$
 $V_o = V_{DD} - I_d R_D$

For active devices,


$$I_D = \frac{k'W}{2L} V_{ov}^2$$

$$V_o = V_{DD} - \frac{k'W}{2L} V_{ov}^2 R_D$$

$$k' = \mu_n C_{ox}$$

$$V_{ov} = V_{GS} - V_t = V_i - V_t$$
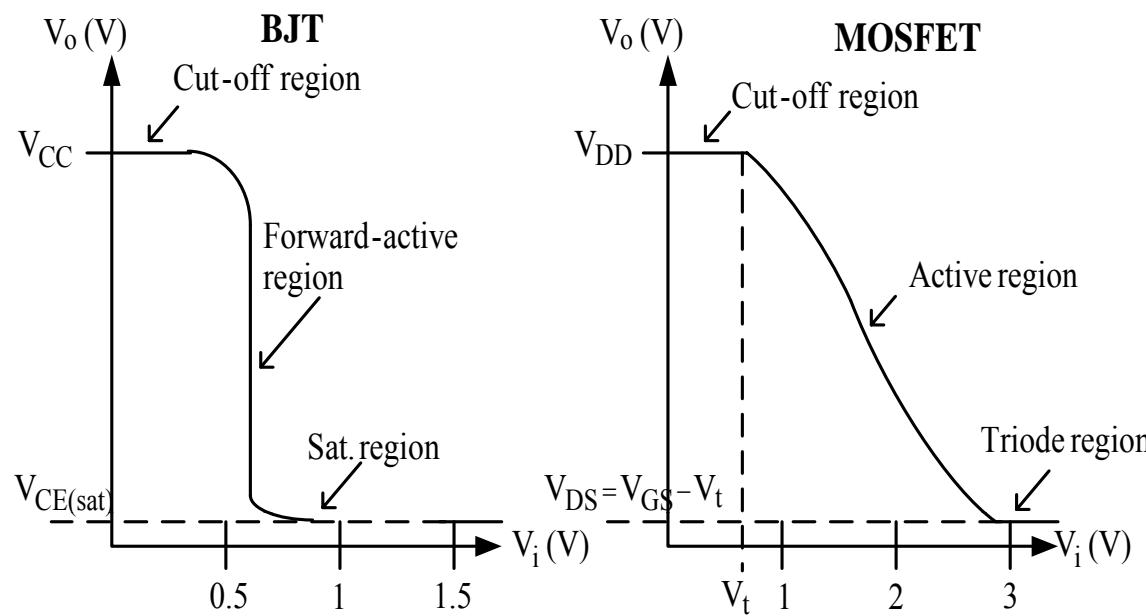
$$V_i \uparrow V_{ov} \uparrow V_o \downarrow$$




$$V_o = V_{DS} \text{ and } V_{DS} < V_{GS} - V_t$$

→ triode operation

$$I_D = \frac{k' W}{2 L} \left[2(V_{GS} - V_t)V_{DS} - V_{DS}^2 \right]$$

Output resistance is low and small-signal voltage gain drops dramatically. The slope of this transfer characteristic at any operating point is the small signal voltage gain at that point. As slope for MOS < slope for BJT,

$$a_v(\text{MOS}) < a_v(\text{BJT})$$

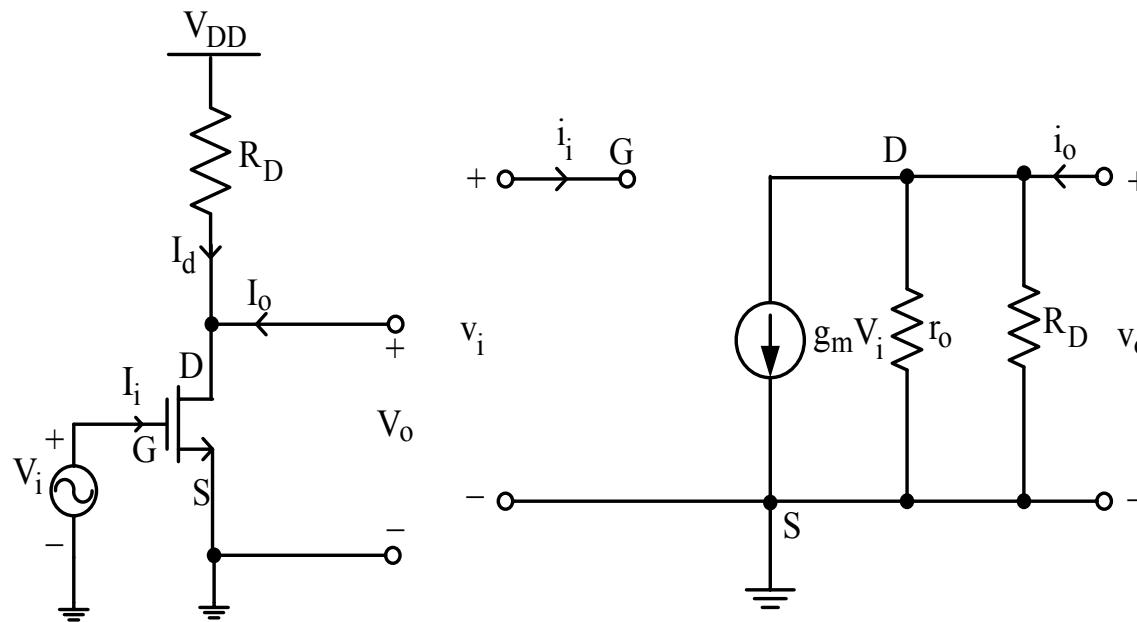


$$G_m = \left. \frac{i_o}{v_i} \right|_{v_o=0} = \frac{g_m v_i}{v_i} = g_m \quad \text{Hence, transconductance of the circuit, } G_m = \text{transconductance of the transistor, } g_m$$

$$R_i = \left. \frac{v_i}{i_i} \right|_{i_i=0} = \infty$$

$$R_o = \left. \frac{v_t}{i_t} \right|_{v_i=0} = r_o \| R_D$$

o/c or unloaded voltage gain,

$$a_v = \left. \frac{v_o}{v_i} \right|_{i_o=0} = -\frac{g_m v_i (r_o \| R_D)}{v_i} = -g_m (r_o \| R_D)$$

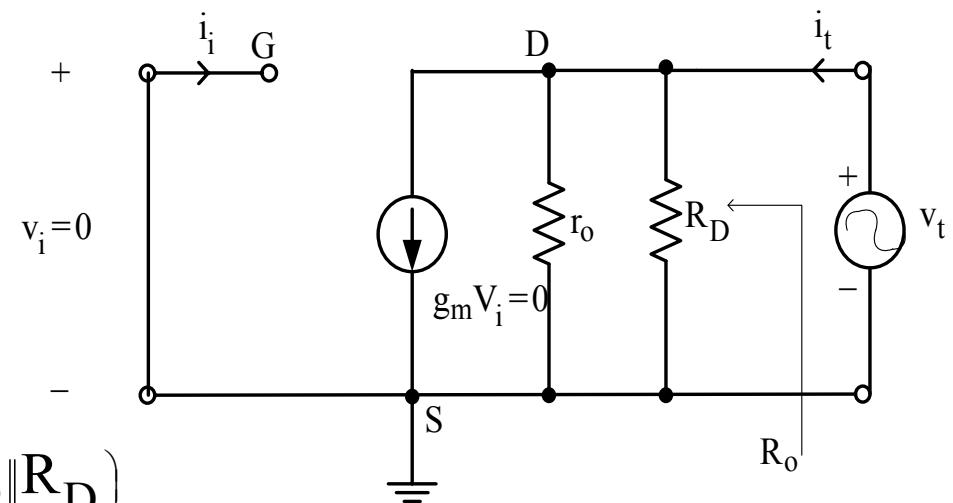

$$a_v = -g_m(r_o \parallel R_D)$$

If R_D is very large, $\lim_{R_D \rightarrow \infty} a_v = -g_m r_o$ which is the max. possible voltage gain of a one-stage CS amplifier.

$$g_m = \sqrt{2I_D \mu_n C_{ox} \frac{W}{L}}$$

$$g_m \propto \sqrt{I_D}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{V_A}{I_D}$$

$$r_o \propto \frac{1}{I_D}$$

$$a_v \propto \frac{\sqrt{I_D}}{I_D}$$

$$a_v \propto \frac{1}{\sqrt{I_D}}$$

$$\text{For BJT, } \lim_{R_C \rightarrow \infty} a_v = -g_m r_o = -\frac{V_A}{V_T}$$

Therefore, max. voltage gain of MOSFET is dependent on the drain current whereas max. voltage gain of BJT is independent of I_C .

For MOS:

$$g_m = k' \frac{W}{L} (V_{GS} - V_t)$$

$$I_D = \frac{k' W}{2 L} (V_{GS} - V_t)^2$$

$$\frac{g_m}{I_D} = \frac{2}{(V_{GS} - V_t)} = \frac{2}{V_{ov}}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{V_A}{I_D}$$

Hence,

$$\lim_{R_D \rightarrow \infty} a_v = -g_m r_o = -g_m \frac{V_A}{I_D} = -\frac{2V_A}{V_{ov}}$$

For BJT:

$$\text{Hence, } R_C \lim_{C \rightarrow \infty} a_v = -g_m r_o = -\frac{V_A}{V_T}$$



$$V_T = 26 \text{ mV}$$

$$V_{ov} = 200 \text{ mV}$$

$$a_{v_MOS} < a_{v_BJT}$$

(Do example page 182)

3.3.3 Common-Base configuration

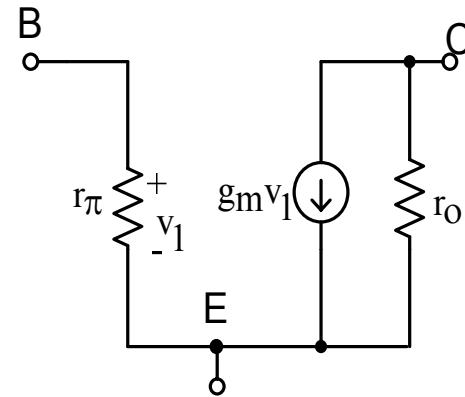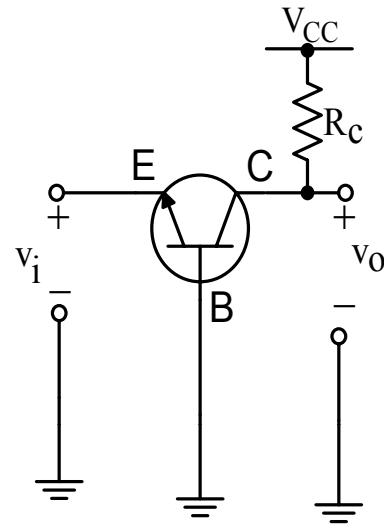


I/p signal applied to E. O/p taken from C. B tied to ac gnd.

The hybrid- π model provides an accurate representation of the small-signal behavior of the transistor independent of the circuit configuration. However, for the common-B, the hybrid- π model becomes tougher to analyze as the dependent current source is connected between the i/p and o/p terminals.

To simplify the analysis of a common-B (CB) amplifier, use a T-model instead.

The T-model at low freq:

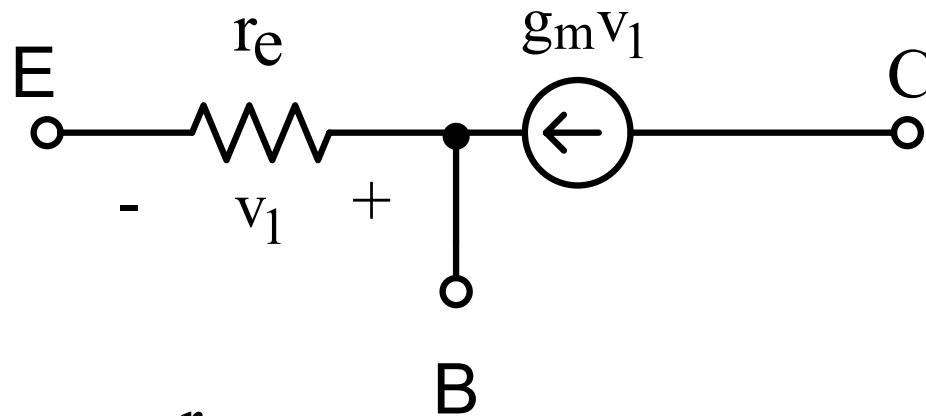

$$r_e = \frac{r_\pi}{1 + g_m r_\pi}$$

$$r_\pi = \frac{\beta_o}{g_m}$$

$$r_e = \frac{r_\pi}{1 + g_m r_\pi} = \frac{\beta_o}{g_m \left(1 + g_m \frac{\beta_o}{g_m}\right)} = \frac{1}{g_m} \frac{\beta_o}{1 + \beta_o} = \frac{\alpha_o}{g_m}$$

Hybrid- π model at low freq:

