




**EEE 241**  
**ANALOG ELECTRONICS**  
**Class 5&6&7&8&9**

**DR NORLAILI MOHD NOH**

---

### 3.3.3 Common-Base configuration

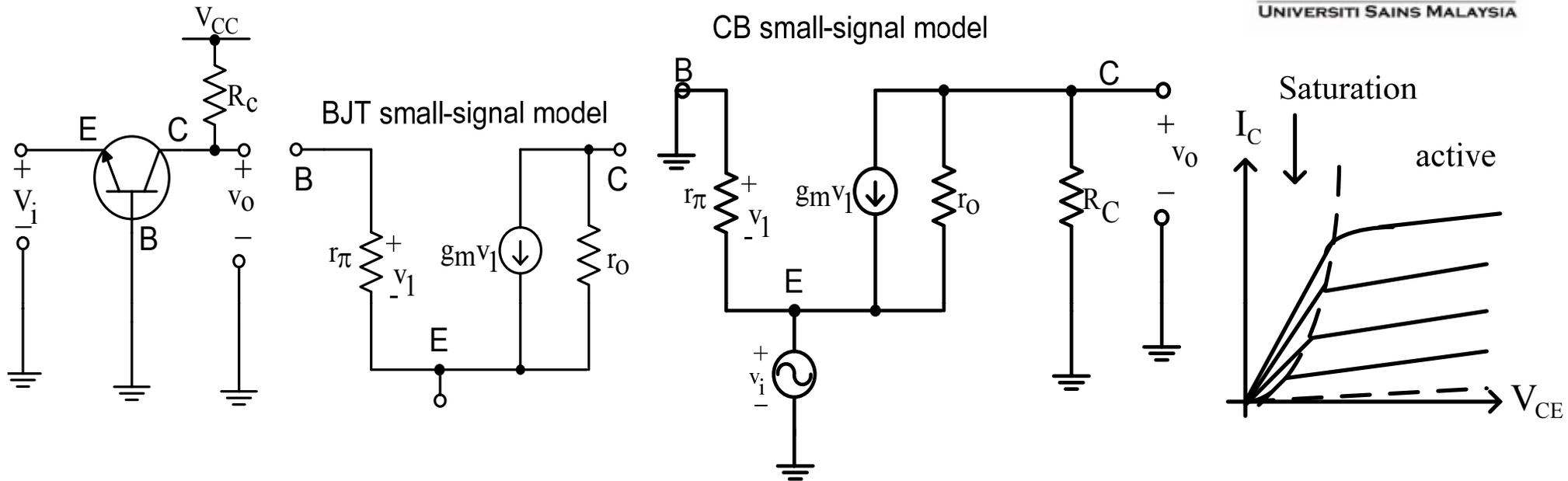


i/p signal applied to E. O/p taken from C. B tied to ac gnd.

The hybrid- $\pi$  model provides an accurate representation of the small-signal behavior of the transistor independent of the circuit configuration. However, for the common-B, the hybrid- $\pi$  model becomes tougher to analyze as the dependent current source is connected between the i/p and o/p terminals.

To simplify the analysis of a common-B (CB) amplifier, use a T-model instead.

The T-model at low freq:

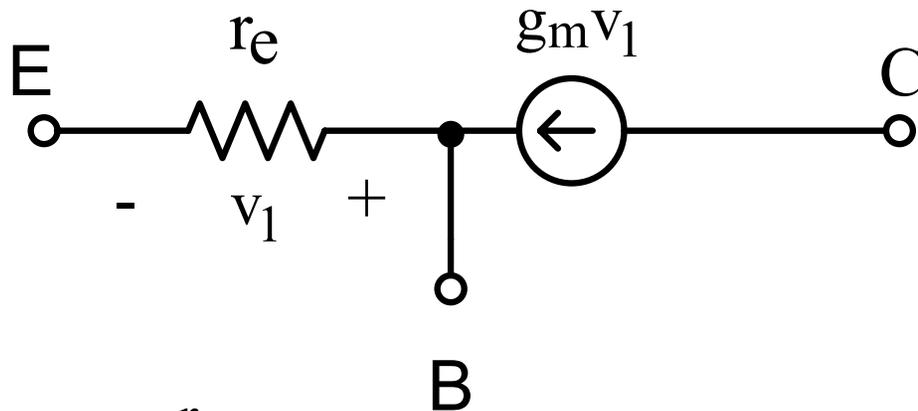


$$r_e = \frac{r_\pi}{1 + g_m r_\pi}$$


$$r_\pi = \frac{\beta_o}{g_m}$$

$$r_e = \frac{r_\pi}{1 + g_m r_\pi} = \frac{\beta_o}{g_m \left( 1 + g_m \frac{\beta_o}{g_m} \right)} = \frac{1}{g_m} \frac{\beta_o}{1 + \beta_o} = \frac{\alpha_o}{g_m}$$


Hybrid- $\pi$  model at low freq:

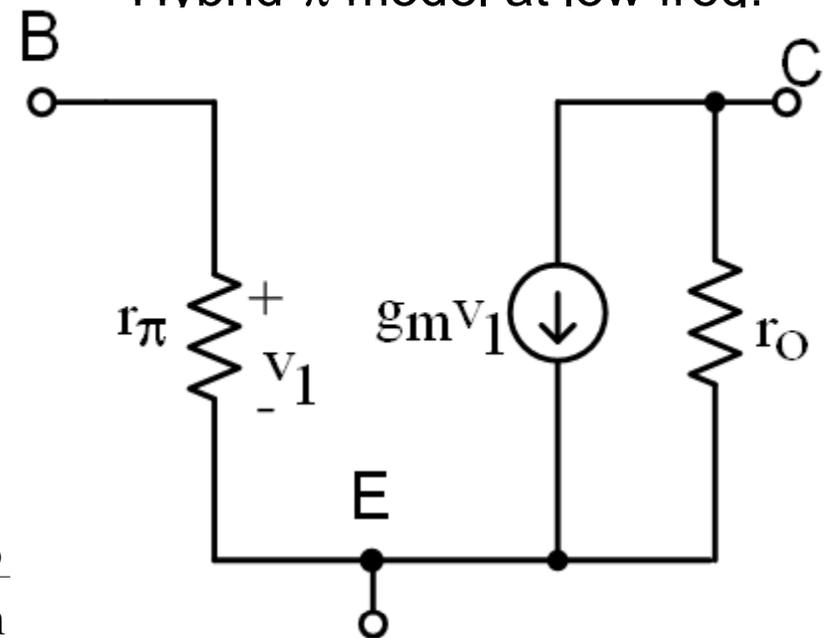



T-model:

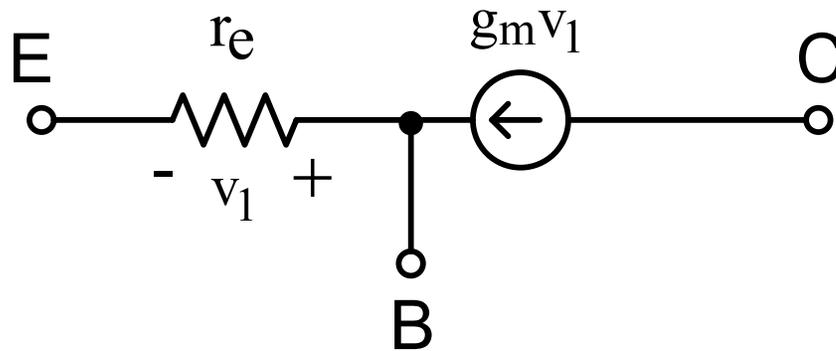


CB hybrid- $\pi$  model

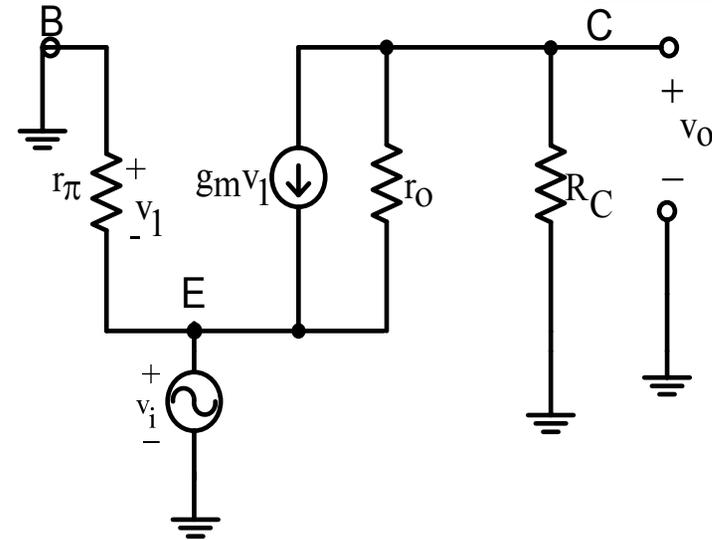


CB topology:

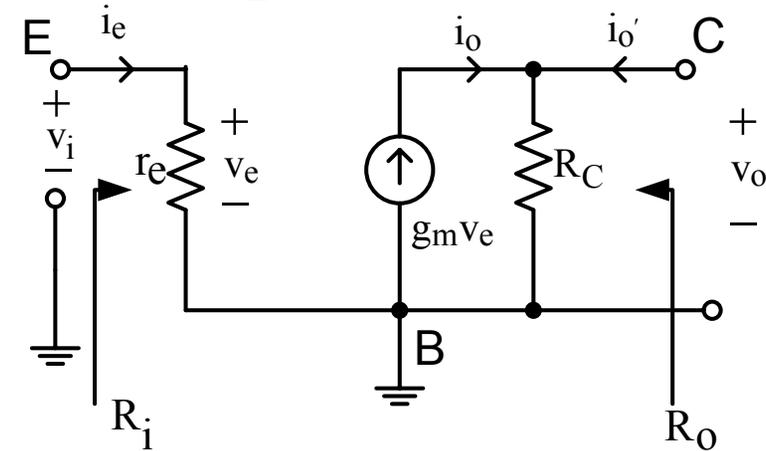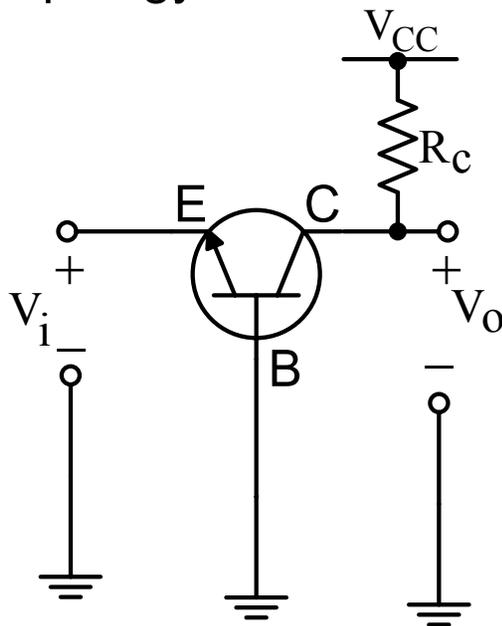

T-model of the CB topology:

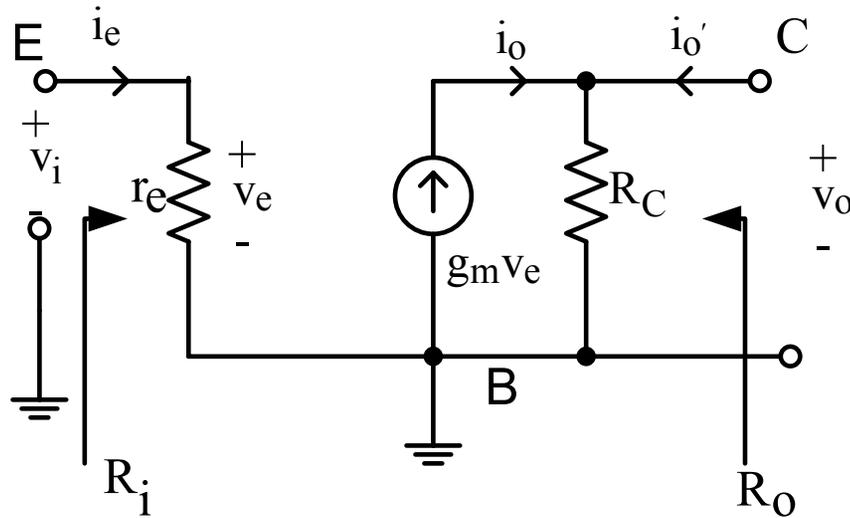


The s/c transconductance:  $G_m = \frac{i_o}{v_i} \Big|_{v_o=0} = \frac{g_m v_e}{v_e} = g_m$

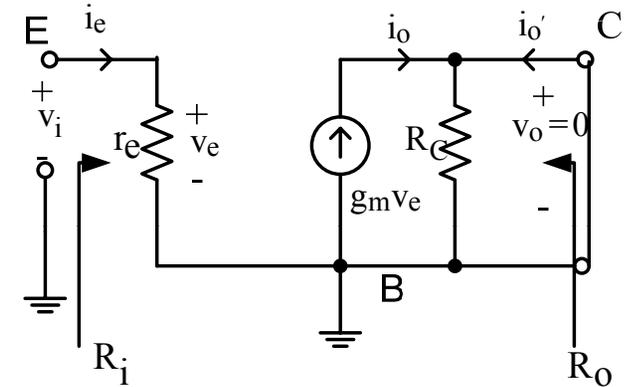

The input resistance:  $R_i = \frac{v_i}{i_e} = \frac{v_e}{i_e} = r_e$

The output resistance:  $R_o = \frac{v_t}{i_t} \Big|_{v_i=0} = R_C$

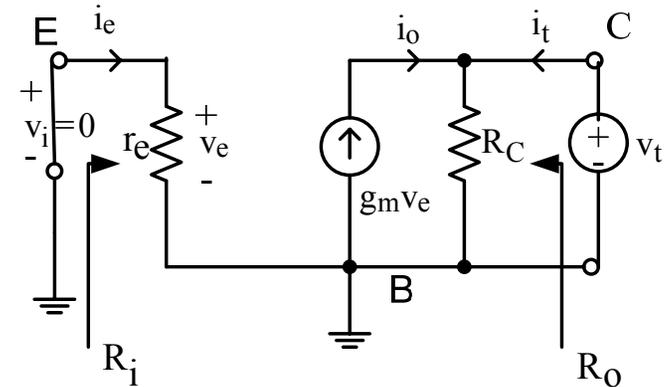

o/c or unloaded voltage gain,

$$a_v = \frac{v_o}{v_i} \Big|_{i_o'=0} = \frac{g_m v_e R_C}{v_e} = g_m R_C \quad \text{and} \quad a_i = \frac{i_o}{i_i} \Big|_{v_o=0} = \frac{g_m v_e}{v_e / r_e} = g_m r_e$$

$$a_i = \left. \frac{i_o}{i_i} \right|_{V_o=0} = \frac{g_m V_e}{V_e / r_e} = g_m r_e$$

Since,  $r_e = \frac{\alpha_o}{g_m}$ , then  $a_i = g_m \frac{\alpha_o}{g_m} \approx 1$

For the CE configuration:  $R_i = r_\pi = \frac{\beta_o}{g_m}$

For the CB configuration:  $R_i = r_e = \frac{\alpha_o}{g_m}$

$$R_{i\_CE} > R_{i\_CB}$$

$$R_{i\_CB} = \frac{\alpha_o}{\beta_o} R_{i\_CE} = \frac{1}{1+\beta_o} R_{i\_CE}$$


$$a_{i\_CB} \approx \alpha_o$$

$$a_{i\_CE} \approx \beta_o$$

$$a_{i\_CB} < a_{i\_CE}$$

$$a_{i\_CB} = \frac{\alpha_o}{\beta_o} a_{i\_CE} = \frac{1}{1+\beta_o} a_{i\_CE}$$

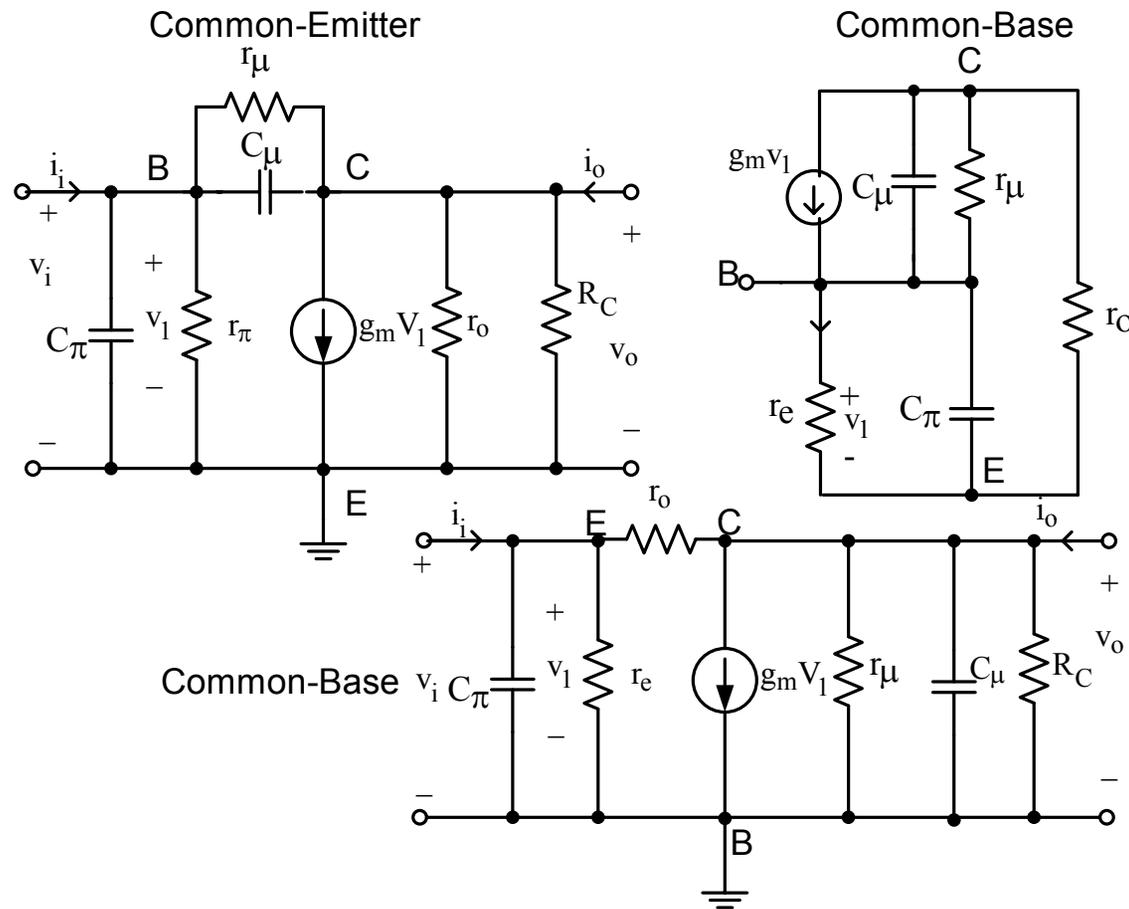In terms of i/p resistance and current gain, the CE amplifier performs better than CB.




$C_{\mu}$  is between B-C. At high freqs., capacitive components are dominant.

For CE,  $C_{\mu}$  is between i/p and o/p. Hence, at high-freqs., there will be a feedback from o/p to i/p.

For CB, i/p is at E and o/p is at C. Therefore,  $C_{\mu}$  will not cause a feedback at high-freqs. CB circuits are used for high-freq. application.

## CB configuration

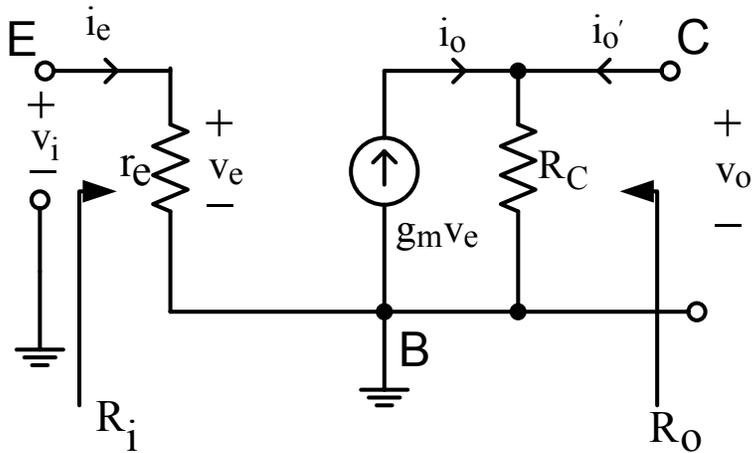

In CB configuration,  $R_o = R_C$


In CE configuration,  $R_o = R_C // r_o$

If  $R_C \rightarrow \infty$ ,  $R_{o\_CB} \rightarrow \infty$  and  $R_{o\_CE} = r_o$


Under this condition,  $R_{o\_CB} > R_{o\_CE}$

Besides using the CB as high freq. amplifier, it can also be used as a current source whose current is nearly independent of the voltage across it (i.e.  $i_o = g_m v_e$ )

## CE configuration

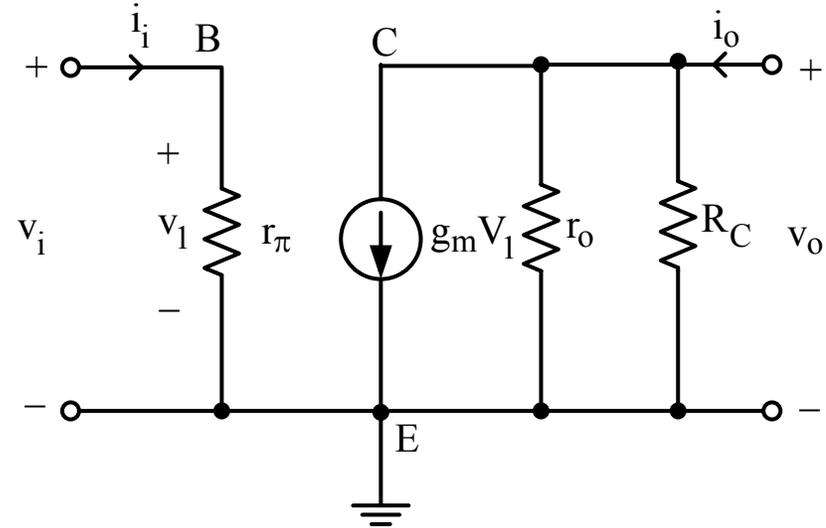

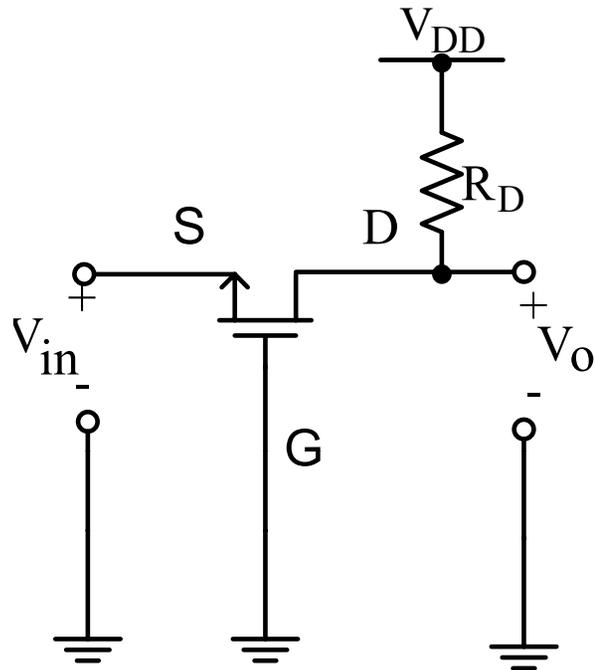
### 3.3.4 Common-gate (CG) configuration.




I/p signal is applied to the S. O/p is taken from the D. G is connected to the ac gnd.


The analysis of CG amplifiers can be simplified if the model is changed from a hybrid- $\pi$  to a T-model.

ac model for FET

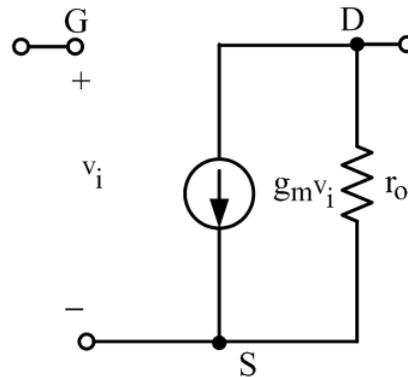

ac model for CG

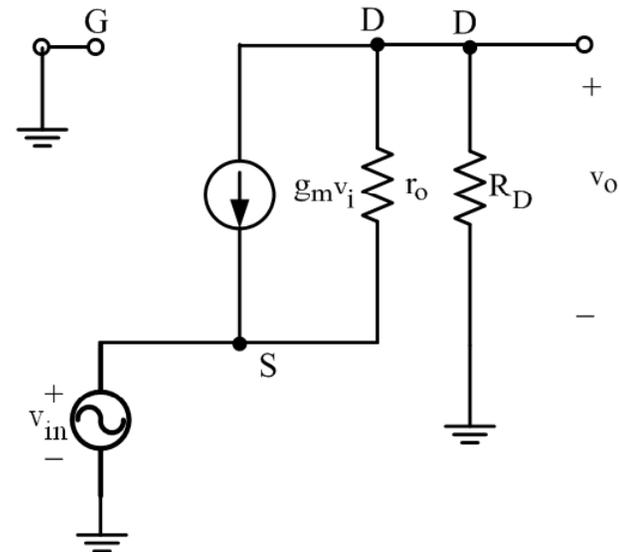

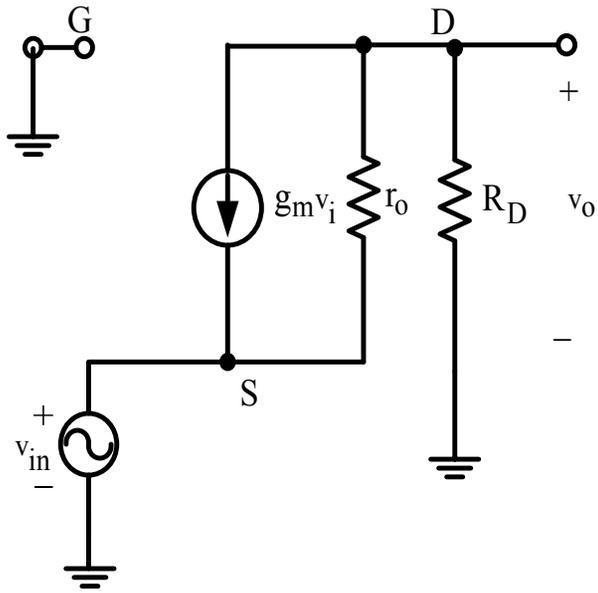




Hybrid- $\pi$  model for FET


$$G_m = \left. \frac{i_o}{v_{in}} \right|_{v_o=0} = \frac{g_m v_{sg}}{v_{sg}} = g_m$$

$$R_i = \frac{v_{in}}{i_i} = \frac{v_{sg}}{i_i} = \frac{1}{g_m}$$


$$R_o = \left. \frac{v_t}{i_t} \right|_{v_i=0} = R_D$$

T-model for CG

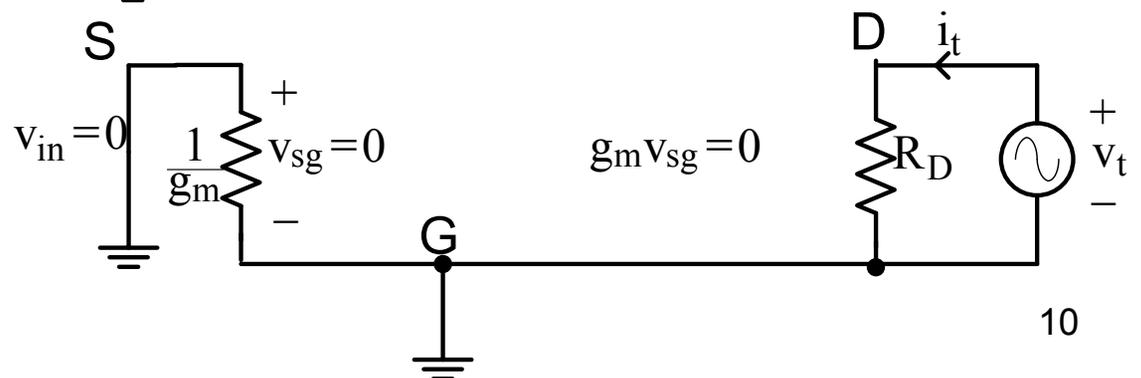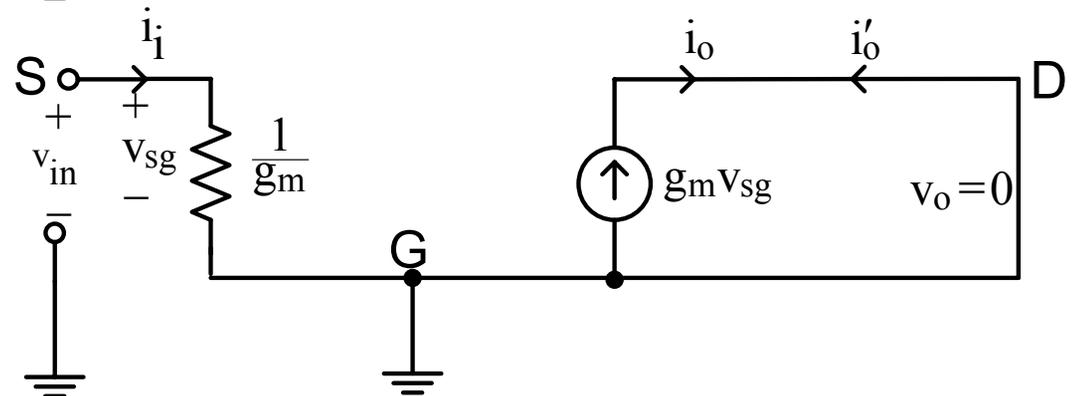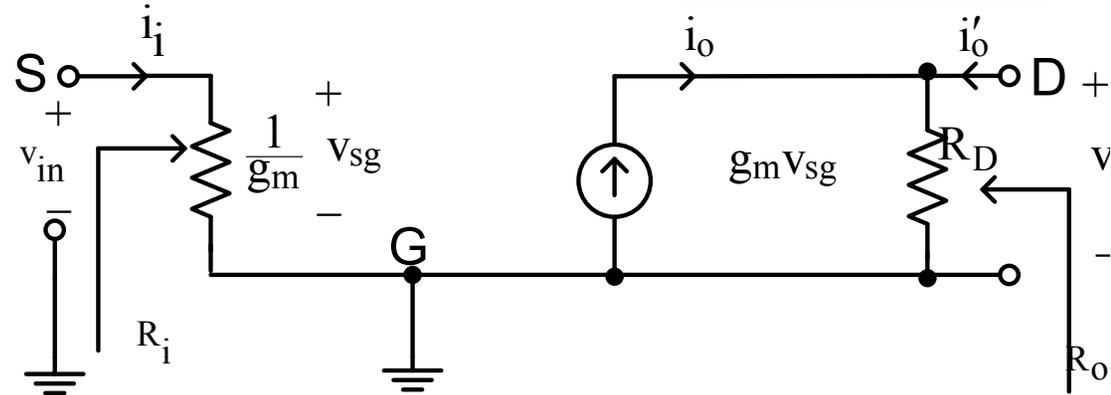

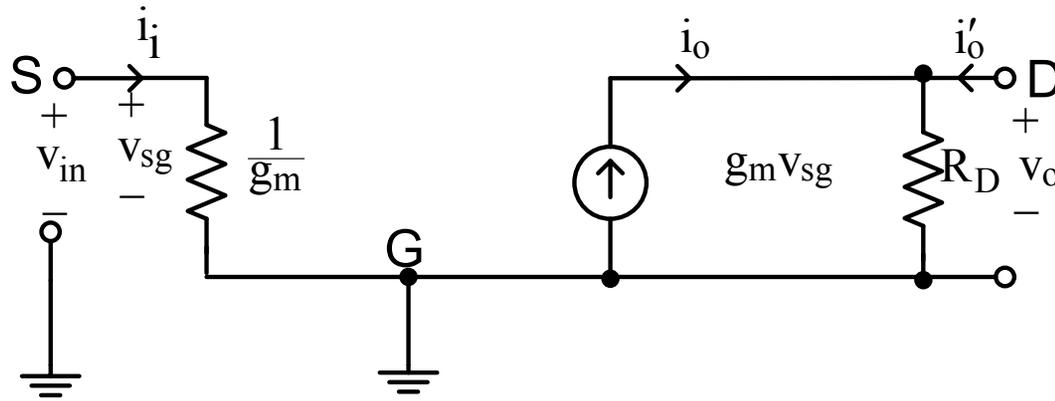


$$a_v = \frac{v_o}{V_{in}} \Big|_{i_o' = 0} = \frac{g_m V_{sg} R_D}{V_{sg}} = g_m R_D$$

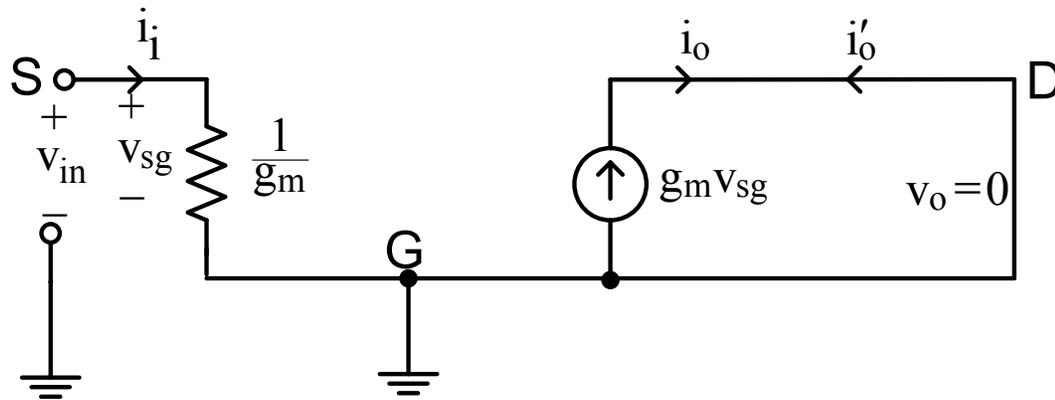


$$a_i = \frac{i_o}{i_i} \Big|_{v_o = 0} = \frac{g_m V_{sg}}{\frac{V_{sg}}{1/g_m}} = g_m \left( \frac{1}{g_m} \right) = 1$$
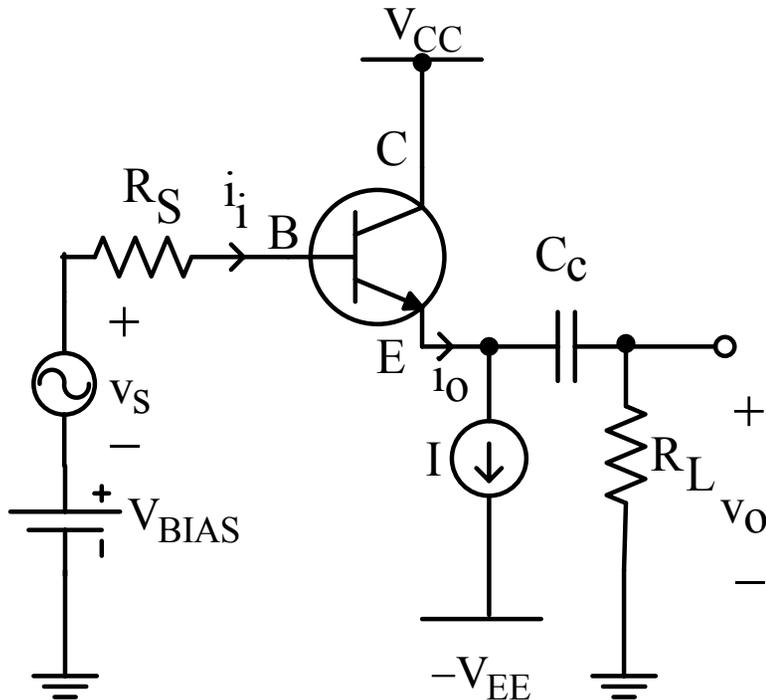
### 3.3.6 Common-collector (CC) configuration (Emitter follower)





i/p signal applied to the B.  
o/p signal taken from the E.

BJT small-signal model

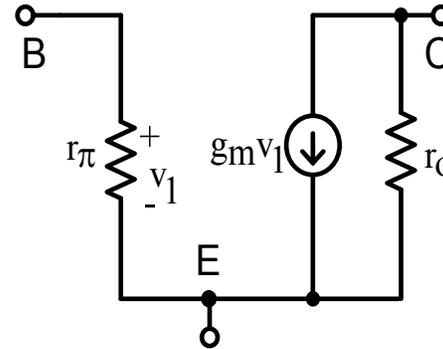

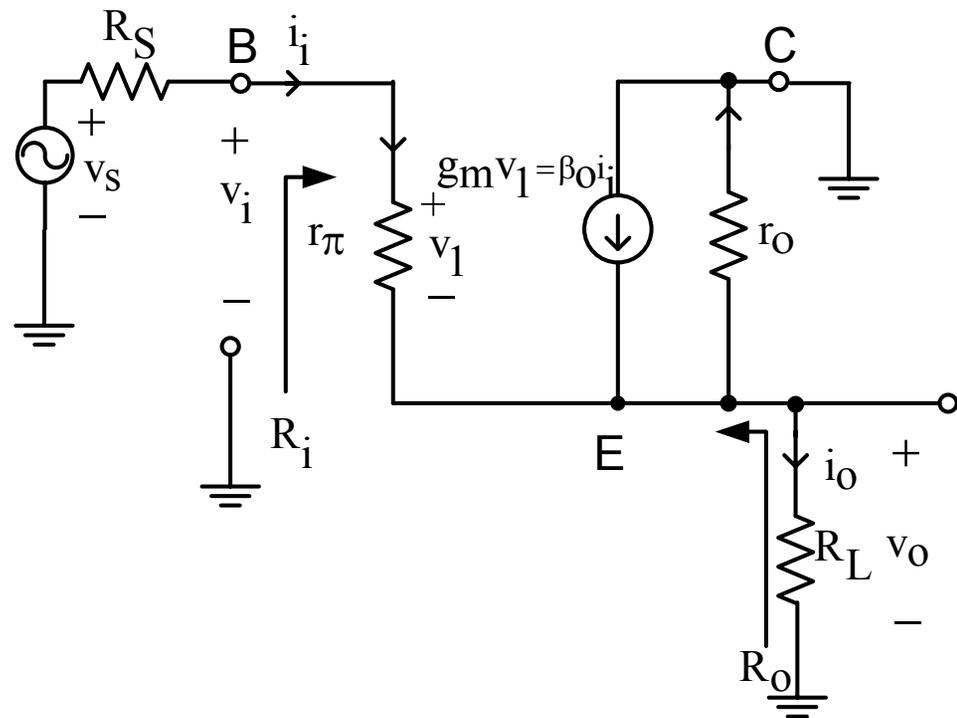Small signal/ac/hybrid- $\pi$  model for a CC circuit



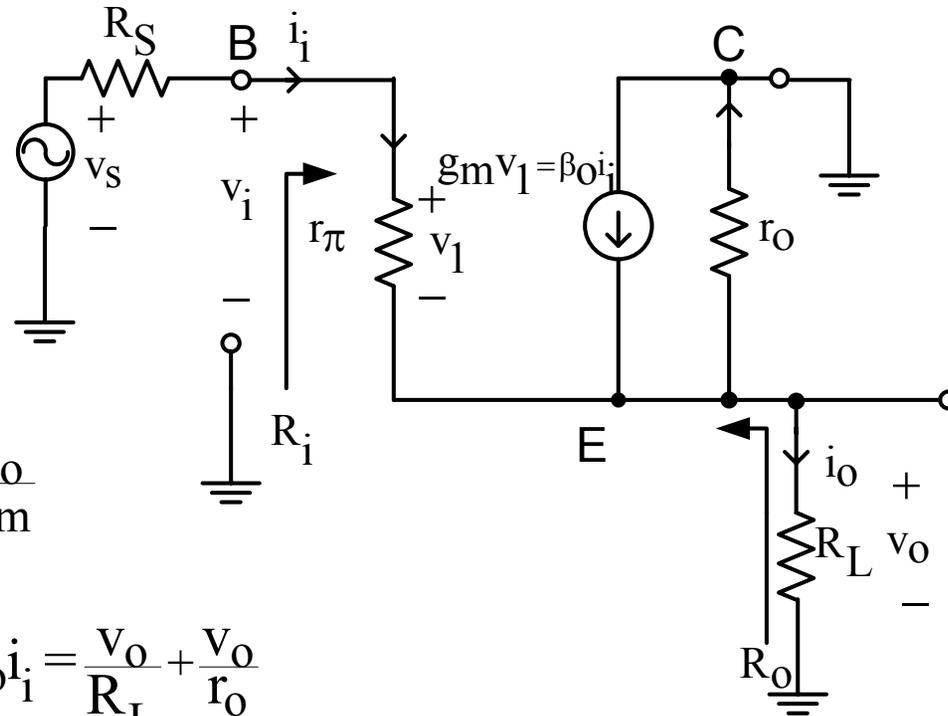

$$r_{\pi} = \frac{\beta_o}{g_m}$$

$$g_m v_1 = g_m i_i r_{\pi} = g_m i_i \frac{\beta_o}{g_m}$$

$$= \beta_o i_i$$

$$\text{KCL at node E, } i_i + \beta_o i_i = \frac{v_o}{R_L} + \frac{v_o}{r_o}$$

$$v_s = i_i (R_S + r_{\pi}) + v_o$$

$$v_i = i_i r_{\pi} + v_o$$

$$R_i = v_i / i_i$$

To determine  $R_i$ :


$$R_i = v_i / i_i$$

$$\text{KCL at node E, } i_i + \beta_o i_i = \frac{v_o}{R_L} + \frac{v_o}{r_o}$$

$$i_i(1 + \beta_o) = (v_i - i_i r_\pi) \left( \frac{1}{R_L} + \frac{1}{r_o} \right)$$

$$i_i \left[ 1 + \beta_o + r_\pi \left( \frac{1}{R_L} + \frac{1}{r_o} \right) \right] = v_i \left( \frac{1}{R_L} + \frac{1}{r_o} \right)$$
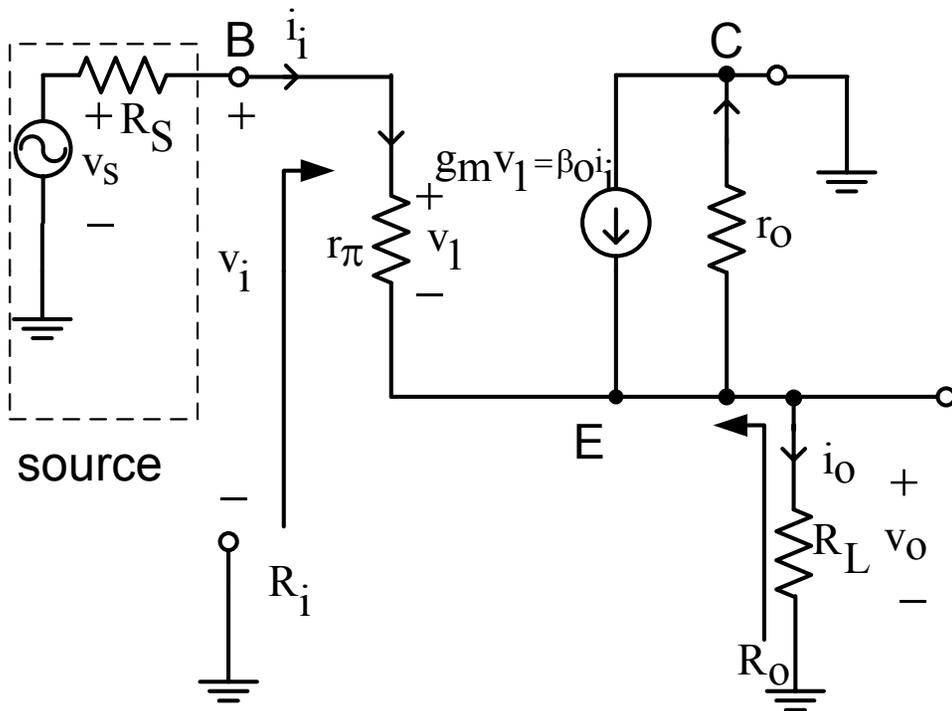
$$R_i = \frac{v_i}{i_i} = \frac{\left[ 1 + \beta_o + r_\pi \left( \frac{1}{R_L} + \frac{1}{r_o} \right) \right]}{\left( \frac{1}{R_L} + \frac{1}{r_o} \right)} \quad \leftarrow \text{enough.}$$




Hence, this circuit is not unilateral as the input resistance depends on the load resistor  $R_L$ .

$$R_i = \frac{1 + \beta_o + r_\pi \left( \frac{1}{R_L} + \frac{1}{r_o} \right)}{\left( \frac{1}{R_L} + \frac{1}{r_o} \right)}$$

For  $R_i$  with no load, i.e.  $R_L = \infty$  :

$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L = \infty}$$
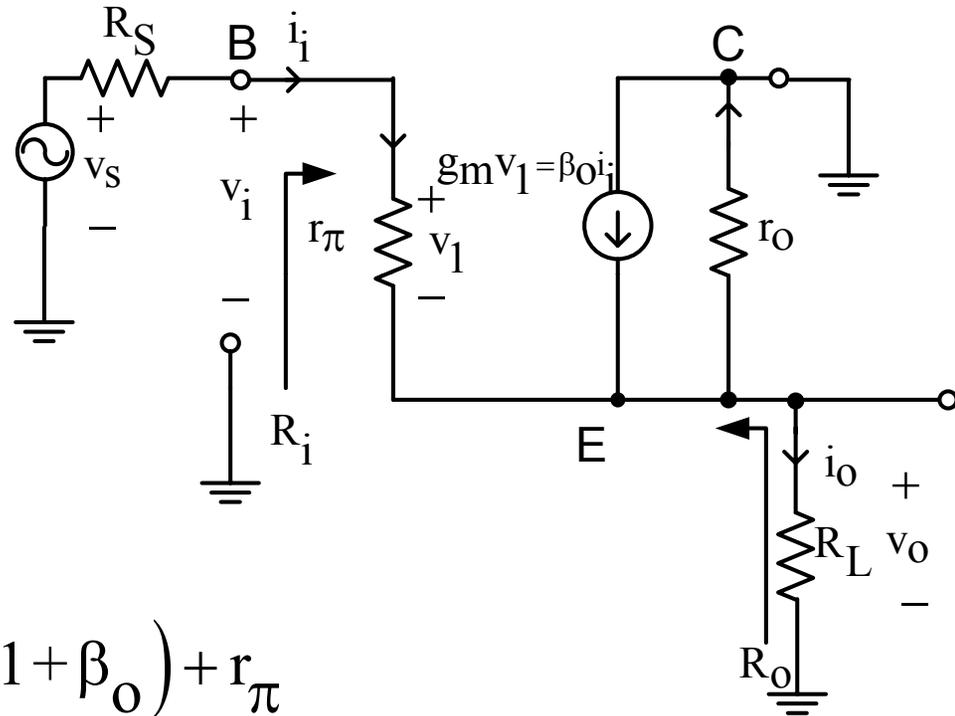
$$R_i = \left[ 1 + \beta_o + r_\pi \left( \frac{1}{r_o} \right) \right] r_o = r_o (1 + \beta_o) + r_\pi$$



To determine  $a_{v-}$ :

Overall voltage gain:  $a_v = v_o / v_s$

At node E,

$$\frac{v_s - v_o}{R_S + r_\pi} + g_m v_1 = v_o \left( \frac{1}{R_L} + \frac{1}{r_o} \right)$$

$$\frac{v_s}{R_S + r_\pi} + g_m \frac{r_\pi (v_s - v_o)}{R_S + r_\pi} = v_o \left( \frac{1}{R_L} + \frac{1}{r_o} + \frac{1}{R_S + r_\pi} \right)$$


Since  $g_m r_\pi = \beta_o$ ,

$$\frac{v_s}{R_S + r_\pi} + \frac{\beta_o (v_s - v_o)}{R_S + r_\pi} = v_o \left( \frac{1}{R_L} + \frac{1}{r_o} + \frac{1}{R_S + r_\pi} \right)$$

$$v_s \left( \frac{1}{R_S + r_\pi} + \frac{\beta_o}{R_S + r_\pi} \right) = v_o \left( \frac{1}{R_L} + \frac{1}{r_o} + \frac{1}{R_S + r_\pi} + \frac{\beta_o}{R_S + r_\pi} \right)$$

$$a_v = \frac{v_o}{v_s} = \frac{(1 + \beta_o) \left( \frac{1}{R_S + r_\pi} \right)}{\left( \frac{1}{R_L} + \frac{1}{r_o} + \frac{1 + \beta_o}{R_S + r_\pi} \right)}$$

← enough.

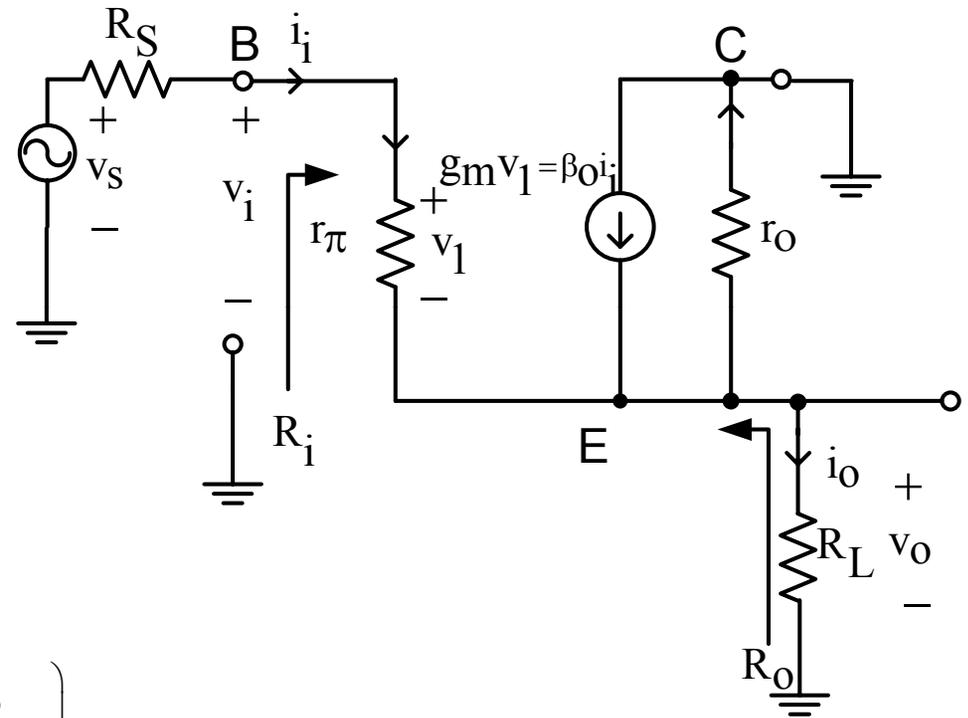

$$\begin{aligned}
 a_v = \frac{v_o}{v_s} &= \frac{(1+\beta_o)\left(\frac{1}{R_s+r_\pi}\right)}{\left(\frac{1}{R_L} + \frac{1}{r_o} + \frac{1+\beta_o}{R_s+r_\pi}\right)} \\
 &= \frac{1}{\frac{1}{(1+\beta_o)\left(\frac{1}{R_s+r_\pi}\right)}\left(\frac{1}{R_L} + \frac{1}{r_o} + \frac{1+\beta_o}{R_s+r_\pi}\right)} \\
 &= \frac{1}{\left(\frac{R_s+r_\pi}{(1+\beta_o)R_L} + \frac{R_s+r_\pi}{(1+\beta_o)r_o} + 1\right)} \\
 &= \frac{1}{\left(\frac{r_o(R_s+r_\pi) + R_L(R_s+r_\pi) + 1}{(1+\beta_o)R_L r_o}\right)} \\
 &= \frac{1}{\left(\frac{(R_s+r_\pi)(r_o+R_L) + 1}{(1+\beta_o)R_L r_o}\right)} \\
 &= \frac{1}{\left(\frac{(R_s+r_\pi)}{(1+\beta_o)R_L // r_o} + 1\right)}
 \end{aligned}$$

Open-circuit overall voltage gain,  
i.e.  $R_L = \infty$  :

$$\begin{aligned}
 a_v &= \frac{(1+\beta_o)\left(\frac{1}{R_s+r_\pi}\right)}{\left(\frac{1}{r_o} + \frac{1+\beta_o}{R_s+r_\pi}\right)} \\
 &= \frac{1}{\frac{1}{(1+\beta_o)\left(\frac{1}{R_s+r_\pi}\right)}\left(\frac{1}{r_o} + \frac{1+\beta_o}{R_s+r_\pi}\right)}
 \end{aligned}$$

Hence,

$$a_v = \frac{v_o}{v_s} \Big|_{R_L = \infty} = \frac{1}{\left(\frac{(R_s+r_\pi)}{(1+\beta_o)r_o} + 1\right)}$$



$$a_v = \frac{1}{\left( \frac{(R_s + r_\pi)}{(1 + \beta_o) R_L // r_o} + 1 \right)}$$

From the  $a_v$  expression,  $a_v$  will always be less than unity.

If  $\beta_o (R_L // r_o) \gg R_s + r_\pi$ , then  $a_v \approx 1$ . This means that the output signal follows the input signal. Hence, this topology is also known as the emitter follower.

If  $r_\pi \gg R_s$ ,  $\beta_o \gg 1$  and  $r_o \gg R_L$ , then  $a_v = \frac{1}{\left( \frac{r_\pi}{(\beta_o) R_L} + 1 \right)}$

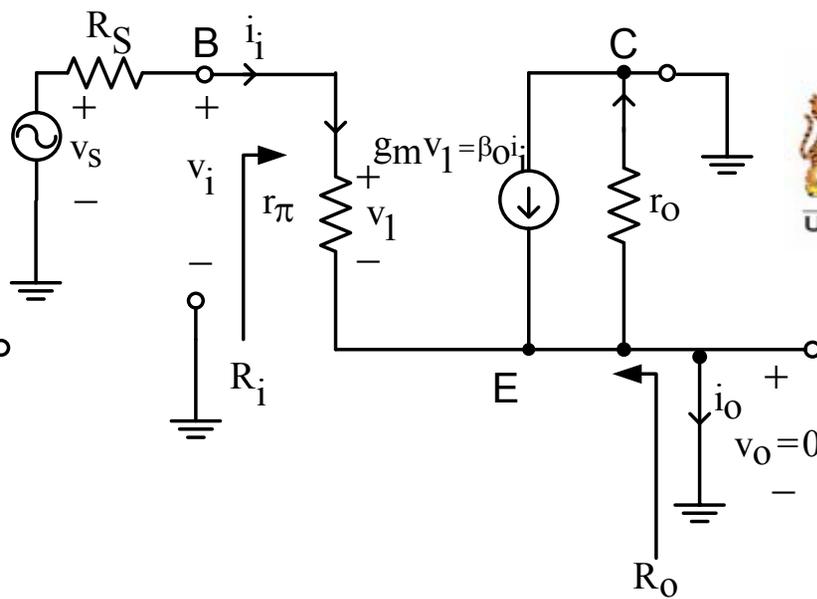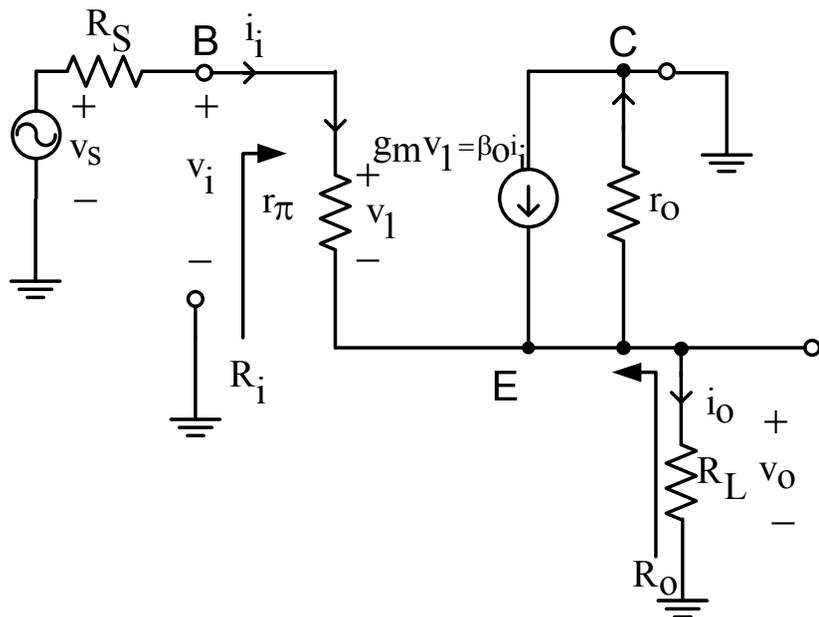Since  $g_m r_\pi = \beta_o$ , then  $a_v = \frac{1}{\left( \frac{1}{g_m R_L} + 1 \right)} = \frac{g_m R_L}{(1 + g_m R_L)}$



To determine the short circuit current gain,  $a_{i-}$ :

$$a_i = \left. \frac{i_o}{i_i} \right|_{v_o=0}$$

$$i_o = i_i + g_m v_1$$

$$v_1 = i_i r_\pi$$

$$i_o = i_i + g_m i_i r_\pi$$


$$a_i = \frac{i_o}{i_i} = \frac{i_i (1 + g_m r_\pi)}{i_i} = 1 + g_m r_\pi = 1 + \beta_o$$

or

$$g_m v_1 = g_m i_i r_\pi = \beta_o i_i$$


$$i_o = i_i + \beta_o i_i = i_i (1 + \beta_o)$$


$$a_i = i_o / i_i = 1 + \beta_o$$

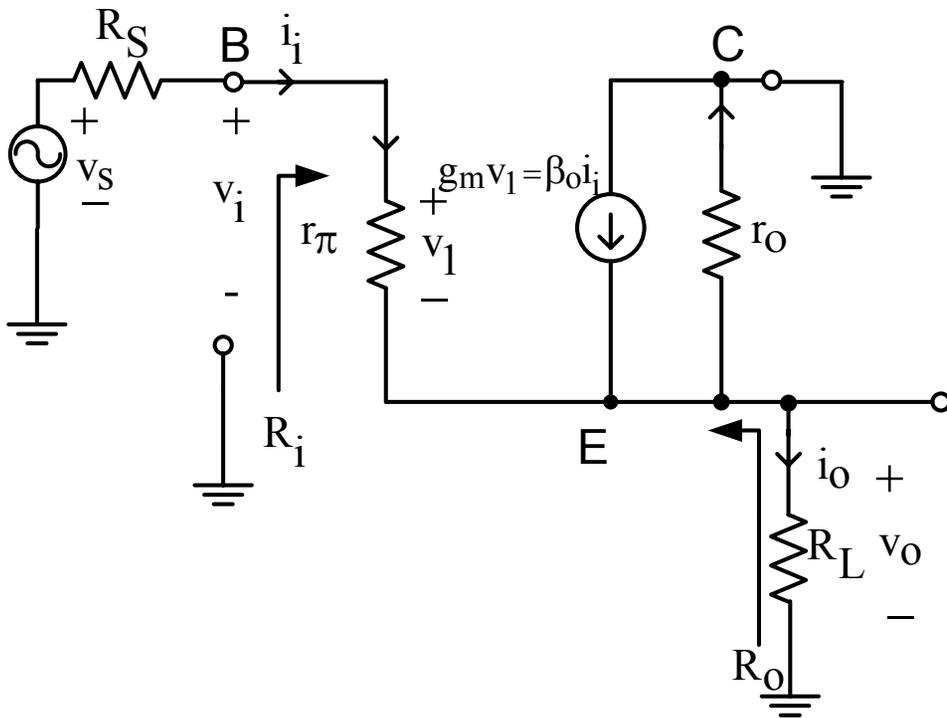

To determine  $R_o$  :

$$R_o = \frac{v_t}{i_t} \Big|_{v_s=0}$$

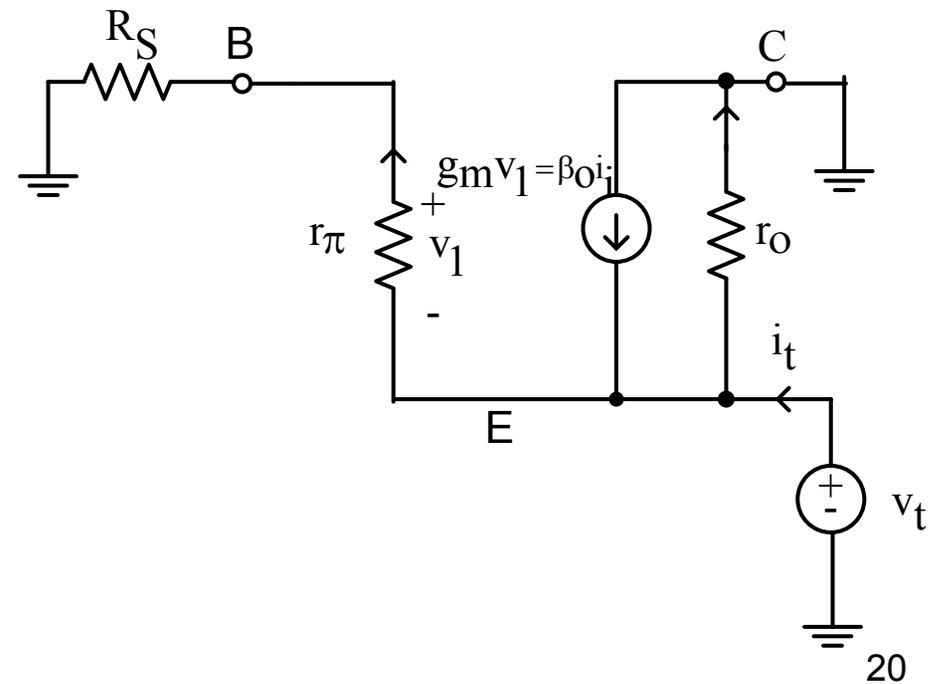

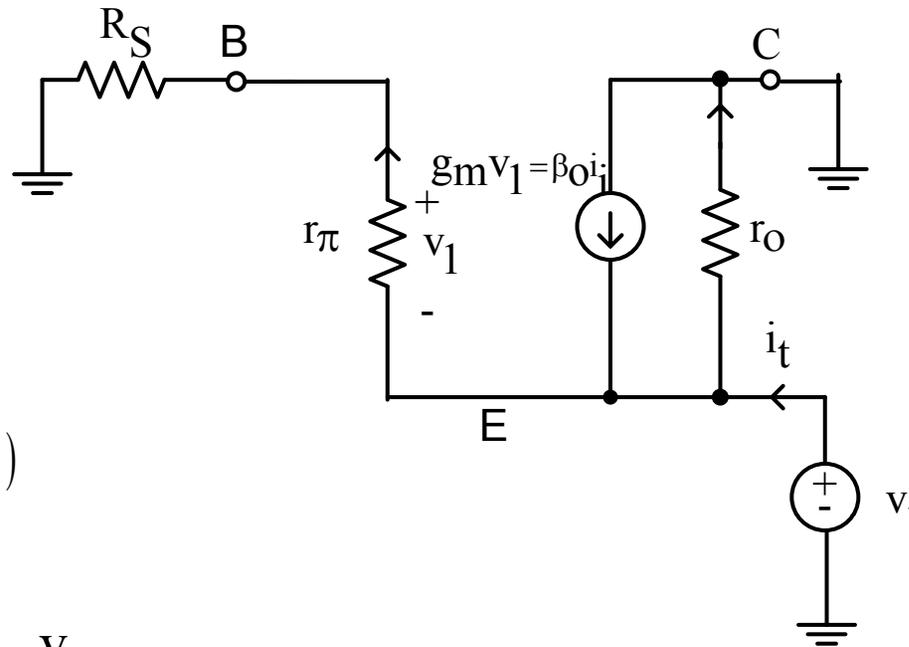

$$v_1 = -\frac{r_\pi}{R_S + r_\pi}(v_t)$$

At node E,

$$i_t + g_m v_1 = \frac{v_t}{r_o} + \frac{v_t}{R_S + r_\pi}$$

$$i_t = \frac{v_t}{r_o} + \frac{v_t}{R_S + r_\pi} + \frac{g_m r_\pi v_t}{R_S + r_\pi}$$

$$R_o = \frac{v_t}{i_t} = \frac{1}{\frac{1}{r_o} + \frac{1 + \beta_o}{R_S + r_\pi}} \quad \leftarrow \text{enough}$$

$$= \left( \frac{R_S + r_\pi}{1 + \beta_o} \right) \parallel r_o$$

Hence, this circuit is not unilateral as the output resistance depends on the source resistance  $R_S$ .

$$R_o = \left( \frac{R_S + r_\pi}{1 + \beta_o} \right) \parallel r_o$$

$$= \left( \frac{R_S}{1 + \beta_o} + \frac{r_\pi}{1 + \beta_o} \right) \parallel r_o$$

$$\text{If } \beta_o \gg 1, \text{ then } R_o = \left( \frac{R_S}{1 + \beta_o} + \frac{r_\pi}{\beta_o} \right) \parallel r_o$$

$$\text{Since } g_m r_\pi = \beta_o, \text{ then } R_o = \left( \frac{R_S}{1 + \beta_o} + \frac{1}{g_m} \right) \parallel r_o$$

$$\text{If } r_o \gg \frac{R_S}{1 + \beta_o} + \frac{1}{g_m}, \text{ then } R_o = \frac{R_S}{1 + \beta_o} + \frac{1}{g_m}$$


$$R_o = \frac{R_S}{1 + \beta_o} + \frac{1}{g_m}$$

$$R_i = r_\pi + (1 + \beta_o)(R_L \parallel r_o)$$


$$a_v = \frac{1}{1 + \frac{R_S + r_\pi}{(1 + \beta_o)(R_L \parallel r_o)}} \approx 1$$

The emitter follower has high i/p resistance, low o/p resistance and near-unity voltage gain. Therefore, it is widely used as an impedance transformer to reduce loading of a preceding signal source by the i/p impedance of a following stage.

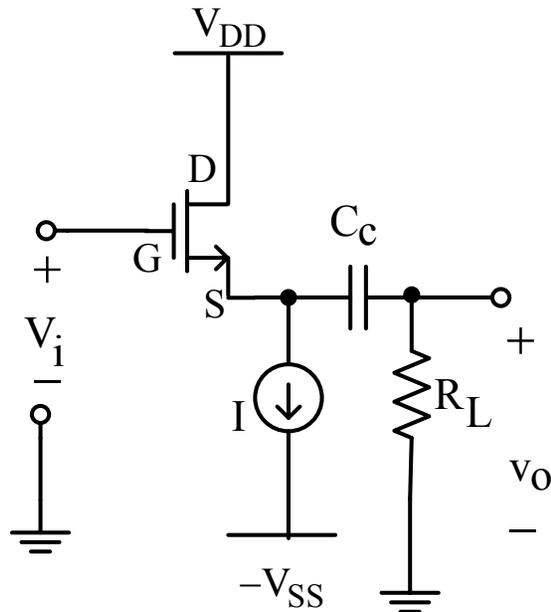
# Common-drain configuration (source follower)



Small-signal for FET

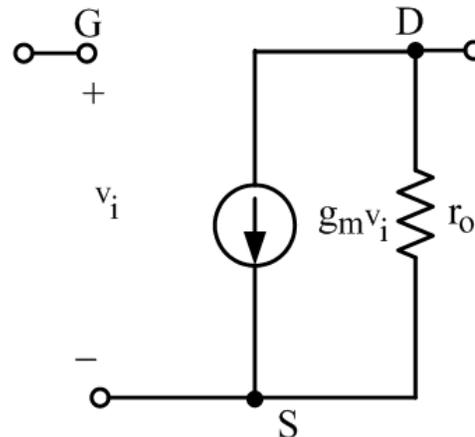

Small-signal for CD

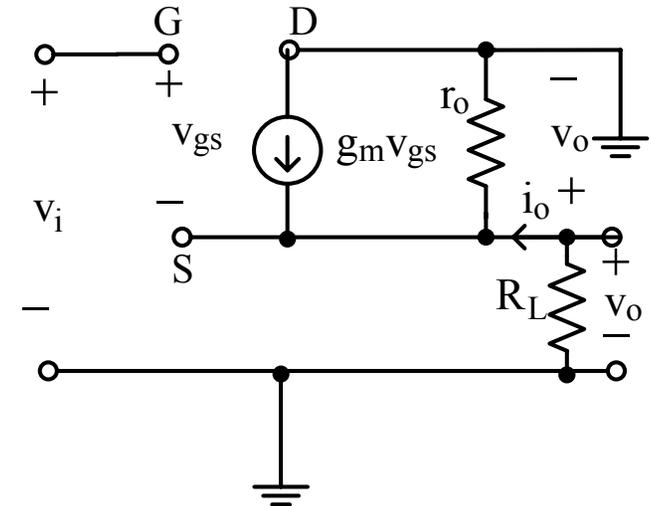

I/p signal applied to G. O/p signal taken from S.  
To determine the open-circuit voltage gain,  $a_v$  :

$$a_v = \left. \frac{v_o}{v_i} \right|_{R_L = \infty, i_o = 0}$$


From KVL around the i/p loop,


$$-v_i + v_{gs} + v_o = 0$$

$$v_i = v_{gs} + v_o$$

KCL at the o/p node:
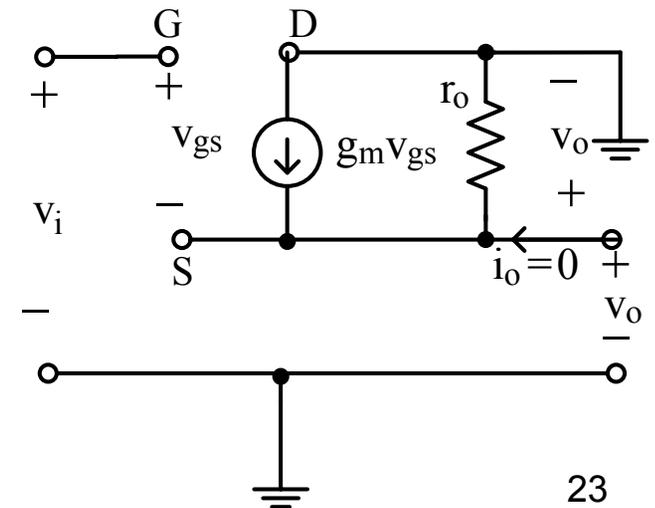
$$g_m v_{gs} = v_o / r_o \quad \text{for } R_L = \infty$$



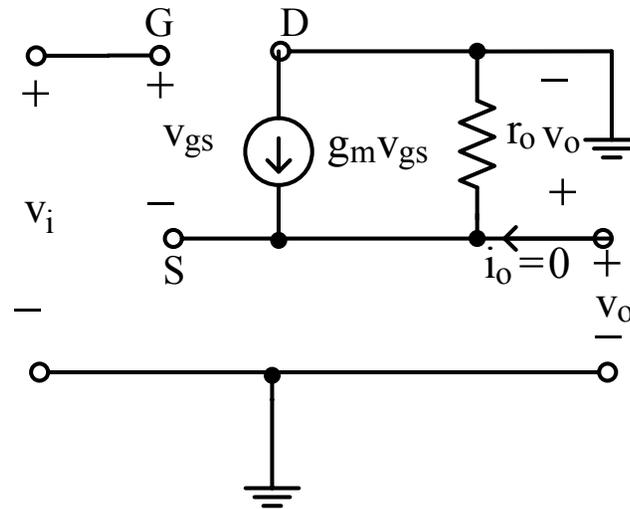

$$g_m V_{gs} = v_o / r_o$$

$$v_i = v_{gs} + v_o$$

$$g_m v_i = v_o \left( \frac{1}{r_o} + g_m \right)$$

$$a_v = \frac{v_o}{v_i} = \frac{g_m}{\left( \frac{1}{r_o} + g_m \right)} \quad \leftarrow \text{enough}$$

$$= \frac{g_m r_o}{1 + g_m r_o}$$

$$a_v = \frac{g_m}{\left( \frac{1}{r_o} + g_m \right)}$$


If  $r_o \rightarrow \infty$ , then

$$a_v = \frac{g_m}{g_m} = 1$$


If  $r_o$  is finite, this gain is  $< 1$ .


To determine  $R_o$  :

$$R_o = \left. \frac{v_t}{i_t} \right|_{v_i=0}$$

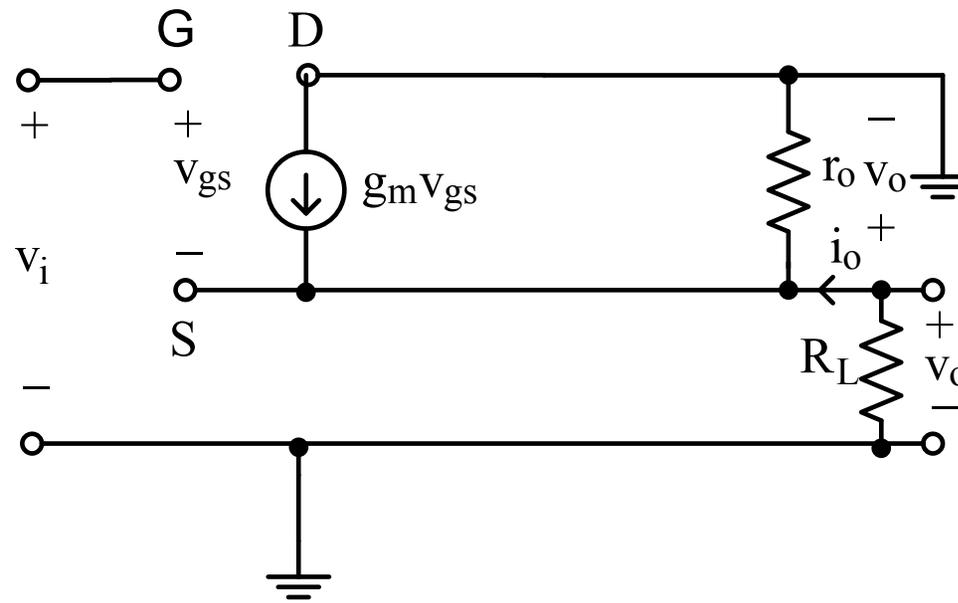

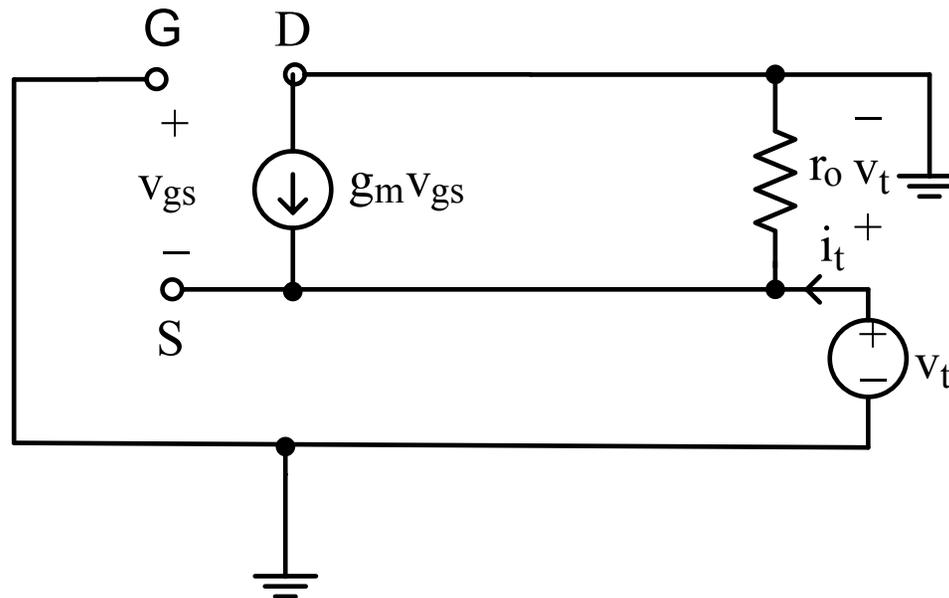The output resistance can be calculated by setting  $v_i = 0$  and driving the output with a voltage source  $v_t$ .



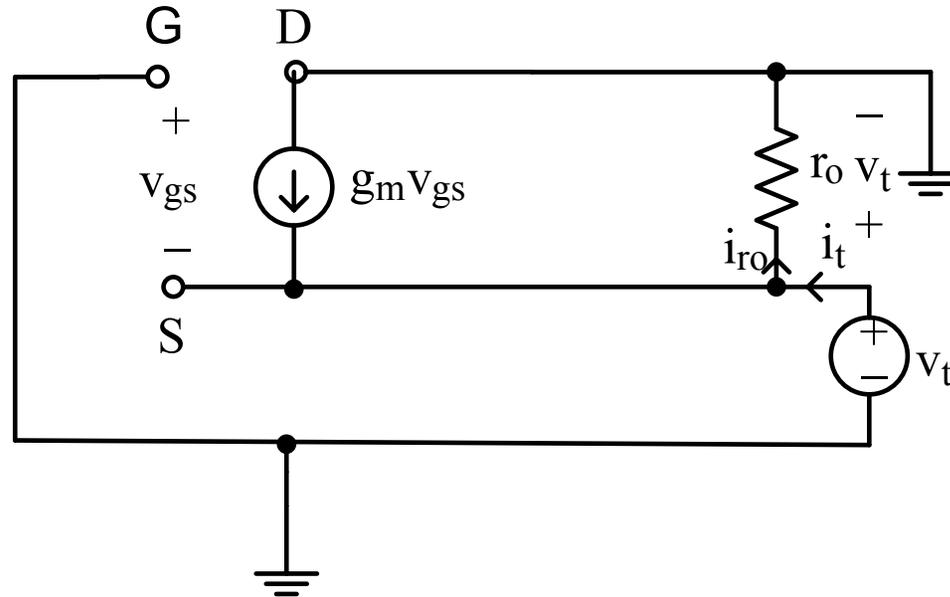

$$V_{gs} = -V_t$$

$$V_{gs} = V_g - V_s = -V_s$$

At the S node,

$$g_m V_{gs} + i_t = \frac{V_t}{r_o}$$

$$i_t = \left( \frac{1}{r_o} + g_m \right) V_t$$

$$R_o = \frac{V_t}{i_t} = \frac{1}{\left( \frac{1}{r_o} + g_m \right)}$$

If  $r_o \rightarrow \infty$ ,

$$R_o = \frac{1}{g_m}$$

	CE	CB	CC
$R_i$	$r_\pi = \frac{\beta_o}{g_m}$	$r_e = \frac{1}{g_m + \frac{1}{r_\pi}}$ $= \frac{1}{g_m \left(1 + \frac{1}{\beta_o}\right)}$ $= \frac{\alpha_o}{g_m}$	$r_\pi + (\beta_o + 1)(R_L \parallel r_o)$
$G_m$	$g_m$	$g_m$	$\frac{1 + \beta_o}{R_S + r_\pi}$
$R_o$	$R_C \parallel r_o$	$R_C$	$\frac{R_S + r_\pi}{1 + \beta_o} \parallel r_o$
$a_v$	$-g_m(R_C \parallel r_o)$	$g_m R_C$	$\frac{1}{1 + \frac{R_S + r_\pi}{(1 + \beta_o)r_o \parallel R_L}}$
$a_i$	$\beta_o$	$g_m r_e = \alpha_o$	$1 + \beta_o$

$$r_\pi = v_i / i_b$$

$$= v_i \beta_o / i_c$$

Since  $g_m = i_c / v_i$ ,

$$r_\pi = \beta_o / g_m$$

$$= \beta_o V_T / I_C$$

	CE	CB	CC
$R_i$	medium	↓	↑
$R_o$	medium	↑	↓
$a_v$	↑	↑	$\leq 1$
$a_i$	↑	$\leq 1$	↑
$a_p = a_v a_i$	↑	$\approx a_v$	$\approx a_i$
i/p-o/p phase shift (voltage)	$180^\circ$	$0^\circ$	$0^\circ$

	CS	CG	CD
$R_i$	$\infty$	$\frac{1}{g_m}$	$\infty$
$G_m$	$g_m$	$g_m$	$g_m$
$R_o$	$R_D \parallel r_o$	$R_D$	$\frac{1}{g_m + \frac{1}{r_o}}$
$a_v$	$-g_m(R_D \parallel r_o)$	$g_m R_D$	$\frac{g_m r_o}{1 + g_m r_o + \frac{r_o}{R_L}}$
$a_i$	$\infty$	1	$\infty$

Open-circuit voltage gain ( $R_L = \infty$ ),

$$a_{vo} = \frac{V_o}{V_i} = \frac{V_o}{i_o} \times \frac{i_o}{V_i} = R_o G_m$$




Short-circuit current gain ( $R_L = 0$ ),

$$a_{is} = \frac{i_o}{i_i} = \frac{i_o}{V_i} \times \frac{V_i}{i_i} = R_i G_m$$

	CS	CG	CD
$R_i$	$\infty$	↓	$\infty$
$R_o$	medium	↑	↓
$a_v$	↑	↑	$< 1$
$a_i$	$\infty$	1	$\infty$
$a_p = a_v a_i$	$\infty$	$\approx a_v$	$\infty$
i/p-o/p phase shift	180° (voltage)	0°	0°

## To generate a T-model for a BJT from a hybrid- $\pi$ model .

The analysis of CB amplifiers can be simplified if the model is changed from a hybrid- $\pi$  to a T-model.

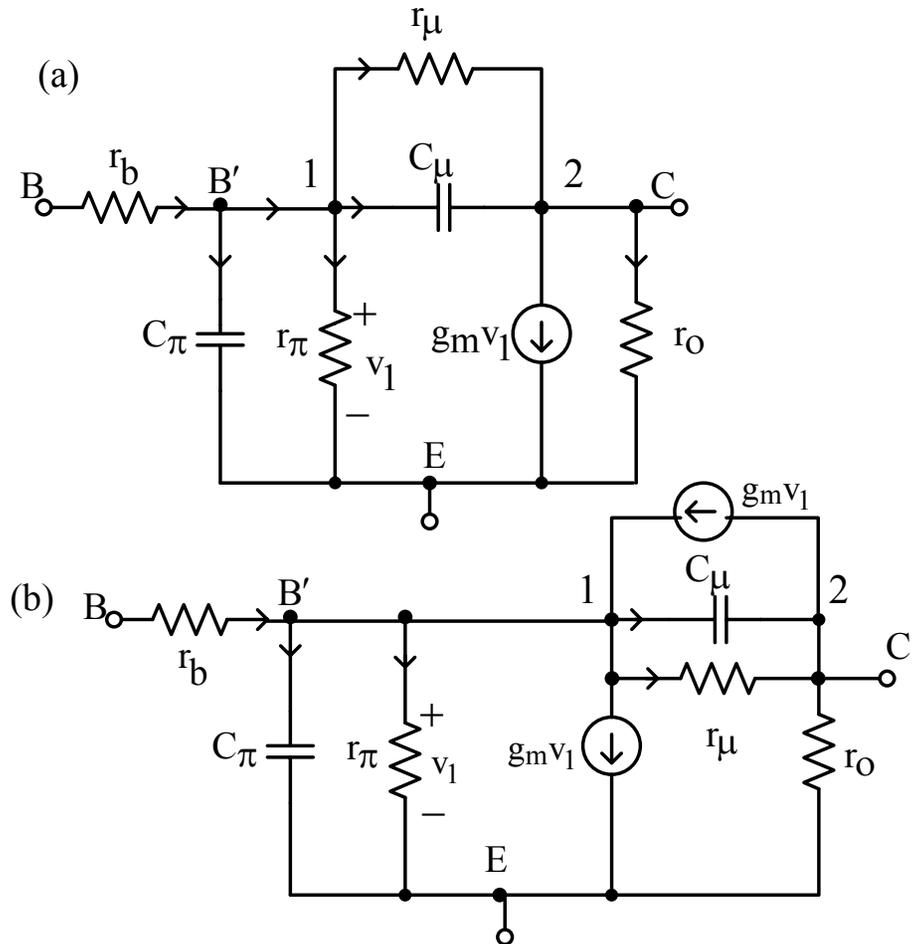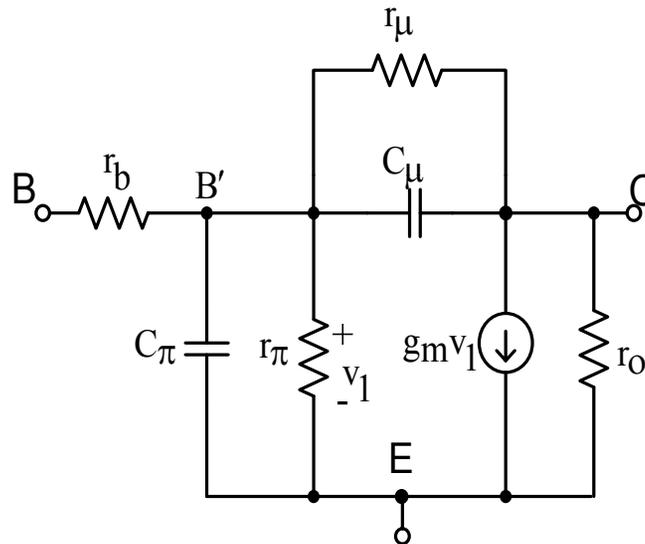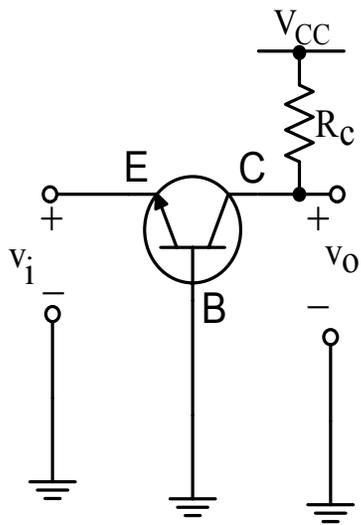


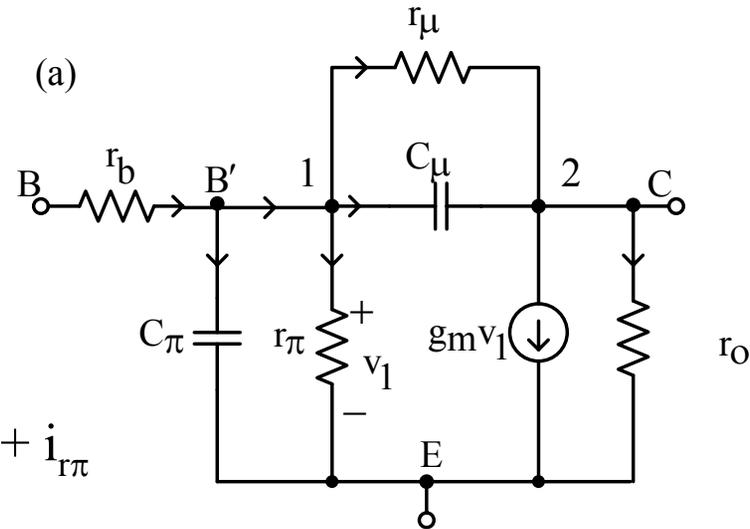


Figure (a):

Node 1:  $i_{rb} = i_{c\mu} + i_{r\mu} + i_{c\pi} + i_{r\pi}$

Node 2:  $i_{c\mu} + i_{r\mu} = g_m v_1 + i_{ro}$

Figure (b):

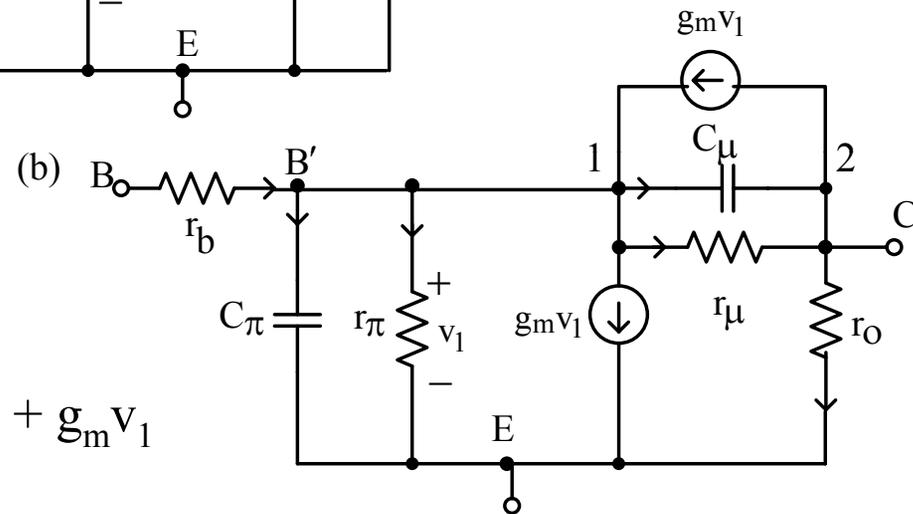


Node 1:  $i_{rb} + g_m v_1 = i_{c\mu} + i_{r\mu} + i_{c\pi} + i_{r\pi} + g_m v_1$

$i_{rb} = i_{c\mu} + i_{r\mu} + i_{c\pi} + i_{r\pi}$

Node 2:  $i_{c\mu} + i_{r\mu} = g_m v_1 + i_{ro}$

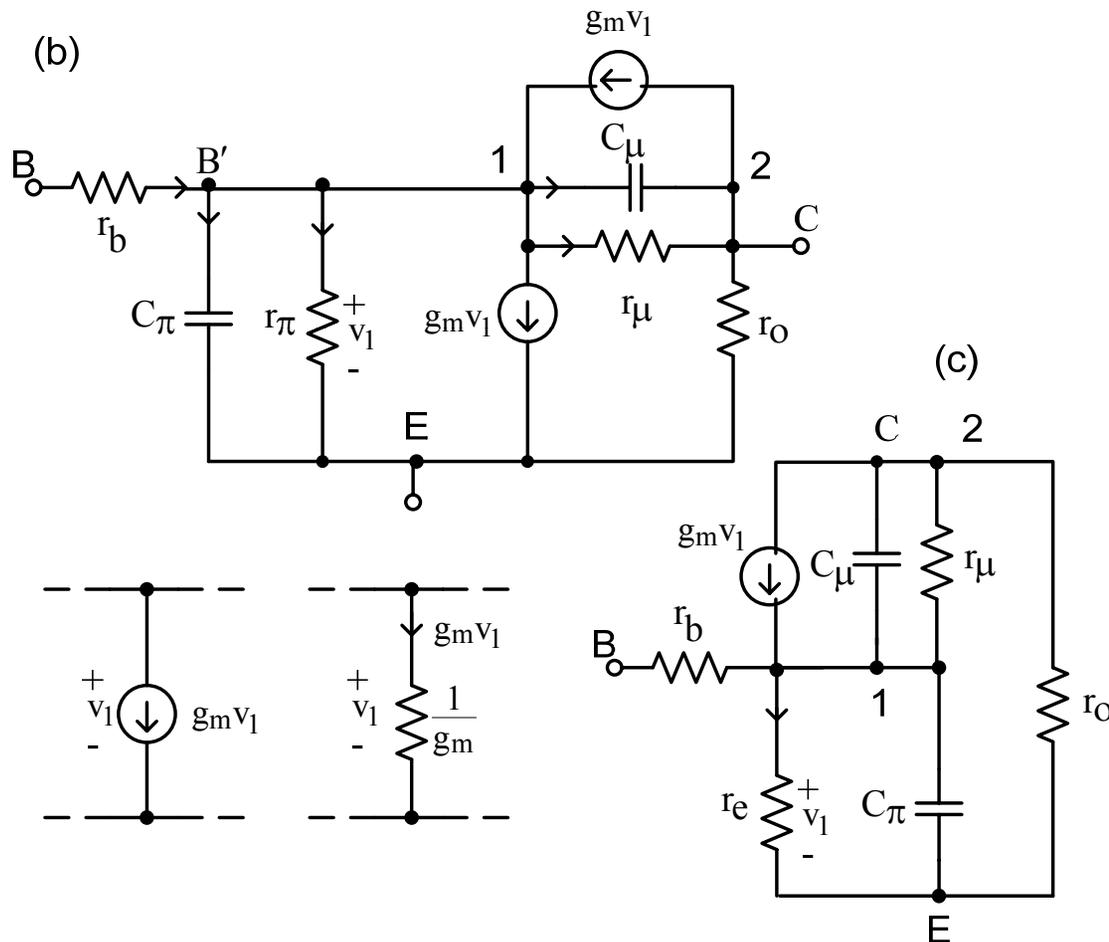
Hence, the change from Figure (a) to Figure (b) does not affect the current flowing in the B.




$$\begin{aligned}
 r_e &= r_\pi \parallel \frac{1}{g_m} \\
 &= \frac{r_\pi \left( \frac{1}{g_m} \right)}{r_\pi + \frac{1}{g_m}} \\
 &= \frac{r_\pi}{1 + g_m r_\pi}
 \end{aligned}$$

$$r_{\pi} = \frac{\beta_o}{g_m}$$

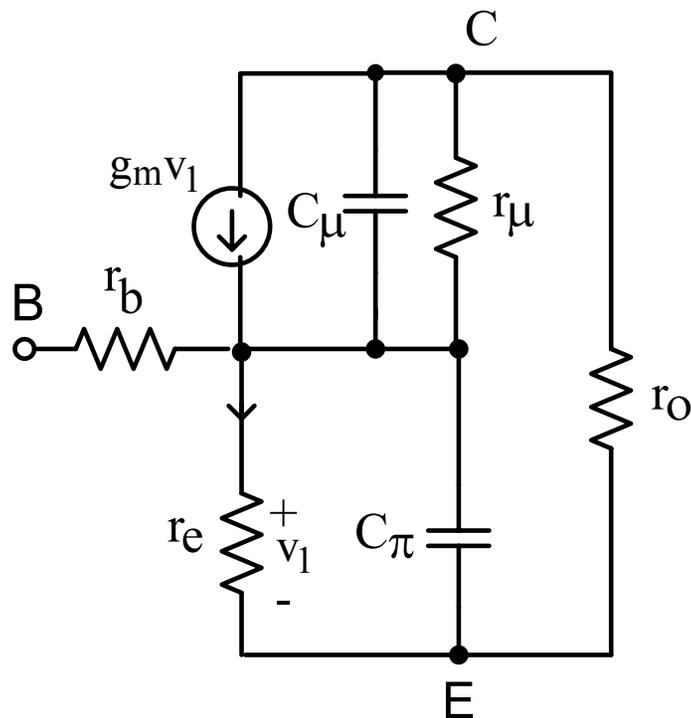
$$r_e = \frac{r_{\pi}}{1 + g_m r_{\pi}} = \frac{\beta_o}{g_m \left( 1 + g_m \frac{\beta_o}{g_m} \right)} = \frac{1}{g_m} \frac{\beta_o}{1 + \beta_o} = \frac{\alpha_o}{g_m}$$



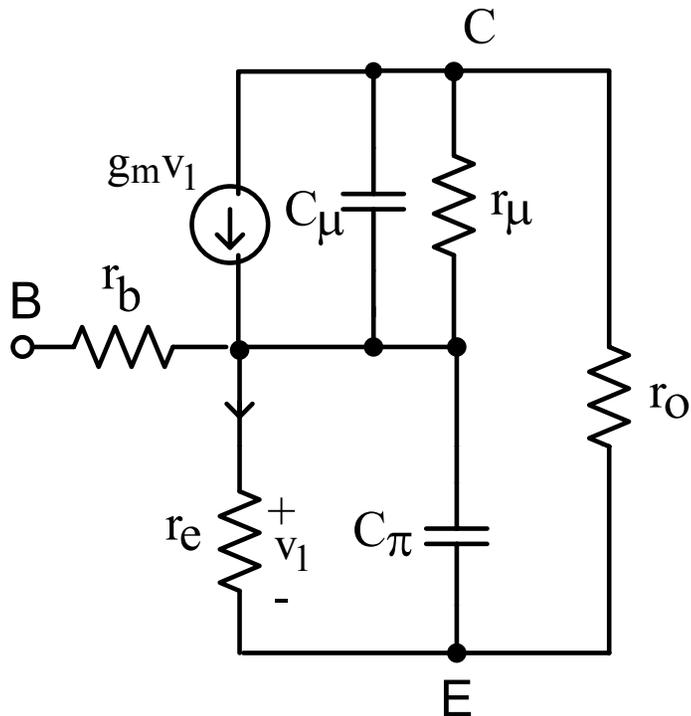At low freqs.,  $C_{\pi}$  and  $C_{\mu}$  are neglected. Assume  $r_b \approx 0$  and  $r_o \approx \infty$ . Hence,  $r_{\mu} \approx \infty$  as  $r_{\mu} = \beta_o r_o$ .



The T-model at low freq.:

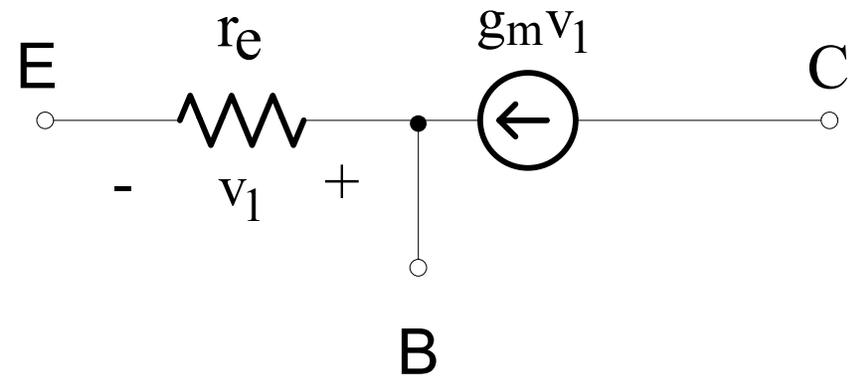


When  $r_o \approx \infty$ , the circuit is said to be unilateral as there is no feedback from o/p (C) to i/p (E).
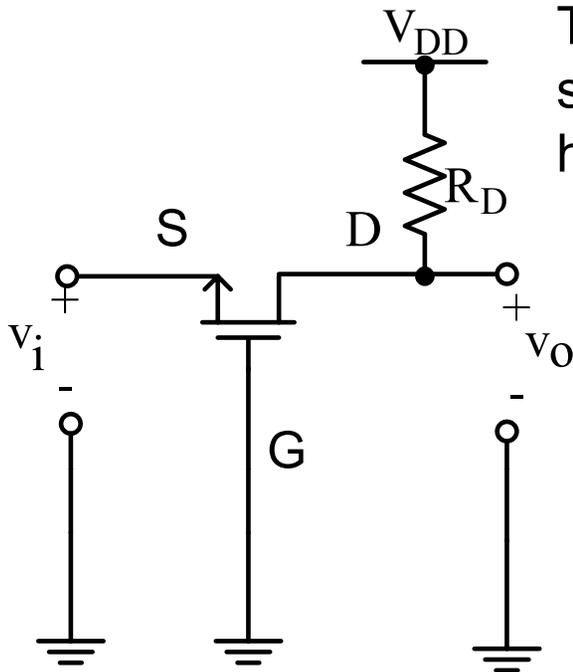
# Generating a T-model for an FET from a hybrid- $\pi$ model.




The analysis of CG amplifiers can be simplified if the model is changed from a hybrid- $\pi$  to a T-model.





CG amplifier

hybrid- $\pi$  of an FET

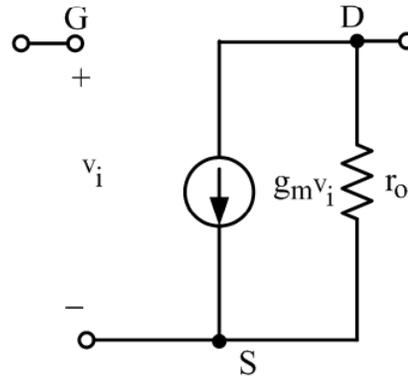

hybrid- $\pi$  of a CG

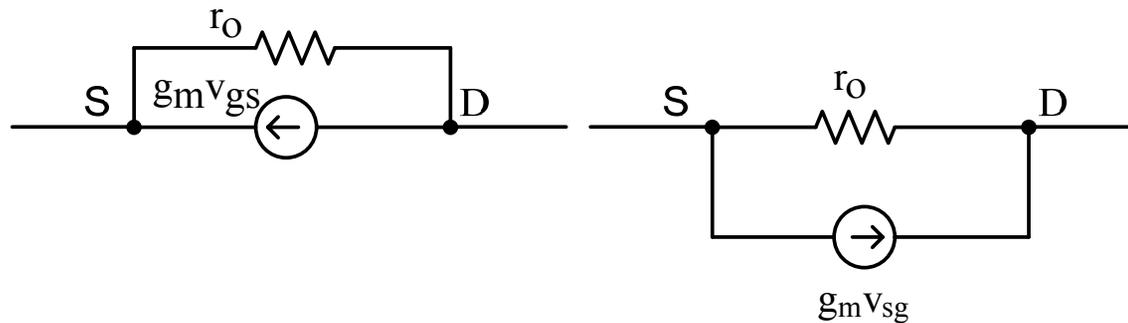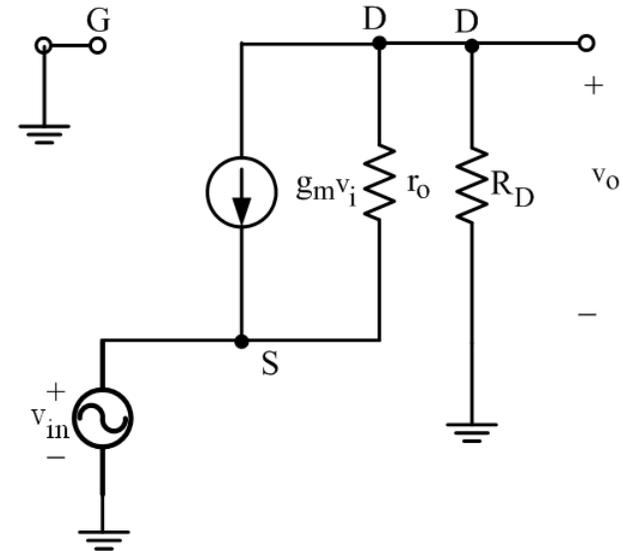

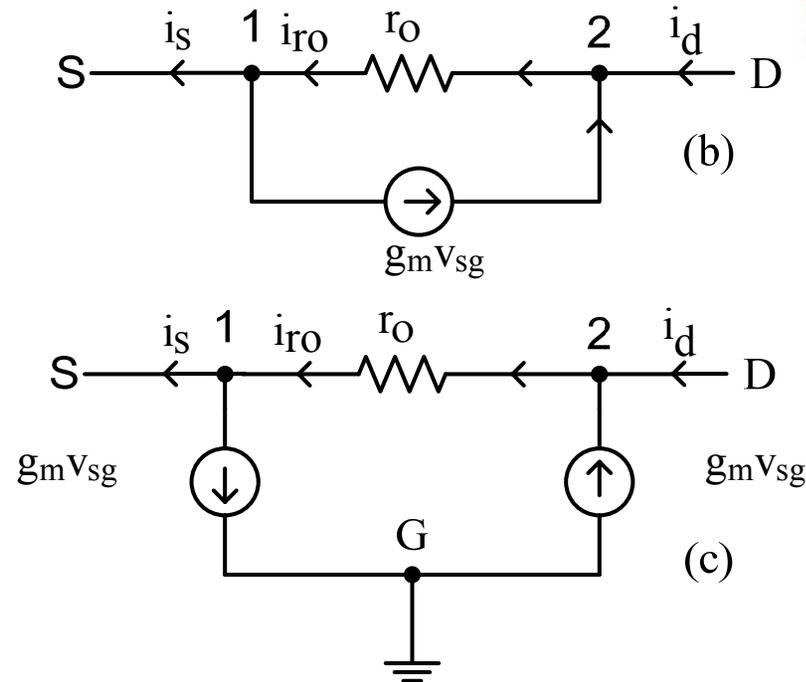
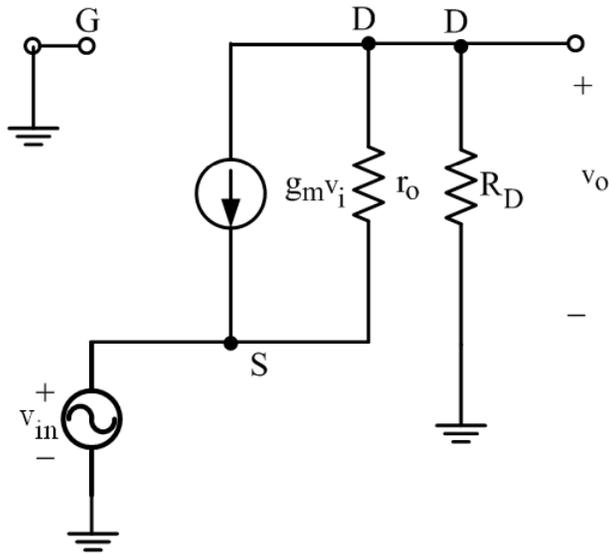


Figure (b):

Node 1:  $i_{r_o} = i_s + g_m v_{sg}$



Node 2:  $i_d + g_m v_{sg} = i_{r_o}$

Figure (c):


Node 1:  $i_{r_o} = i_s + g_m v_{sg}$

Node 2:  $i_d + g_m v_{sg} = i_{r_o}$

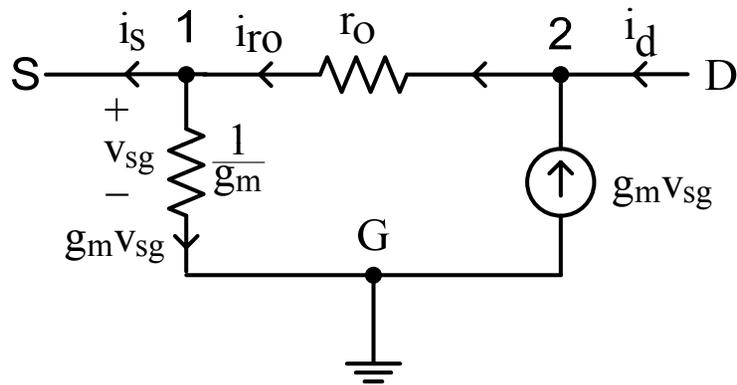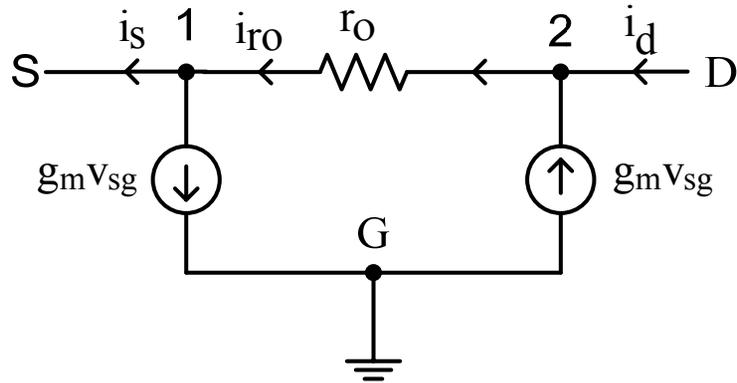Equal currents are pushed into and pulled out of the G as the equations that describe the operation of the circuits are identical.



For  $r_o \rightarrow \infty$  :

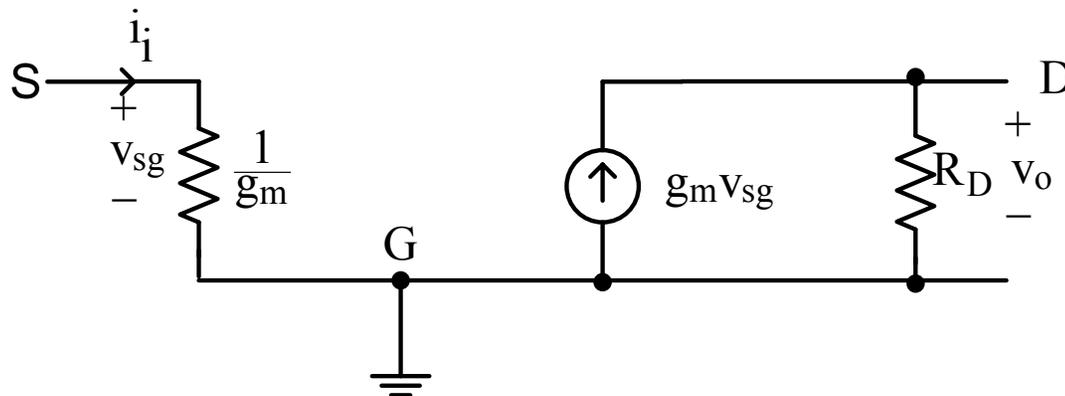

If  $r_o$  is finite, the circuit is bilateral because of the feedback. If  $r_o \rightarrow \infty$ , the cct. is unilateral.

