

CHAPTER 1: BASIC CONCEPTS

1.1 Introduction

- An electrical circuit is an interconnection of several elements. It is a mathematical model that approximates the behavior of an actual electrical system.
- Circuit theory is the study of *analyzing* an electrical circuit.

1.2 International System of Units (SI)

- SI is an international measurement language.
- There are six principal units.

Quantity	Basic unit	Symbol
Length	meter	m
Mass	kilogram	kg
Time	second	s
Electric current	ampere	A
Thermodynamic temperature	kelvin	K
Luminous intensity	candela	cd

- The SI units also uses prefixes based on the power of 10 to relate larger and smaller units to the basic unit.


Multiplier	Prefix	Symbol
10^{18}	exa	E
10^{15}	peta	P
10^{12}	tera	T
10^9	giga	G
10^6	mega	M
10^3	kilo	k
10^2	hecto	h
10	deka	da
10^{-1}	deci	d
10^{-2}	centi	c
10^{-3}	mili	m
10^{-6}	micro	μ
10^{-9}	nano	n
10^{-12}	pico	p
10^{-15}	femto	f
10^{-18}	atto	a

1.3 Charge and Current

- Most basic quantity in an electric circuit – *electric charge*

Charge, e , is an electrical property of the atomic particles of which matter consists, measured in coulomb (C)

- Elementary physics – all matter is made of atoms that consists of electrons, protons and neutrons.
- The charge, e of electron is negative and equal in magnitude to 1.602×10^{-19} C.
- A proton carries a positive charge of the same magnitude as the electron.
- Notes on electric charge:
 - (i) Coulomb is a large unit for charges. $1\text{C} = 1/(1.602 \times 10^{-19}) = 6.24 \times 10^{18}$ electrons.
 - (ii) Charges are integral multiples of the electron charge.
 - (iii) The *law of conservation of charge* – charge can neither be created nor destroyed, only transferred.
- Electric charge is mobile.
- The motion of charges creates electric current, I .

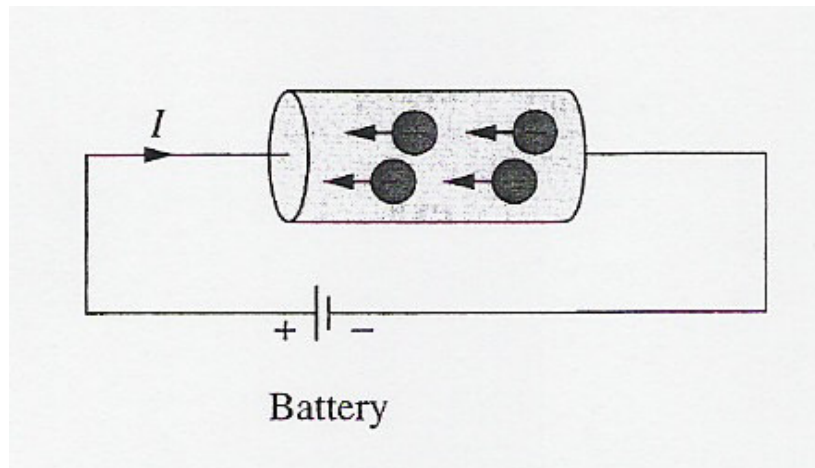

Rajah 1.1

- The current flow in a conductor:

Electric current, I , is the time rate of change of charge, measured in amperes (A).

- The relationship between current i , charge q and time t is

$$i = \frac{dq}{dt} \quad (1.1)$$

where current is measured in amperes (A) and

1 ampere = 1 coulomb/second

- From Equation 1.1, the charge transferred between time t_0 to t is obtained using

$$q = \int_{t_0}^t i dt \quad (1.2)$$

- Two types of current:
 - (i) direct current (dc)

A direct current is a current that remains constant with time

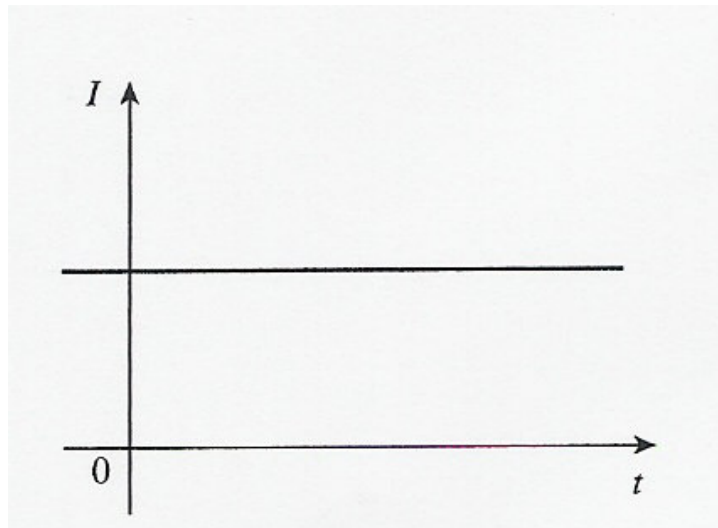


Figure 1.2

- (ii) alternating current (ac)

A alternating current is a current that varies sinusoidally with time

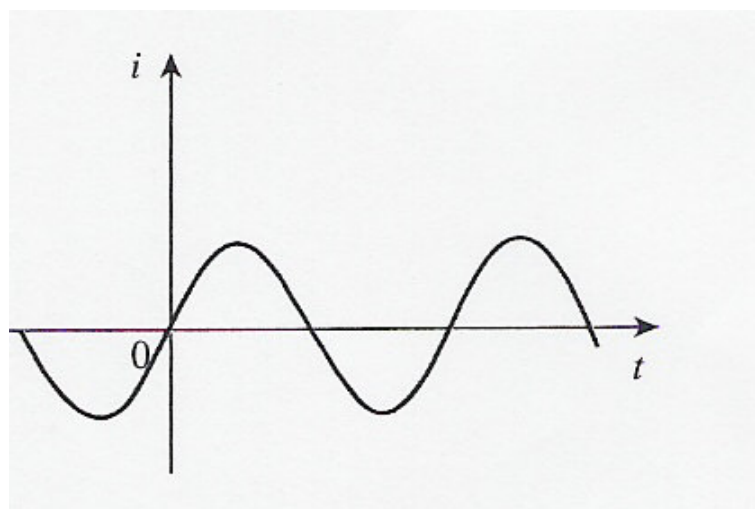


Figure 1.3

- Examples:

- (i) The total charge entering a terminal is given by $q = (10 - 10e^{-2t}) \text{ mC}$. Calculate the current at $t = 0.5 \text{ s}$.

$$\begin{aligned} i &= \frac{dq}{dt} = \frac{d}{dt} (5t \sin 4\pi t) \text{ mC} / \text{s} \\ &= (5 \sin 4\pi t + 20\pi t \cos 4\pi t) \text{ mA} \end{aligned}$$

At $t=0.5$,

$$\begin{aligned} i &= 5 \sin 2\pi + 10\pi \cos 2\pi = 0 + 10\pi \\ &= 31.42 \text{ mA} \end{aligned}$$

- (ii) The current flowing through an element is

$$i = \begin{cases} 2 \text{ A} & 0 < t < 1 \\ 2t^2 \text{ A} & t > 1 \end{cases}$$

Calculate the charge entering the element from $t = 0$ to $t = 2 \text{ s}$.

$$\begin{aligned} q &= \int_0^2 i dt = \int_0^1 2 dt + \int_1^2 2t^2 dt \\ &= 2t \Big|_0^1 + \frac{2t^3}{3} \Big|_1^2 = (2 - 0) + \left(\frac{16}{3} - \frac{2}{3} \right) = \frac{20}{3} \text{ C} \end{aligned}$$

1.4 Voltage

- Voltage is an external electromotive force (emf) (typically represented by the battery) which performs work to move the electron in a conductor.
- Also known as potential difference between two points.

Voltage, v_{ab} between two points a and b in a electric circuit is the energy (or work) needed to move a unit charge from a to b .

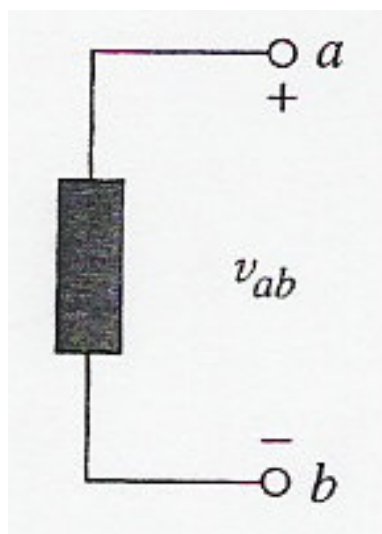


Figure 1.4

- Mathematically:

$$v_{ab} = \frac{dw}{dq} \quad (1.3)$$

where w is energy in joules (J) and q is charge in coulombs (C).

- Voltage is measured in volts (V), where
1 volt = 1 joule/coulomb = 1 newton meter/coulomb
- Examples:

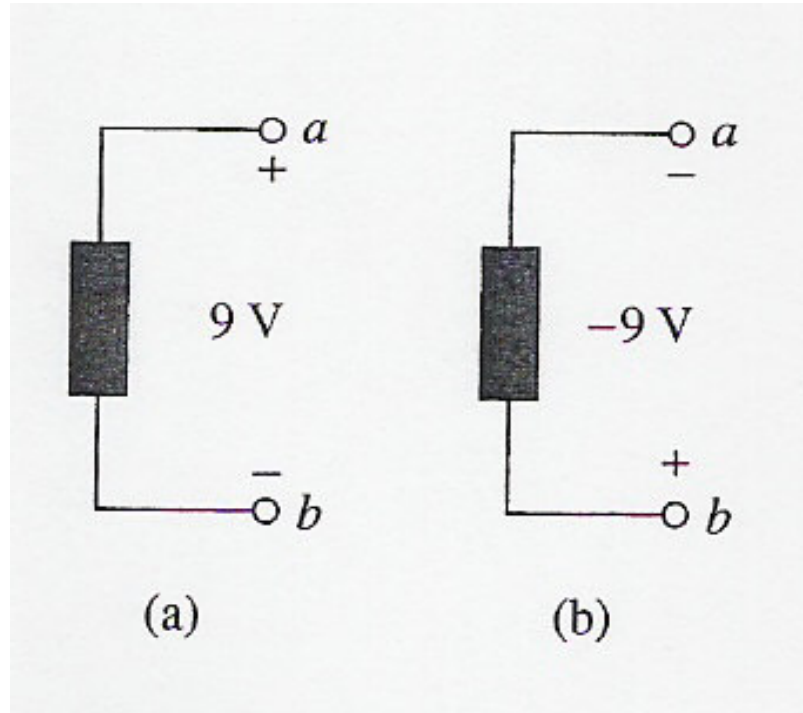


Figure 1.5

For case (a), $v_{ab} = 9V$ and for case (b) $v_{ba} = -9V$

1.5 Power and Energy

- Definition of power

Power is the time rate of expanding or absorbing energy, measured in watts (W)


- Mathematically can be defined as:

$$p = \frac{dw}{dt} \quad (1.4)$$

$$p = \frac{dw}{dq} \cdot \frac{dq}{dt} = vi \quad (1.5)$$

where p is power in watts (W), w is energy in joules (J) and t is time in seconds (s).

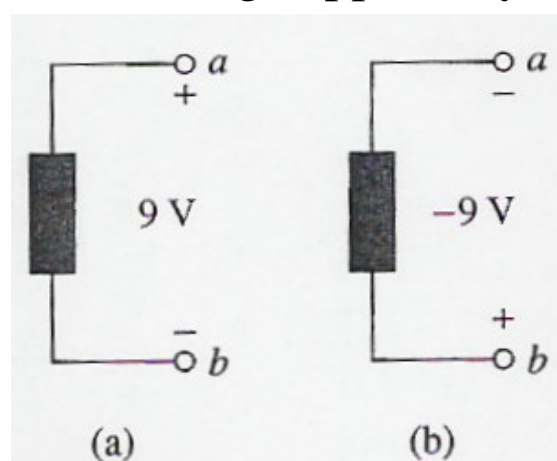- +power – power is delivered to/absorbed by element.
- -power – power is being supplied by element.



(a) absorbing power

(b) supplying power

Figure 1.6

- +Power absorbed = -Power supplied
- The law of conversion of energy – the algebraic sum of power in a circuit at any instant of time must be zero:

$$\sum p = 0 \quad (1.6)$$

- From Equation (1.5), the energy absorbed or supplied by an element from time t_0 to t is

$$w = \int_{t_0}^t p dt = \int_{t_0}^t v i dt \quad (1.7)$$

Energy is the capacity to do work, measured in joules (J)

- Examples:
 - (i) Find the power delivered to an element at $t = 5$ s if the current entering its positive terminal is:

$$i = 5 \cos 60\pi t \text{ A}$$

and the voltage is:

$$v = 3 \frac{di}{dt}$$

$$v = 3 \frac{di}{dt} = 3(-60\pi) 5 \sin 60\pi t$$

$$v = -900\pi \sin 60\pi t \text{ V}$$

$$\therefore p = iv = -4500\pi \sin 60\pi t \cos 60\pi t \text{ W}$$

- (ii) A stove element draws 15 A when connected to a 120 V line. How long does it take to consume 30 kJ?

$$w = pt$$

$$t = \frac{w}{p} = \frac{w}{iv} = \frac{30 \times 10^3}{(15)(120)} = 16.67 \text{ s}$$

1.6 Circuit Elements

- Two types of elements:
 - (i) Active elements
 - Capable of generating energy.
 - i.e. generators, batteries, op-amp
 - (ii) Passive elements
 - Not capable of generating energy.
 - i.e. resistors, capacitors, inductors
- Two types of sources (current or voltage):

Type 1:

An ideal independent source is an active element that provides a specified voltage or current that is completely independent of other circuit elements.

The symbol for independent sources:

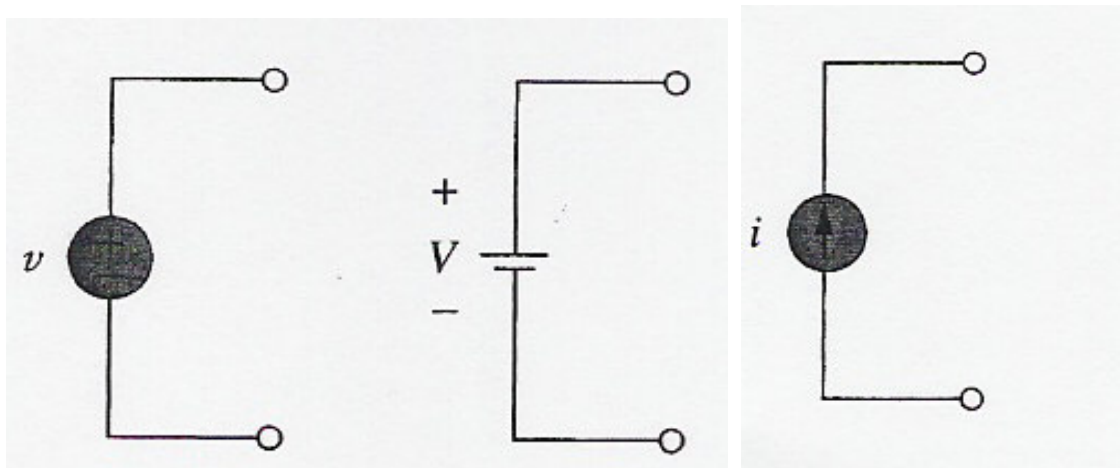


Figure 1.7

Type 2:

An ideal dependent (or controlled) source is an active element in which the source quantity is controlled by another voltage or current.

Example of dependent source: transistor, op-amp

The symbol for dependent source:

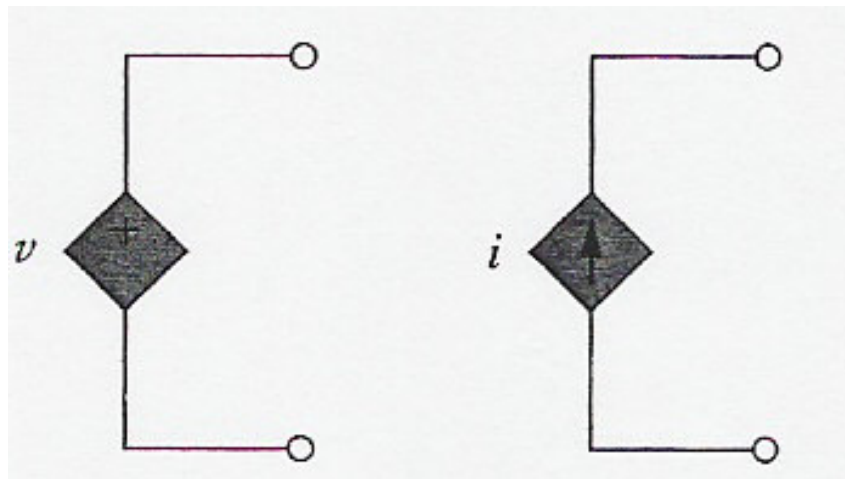


Figure 1.8