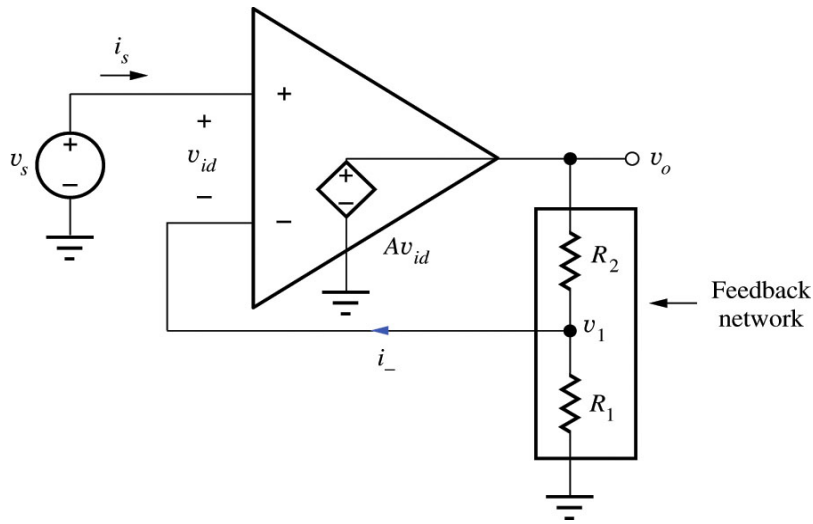


Non-ideal Operational Amplifier

- Various error terms arise in practical operational amplifiers due to non-ideal behavior.
- Some of the non-ideal characteristics include:
 1. Finite open-loop gain that causes gain error
 2. Nonzero output resistance
 3. Finite input resistance
 4. Finite CMRR
 5. Common-mode input resistance
 6. DC error sources
 7. Output voltage and current limits

Finite Open-loop Gain



$$v_o = Av_{id} = A(v_s - v_1) = A(v_s - \beta v_o)$$

$$A_v = \frac{v_o}{v_s} = \frac{A}{1 + A\beta}$$

$A\beta$ is called loop gain.

For $A\beta \gg 1$,

$$A_{ideal} = \frac{1}{\beta} = 1 + \frac{R_2}{R_1}$$

$$\begin{aligned} v_{id} &= v_s - v_1 = v_s - \beta v_o \\ &= v_s - \frac{A\beta}{1 + A\beta} v_s = \frac{v_s}{1 + A\beta} \end{aligned}$$

No longer zero, v_{id} is small for large $A\beta$.

$$v_1 = \frac{R_1}{R_1 + R_2} v_o = \beta v_o$$

$$\beta = \frac{R_1}{R_1 + R_2}$$

is called
feedback factor.

Gain Error

Gain Error is given by

GE= (ideal gain)-(actual gain)

For non-inverting amplifier,

$$GE = \frac{1}{\beta} - \frac{A}{1+A\beta} = \frac{1}{\beta(1+A\beta)}$$

Gain error is also expressed as a fractional or percentage error.

$$FGE = \frac{\frac{1}{\beta} - \frac{A}{1+A\beta}}{\frac{1}{\beta}} = \frac{1}{1+A\beta} \cong \frac{1}{A\beta}$$

Gain Error: Example

Problem: Find ideal and actual gain and gain error is percent

Given data: Closed-loop gain of 200 (46 dB), open-loop gain of op amp is 10,000 (80 dB).

Approach: Amplifier is designed to give ideal gain and deviations from ideal case are determined. Hence,




R1 and *R2* aren't designed to compensate for finite open-loop gain of amplifier.

Analysis:

$$A_v = \frac{A}{1 + A\beta} = \frac{10^4}{1 + \frac{10^4}{200}} = 196$$

$$\text{FGE} = \frac{200 - 196}{200} = 0.02$$

Nonzero Output Resistance

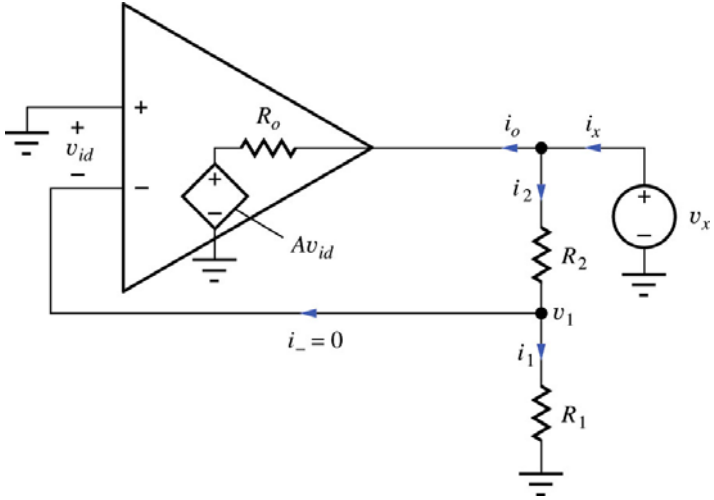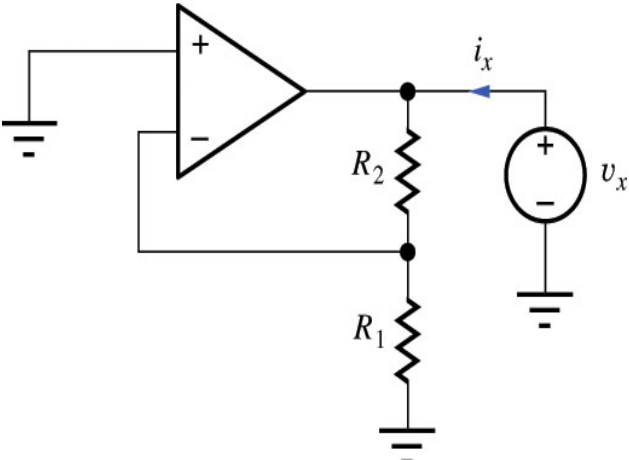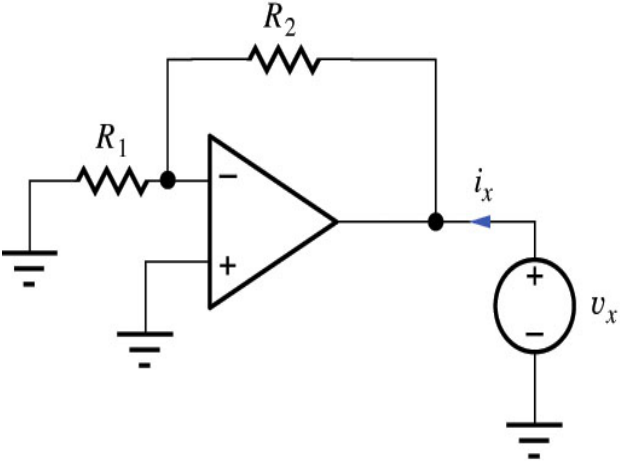

Output terminal is driven by test source v_x and current i_x is calculated to determine output resistance (all independent sources are turned off). The equivalent circuit is same for both inverting and non-inverting amplifiers.

$$R_{out} = \frac{v_x}{i_x}$$

Nonzero Output Resistance (contd.)

Analysis: $i_x = i_o + i_2$ Also, $v_{id} = -v_1$ and $v_1 = \frac{R_1}{R_1 + R_2} v_x = \beta v_x$

$$i_o = \frac{v_x - A v_{id}}{R_o} \quad i_2 = \frac{v_x}{R_1 + R_2}$$

$$\therefore \frac{1}{R_{out}} = \frac{i_x}{v_x} = \frac{1 + A\beta}{R_o} + \frac{1}{R_1 + R_2}$$

Thus, shunt feedback at output reduces R_{out} .

$$\therefore R_{out} = \frac{R_o}{1 + A\beta} \parallel (R_1 + R_2)$$

Since, $R_o/(1+A\beta) \ll (R_1+R_2)$, $R_{out} \cong \frac{R_o}{1+A\beta}$ If A is infinite, $R_{out}=0$

Open-loop Gain Design: Example


- **Problem:** Design non-inverting amplifier and find open-loop gain
- **Given Data:** $A_v=35$ dB, $R_{out}=0.2\Omega$, $R_o = 250\Omega$
- **Analysis:**

$$|A_v|=10^{35\text{dB}/20\text{dB}}=56.2 \quad \beta=\frac{1}{A_v}=\frac{1}{56.2}$$

$$R_{out}=\frac{R_o}{1+A\beta}\leq 0.2\Omega$$

$$\therefore A\geq\frac{1}{\beta}\left(\frac{R_o}{R_{out}}-1\right)=56.2\left(\frac{250}{0.2}-1\right)=7.03\times 10^4=96.9\text{dB}$$

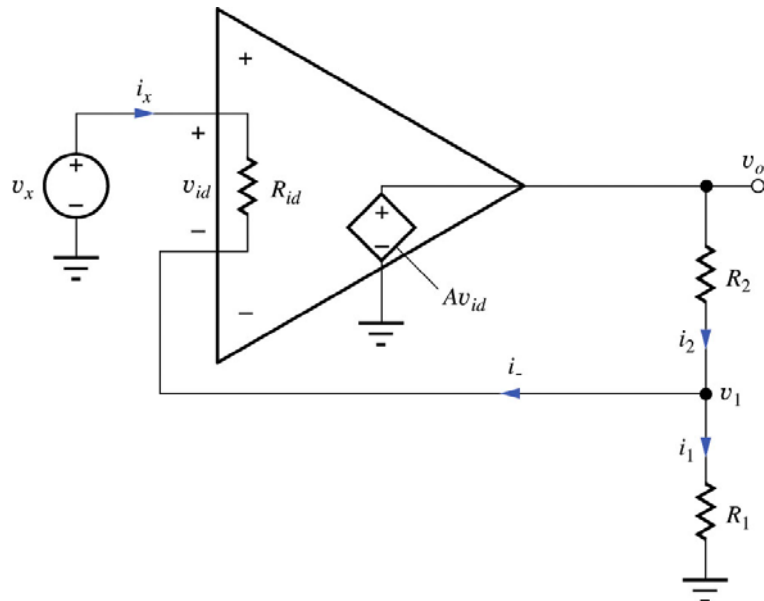Finite Input Resistance: Non-inverting Amplifier



Test voltage source v_x is applied to input and current i_x is calculated.

$$i_x = \frac{v_x - v_1}{R_{id}} \quad v_1 = i_1 R_1 \cong i_2 R_1$$

Assuming $i_1 \ll i_2$ implies $i_1 = i_2$.

$$v_1 \cong \frac{R_1}{R_1 + R_2} v_o = \beta v_o$$


$$= \beta (A v_{id}) = A \beta (v_x - v_1)$$

$$v_1 = \frac{A \beta}{1 + A \beta} v_x$$

$$\therefore i_x = \frac{v_x - \frac{A \beta}{1 + A \beta} v_x}{R_{id}} = \frac{v_x}{(1 + A \beta) R_{id}}$$

$$R_{in} = R_{id} (1 + A \beta)$$

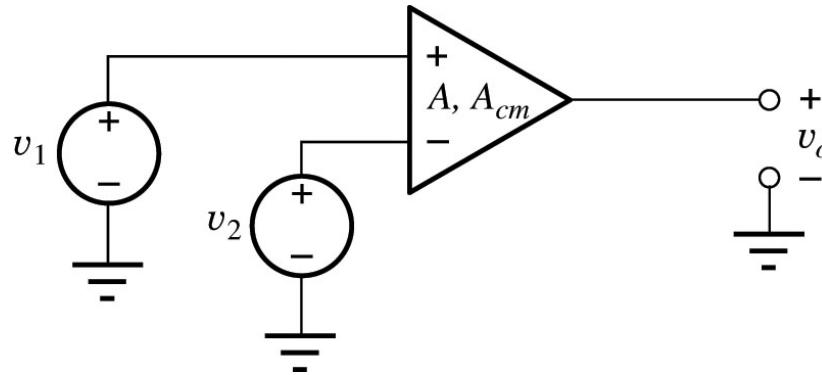
Finite Common-Mode Rejection Ratio (CMRR)



A real amplifier responds to signal common to both inputs, called common-mode input voltage. In general,

$$\begin{aligned} v_o &= A(v_1 - v_2) + A_{cm} \left(\frac{v_1 + v_2}{2} \right) \\ &= A(v_{id}) + A_{cm}(v_{ic}) \end{aligned}$$

Voltage Follower Gain Error due to CMRR

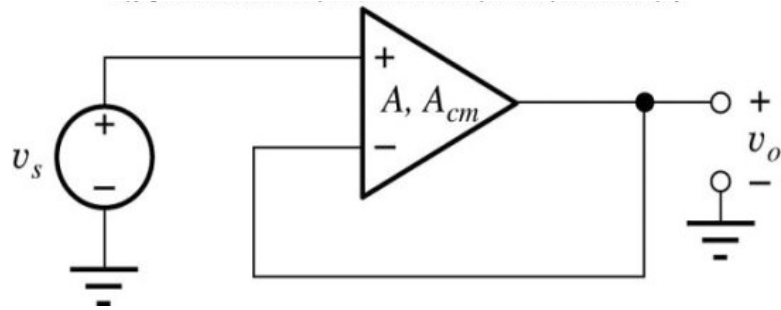

$$v_{id} = v_s - v_o \quad v_{ic} = \frac{v_s + v_o}{2}$$

$$v_o = A \left((v_s - v_o) + \frac{(v_s + v_o)}{2CMRR} \right)$$

$$A_v = \frac{v_o}{v_s} = \frac{A \left(1 + \frac{1}{2CMRR} \right)}{1 + A \left(1 - \frac{1}{2CMRR} \right)}$$

Ideal gain for voltage follower is unity, gain error

$$GE = 1 - A_v = \frac{1 - \frac{A}{2CMRR}}{1 + A \left(1 - \frac{1}{2CMRR} \right)}$$

Since, both A and CMRR are normally $\gg 1$,

$$GE \cong \frac{1}{A} - \frac{1}{CMRR}$$


First term is due to finite amplifier gain, second term shows that CMRR may introduce an even larger error.

DC Error Sources: Input-Offset Voltage

With inputs being zero, the amplifier output rests at some dc voltage level instead of zero. The equivalent dc **input offset voltage** is

$$V_{OS} = \frac{V_O}{A}$$

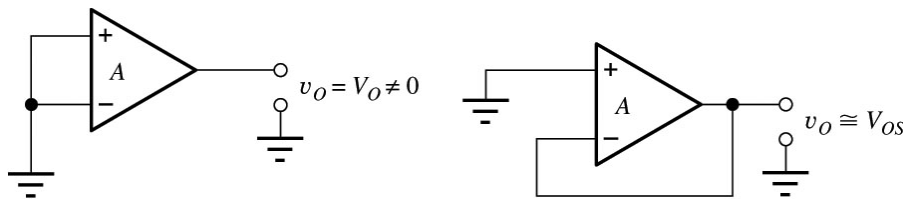The amplifier is connected as voltage-follower to give output voltage equal to offset voltage.



To include effect of offset voltage

$$v_O = A \left(v_{id} + \frac{v_{ic}}{\text{CMRR}} + V_{OS} \right)$$

If $v_{id} = 0$,

$$v_O = A \left(\frac{v_{ic}}{\text{CMRR}} + V_{OS} \right) = A(v_{OS})$$

$$\therefore \text{CMRR} = \frac{v_{ic}}{v_{OS}} \mu\text{V/V}$$

Thus, CMRR is a measure of how total offset voltage changes from its dc value when common-mode voltage is applied.