

## EEM 323/3 - Assignment

1. A platinum resistance sensor has a resistance of  $100\ \Omega$  at  $0\ ^\circ\text{C}$  and a temperature coefficient of resistance of  $4 \times 10^{-3}\ ^\circ\text{C}^{-1}$ . Given that a  $15\ \text{V}$  supply is available, design a deflection bridge giving an output range of  $0$  to  $100\ \text{mV}$  for an input range of  $0$  to  $100\ ^\circ\text{C}$ :
  - (a) using the procedure discussed in lectures.
  - (b) using the linear approximation discussed in lectures.
  - (c) how should the circuit be altered if the input range is changed to  $50$  to  $150\ ^\circ\text{C}$ ?

Give values for all circuit components and assume a high impedance load.

2. The resistance  $R_\theta$  (k $\Omega$ ) of a thermistor at  $\theta^\circ\ \text{K}$  is given by:

$$R_\theta = 1.68 \left[ 3050 \left( \frac{1}{\theta} - \frac{1}{298} \right) \right]$$

The thermistor is incorporated into the deflection bridge circuit shown in Fig. 2

- (a) Assuming that  $V_{out}$  is measured with a detector of infinite impedance, calculate:
  - (i) the range of  $V_{out}$  corresponding to an input temperature range of  $0$  to  $50\ ^\circ\text{C}$ .
  - (ii) the non-linearity at  $12\ ^\circ\text{C}$  as a percentage of full-scale deflection.
- (b) Calculate the effect on the range of  $V_{out}$  of reducing the detector impedance to  $1\ \text{k}\Omega$ .

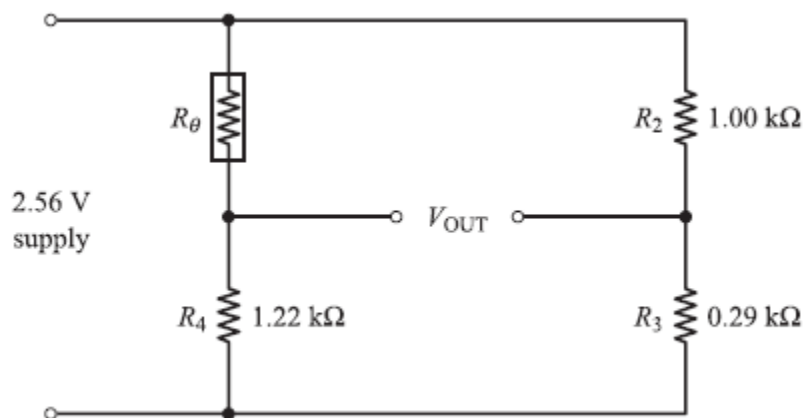


Fig. 2

3. Fig. 3 shows a four-lead bridge circuit;  $R_c$  is the resistance of the leads connecting the sensor to the bridge circuit. Show that  $E_{Th} \approx V_s \left( \frac{R_0}{R_3} \right) \alpha T$ , i.e. the bridge output voltage is unaffected by changes in  $R_c$ . State all assumptions.

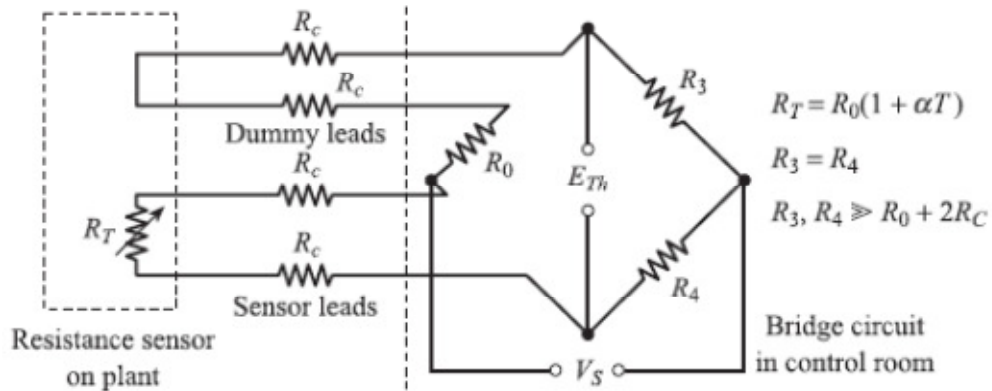


Fig. 3

4. A low-voltage Schering bridge shown in Fig. 4 is used to measure the unknown permittivity of a specimen using 2-plate capacitor,  $C_1$  with area  $A$  and distance  $d$ .

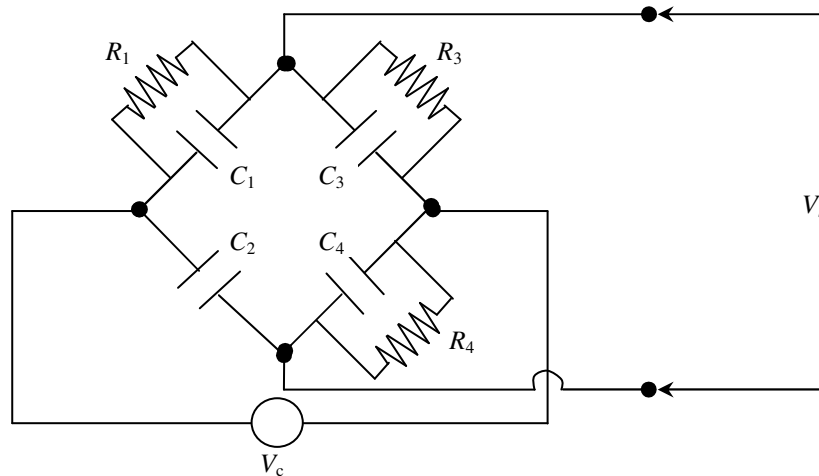


Fig. 4

Referring to Fig. 4,  $R_1$  is a stray resistor,  $R_3$  and  $R_4$  are pure non-reactive resistors, and  $C_2$ ,  $C_3$  and  $C_4$  are pure non-reactive capacitors. Without the specimen the following balanced condition are attained:  $C_3 = C_4 = 120$  pF,  $C_2 = 140$  pF and  $R_3 = R_4 = 5000 \Omega$ . With the specimen the values changed to  $C_3 = 200$  pF,  $C_4 = 1000$  pF,  $C_2 = 900$  pF, and  $R_3 = R_4 = 500 \Omega$ . If  $V_c = 10$  V (RMS) and  $\omega = 5000$  rad/s, calculate the relative permittivity of the specimen.

5. (a) List common source of errors in AC bridge circuits. Hence, state several precautions that should be taken to reduce the errors.
- (b) In designing a sensing circuit for measuring the level of oil ( $\epsilon_{oil}$ ) inside a tank, the capacitive level sensor has been proposed. Meanwhile, the simplified four-arm De-Sauty bridge has been suggested for signal detection. Figure 1 shows the instrumentation and measurement system. In this figure  $R_4$  and  $C_2$  are pure resistance and capacitance respectively,  $C_h$  is the sensor capacitance at a height  $h$  of the oil and  $R_4$  is the variable resistance.

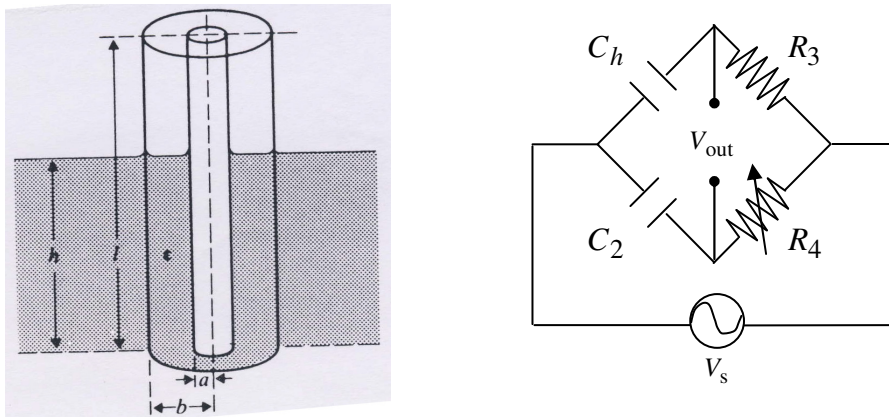


Fig. 5

The relationship between  $C_h$  and  $h$  of the capacitive sensor is as follows:

$$C_h = \frac{2\pi\epsilon_0}{\log_e\left(\frac{b}{a}\right)} [1 + (\epsilon_{oil} - 1)h]$$

- (i) Derive the balanced conditions of Fig. 5,

(ii) Calculate  $h$  when at balance  $C_2 = 1000 \mu\text{F}$ ,  $R_4 = 10 \Omega$ ,  $R_3 = 1250 \Omega$ ,  $\epsilon_0 = 1$ ,  $\epsilon_{\text{oil}} = 3$ ,  $b = 2 \text{ cm}$  and  $a = 0.5 \text{ cm}$ ,

(iii) State the main source of error in 1(b) (ii).

6. (a) Explain the important of the quality factor  $Q$  and the damping factor  $\xi$  in filter design.

(b) The Sallen-Key second order low pass filter is shown in Fig. 6.

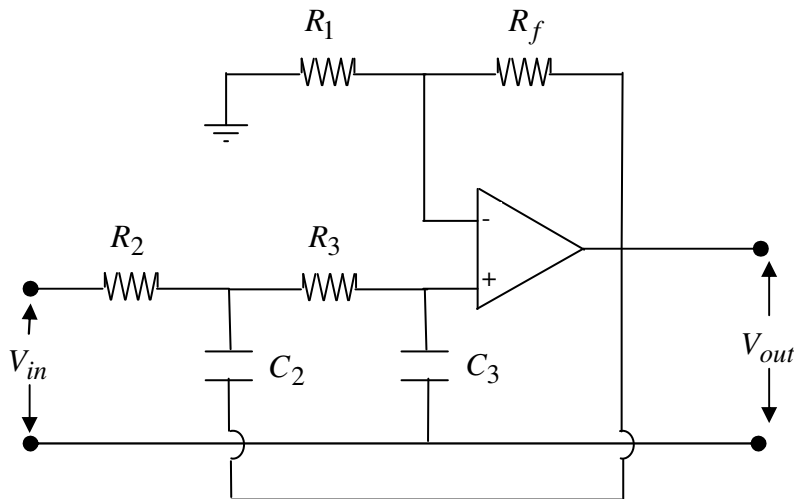


Fig. 6

Prove the transfer function of the above filter is given by

$$H(s) = \frac{\frac{G}{R_2 R_3 C_2 C_3}}{s^2 + \left( \frac{R_3 C_3 + R_2 C_3 + R_2 C_2 - G R_2 C_2}{R_2 R_3 C_2 C_3} \right) s + \frac{1}{R_2 R_3 C_2 C_3}}$$

and  $G = 1 + \frac{R_f}{R_1}$ .

Assuming  $R_2 = R$ ,  $R_3 = 2R$ ,  $C_2 = C$ ,  $C_3 = 2C$  and  $R_f = R_1$ ,

- (i) Design filter in Figure 2 such that the resonance frequency  $\omega_o = 1000 \text{ rad/sec}$ ,
- (ii) From 2(b)(ii), calculate the Q and damping  $\xi$  factors of the filter,
- (iii) Hence, modify Figure 2 so that the above filter has the Butterworth response such that  $|H(j\omega_0)| = 1$  or 0 dB.

7. (a) Explain the terms (i) resolution, (ii) quantum error, (iii) acquisition time  $t_{aq}$ , (iv) aperture time  $t_{ap}$  and (v) settling time  $t_s$  with respect to the analogue-to-digital converter.

(b) The 4-bit  $R - 2R$  type digital-to-analogue converter is shown in Fig. 7.

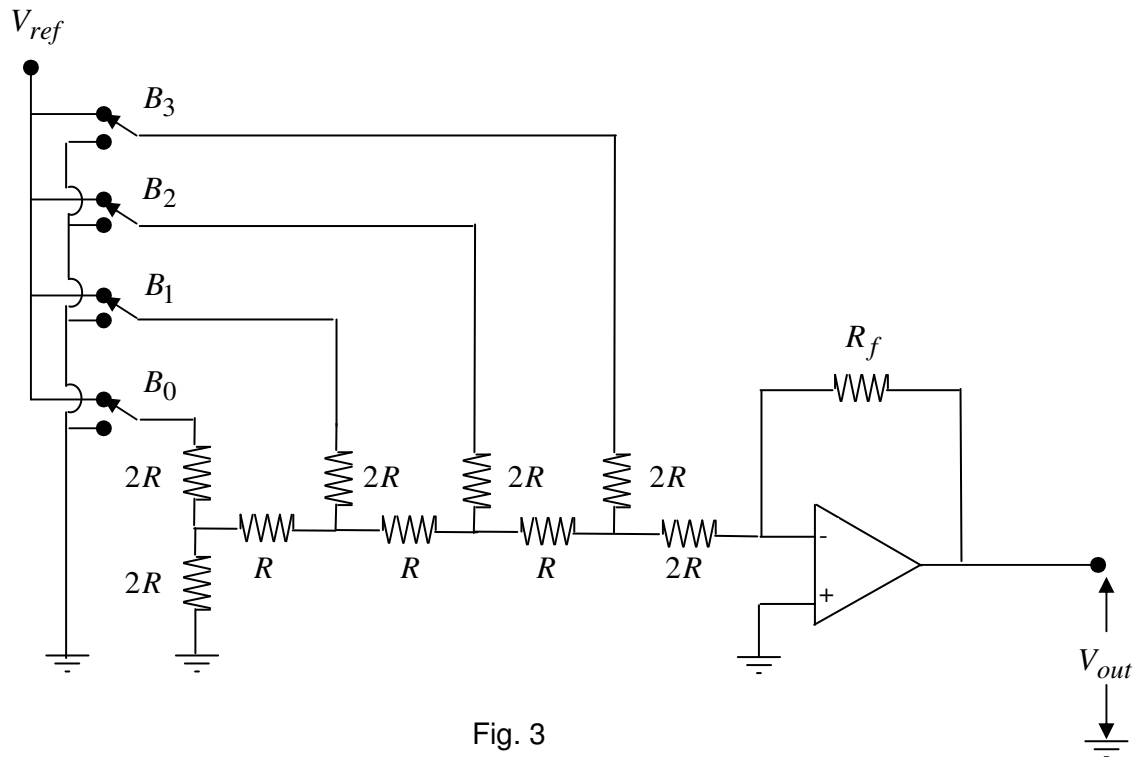


Fig. 3

- (i) Derive the output  $V_{out}$  when the most significant bit (MSB) is turned on only,
- (ii) Repeat 3(b)(i) for the least significant bit (LSB),
- (iii) Repeat 3(b)(i) for an input  $B_3B_2B_1B_0 = 1001$ ,
- (iv) From 3(b)(i-iii) derive the general expression for  $V_{out}$ .