

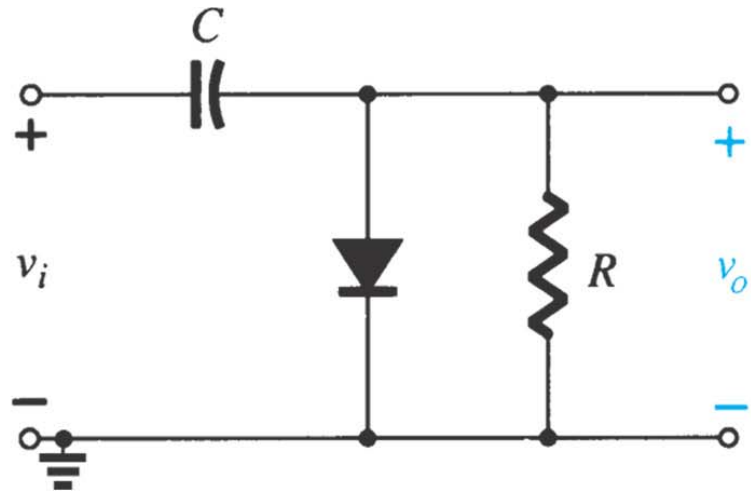


CLAMPERS

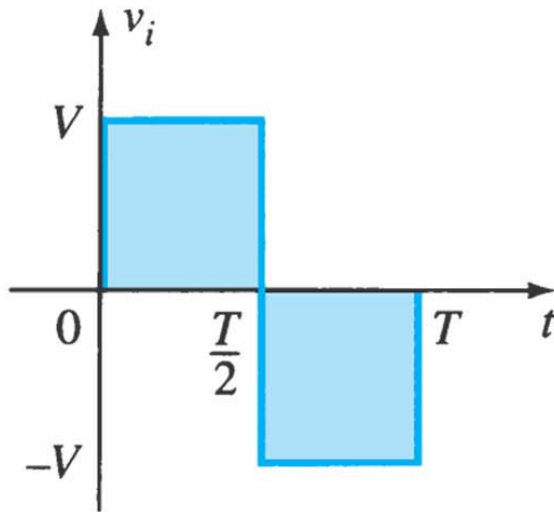


A clamper is a network constructed of a diode, a resistor and a capacitor that shifts a waveform to a different dc level without changing the appearance of the applied signal.

Analysis (ideal diode)

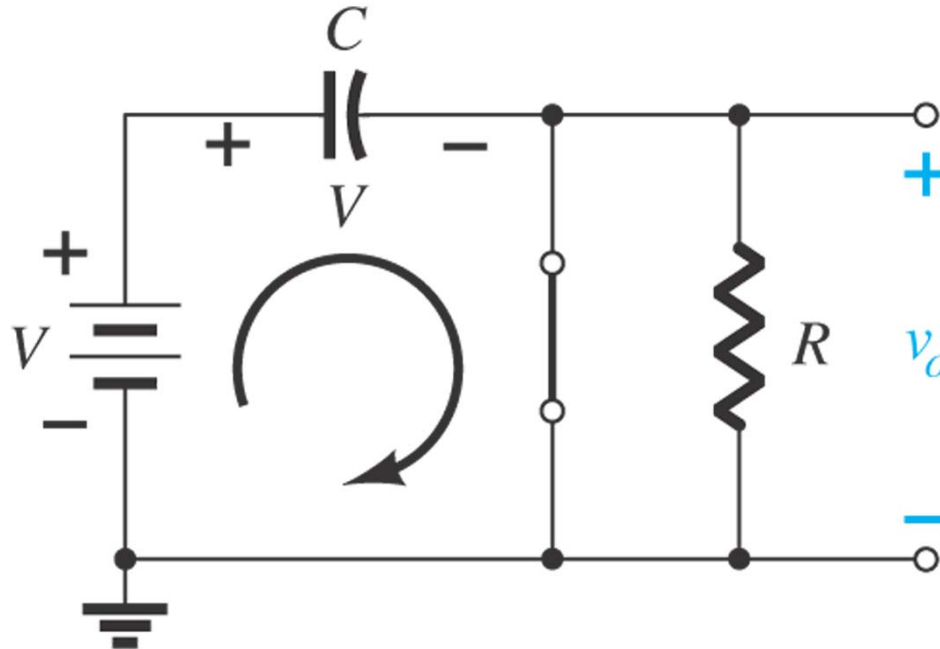

Operation at forward biased, the diode is short circuited (i.e “on” state). The voltage will be $v_o = 0$ since the current is shorted thru diode and the capacitor is charged up to a voltage V .

Analysis

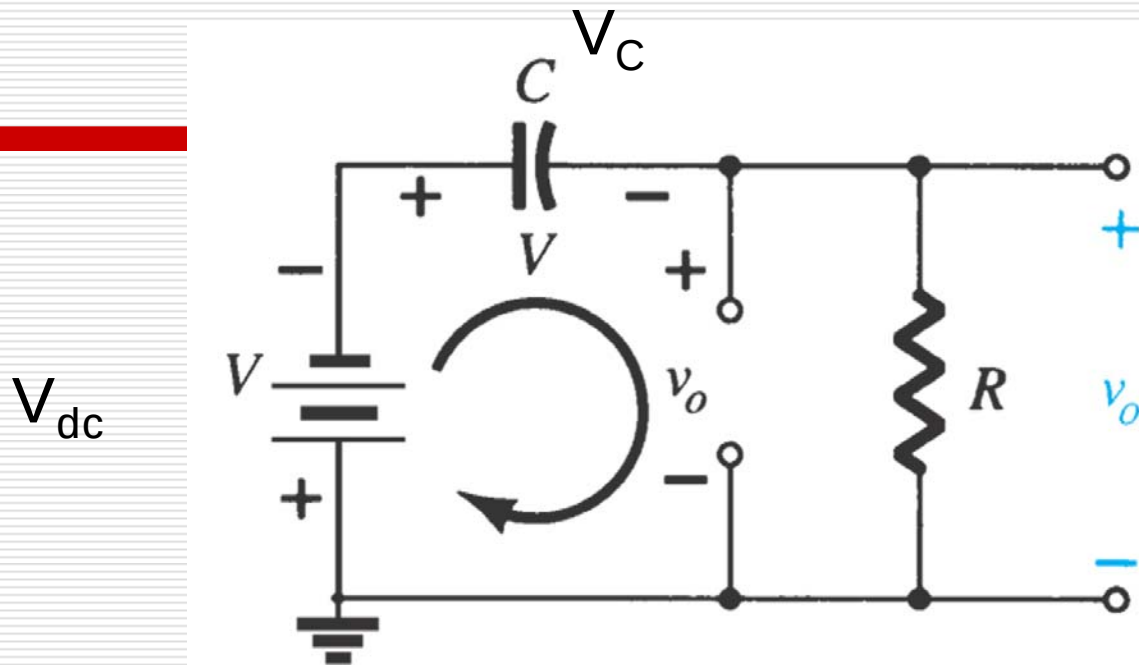


During reverse biased, the diode is open circuited (i.e “off” state). The voltage will be $v_o = 0$ since the current is shorted thru diode. The voltage across R will be


$$V_{dc} + V_c = -V + (-V) = -2V$$

Result



Input

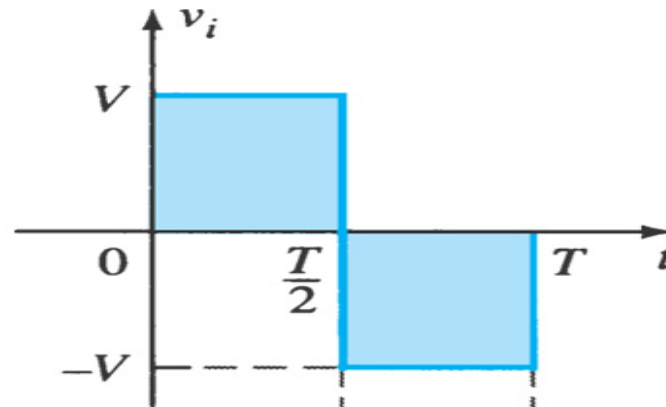

Output

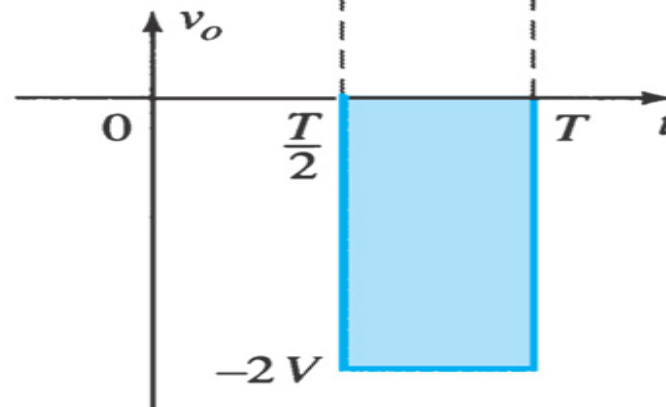


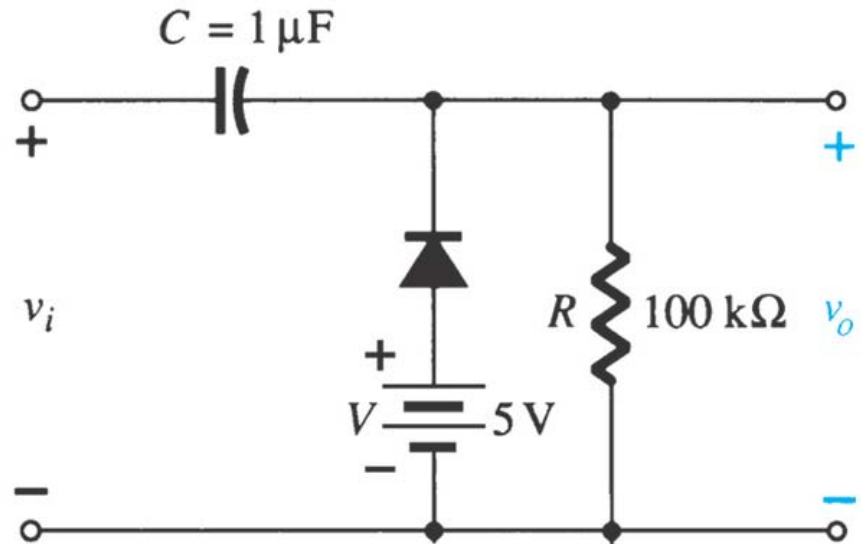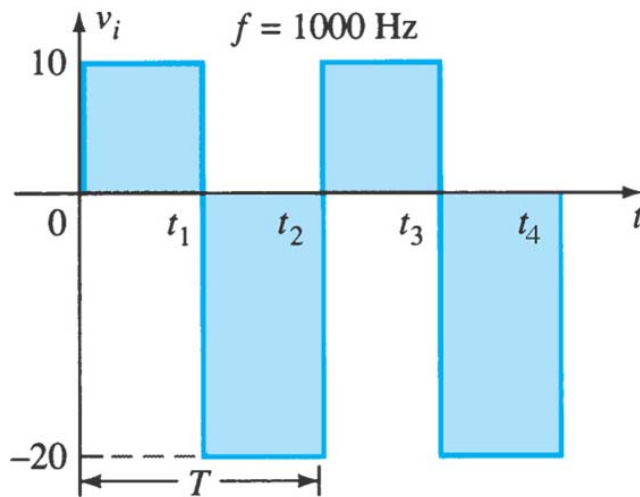Determine v_o for the following network with the input shown (for ideal diode).



Solution: Frequency is 1000Hz, then the period will be $1/f = 1\text{ms}$, so the interval for each level state is $t_1 = 0.5\text{ms}$. At first interval the diode is open circuited, so no current at output, therefore $v_o = 0$


Analysis (forward biased)

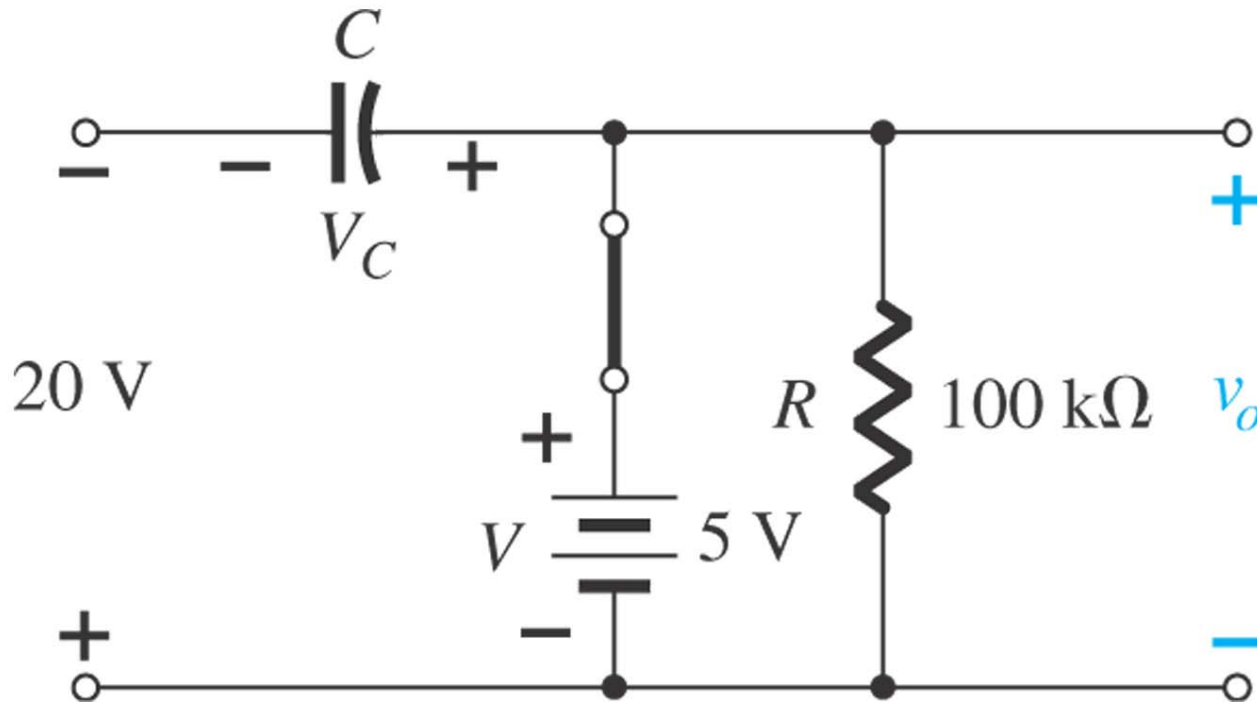

At 2nd interval, the diode is short circuited, the voltage across R will be the same as across the battery (parallel) $V_o = 5\text{ V}$

The voltage that charge up the capacitor, Applying KVL
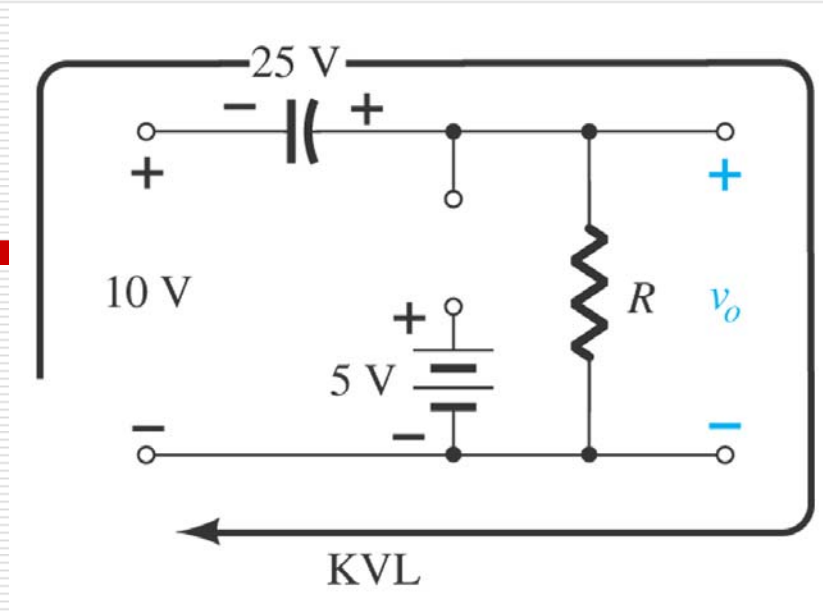
$$-20\text{ V} + V_C - 5\text{ V} = 0, \text{ then } V_C = 25\text{ V}$$



The third interval will make the diode open circuited again and current start to flow in the resistor (discharged the capacitor).



Applying the KVL $+10V + 25V - v_o = 0$
 Give us $v_o = 35V$

Noted : the discharge time is can be determined as $t = RC$


$$RC = 100k\Omega \times 0.1mF = 0.01s = 10ms$$

Total discharge $5t = 5 \times 10ms = 50ms$ which is $\gg$ interval time which allow the capacitor to hold significantly the input voltage.


The result

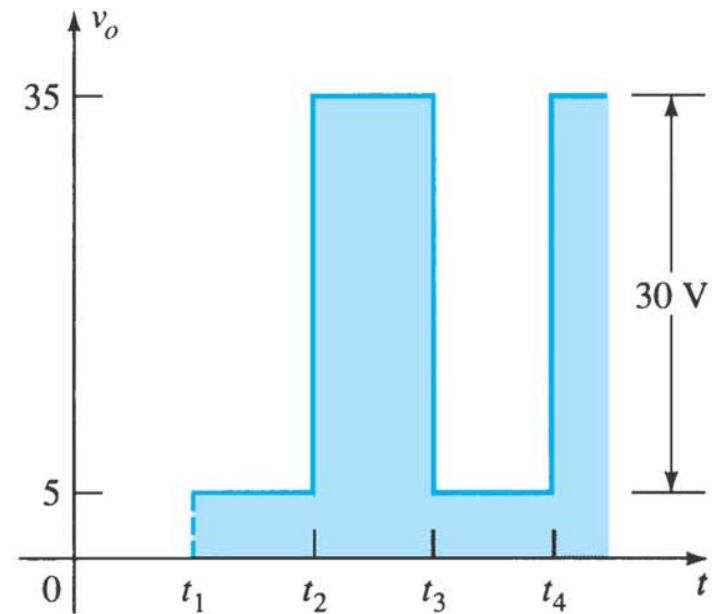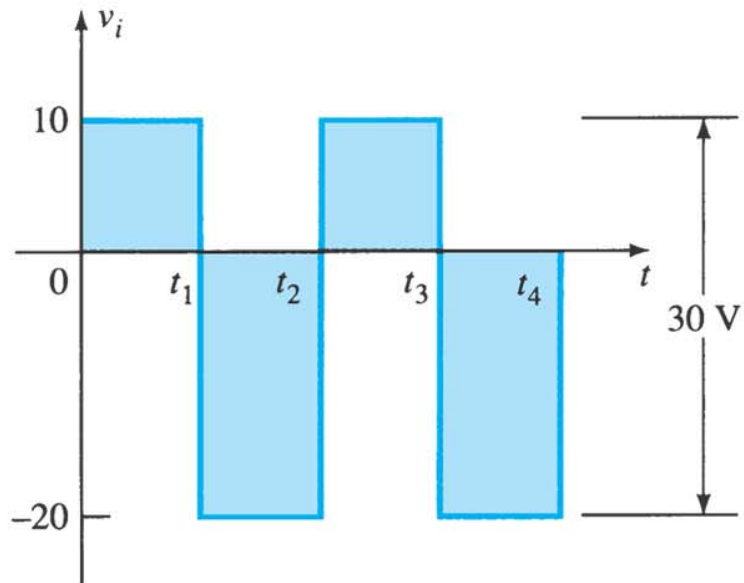

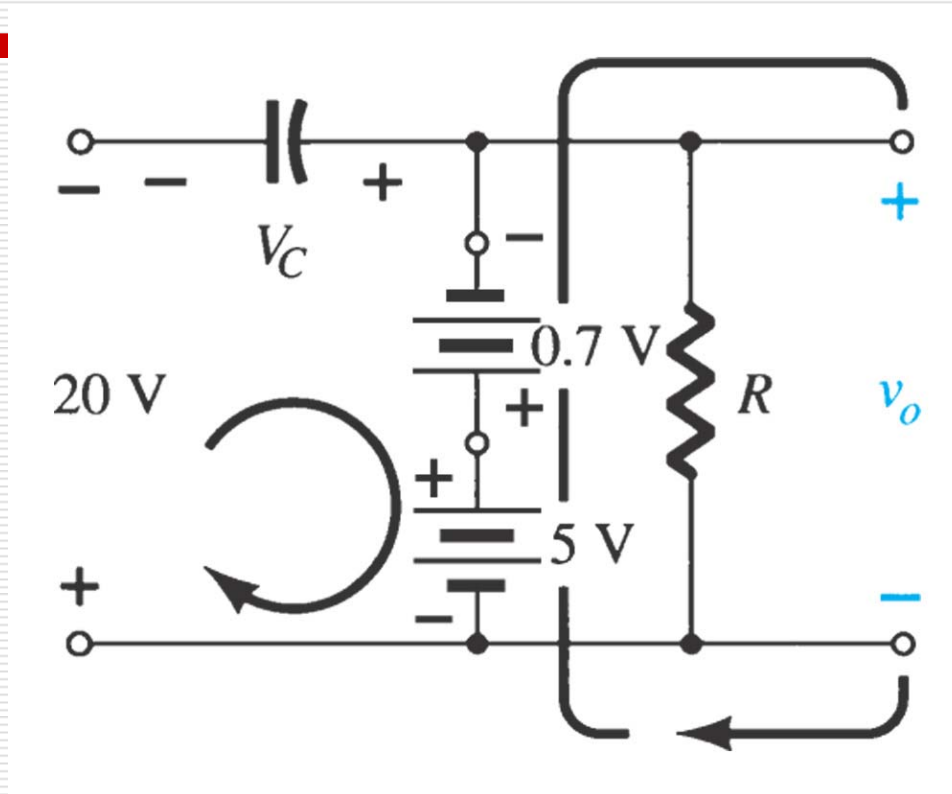Practical case with diode of $V_k = 0.7\text{V}$




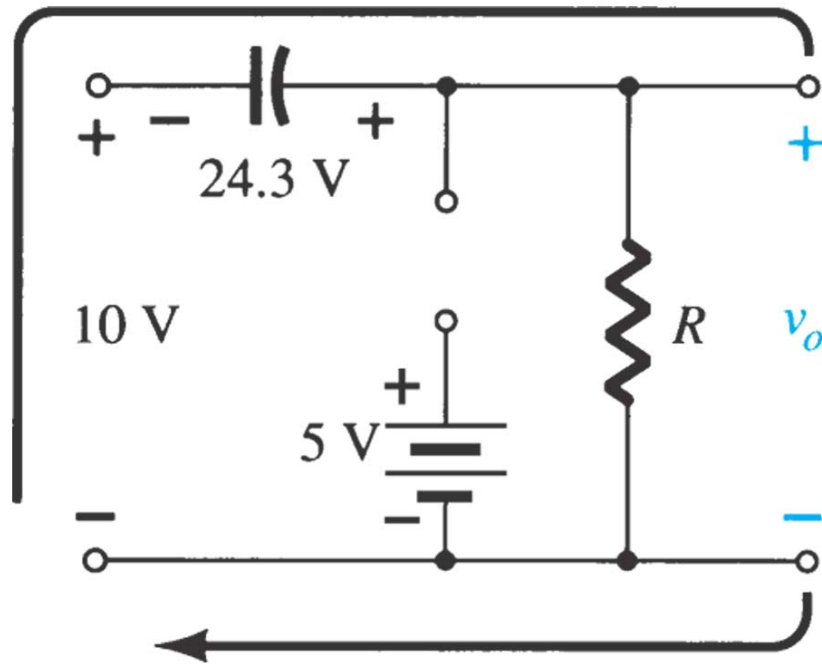At second interval $v_o = 5\text{V} - 0.7\text{V} = 4.3\text{V}$
 and the charging up voltage $-20\text{V} - 5\text{V} + 0.7\text{V} + V_C = 0$
 Therefore $V_C = 24.3\text{V}$



Circuit














result

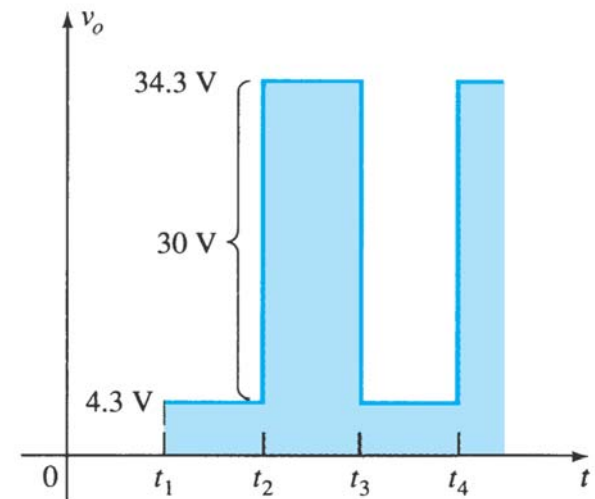




The third interval we have
 $10\text{V} + 24.3\text{V} - v_o = 0$
 Thus $v_o = 34.3\text{V}$

Clamping Networks


Other example of clampers

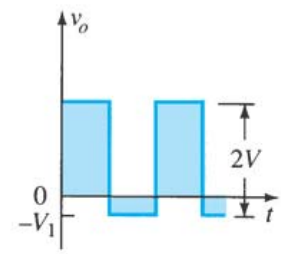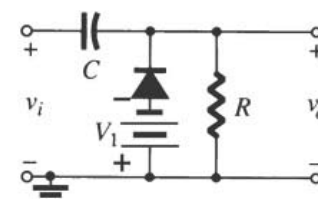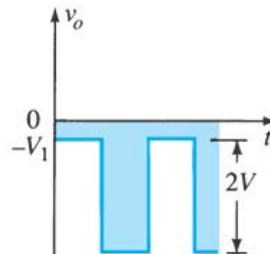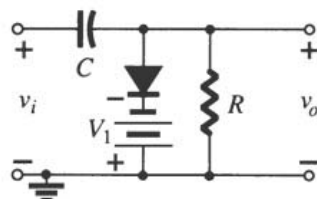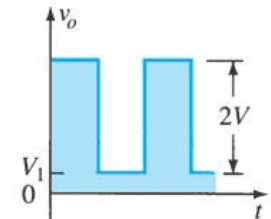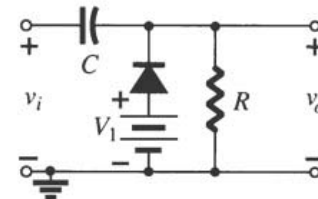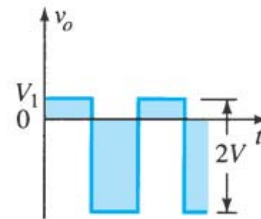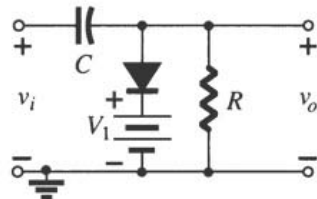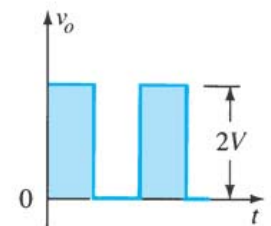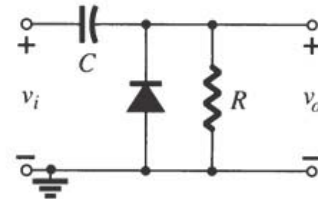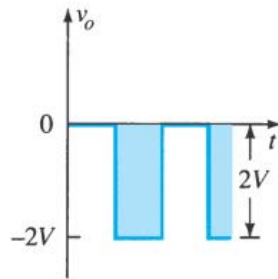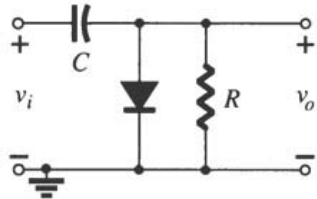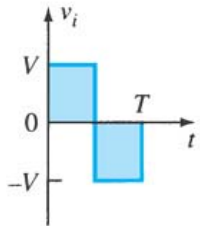

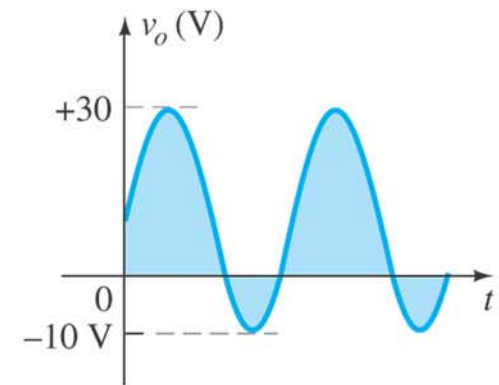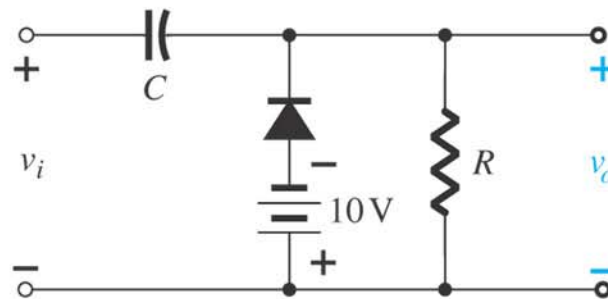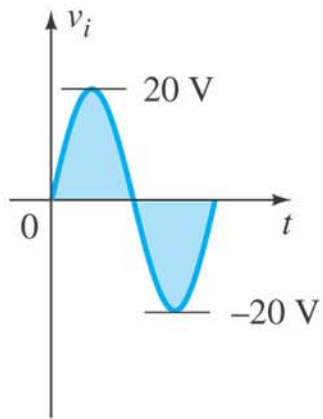The clamper also work well for sinusoidal wave.



ZENER DIODES

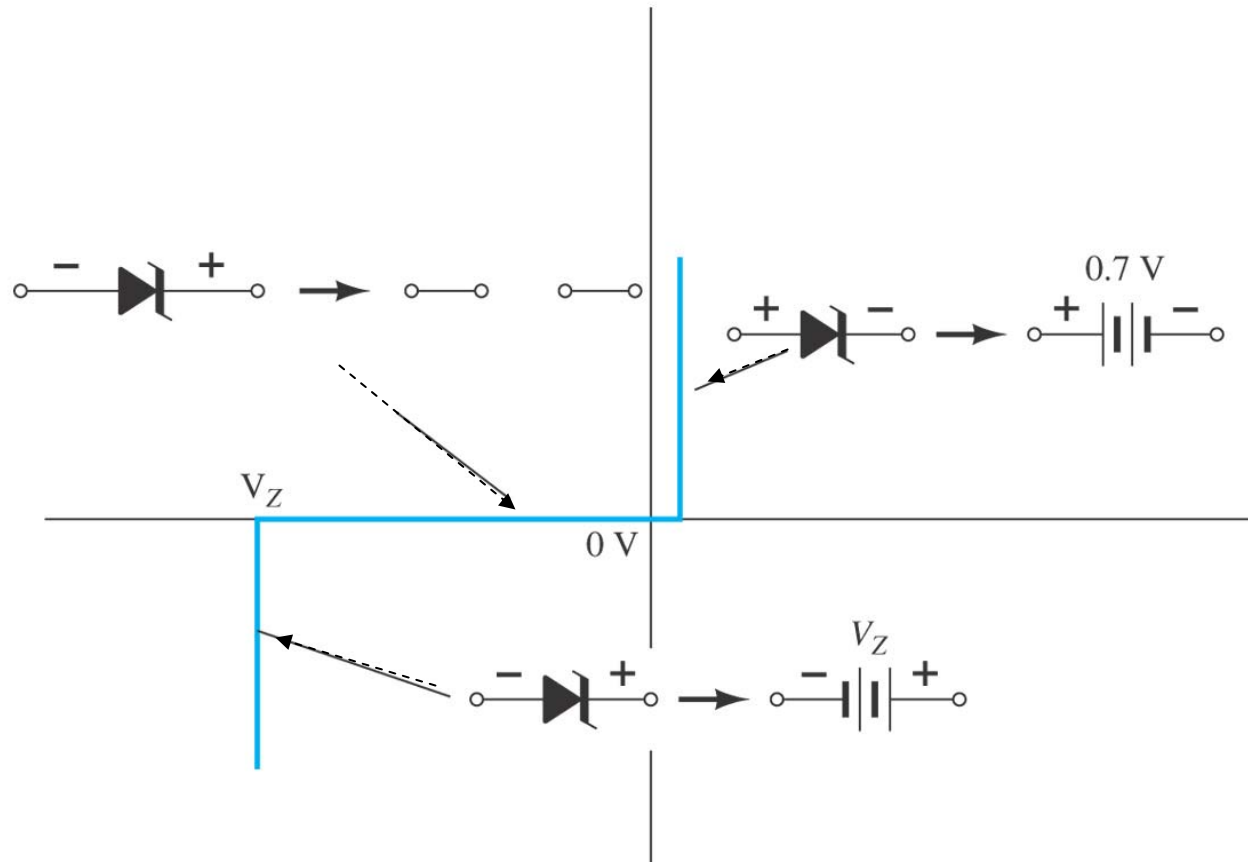

Showing the equivalent circuit at each state in V-I characteristic

Determine

- (i) the voltages at references Vo1 and Vo2
- (ii) the current thru LED and the power delivered by the supply
- (iii) How does the power absorbed by the LED compare to that 6V Zener diode

$$V_{o1} = V_{Z2} + V_K = 3.3V + 0.7V = 4.0V$$


$$V_{o2} = V_{o1} + V_K = 4V + 6V = 10V$$

$$I_R = I_{LED} = \frac{V_R}{R} = \frac{40V - V_{o2} - V_{LED}}{1.3k\Omega} = \frac{40V - 10V - 4V}{1.3k\Omega} = 20mA$$



$$\text{Power delivered } P_s = EI_s = EI_R = (40V)(20mA) = 800mW$$

$$\text{Absorbed by LED } P_{LED} = V_{LED} I_{LED} = (4V)(20mA) = 80mW$$

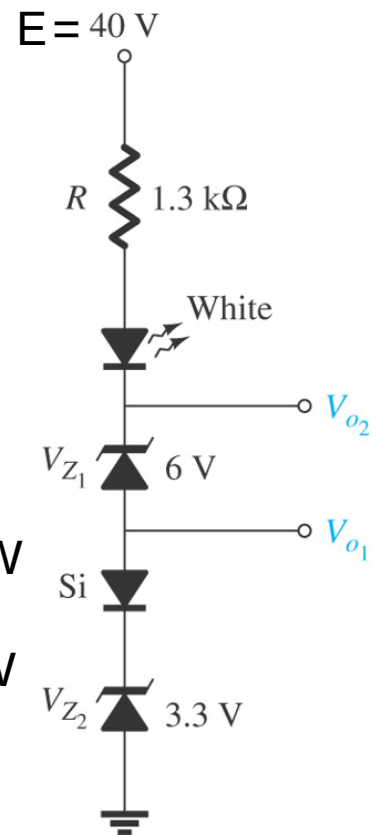
$$\text{Absorbed by Zener } P_Z = V_Z I_Z = (6V)(20mA) = 120mW$$



A LIMITER

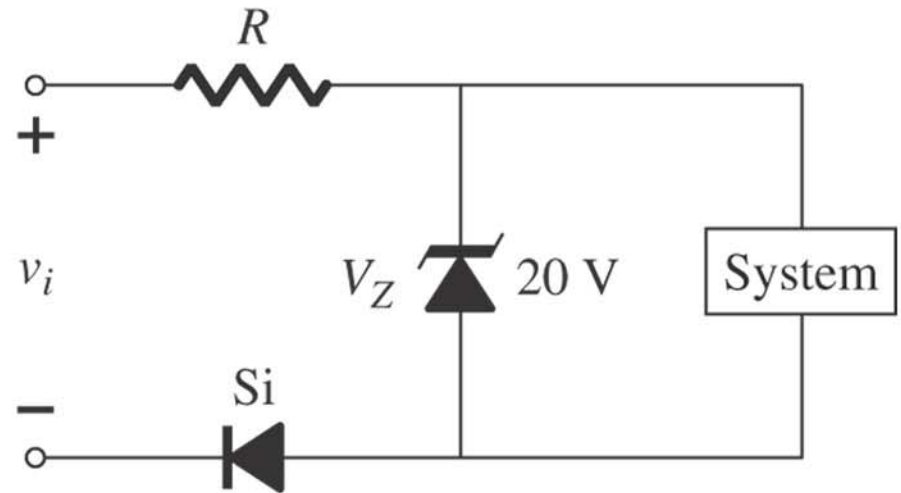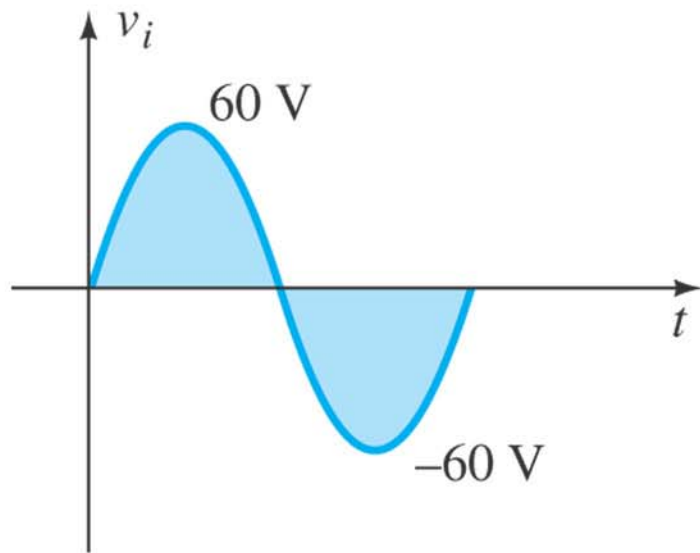


Analysis

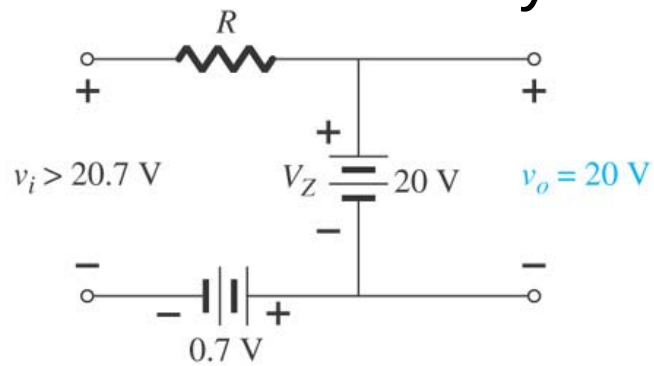


(a)

First half

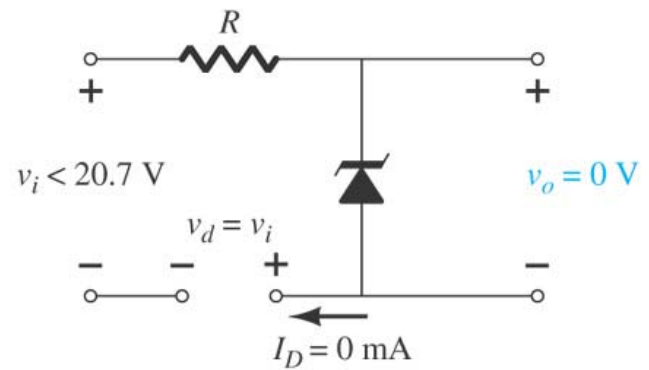


(b)

2nd half

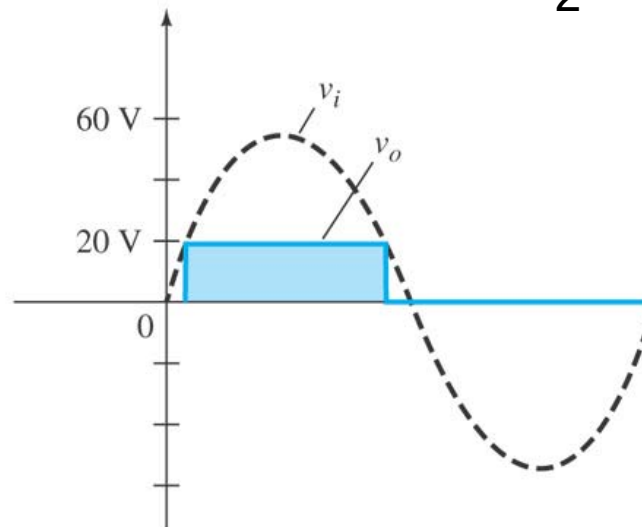


(c)

Fixed V_i and R as a dc regulator

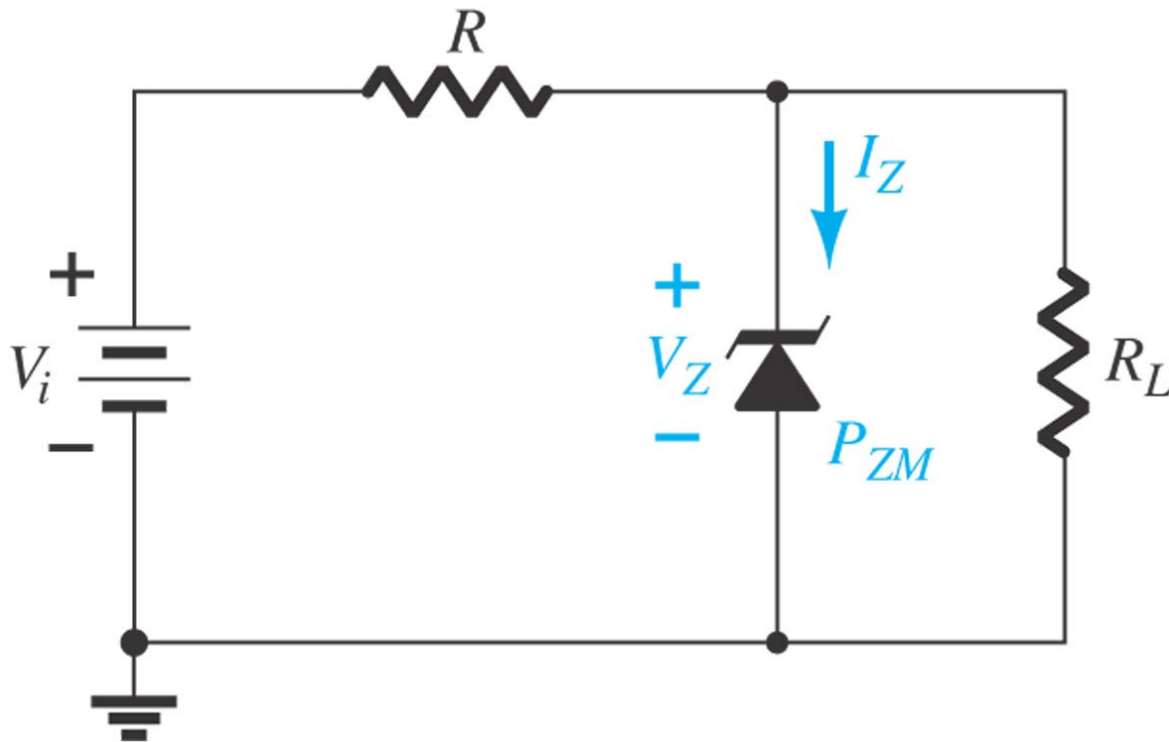

A simplest Zener diode regulator network

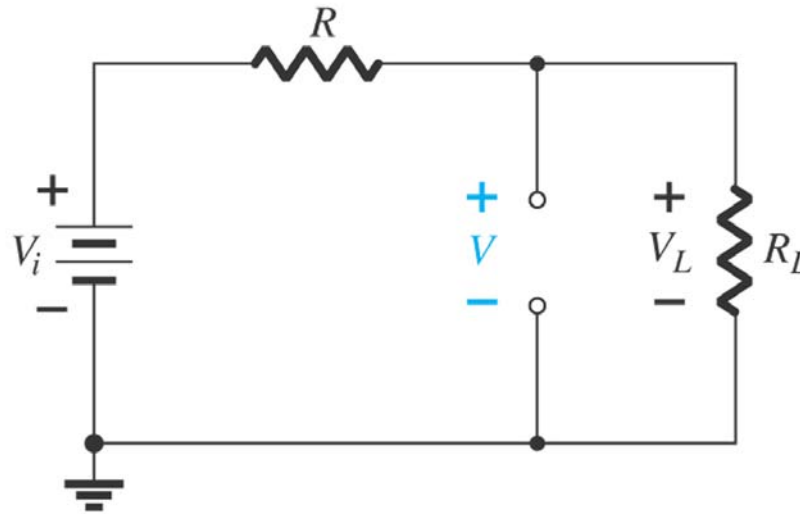To determine the state of Zener diode by removing the diode from the network



Thus applying voltage divider rule


$$V = V_L = \frac{R_L V_i}{R + R_L}$$

If $V \geq V_Z$, the Zener diode is on.

If $V < V_Z$, the Zener diode is off.

Zener equivalent for the “on” situation
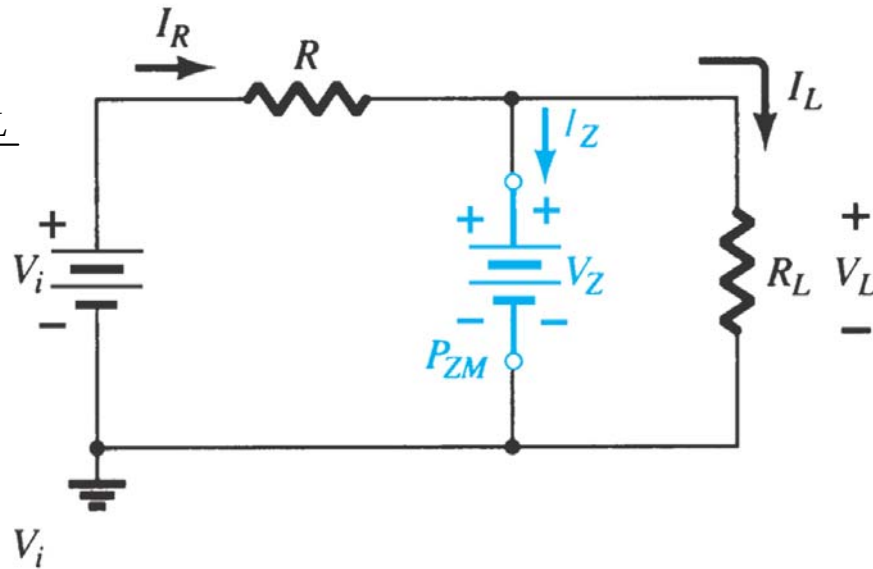
$$I_R = \frac{V_R}{R} = \frac{V_i - V_L}{R}$$



$$I_L = \frac{V_L}{R_L}$$


Since Zener is directly parallel to R_L , then $V_L = V_Z$

Zener current, applying Kirchhoff's current law $I_R = I_Z + I_L$



Thus $I_Z = I_R - I_L$

And Power $P_Z = V_Z I_Z$

Ex: Determine V_L , V_R , I_Z and P_Z

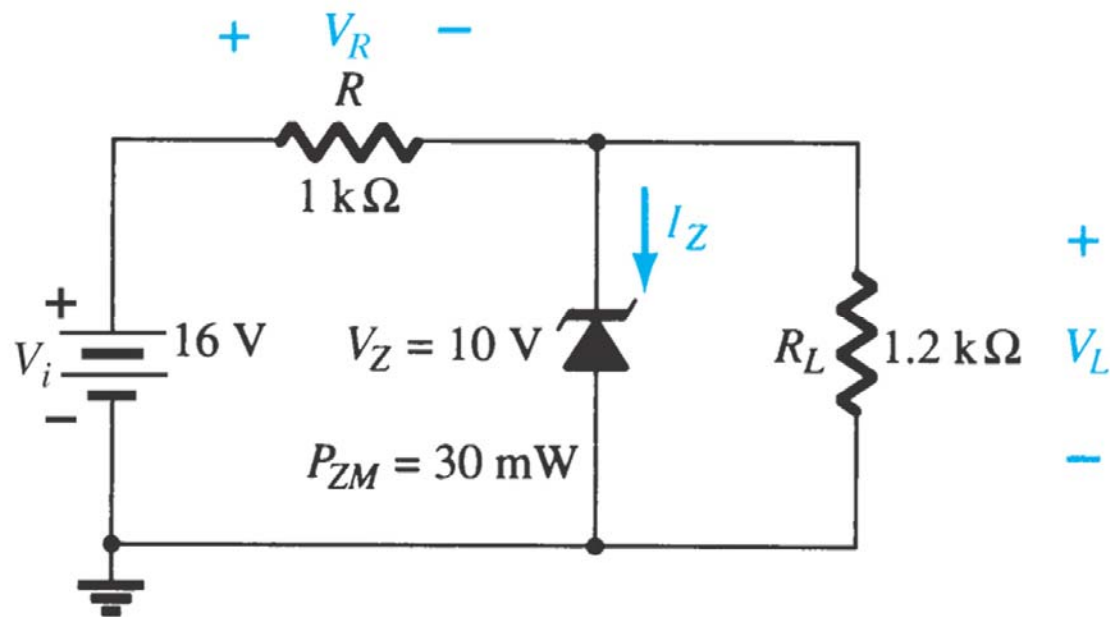

Solution

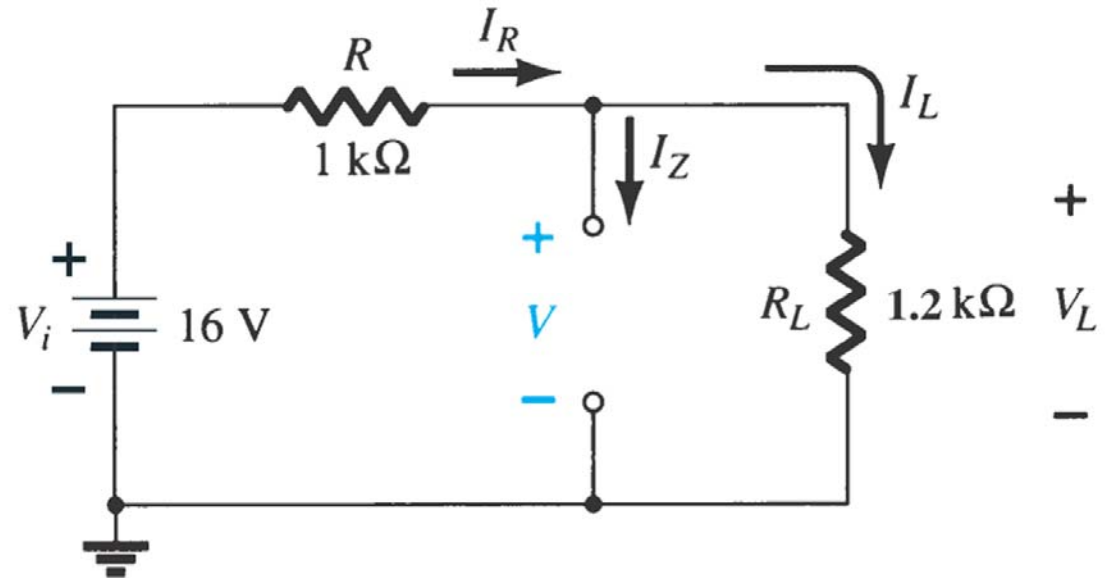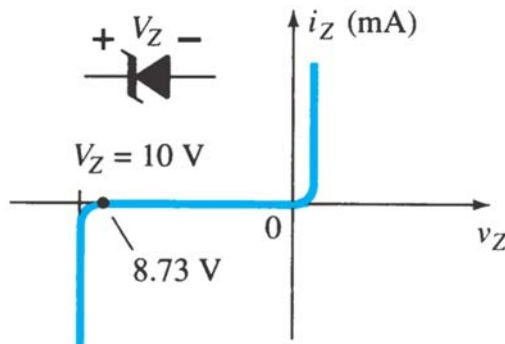

Applying voltage divider rule
$$V = \frac{R_L V_i}{R + R_L} = \frac{1.2\text{ k}\Omega (16\text{ V})}{1\text{ k}\Omega + 1.2\text{ k}\Omega} = 8.73\text{ V}$$

Since $V = 8.73\text{ V}$ is less than 10 V , the diode is in the “off” state


Thus $V_L = V = 8.73\text{ V}$ And $V_R = V_i - V_L = 16\text{ V} - 8.73\text{ V} = 7.27\text{ V}$

Since the Zener is off, then $I_Z = 0$ and $P_Z = V_Z I_Z = 0\text{ W}$

Ex: Determine V_L , V_R , I_Z and P_Z

Applying voltage divider rule
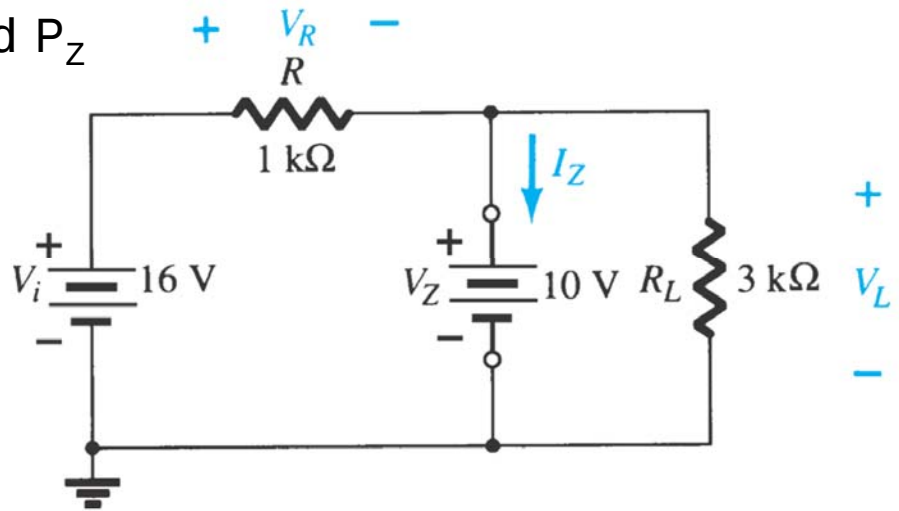
$$V = \frac{R_L V_i}{R + R_L} = \frac{3k\Omega(16V)}{1k\Omega + 3k\Omega} = 12V$$



Since $V=12V$ is greater than $V_Z=10V$, the Zener is in “on” state

Therefore $V_L=V_Z=10V$ and $V_R = V_i - V_L = 16V - 10V = 6V$

$$I_L = \frac{V_L}{R_L} = \frac{10V}{3k\Omega} = 3.33mA \qquad I_R = \frac{V_R}{R} = \frac{6V}{1k\Omega} = 6mA$$

and
$$I_Z = I_R - I_L = 6mA - 3.33mA = 2.67mA$$

To determine the resistor range

To determine the minimum load that can turn on the diode
So that $V_L = V_Z$ ' that is

$$V_L = V_Z = \frac{R_L V_i}{R_L + R}$$

Solving for R_L ' we have

$$R_{L\min} = \frac{RV_Z}{V_i - V_Z} \quad \text{and} \quad I_{L\min} = \frac{V_L}{R_L} = \frac{V_Z}{R_{L\min}}$$

Thus any resistance value greater than $R_{L\min}$ will ensure that the Zener diode is in the “on” state

To determine the resistor range

Once the diode is in the “on” state, the voltage across R remains fixed at

$$V_R = V_i - V_Z$$

And IR remains fixed at $I_R = \frac{V_R}{R}$

The Zener current $I_Z = I_R - I_L$


But the I_Z is limited by the manufacturer I_{ZM} , then

$$I_{Lmin} = I_R - I_{ZM}$$

And the maximum load resistance as $R_{Lmin} = \frac{V_Z}{I_{Lmin}}$

Determine the range of R_L and I_L that will result in V_{RL} being maintained at 10V

Calculating for
minimum load
 R_{Lmin}

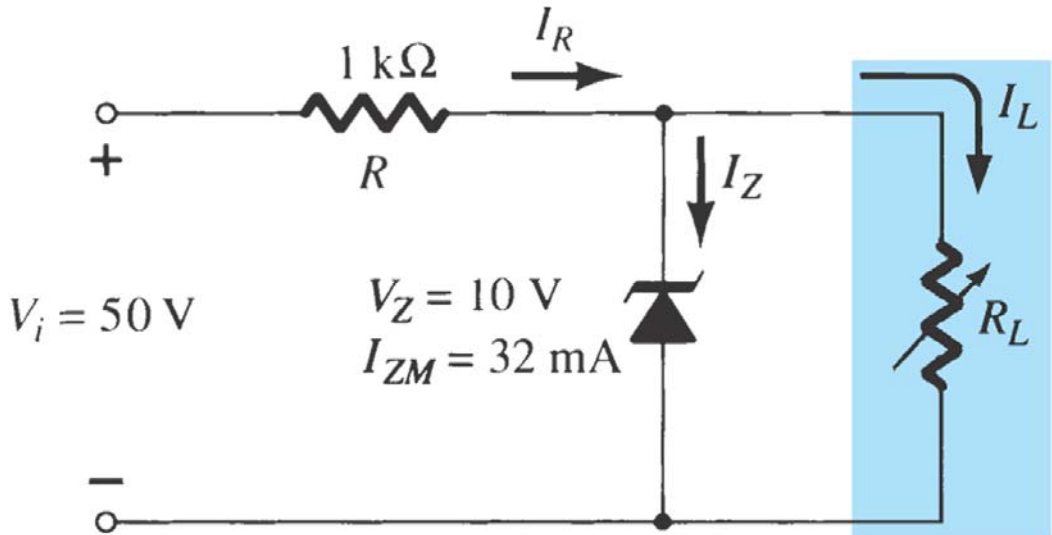

$$R_{Lmin} = \frac{RV_Z}{V_i - V_Z} = \frac{(1\text{k}\Omega)(10\text{V})}{50\text{V} - 10\text{V}} = \frac{10\text{k}\Omega}{40} = 250\Omega$$

The voltage across the resistor R is $V_R = V_i - V_Z = 50\text{V} - 10\text{V} = 40\text{V}$

This will give us

$$I_R = \frac{V_R}{R} = \frac{40\text{V}}{1\text{k}\Omega} = 40\text{mA}$$


Continue

The minimum level of I_L is $I_{L\min} = I_R - I_{ZM} = 40\text{mA} - 32\text{mA} = 8\text{mA}$


Maximum load $R_{L\max}$,

$$R_{L\max} = \frac{V_Z}{I_{L\min}} = \frac{10\text{V}}{8\text{mA}} = 1.25\text{k}\Omega$$

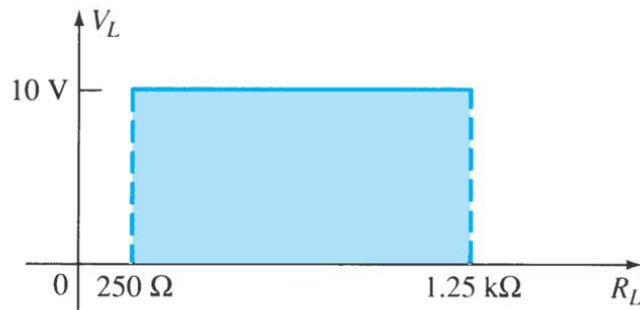Power $P_{\max} = V_Z I_{ZM} = (10\text{V})(32\text{mA}) = 320\text{mW}$



(a)

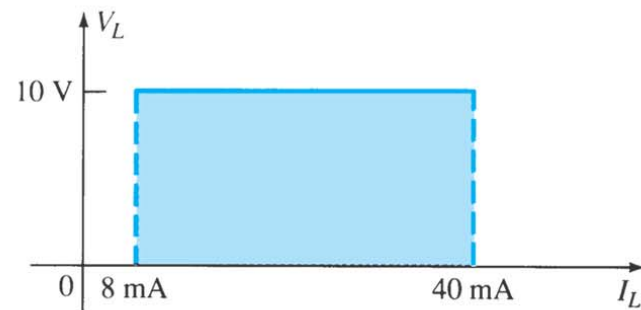

(b)

Fixed R_L and Variable V_i

The voltage V_i must be sufficiently large to turn the Zener diode on. The minimum turn on voltage $V_i = V_{i\min}$ is

$$V_L = V_Z = \frac{R_L V_i}{R_L + R} \quad \text{therefore} \quad V_{i\min} = \frac{(R_L + R)V_Z}{R_L}$$


Since the maximum Zener current I_{ZM} , Thus $I_{ZM} = I_R - I_L$

$$\text{Then } I_{R\max} = I_{ZM} + I_L$$

The maximum voltage

$$V_{i\max} = V_{R\max} + V_Z \quad \text{or} \quad V_{i\max} = I_{R\max} R + V_Z$$

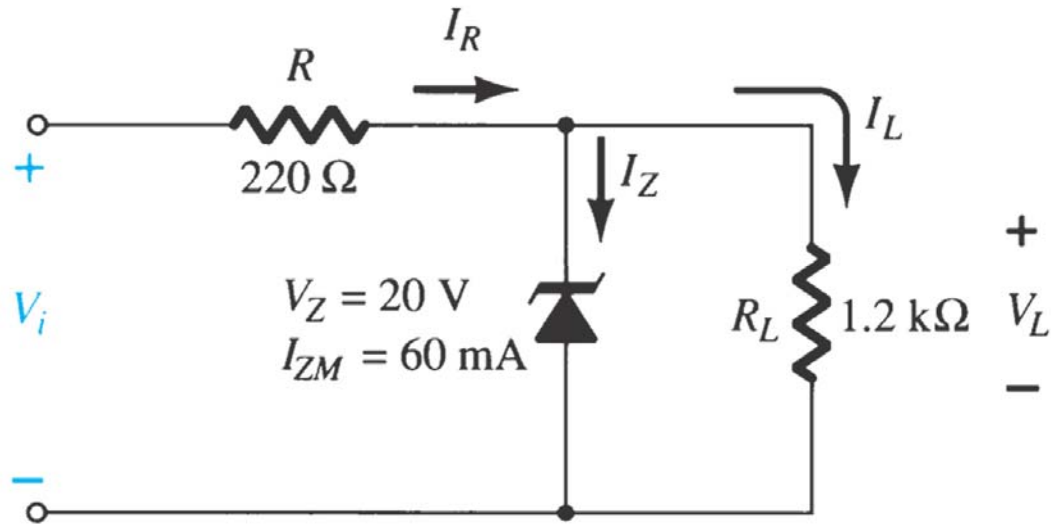Determine the range of values of V_i that will maintain the Zener diode in the “on” state.



Using the formula given before

$$V_{i\min} = \frac{(R_L + R)V_Z}{R_L} = \frac{(1200\Omega + 220\Omega)(20\text{V})}{1200\Omega} = 23.67\text{V}$$

$$I_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L} = \frac{20\text{V}}{1.2\text{k}\Omega} = 16.67\text{mA}$$


$$V_{i\max} = I_{R\max}R + V_Z$$


Continue

$$I_{R_{\max}} = I_{ZM} + I_L = 60\text{mA} + 16.67\text{mA} = 76.67\text{mA}$$

$$V_{i_{\max}} = I_{R_{\max}} R + V_Z = (76.67\text{mA})(0.22\text{k}\Omega) + 20\text{V} = 36.87\text{V}$$

The V_i range is plotted below

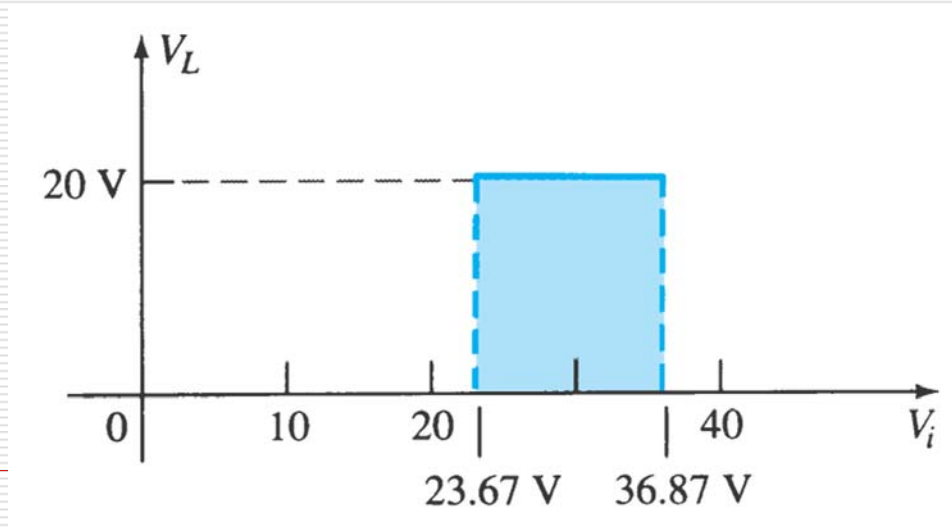


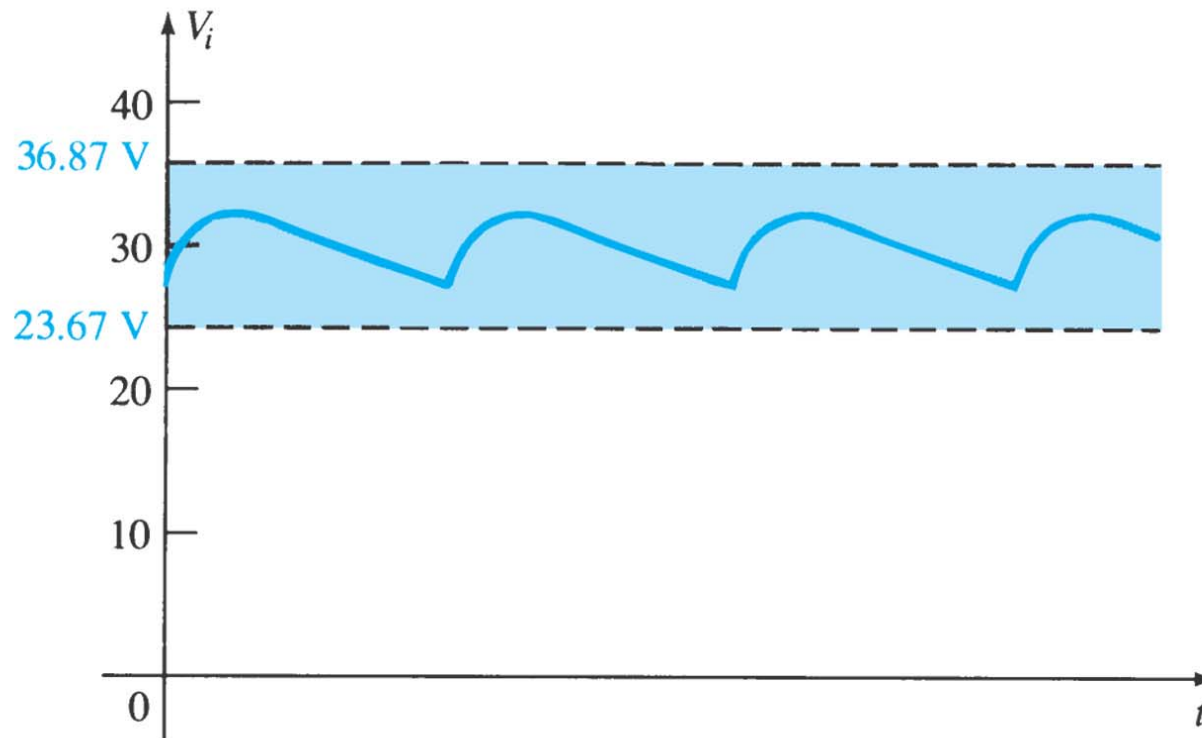


If the input is a ripple from full-wave rectified and filtering as shown, as long as within the specified voltage, the output will still remain constant at 20V.


Voltage Multiplier

HALF-WAVE VOLTAGE DOUBLER

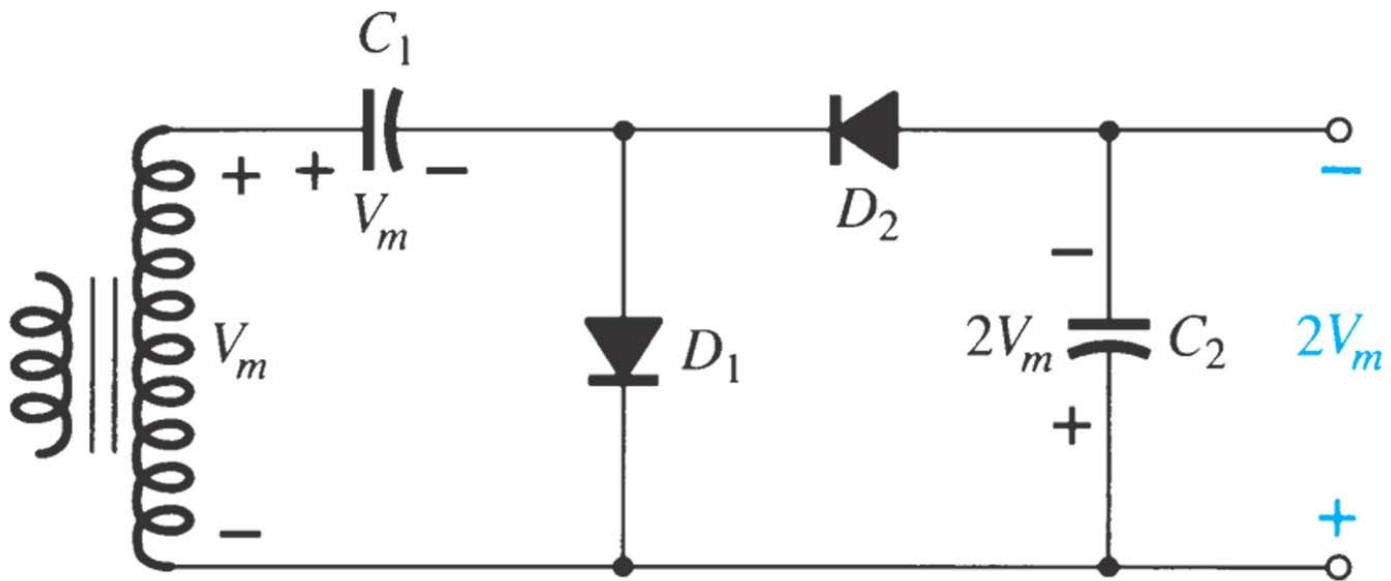

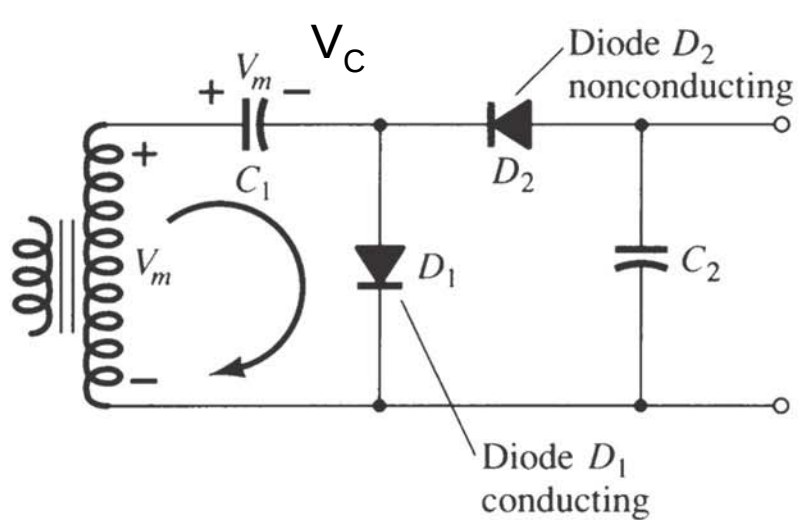

(a)

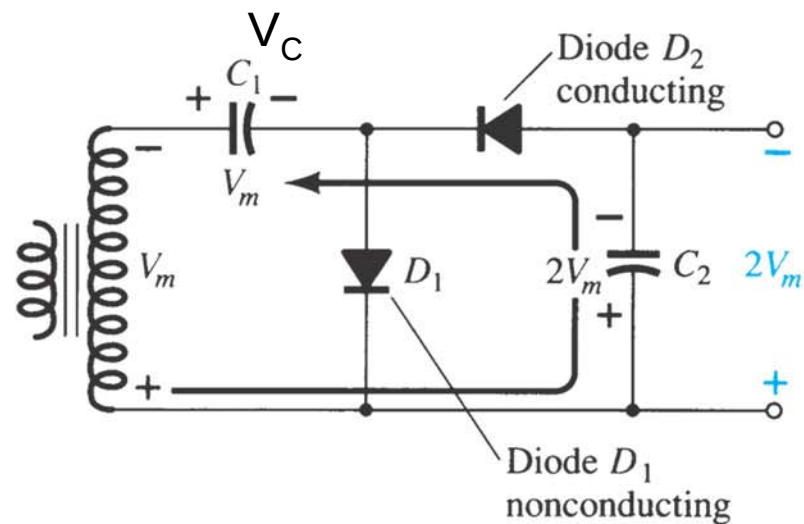



(b)

(a) During the positive voltage half-cycle across the transformer, the diode D_1 conducts and D_2 is cut off. The capacitor C_1 charges up to peak rectified voltage V_m .

(b) Second half cycle, D_2 conducts and D_1 is cut-off. Now the capacitor C_2 is charged up with $V_m + V_C = V_m + V_m = 2V_m$

FULL-WAVE VOLTAGE DOUBLER

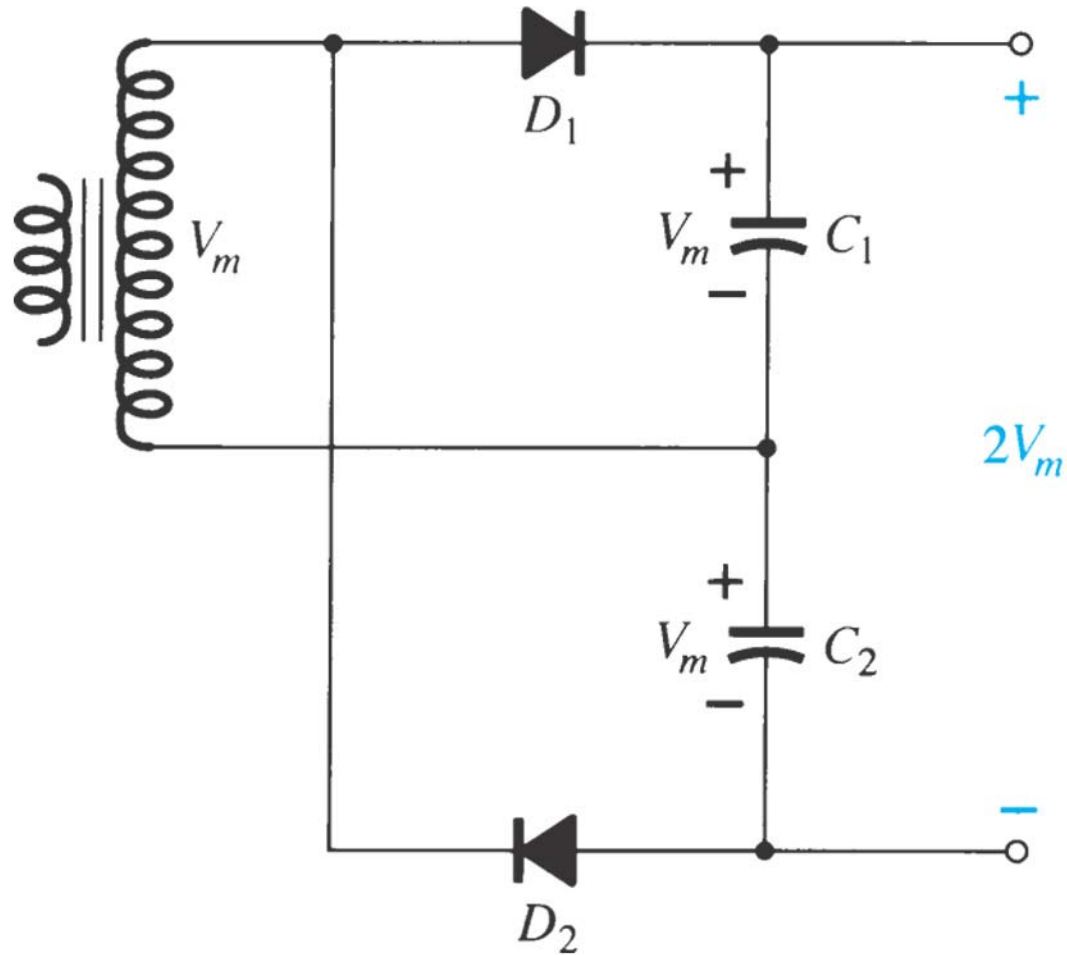


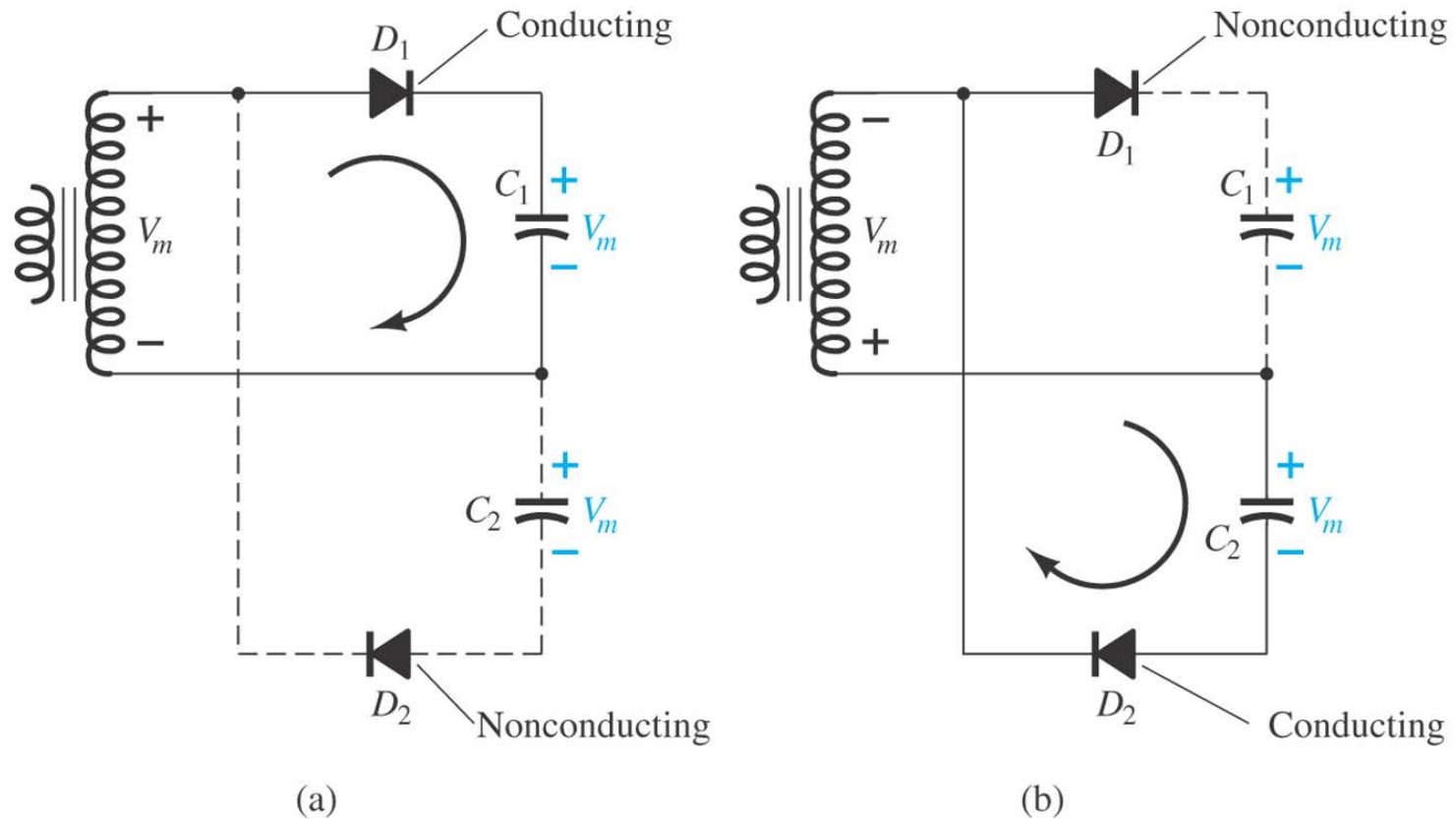

(a) Positive cycle, D_1 is conducting, thus charging C_1 to V_m . D_2 is not conducting so charging on capacitor C_2 .

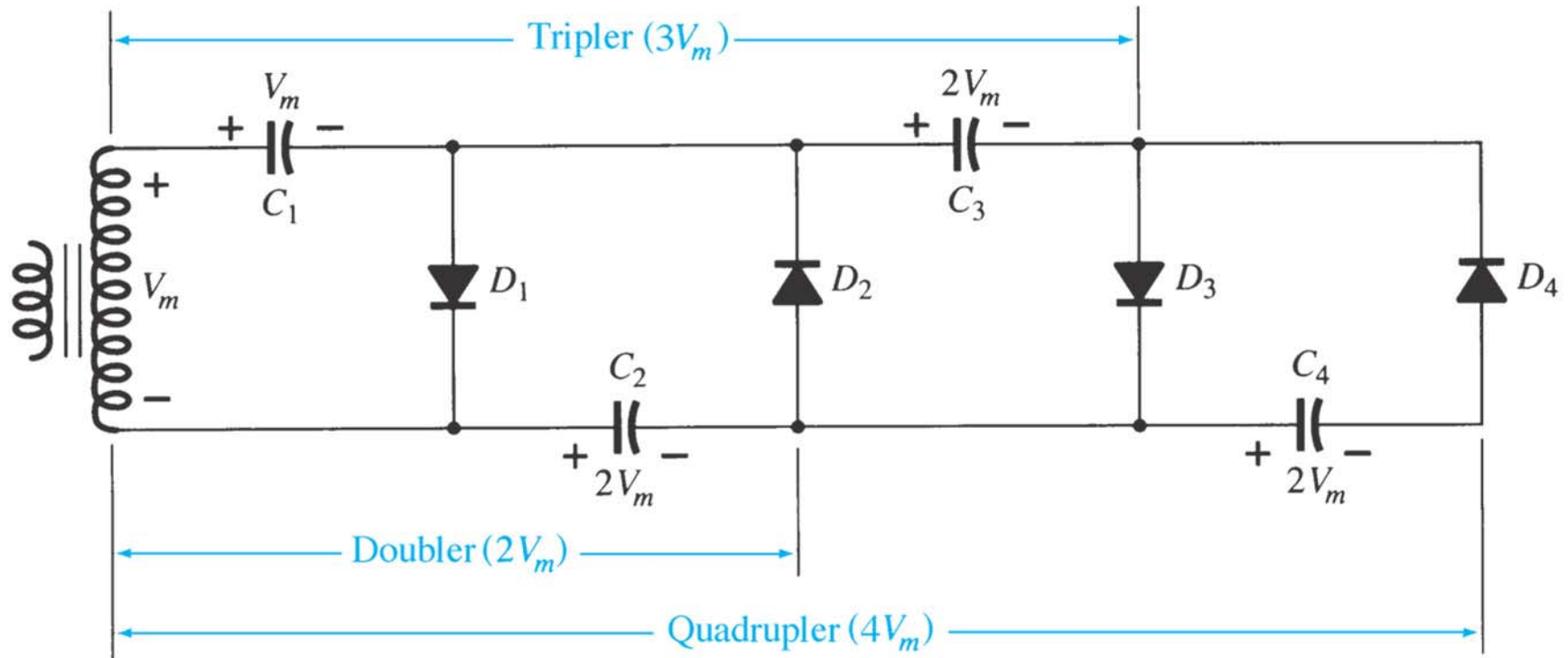
(b) Negative cycle, D_2 is conducting, thus charging C_2 to V_m . D_1 is not conducting so C_1 still maintain the charging voltage

HALF-WAVE DOUBLER, TRIPLER AND QUADRUPLER




By arranging alternately capacitor and diode, we are able to obtain voltage doubler, tripler and quadrupler. C₁ plus transformer charging C₂. C₂ charging C₃ and C₃ charging C₄.

Protective configuration

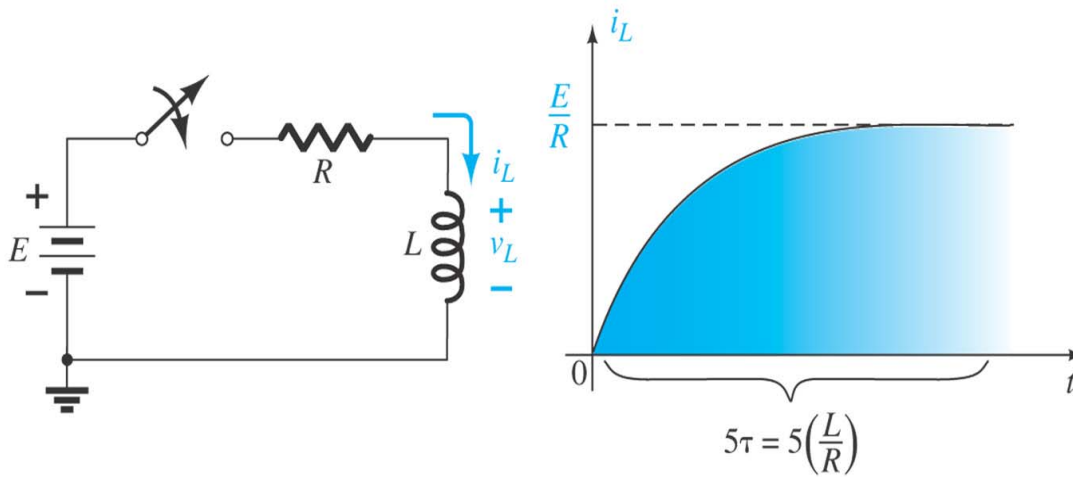


Transient phase of a simple RL cct

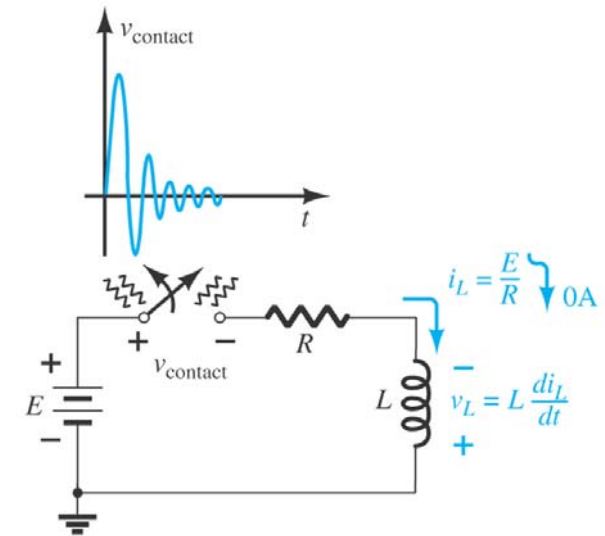

Arcing during opening the switch

Trying to change the current through an inductive element too quickly may result in an inductive kick that could damage surrounding elements or the system itself

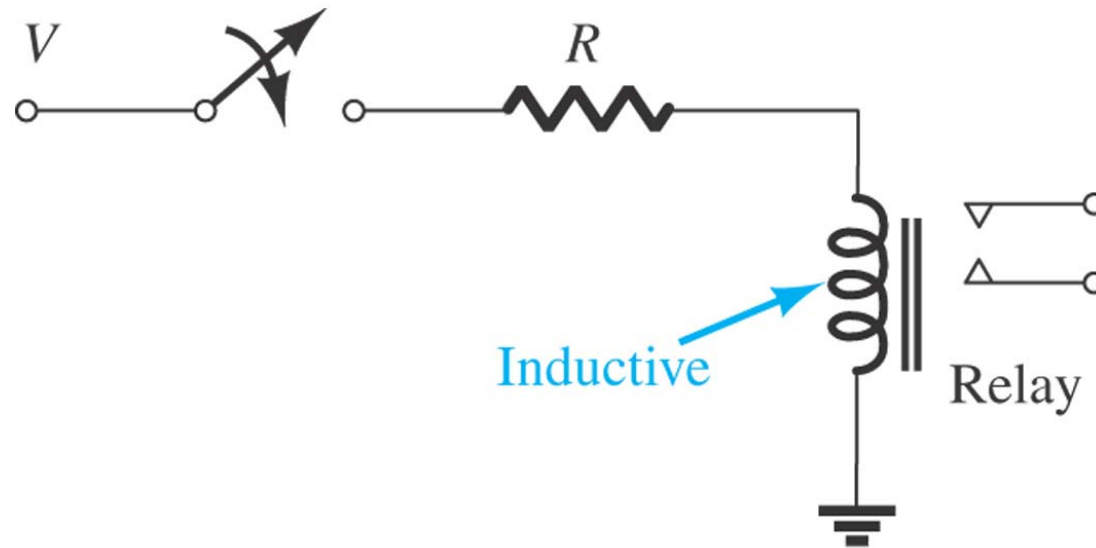
The RL circuit may be used to control the relay



(a)

During closing the switch the coil will gain a steady current.
When closing, the arcing may cause the problem to the relay.

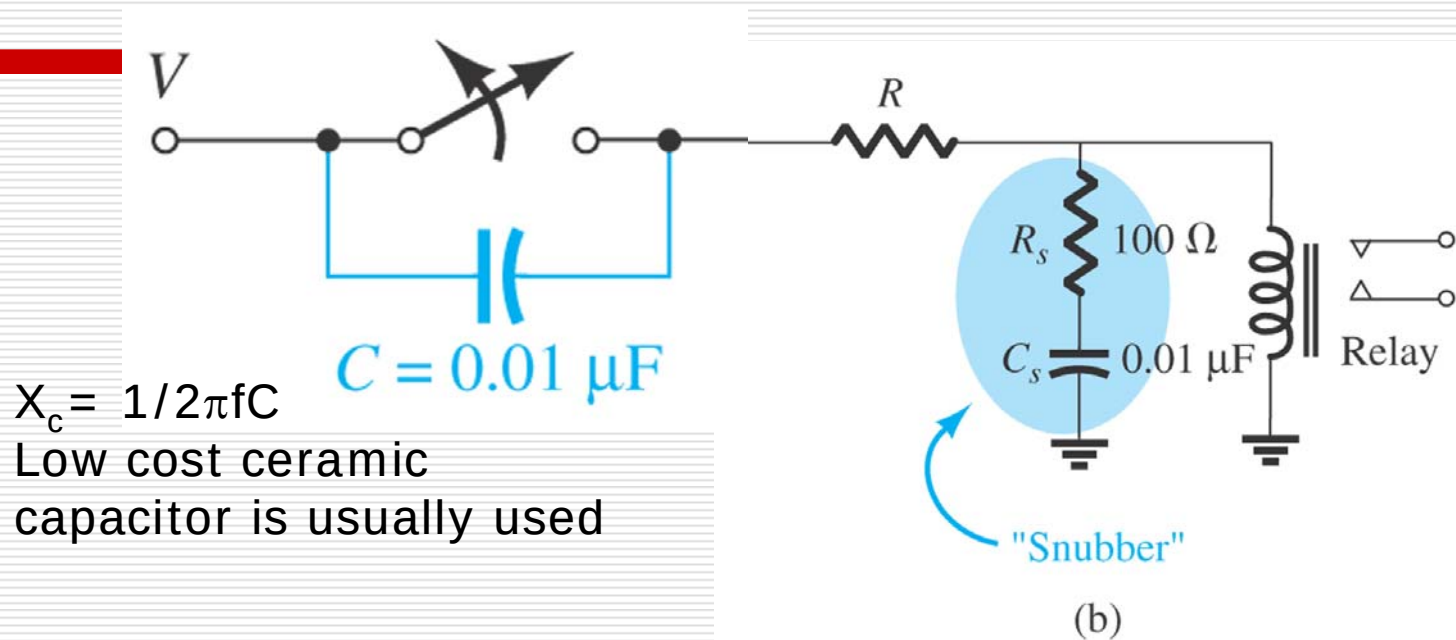This is the cheapest circuit to protect the switching system.




A capacitor is parallel to the switch. It is acting as a bypass (or shorting) the high frequency component.

A snubber is also to short circuit the high frequency component


The resistor in series is to protect the surge current.

Diode protection for RL circuit

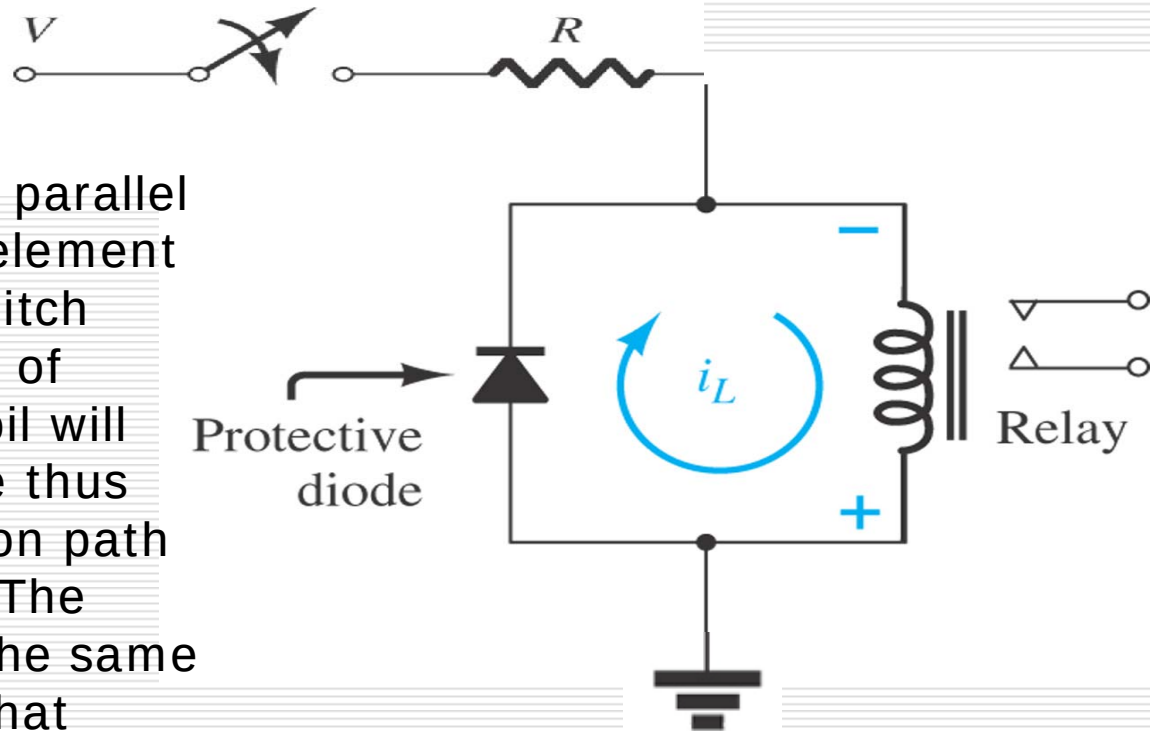A diode is placed parallel to the inductive element (relay). When switch open the polarity of voltage across coil will turn on the diode thus provide conduction path for the inductor. The diode must has the same current level to that current passing the coil




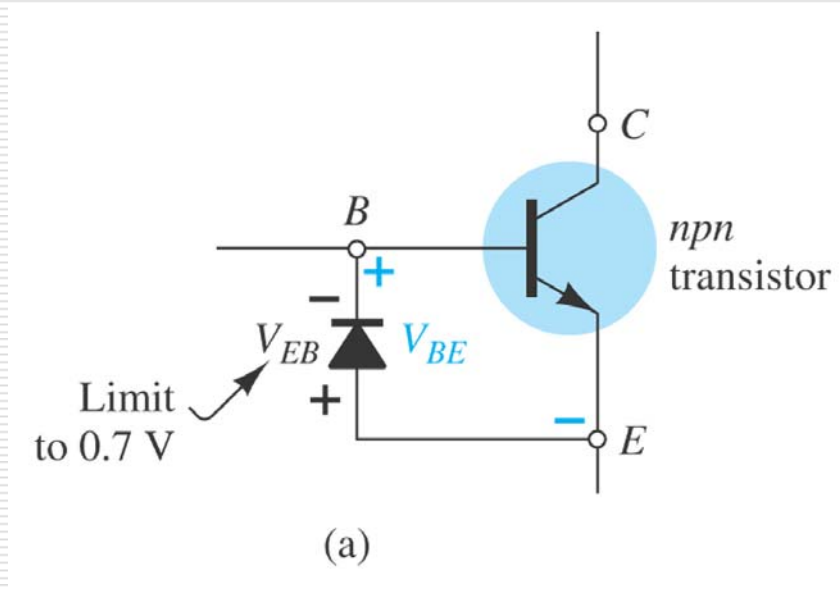Diode protector to limit the emitter –base voltage





V_{BE} is limited to 0.7V (knee voltage of the silicon diode)

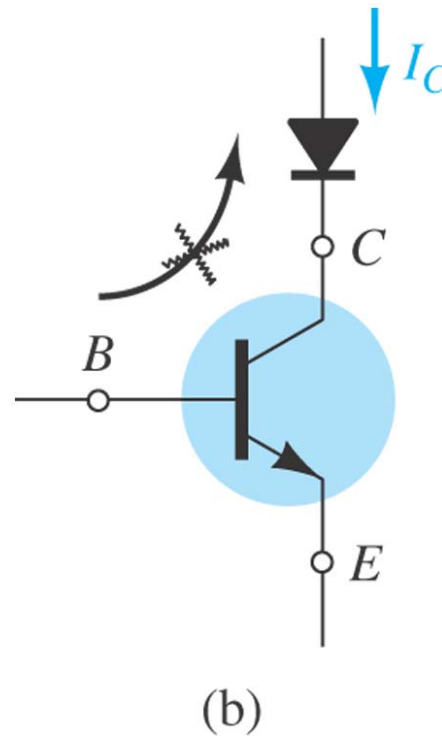Diode protection to prevent a reversal in collection current




A current from B to C will be blocked by the diode

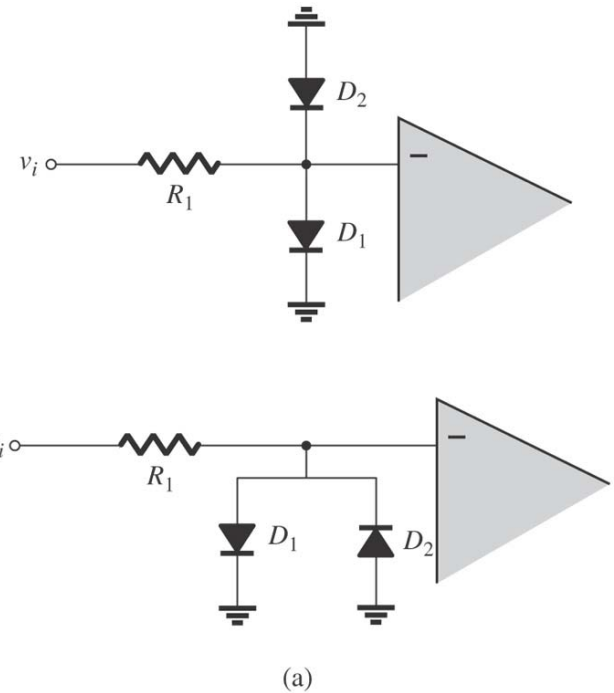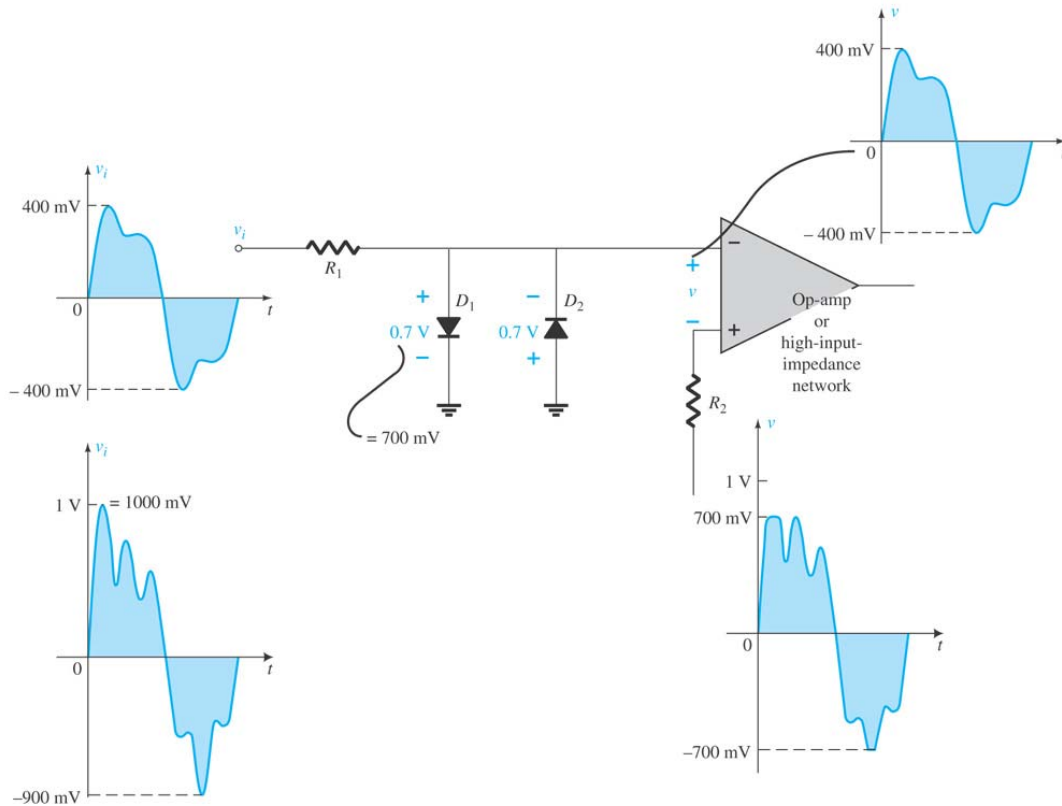Diodes can be used to limit the input of OPAM to 0.7V




Same appearance

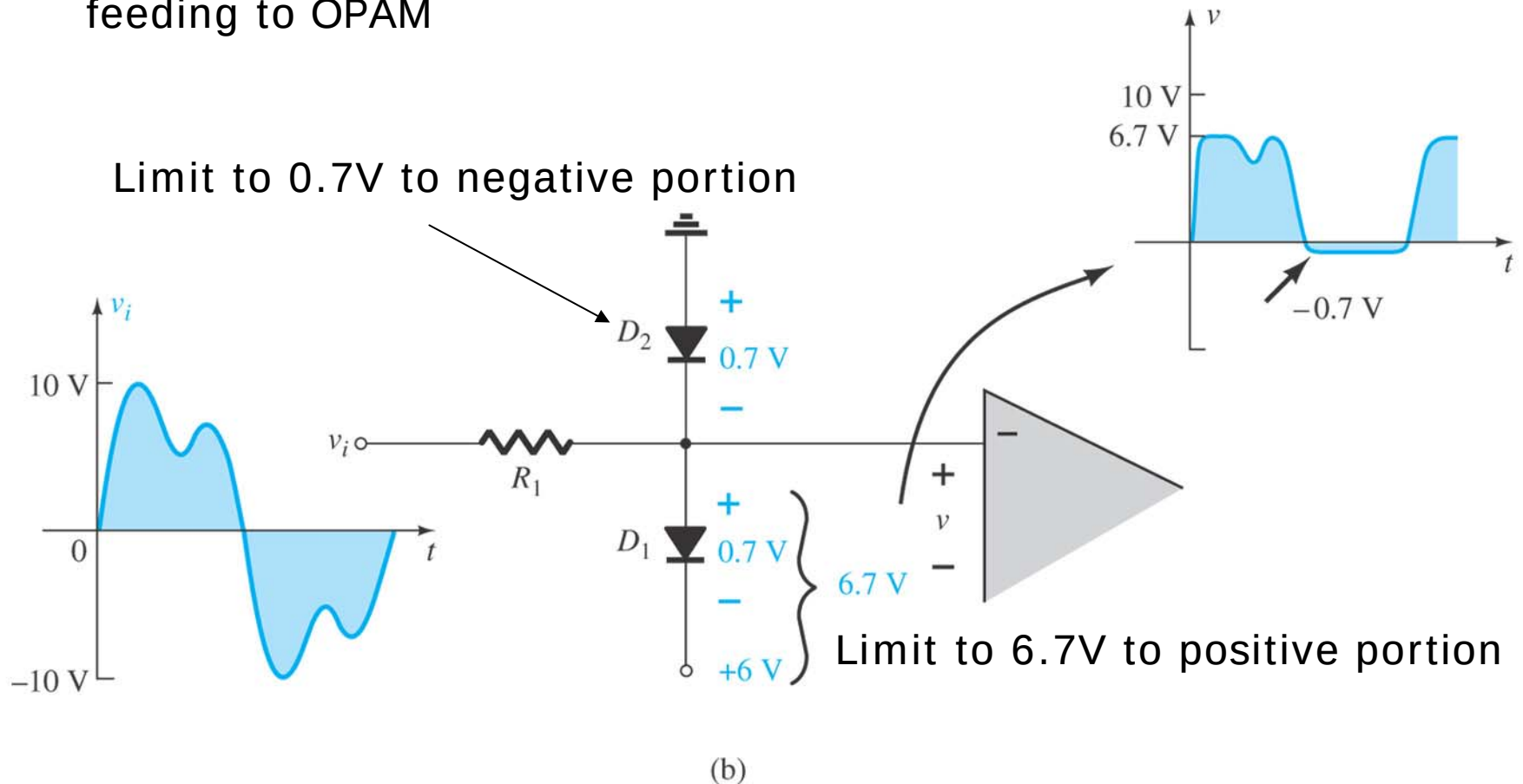Introduce voltage to increase limitation of the positive portion and limit to 0.7V to the negative portion before feeding to OPAM




POLARITY INSURANCE

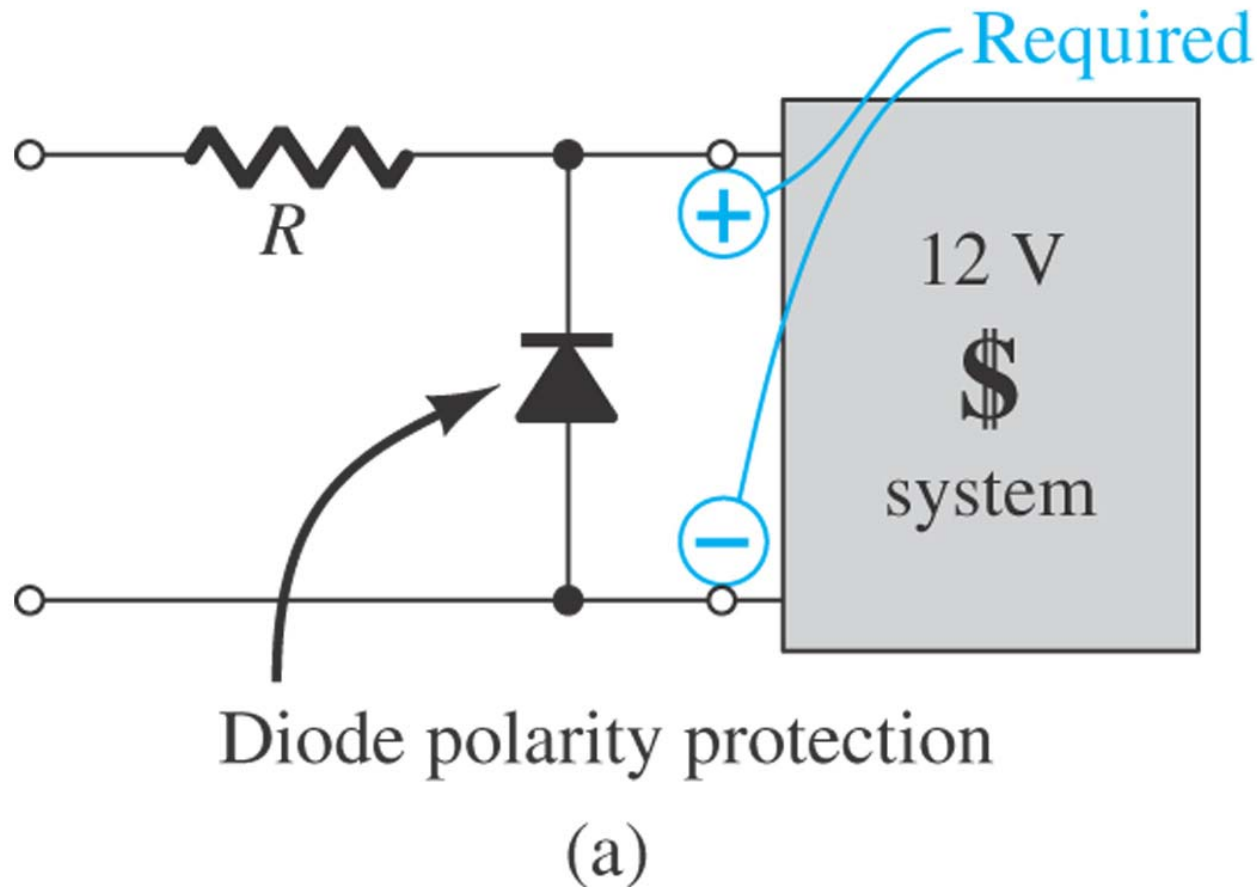


This circuit is to prevent from mistaken connecting the battery with wrong polarity

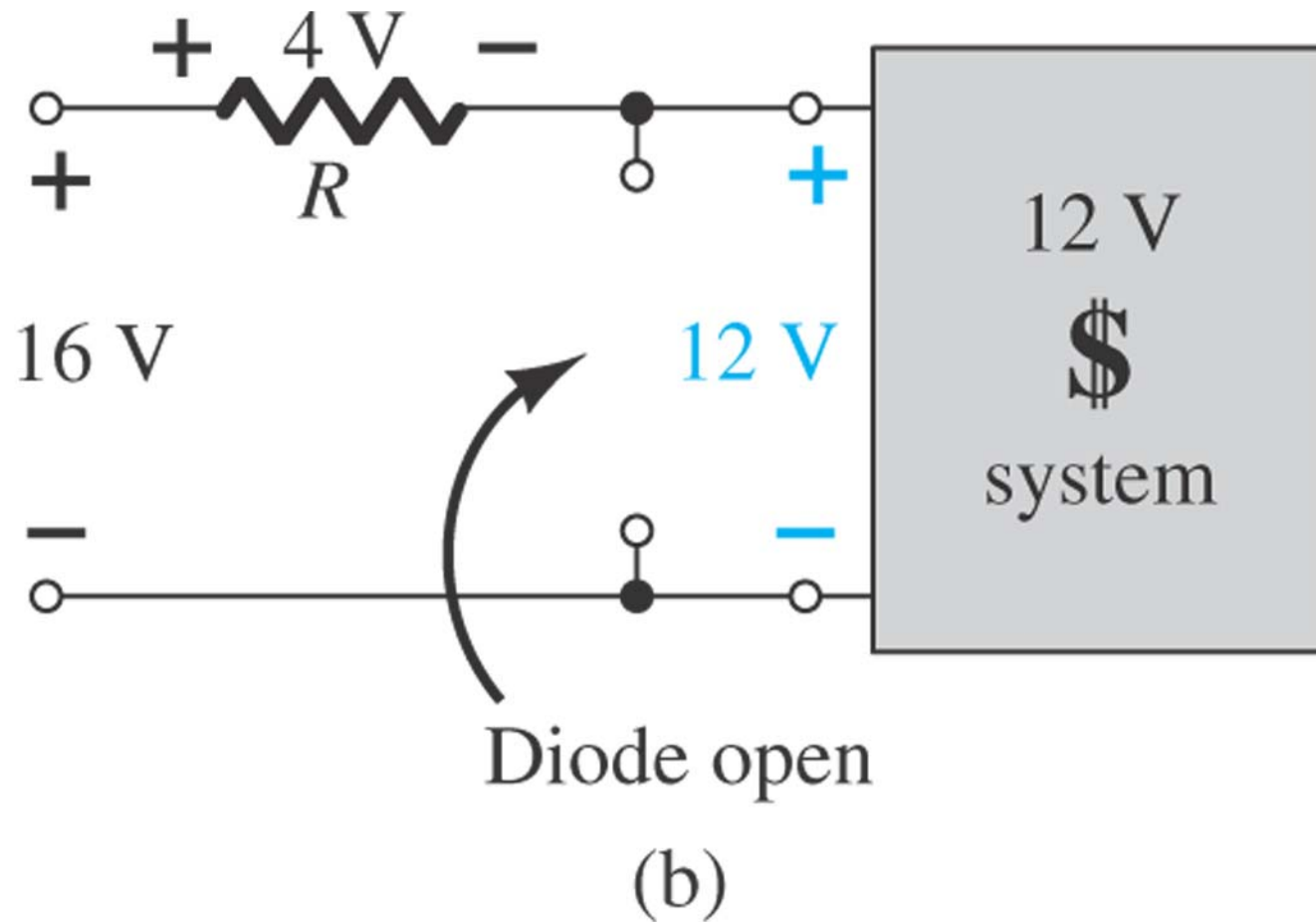If the polarity is okay then the diode circuit is in open state




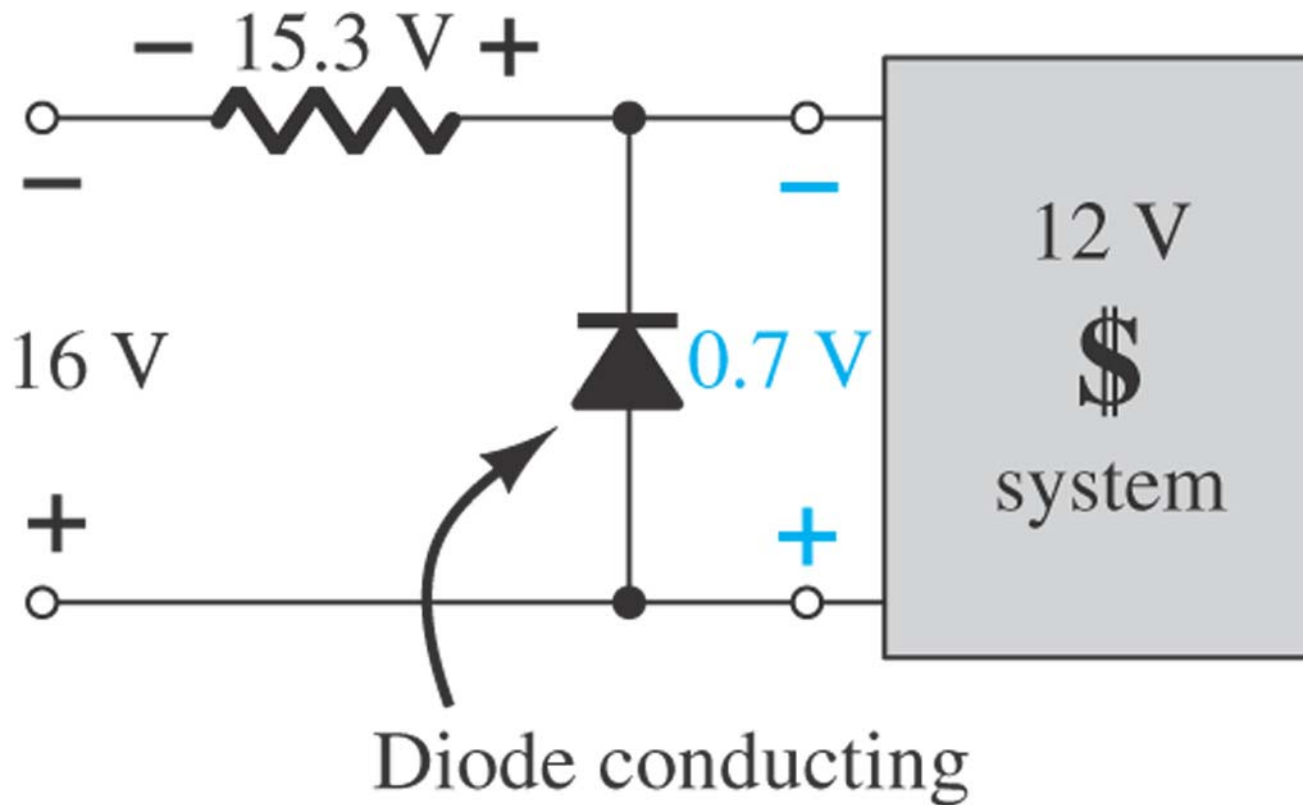If the polarity is not okay then the current is bypass thru diode.
This will stop the battery to damage the \$ system




(c)

Battery –powered backup

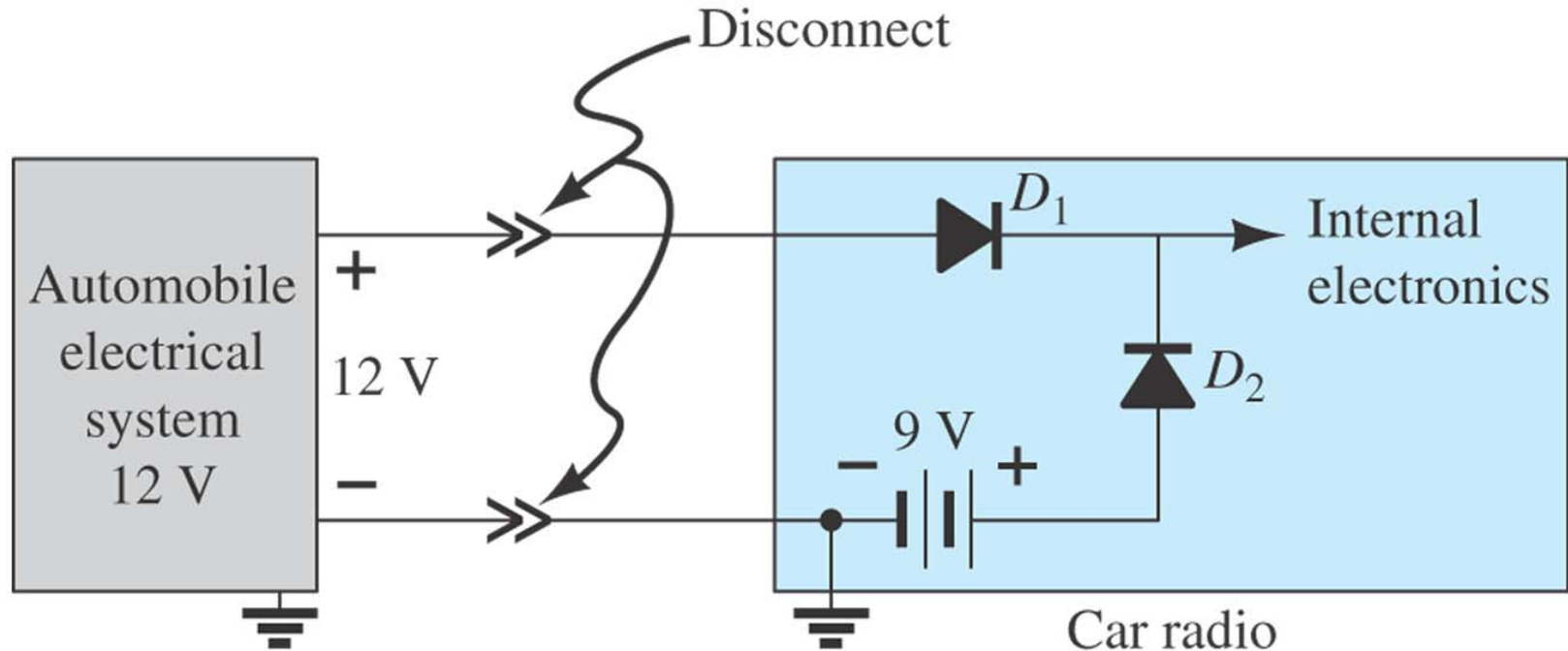


When electrical power is connected D_1 is "on" state and D_2 will be "off" state, thus only electrical power is functioned. When electrical power is disconnected D_1 is "off" state and D_2 is conducted, thus the power will come from the battery.

Polarity detector using diodes and LED

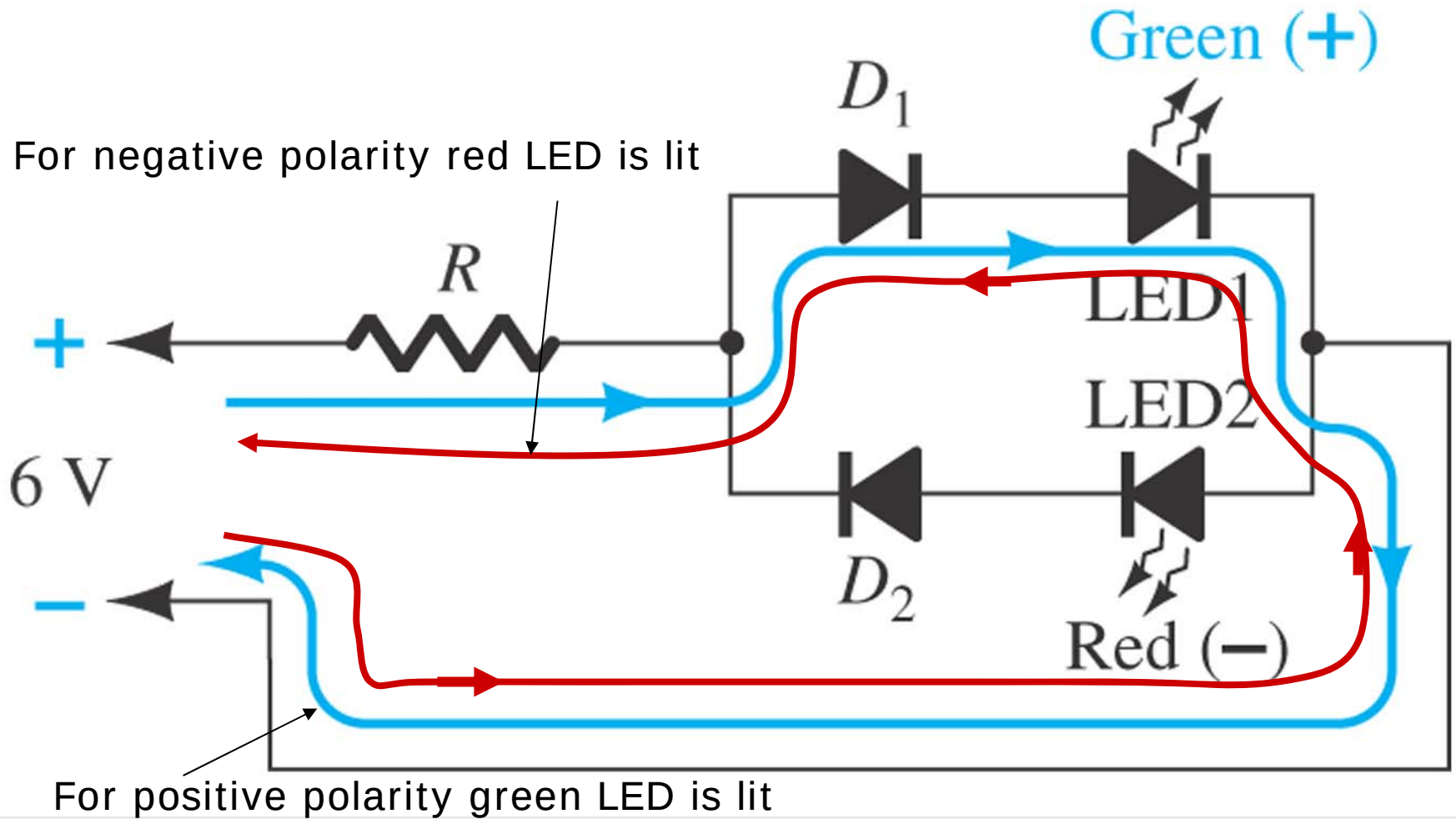


LED diodes are arranged for EXIT sign display.

EXIT

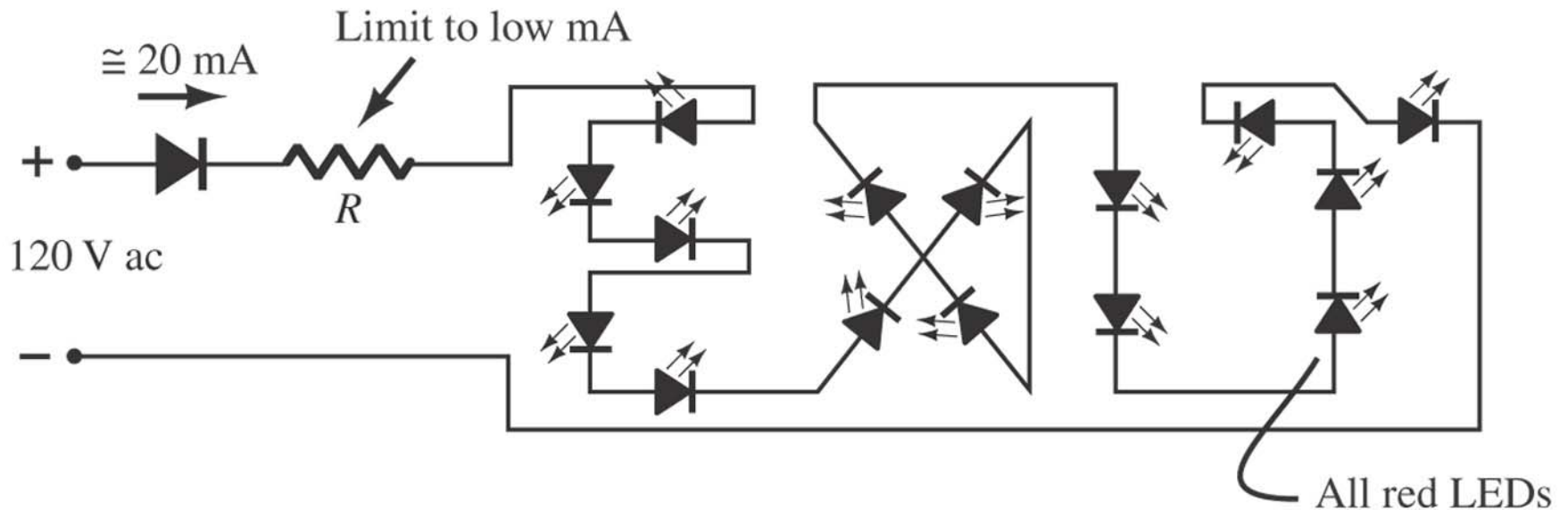


Voltage Reference Levels circuit

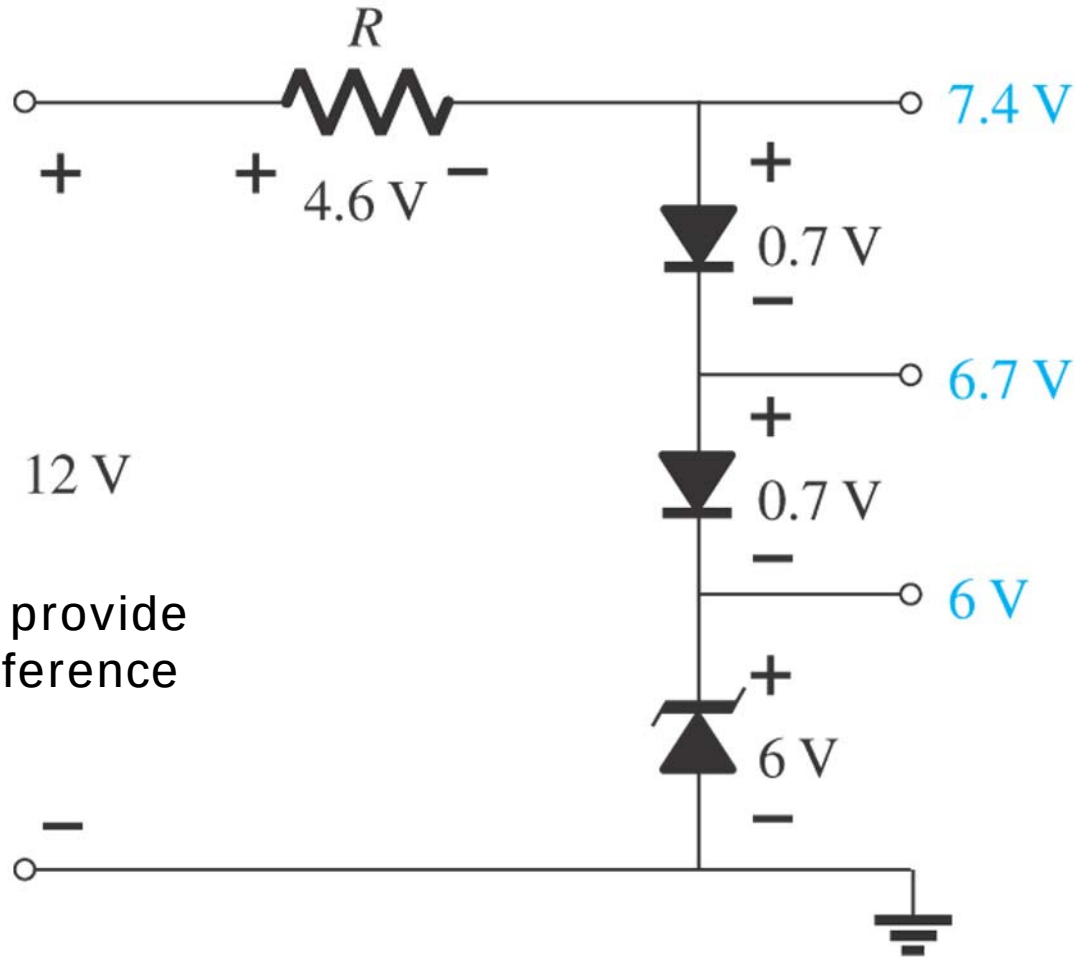


This circuit provide
different reference
levels

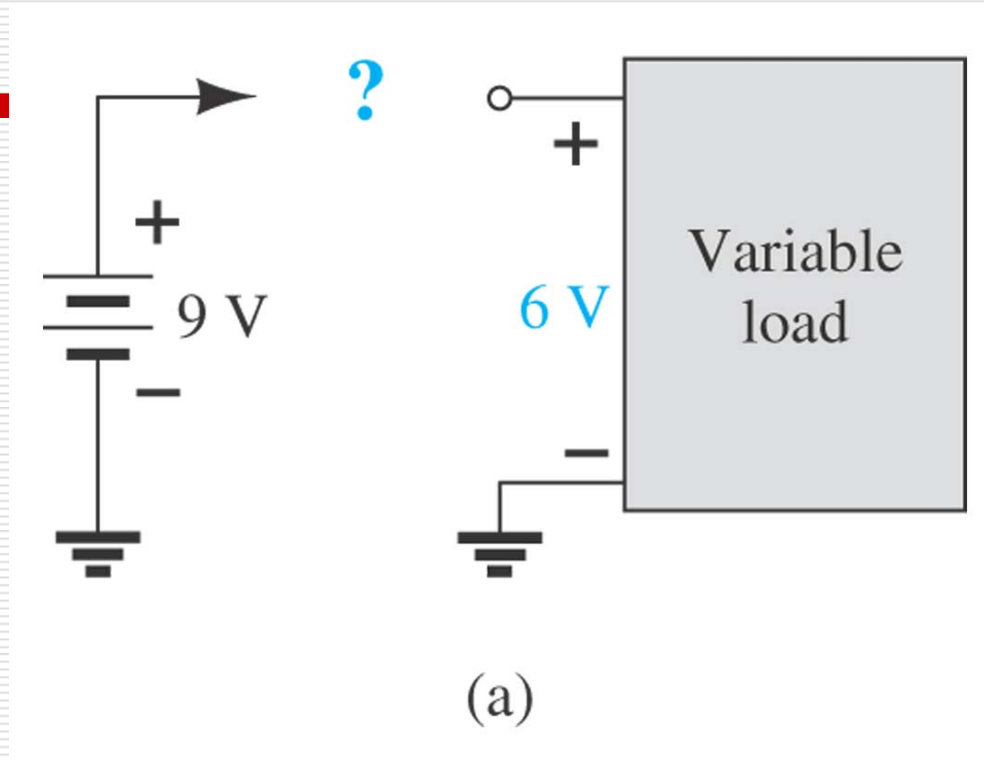To establish a voltage level insensitive to the load current



A battery is connected to a network that has different voltage supply and variable load. The battery available is 9V but the network require 6V. How?

Using external resistor

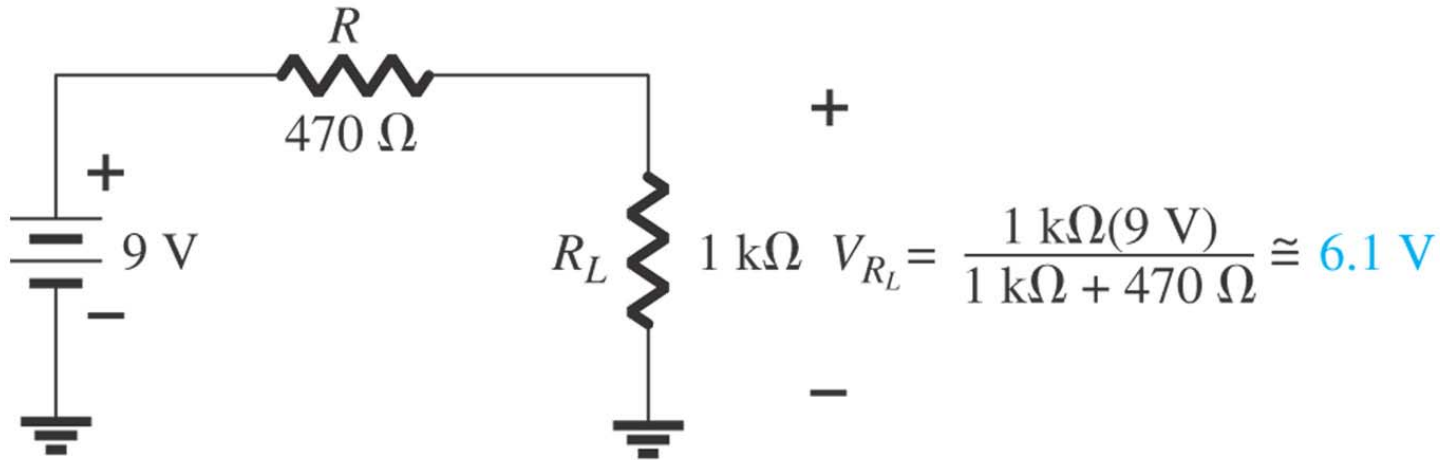


(b)

Let's say the load is $1\ \text{k}\Omega$, then using voltage divider, we determine the value of external resistor we obtain approximately $470\ \Omega$. We calculate the V_{R_L} , give us $6.1\ \text{V}$.

Now if we change the load to $600\ \Omega$ but the external still same, then V_{R_L} become $4.9\ \text{V}$... thus the system will not operate correctly!!




Using diode

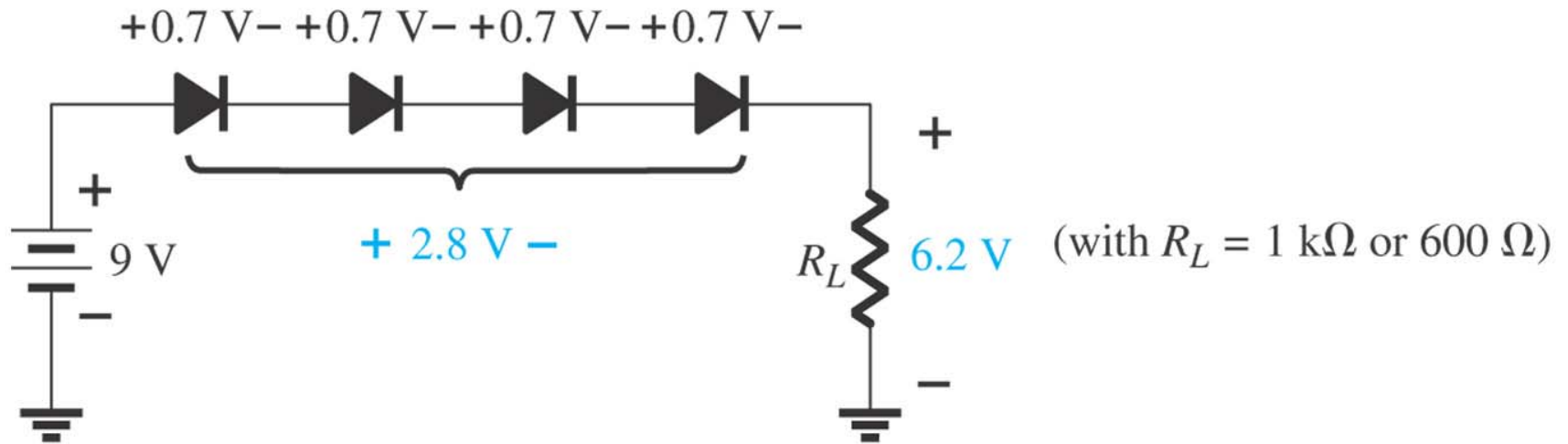

(c)


Using diode the voltage can be converted using 4 silicon diode which give a drop of voltage around 2.8 V , thus the required voltage of 6.2 V is obtained. This network does not sensitive to the load.

AC regulator and square-wave generator

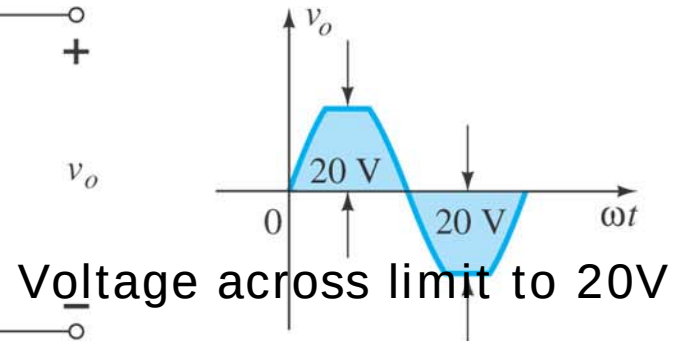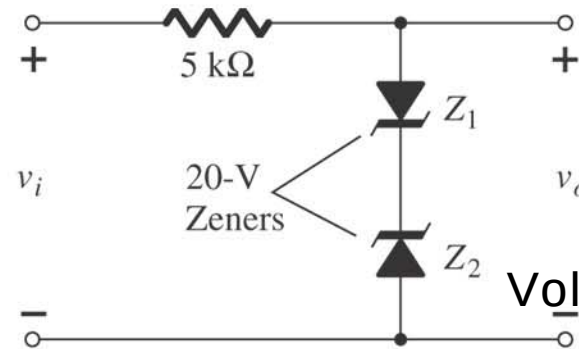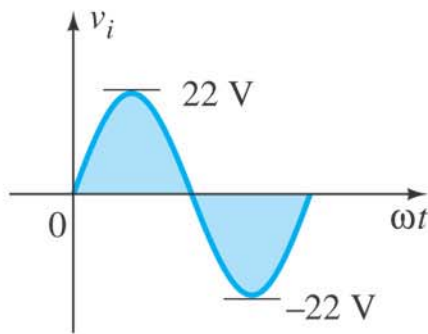

Voltage across limit to 20V

(a)

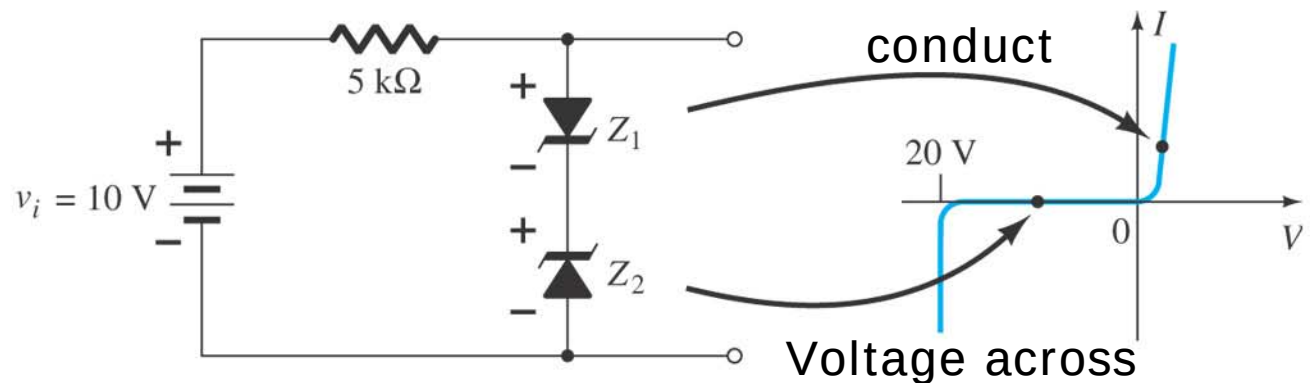

Voltage across corresponding to the input if less than 20V

(b)

Same configuration to produce square -wave

