

EEM 323/3 - Assignment

1. A platinum resistance sensor has a resistance of 100Ω at 0°C and a temperature coefficient of resistance of $4 \times 10^{-3} \text{ }^\circ\text{C}^{-1}$. Given that a 15 V supply is available, design a deflection bridge giving an output range of 0 to 100 mV for an input range of 0 to 100°C :
 - (a) using the procedure discussed in lectures.
 - (b) using the linear approximation discussed in lectures.
 - (c) how should the circuit be altered if the input range is changed to 50 to 150°C ?

Give values for all circuit components and assume a high impedance load.

2. The resistance $R_\theta(\Omega)$ of a thermistor varies with temperature $\theta^\circ\text{K}$ according to the following equation

$$R_\theta = 0.0585 e^{\left(\frac{3260}{\theta}\right)}$$

Design the deflection bridge incorporating the thermistor to the following specification:

- (a) input range $0 - 50^\circ\text{C}$;
 - (b) output range $0 - 1.0 \text{ V}$;
 - (c) non-linearity, $N(I) \leq 5.0 \%$
3. Fig. 1 shows a four-lead bridge circuit; R_c is the resistance of the leads connecting the sensor to the bridge circuit. Show that $E_{Th} \approx V_s \left(\frac{R_0}{R_3} \right) \alpha T$, i.e. the bridge output voltage is unaffected by changes in R_c . State all assumptions.

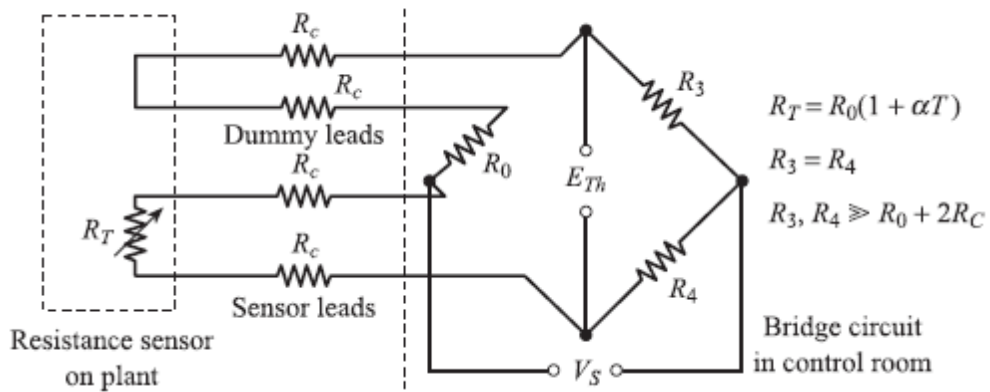


Fig. 1

4. A low-voltage Schering bridge shown in Fig. 2 is used to measure the unknown permittivity of a specimen using 2-plate capacitor, C_1 with area A and distance d .

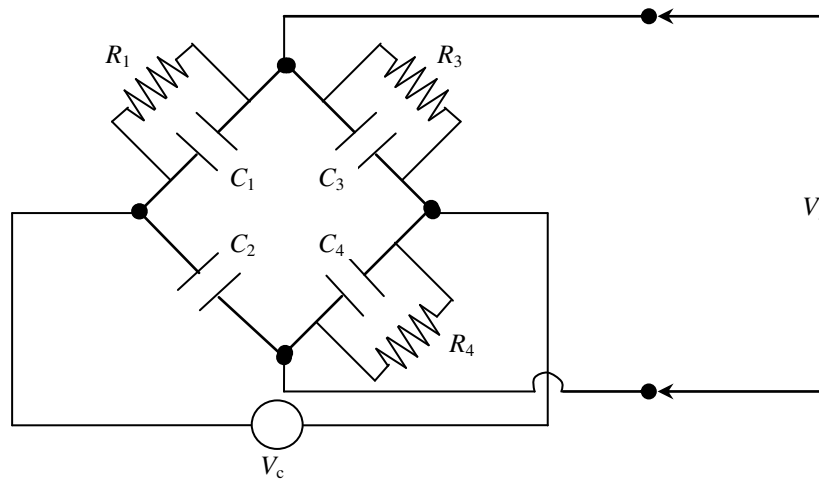


Fig. 2

Referring to Fig. 2, R_1 is a stray resistor, R_3 and R_4 are pure non-reactive resistors, and C_2 , C_3 and C_4 are pure non-reactive capacitors. Without the specimen the following balanced condition are attained: $C_3 = C_4 = 120 \text{ pF}$, $C_2 = 140 \text{ pF}$ and $R_3 = R_4 = 5000 \Omega$. With the specimen the values changed to $C_3 = 200 \text{ pF}$, $C_4 = 1000 \text{ pF}$, $C_2 = 900 \text{ pF}$, and $R_3 = R_4 = 500 \Omega$. If $V_c = 10 \text{ V (RMS)}$ and $\omega = 5000 \text{ rad/s}$, calculate the relative permittivity of the specimen.

5. (a) List common source of errors in AC bridge circuits. Hence, state several precautions that should be taken to reduce the errors.
- (b) In designing a sensing circuit for measuring the level of oil (ϵ_{oil}) inside a tank, the capacitive level sensor has been proposed. Meanwhile, the simplified four-arm De-Sauty bridge has been suggested for signal detection. Figure 3 shows the instrumentation and measurement system. In this figure R_4 and C_2 are pure resistance and capacitance respectively, C_h is the sensor capacitance at a height h of the oil and R_4 is the variable resistance.

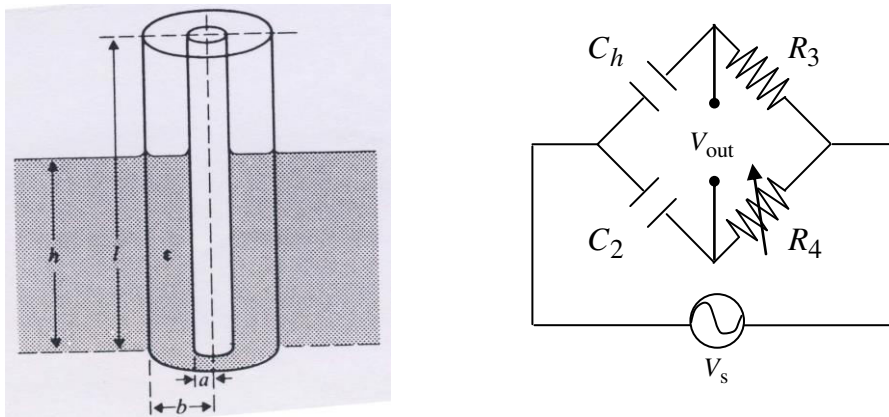


Fig. 3

The relationship between C_h and h of the capacitive sensor is as follows:

$$C_h = \frac{2\pi\epsilon_0}{\log_e\left(\frac{b}{a}\right)} [1 + (\epsilon_{oil} - 1)h]$$

- (i) Derive the balanced conditions of Fig. 3,

(ii) Calculate h when at balance $C_2 = 1000 \mu\text{F}$, $R_4 = 10 \Omega$, $R_3 = 1250 \Omega$, $\epsilon_0 = 1$, $\epsilon_{\text{oil}} = 3$, $b = 2 \text{ cm}$ and $a = 0.5 \text{ cm}$,

(iii) State the main source of error in 1(b) (ii).

6. (a) Explain the important of the quality factor Q and the damping factor ξ in filter design.

(b) The Sallen-Key second order low pass filter is shown in Fig. 4.

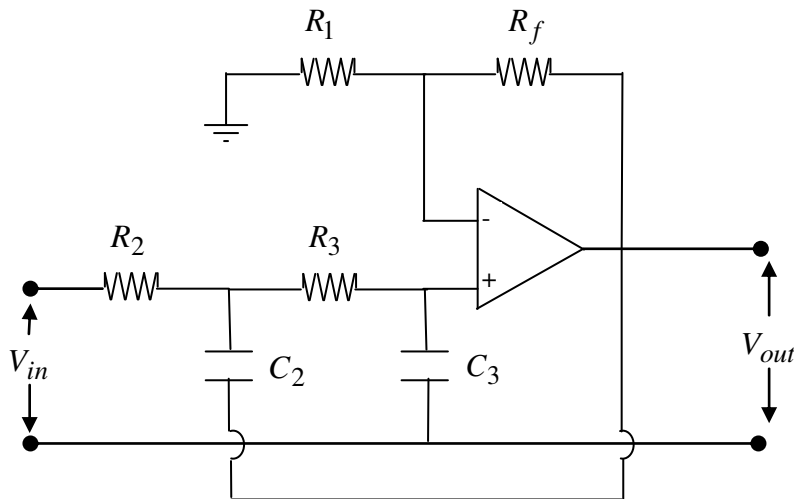


Fig. 4

Prove the transfer function of the above filter is given by

$$H(s) = \frac{\frac{G}{R_2 R_3 C_2 C_3}}{s^2 + \left(\frac{R_3 C_3 + R_2 C_3 + R_2 C_2 - G R_2 C_2}{R_2 R_3 C_2 C_3} \right) s + \frac{1}{R_2 R_3 C_2 C_3}}$$

and $G = 1 + \frac{R_f}{R_1}$.

Assuming $R_2 = R$, $R_3 = 2R$, $C_2 = C$, $C_3 = 2C$ and $R_f = R_1$,

(i) Design filter in Figure 4 such that the resonance frequency $\omega_o = 1000 \text{ rad/sec}$,

(ii) From 2(b)(ii), calculate the Q and damping ζ factors of the filter,

(iii) Hence, modify Figure 2 so that the above filter has the Butterworth response such that $|H(j\omega_0)| = 1$ or 0 dB.

7. (a) Explain the terms (i) resolution, (ii) quantum error, (iii) acquisition time t_{aq} , (iv) aperture time t_{ap} and (v) settling time t_s with respect to the analogue-to-digital converter.

(b) The 4-bit $R - 2R$ type digital-to-analogue converter is shown in Fig. 5.

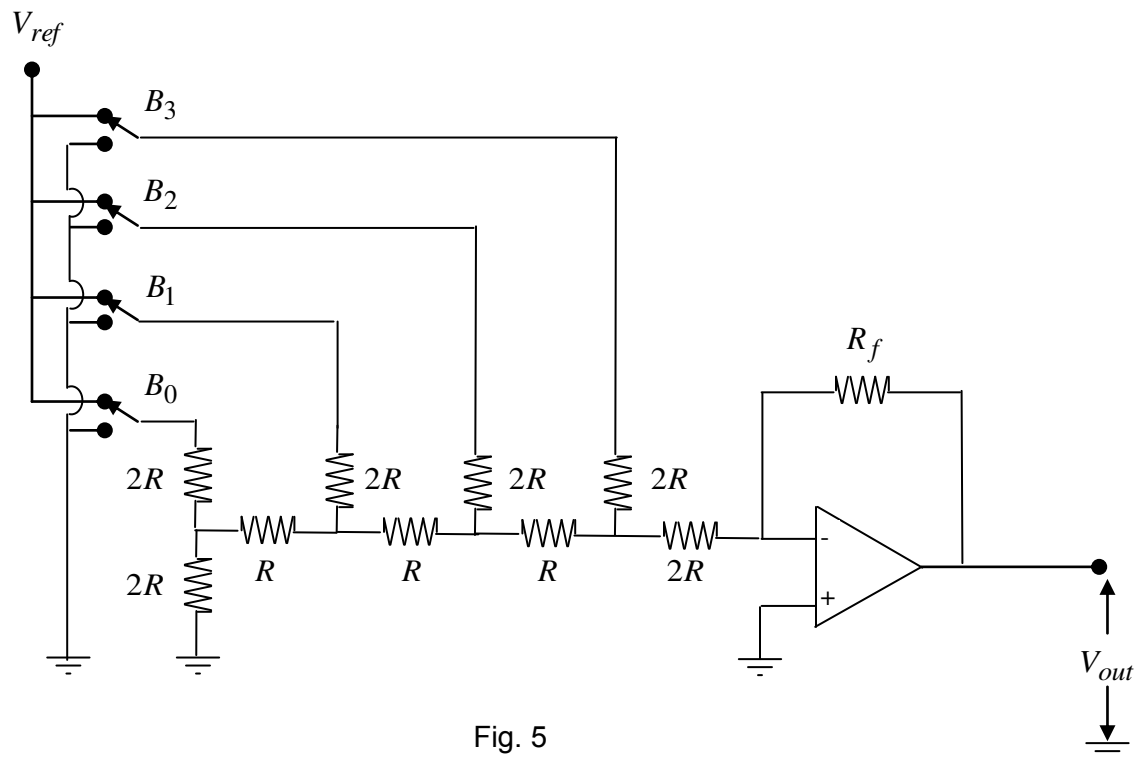


Fig. 5

- (i) Derive the output V_{out} when the most significant bit (MSB) is turned on only,
- (ii) Repeat 3(b)(i) for the least significant bit (LSB),
- (iii) Repeat 3(b)(i) for an input $B_3B_2B_1B_0 = 1001$,
- (iv) From 3(b)(i-iii) derive the general expression for V_{out} .